

# MPS Professional Audio power solution

HR1210 Digital PFC&LLC Controller+Flyback HF500-X



2020.12.28



# Professional audio power




产品展示:

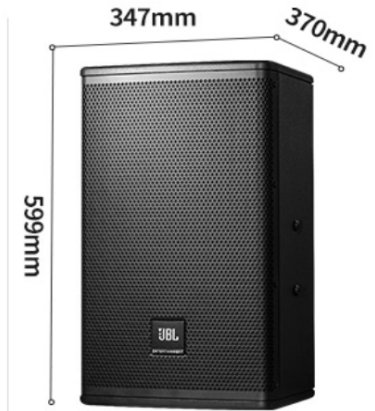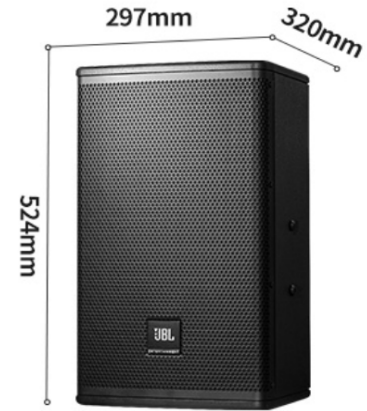

|                    |                                 |                                 |
|--------------------|---------------------------------|---------------------------------|
| 系统类型               | 10英寸, 两路, 低音反射                  | 12英寸, 两路, 低音反射                  |
| 频响 (-10dB)         | 50 Hz-20 kHz                    | 47 Hz-20 kHz                    |
| 频率响应 ( $\pm 3$ dB) | 85 Hz-18 kHz                    | 80 Hz-18 kHz                    |
| 灵敏度                | 94分贝                            | 95分贝                            |
| 标称阻抗               | 8欧姆                             | 8欧姆                             |
| 大声压级 (1m)          | 119 dB (峰值125 dB)               | 121 dB (峰值127 dB)               |
| 额定功率               | (连续/程序/峰值)<br>300瓦/ 600瓦/ 1200瓦 | (连续/程序/峰值)<br>400瓦/ 800瓦/ 1600瓦 |

# Professional audio power

## Block diagram:

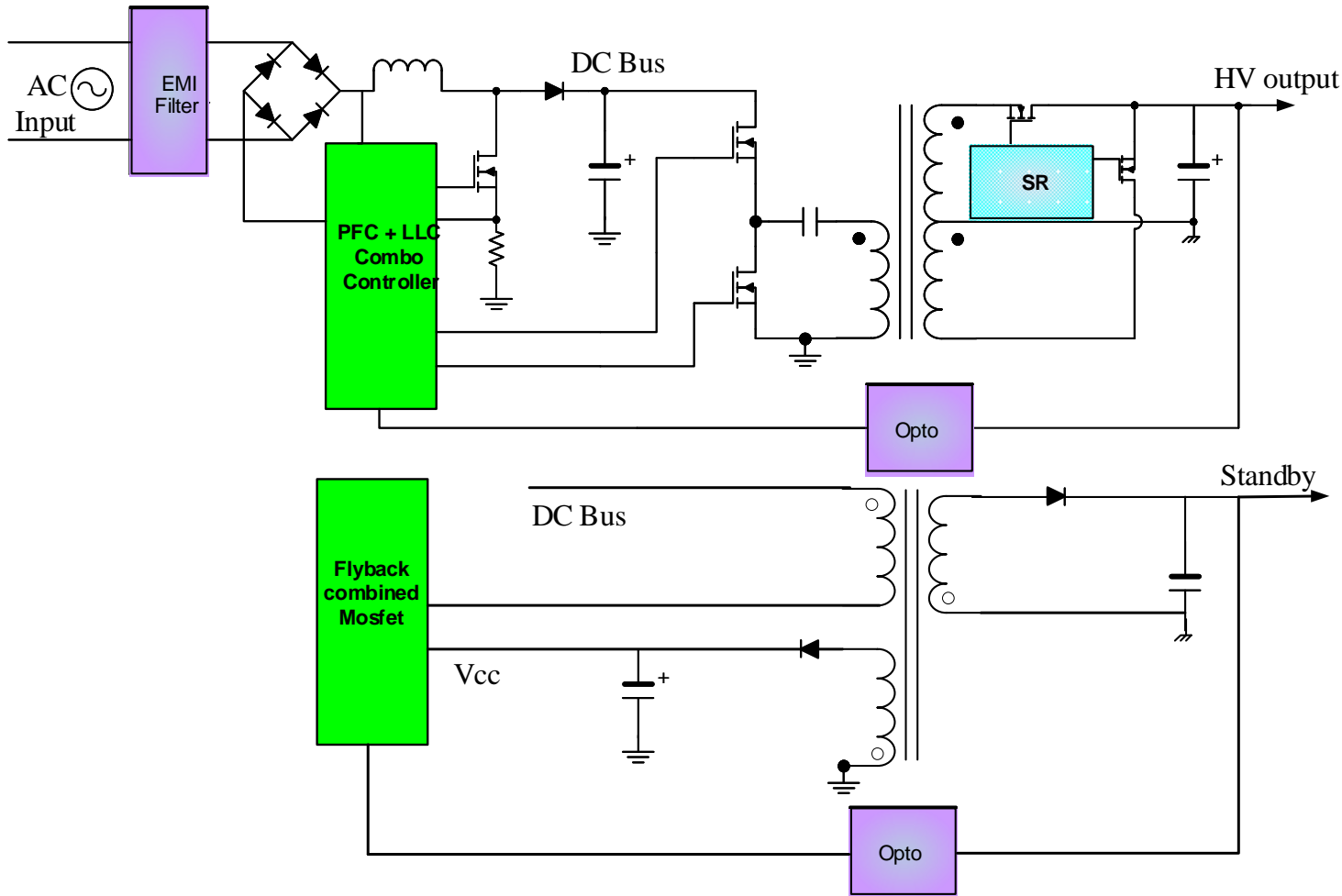

## Power spec:

- Peak power up to 1kW, standby within 20W
- Load transient speed is fast with ms level and frequently
- HV output have large cap, usually >1500uF

## AC-DC solution need:


- High power density and efficiency
- High reliability but easy to design
- Full protection feature

## MPS total solution:

- HR1210: PFC+LLC combin controller
- HF500-X: Flyback combined Mosfet

# HR1210 Typical Application

## CCM/DCM PFC + Current Mode LLC

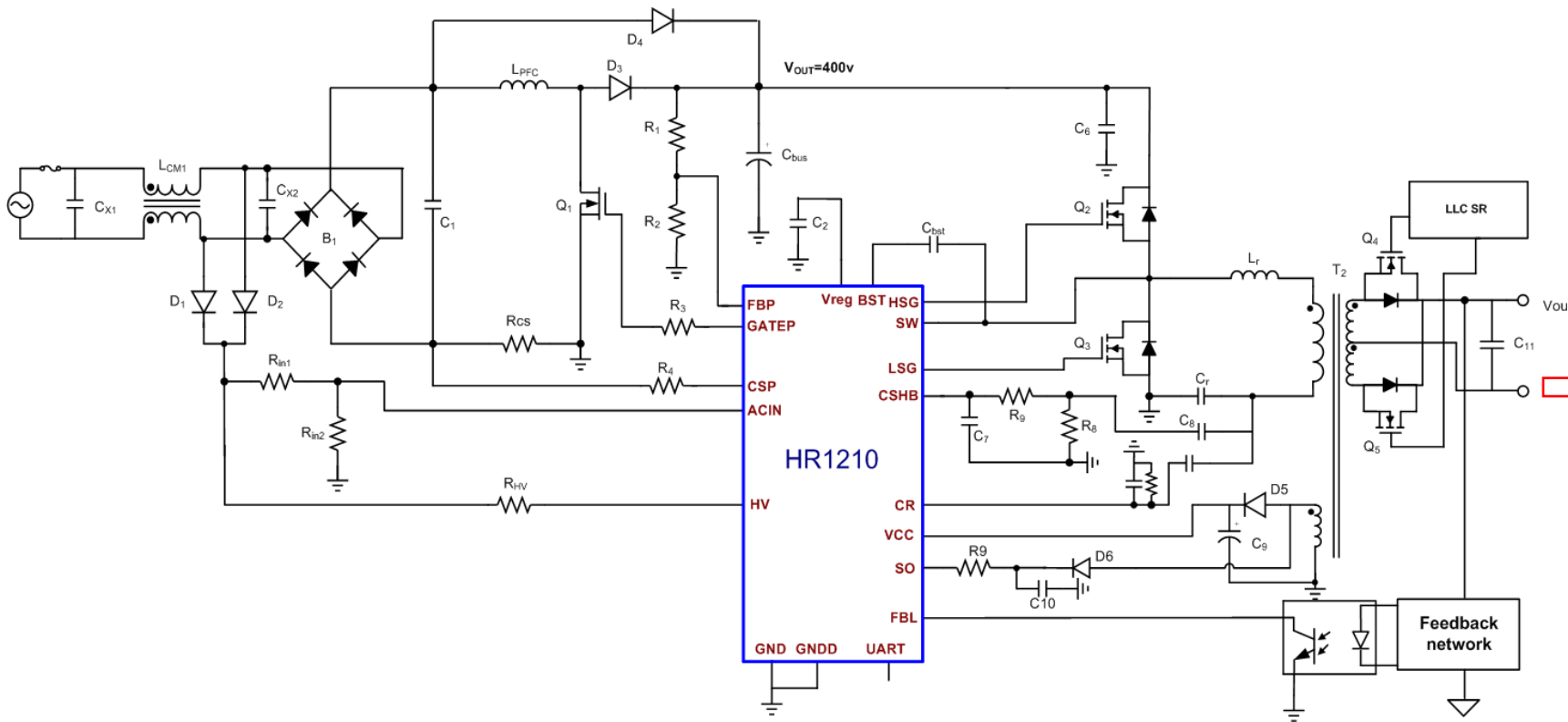


- SOIC-20 & TSSOP-20
- Full Digital Solution
- CCM/DCM of PFC
- Current/Voltage Mode LLC

HR1210

- Ultra-low no load power loss (Pin<100mW @ No Load)
- Improved and accurate burst mode control ( $\eta > 80\%$  @ Pout=8W)
- UART Interface
- GUI for design (Both PFC & LLC)

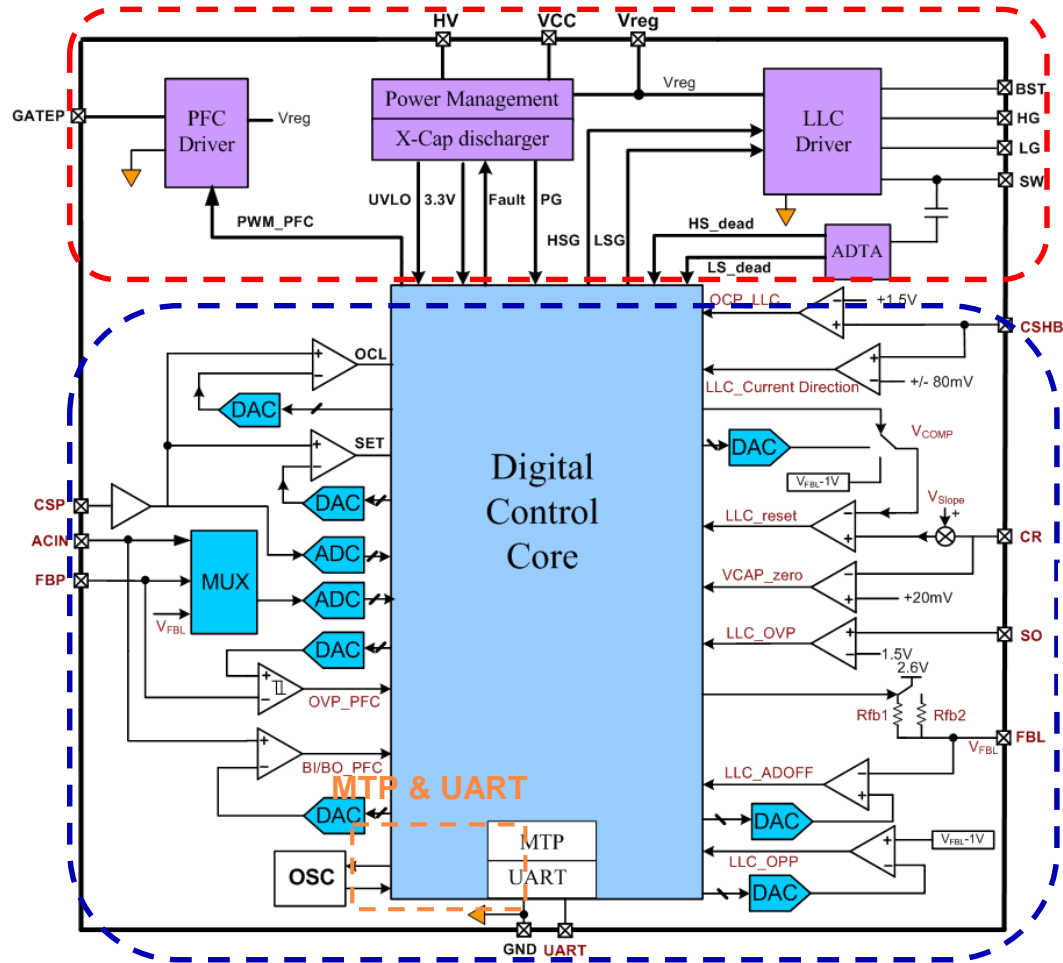
# HR1210 Typical Application

Driver, Power Manager, X-cap discharge, ADTA



PFC + LLC Control

## PACKAGE REFERENCE

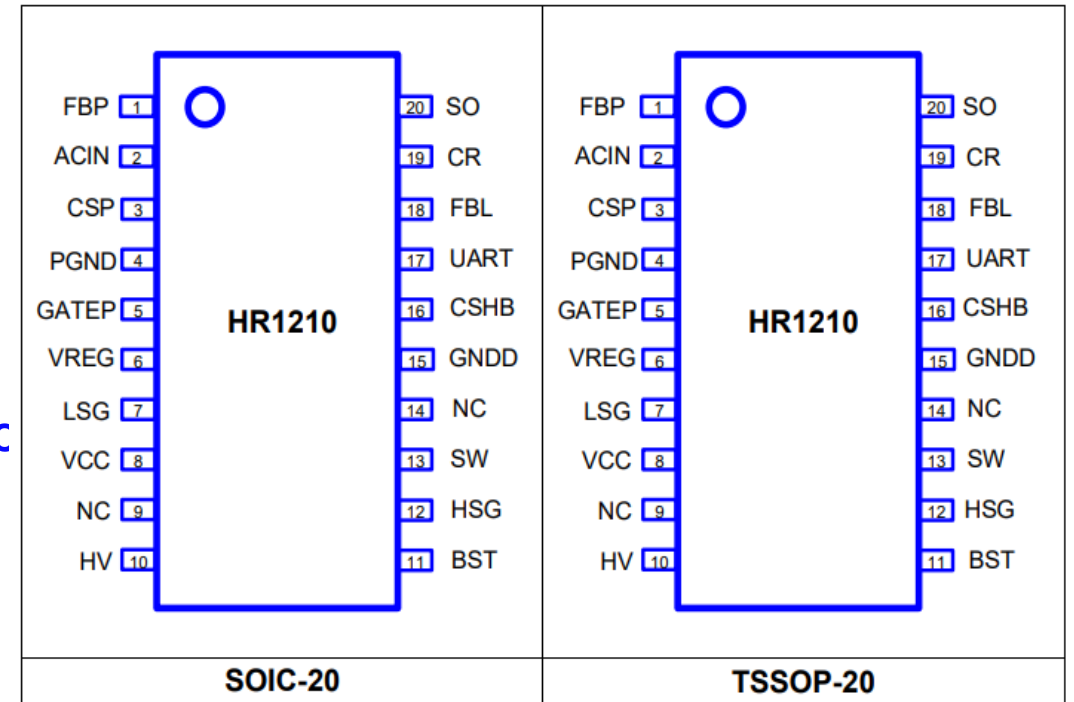

# HR1210 Key Features

## System:

- **Pin<100mW@Pout=0mW**
- **High voltage current source for start up & Smart X-cap discharger**
- **UART Interface & GUI for parameters program**


## PFC:

- **CCM/DCM operation of digital PFC (Max. Switching up to 250KHz)**
- **High PF due to cap current compensation (>0.95@ 20% load)**
- **Programmable frequency Jitter to improve EMI.**
- **Digital PI for control loop**
- **Programmable AC BI/BO, OVP, OCL, OLP**

## LLC:

- **Current Mode / Voltage Mode Control**
- **Adaptive dead time adjustment (230ns~1us)**
- **Anti capacitive mode operation of LLC**
- **Programmable BI/BO, SCP, OPP**
- **Skip mode & frequency controlled Burst mode for better light load efficiency & low audible noise**


# HR1210-HVCS and X-cap discharge

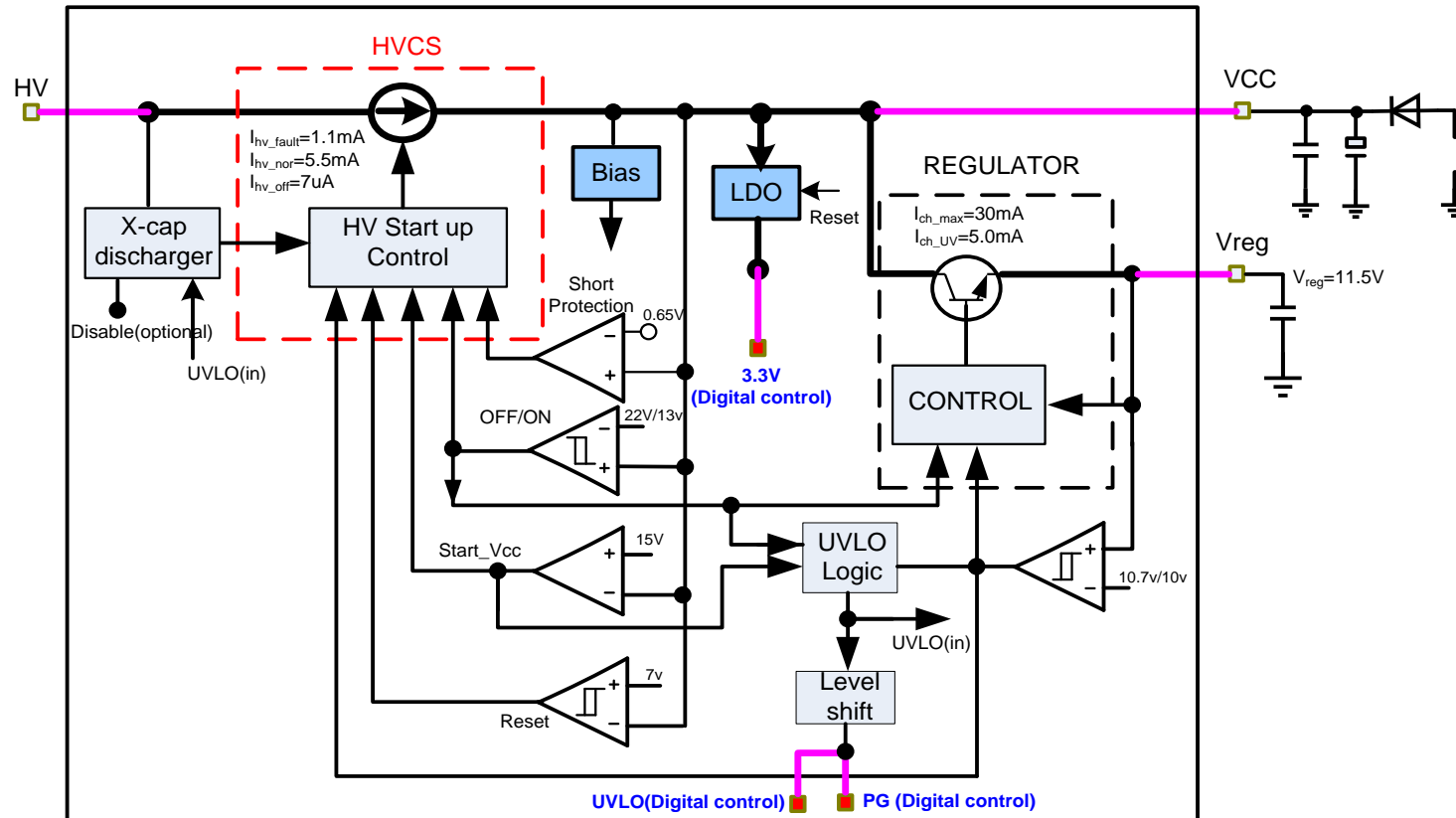

- A high voltage current source (HVCS) internal HV pin is used to power up VCC
- An internal 3.3V LDO is used to power digital control
- An internal 11V regulator is used to power the gate driver (Vreg)
- UVLO and PG logic signal is generated for the digital control set-up
- X-cap Discharge is detected on HV pin

# HR1210-HVCS and X-cap discharge

## Power Supply:

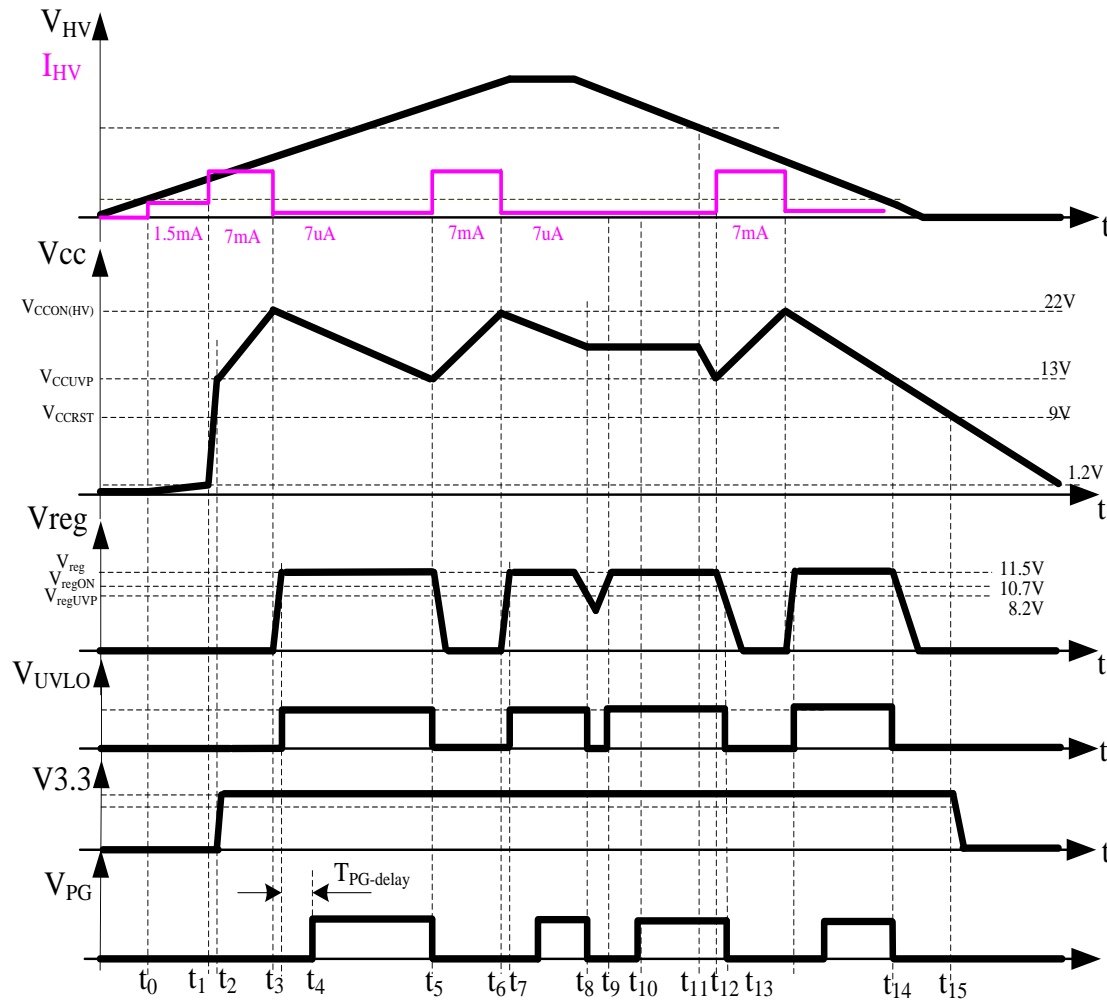

Normal Mode:  $V_{HV}$  is sinusoid

$t_0$ :  $V_{HV-PK} > 35V$ , HVCS start charge  $V_{CC}$ .

$t_0 \sim t_1$ : 3.3v (digital control) power set-up

$t_3$ :  $V_{CC} > 22V$ , HVCS turn off, Vreg LDO (driver supply) works

$t_3$ : UVLO is high, digital control stand-by to operate

$t_4$ : PG (power good) is high, digital control starts soft-start


$t_4 \sim t_5$ : Capacitor value on  $V_{CC}$  determine this period.

$t_5 \sim t_8$ : Digital control stop work when  $V_{CC} < 13V$  or  $V_{reg} < 8.9V$



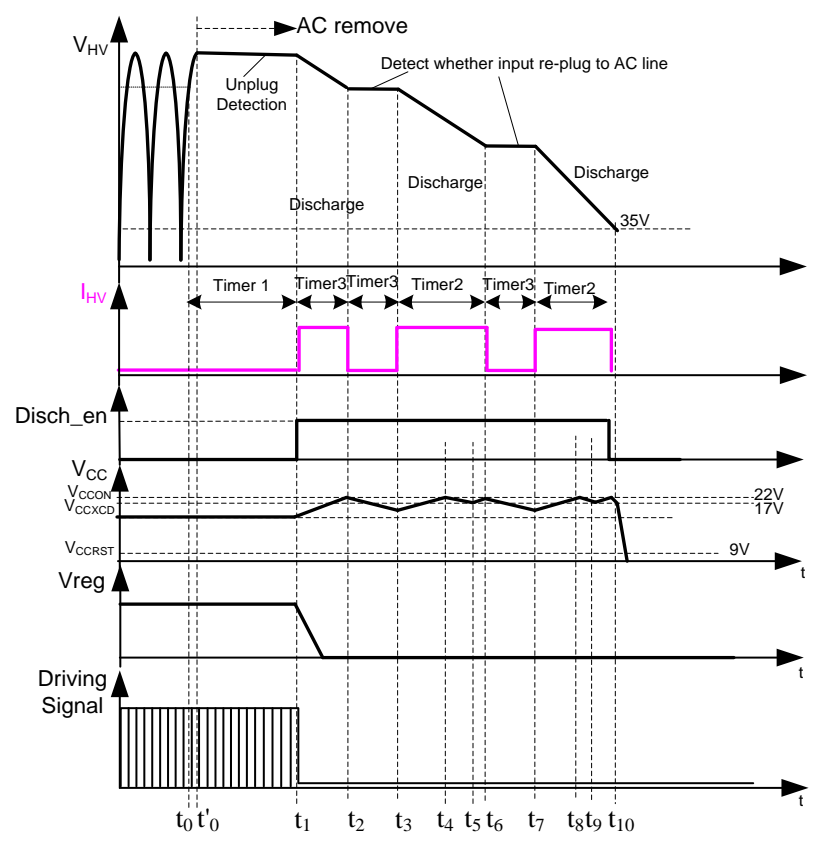
# HR1210-HVCS and X-cap discharge

X-Cap Discharger: When  $V_{HV}$  is DC or Open.  $V_{CC}$  will regulate in 17v~22v




AC Removed and Don't Recovery

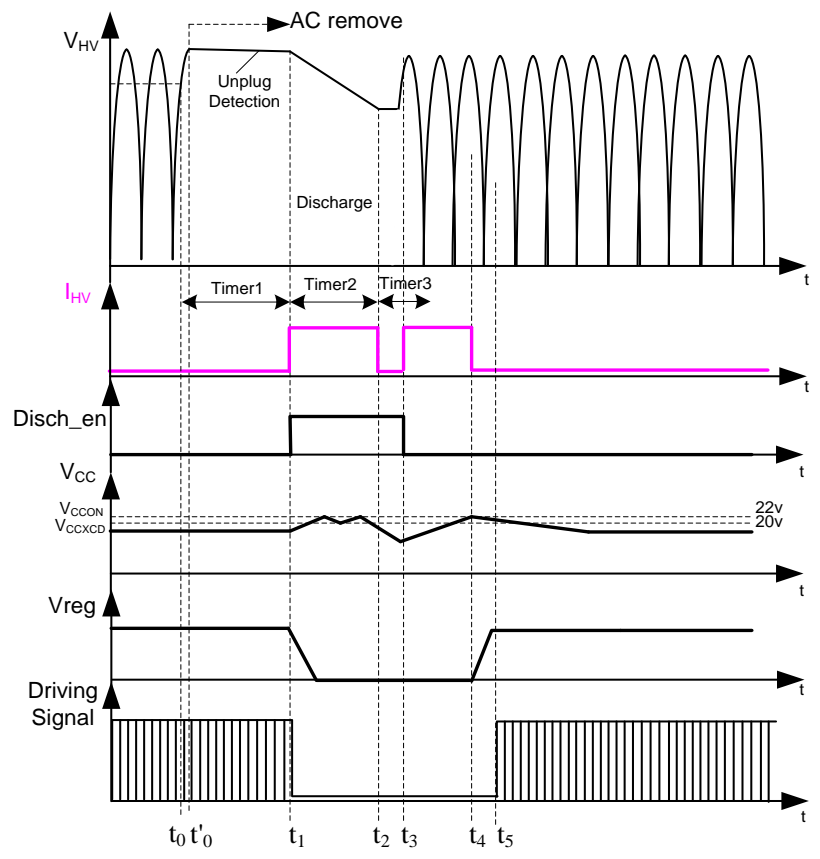

AC Remove but Recovery

# HR1210-PFC+LLC digital control timing

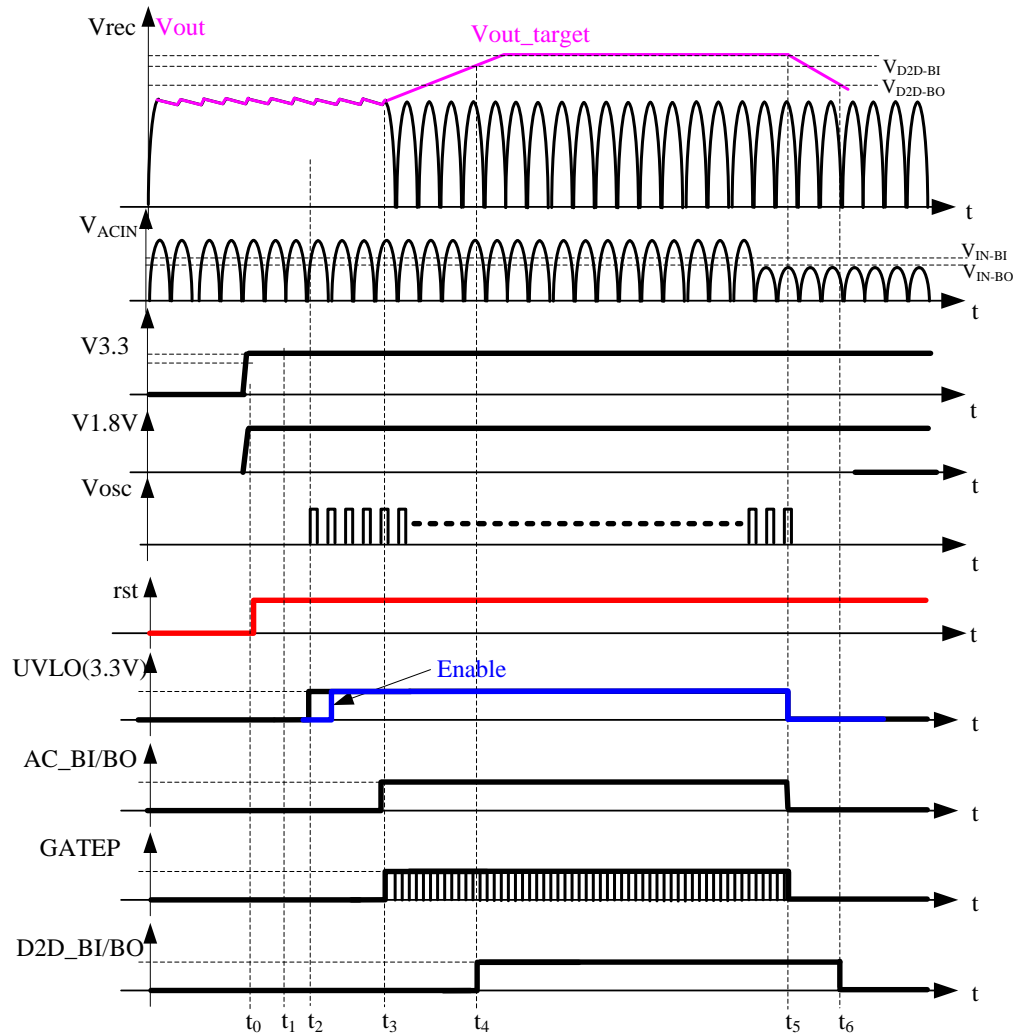

t<sub>0</sub>: Internal 1.8V supply set-up when 3.3V is ready, rst signal set-up to reset digital.

t<sub>2</sub>: UVLO high, digital control start works, sense FBP, FBL, ACIN, CSP voltage

t<sub>2</sub>~t<sub>3</sub>:  $V_{in} > V_{in-BI}$ , with a timer, PFC start works


t<sub>3</sub>~t<sub>4</sub>: PFC Soft Start, LLC works when  $V_{out} > V_{D2D\_BI}$

t<sub>4</sub>~t<sub>5</sub>: Normal operation

t<sub>5</sub>:  $V_{in} < V_{in-BO}$  with a timer, PFC stops switching

t<sub>6</sub>:  $V_{out} < V_{D2D-BO}$ , LLC stops switching.


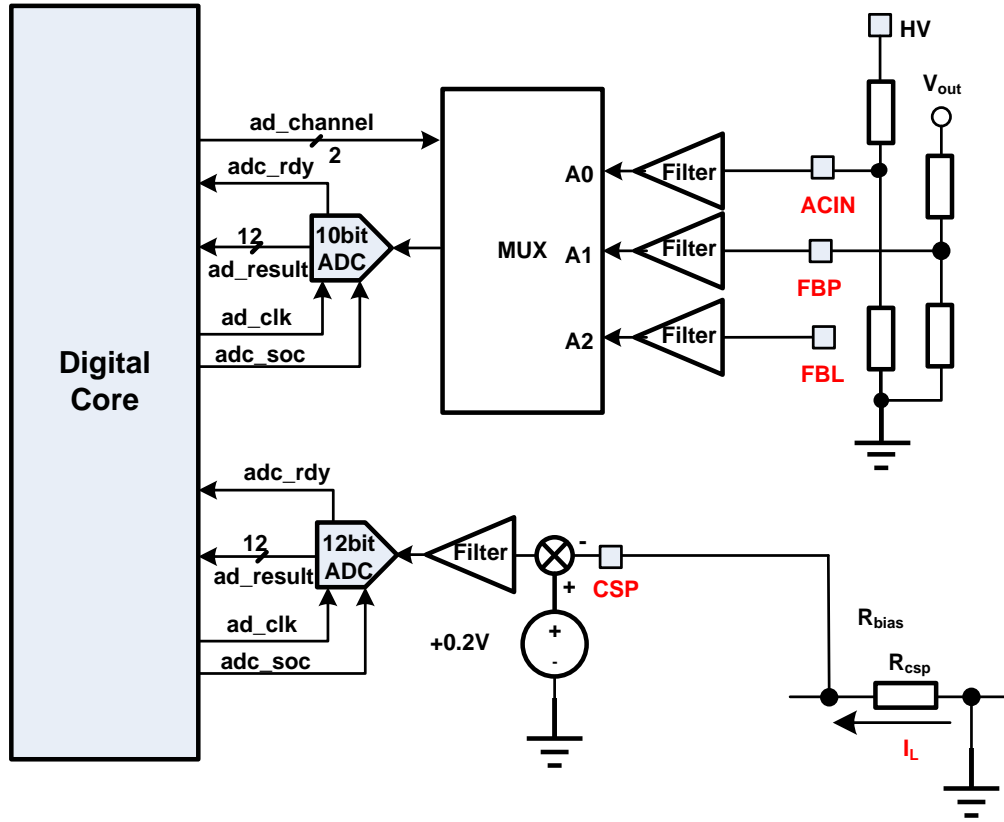
# HR1210-PFC+LLC digital control sampling



- The digital core need to sample FBP (PFC output), ACIN (PFC input) & CSP (PFC inductor current) for PFC control
- The digital core need to sample FBL (LLC Feedback) for LLC control
- The FBP, FBL & ACIN is sampled by a 10bit ADC through a controlled MUX
- The CSP is sampled by a 12bit ADC
- The CSP is a negative voltage with internal biased by a 0.2V voltage source, so the sampled voltage of CSP is actually  $0.2V - V_{CSP}$ .

# HR1210-PFC digital control

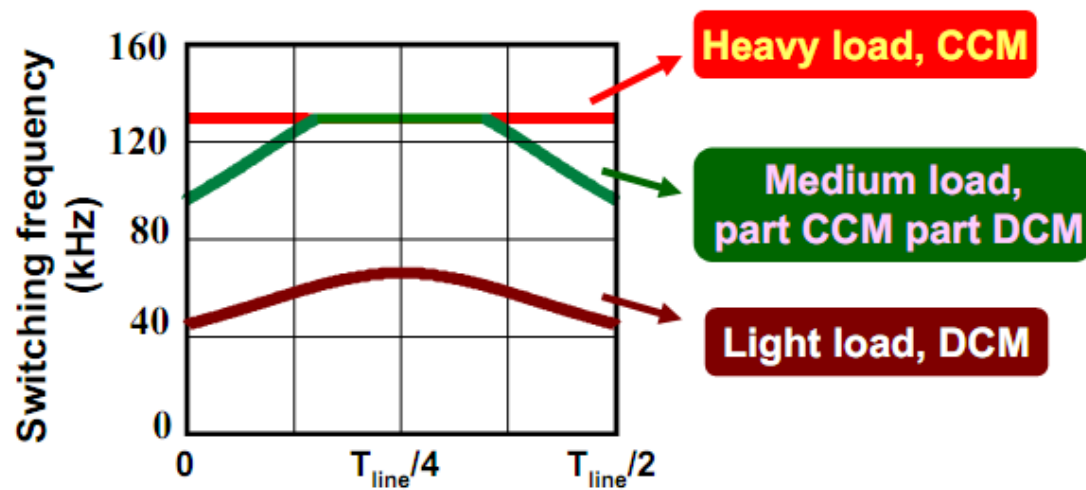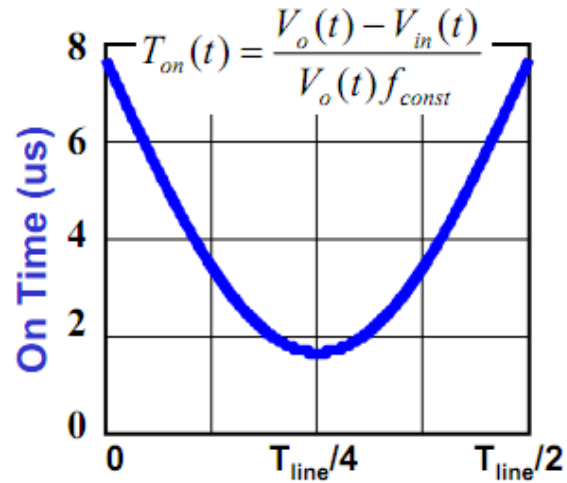
## Digital PFC: Quasi-fixed On Time Control




- By fix the Ton profile at different load conditions, switching frequency at light load can be reduced.
- On time is adaptively changed based on instantaneous input voltage.
- Light load efficiency can be improved.

# HR1210-PFC digital control


## Flowchart in 1 switching cycle:

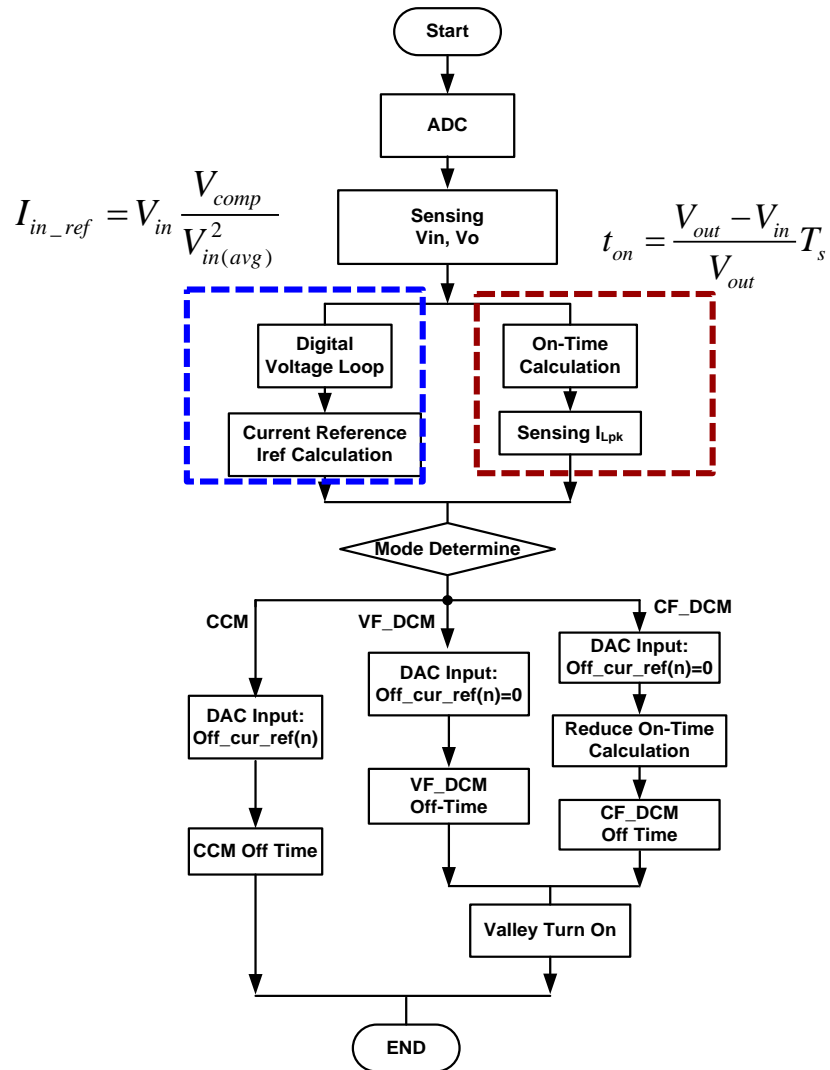


CCM:  $I_{pk}(n) < 2I_{ref}(n)$

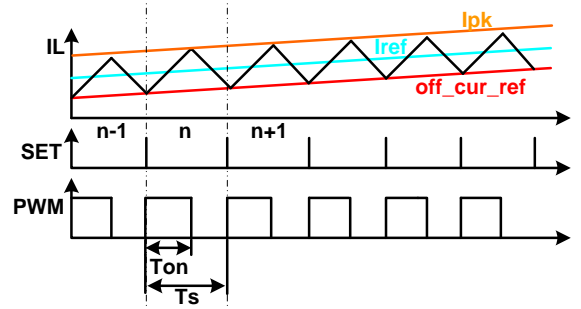

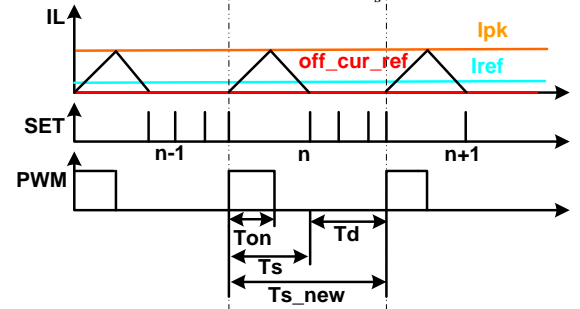DCM:  $I_{pk}(n) > 2I_{ref}(n) \cdot \frac{T_{s\_max}}{T_s}$




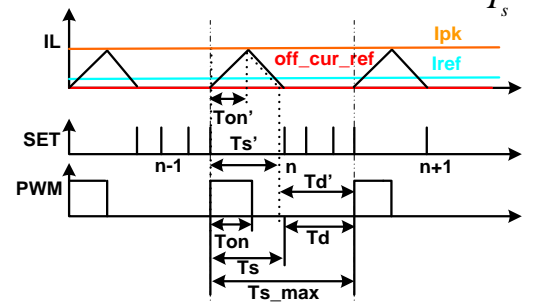
CF-DCM:  $2I_{ref}(n) < I_{pk}(n) < 2I_{ref}(n) \cdot \frac{T_{s\_max}}{T_s}$



# HR1210-PFC digital control
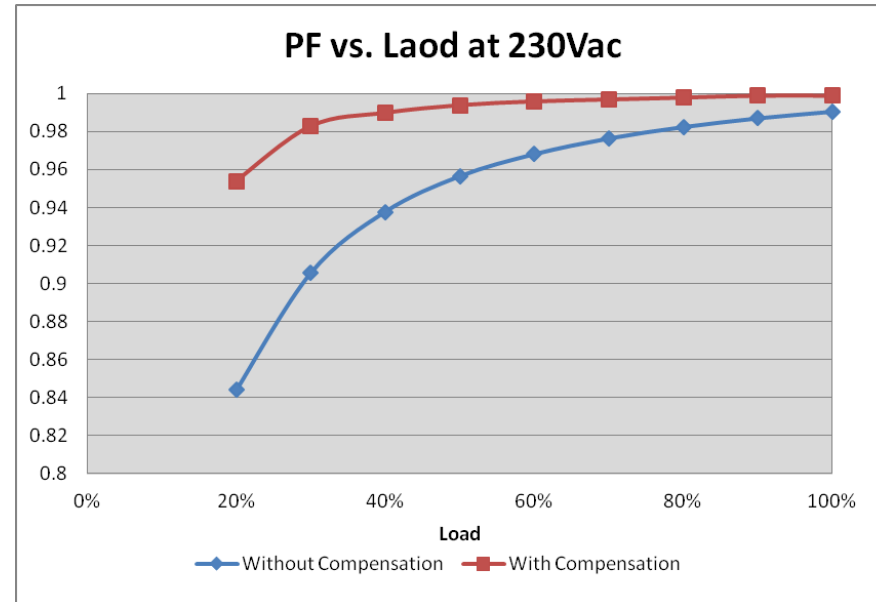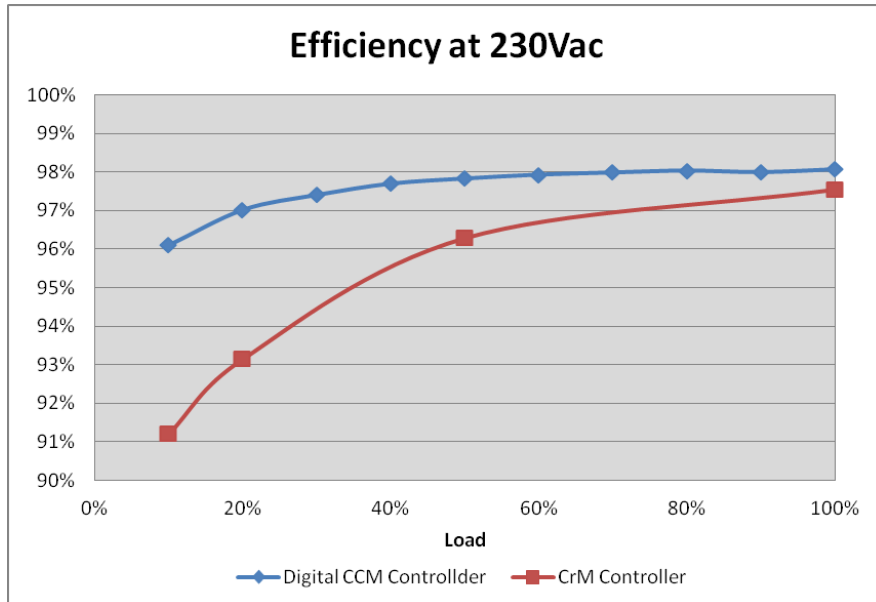
## Key Performance:


- High light load Efficiency, >96% @ 10% load of 400w output
- High light load PF, >0.95 @ 20% load for 400w output.



# HR1210-PFC digital control


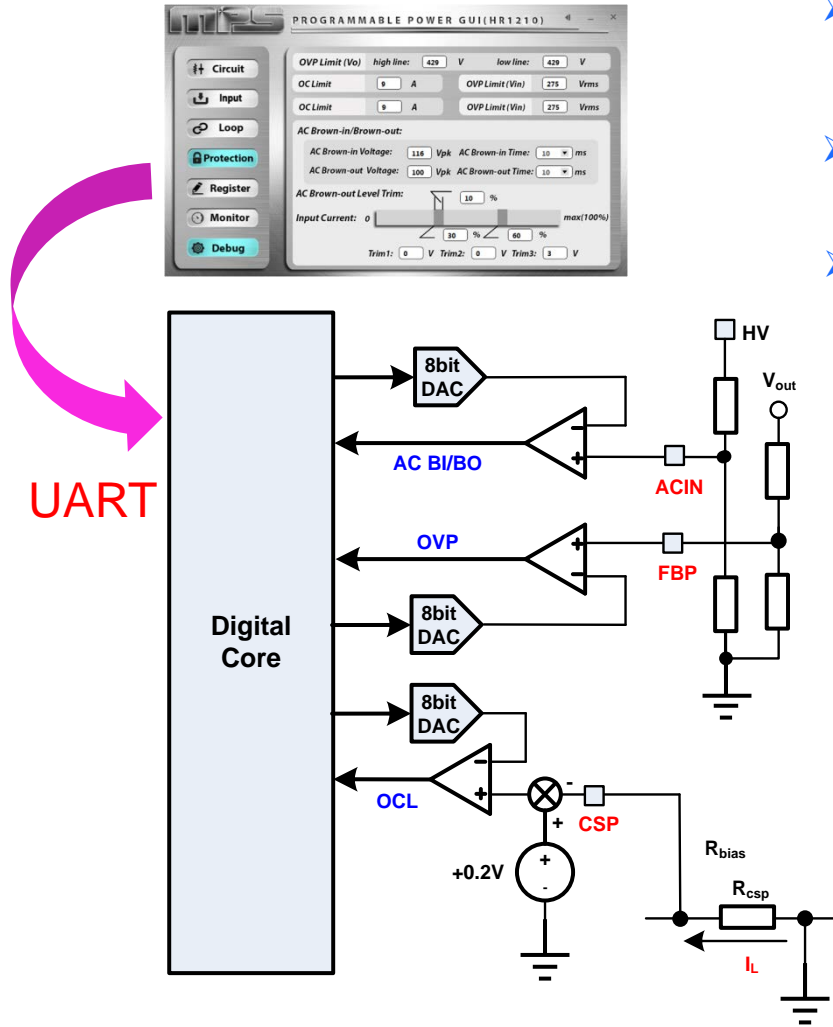
## PFC Protection:

- The digital core control the threshold for AC BI/BO, OVP & OCL protection for PFC.
- A 8bit DAC is used for the output of the threshold of the protection
- By setting in GUI, the thresholds for these protection can be programmed through UART interface on IC.



# HR1210-PFC digital control

## LLC Current Mode Control:

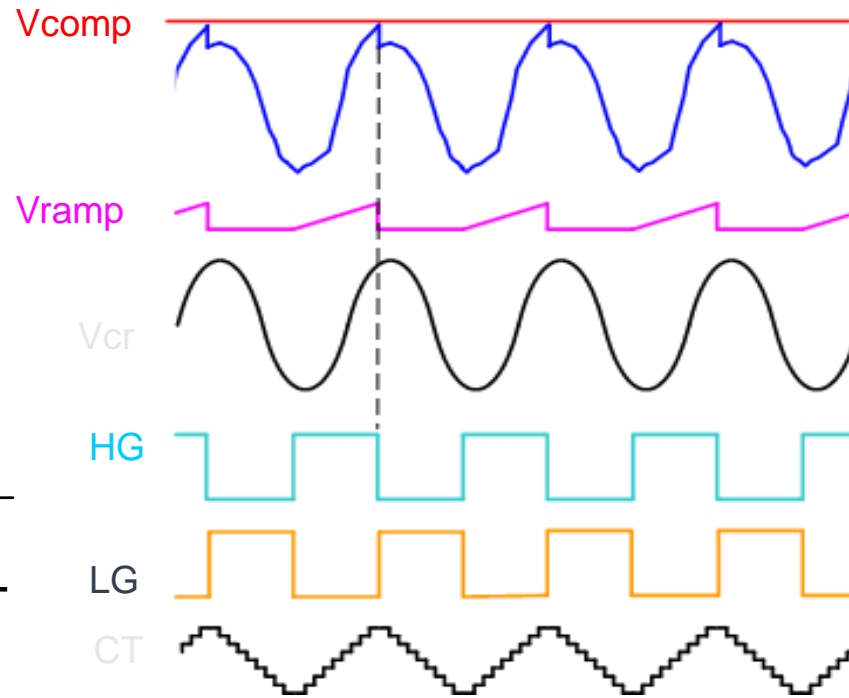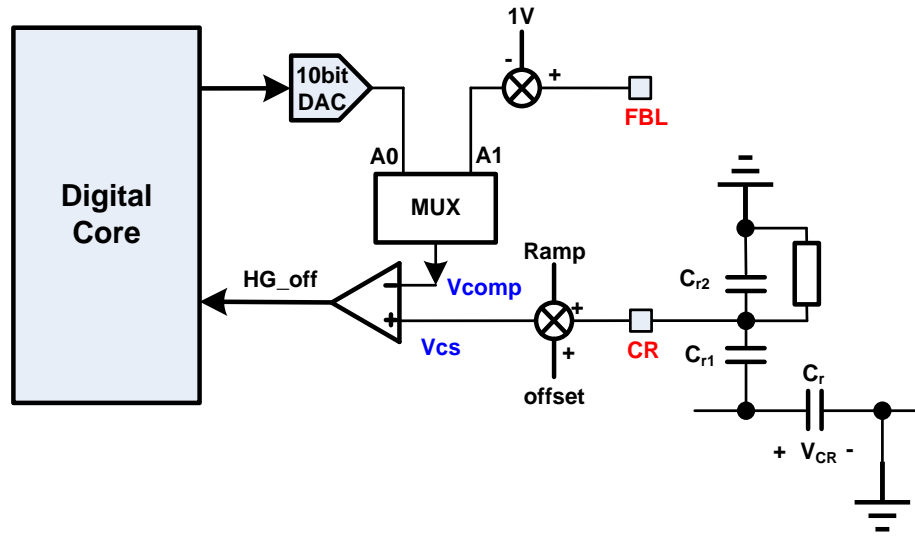


- The voltage on resonant cap ( $C_r$ ) is compared with internal reference ( $V_{comp}$ ) to generate the HG-off signal
- The LG on time is equal with HG on time by an internal
- The Internal reference ( $V_{comp}$ ) is derived from FBL pin voltage or digital core (10 bit DAC), depend by LLC operating state:  
When in steady state,  $V_{comp} = V_{FBL} - 1V$   
When in Skip or burst mode,  $V_{comp} = V_{DAC}$  which determined by digital core



# HR1210-LLC digital control


## LLC Operating Mode:

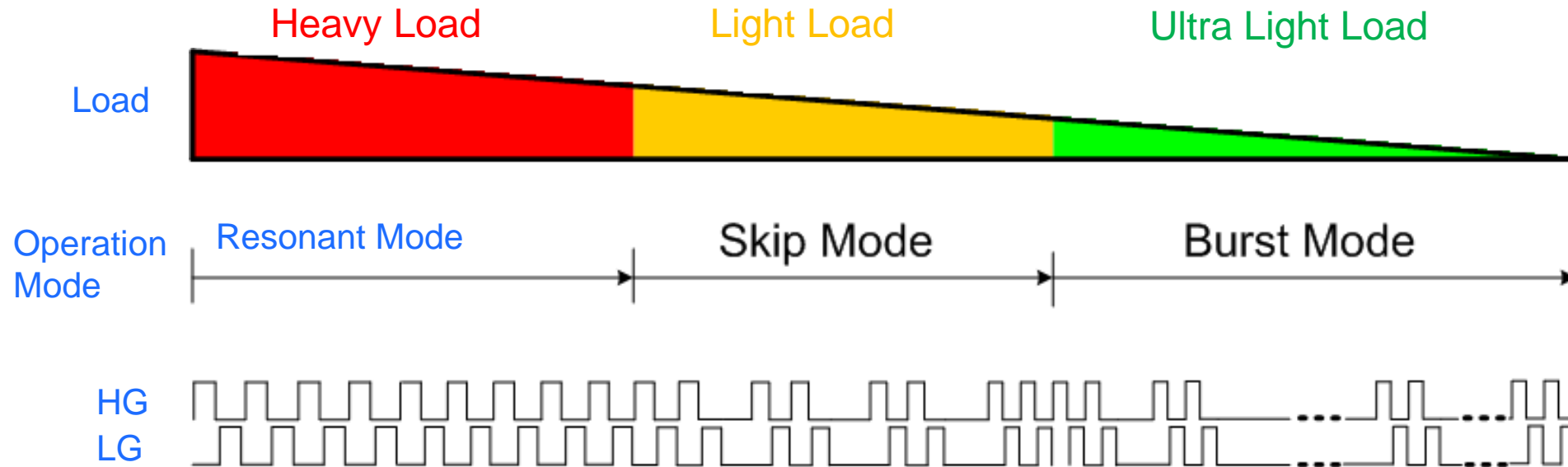


- LLC changes operation mode according to the load.
- It works in Resonant Mode (normal operation) at heavy load, switching to Skip Mode at lighter load and change to Burst Mode at ultra light load or no load.
- When run into Burst Mode, it works in PWM burst pattern to reduce audible noise.

# HR1210-LLC digital control

## LLC Skip Mode:

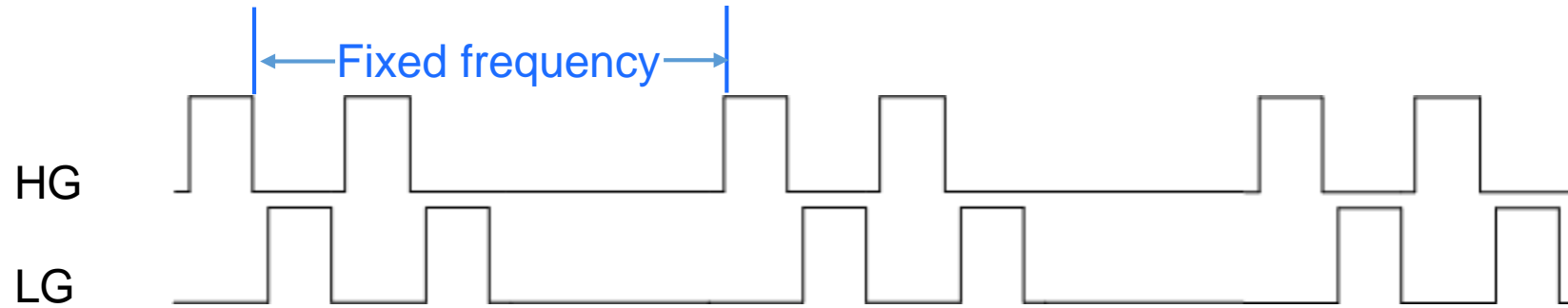


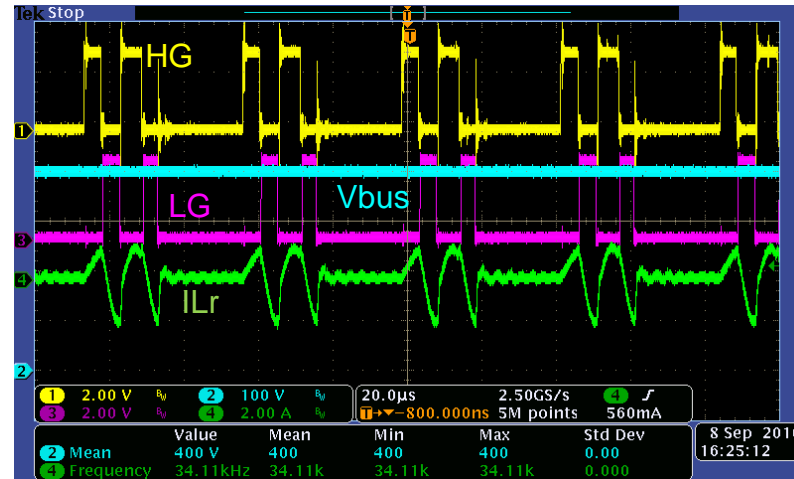- At light load, HG & LG stops switching for a certain period every N cycles (programmable)
- The skip frequency is kept at  $f_s$  (programmable)




# HR1210-LLC digital control

## LLC Burst Mode:


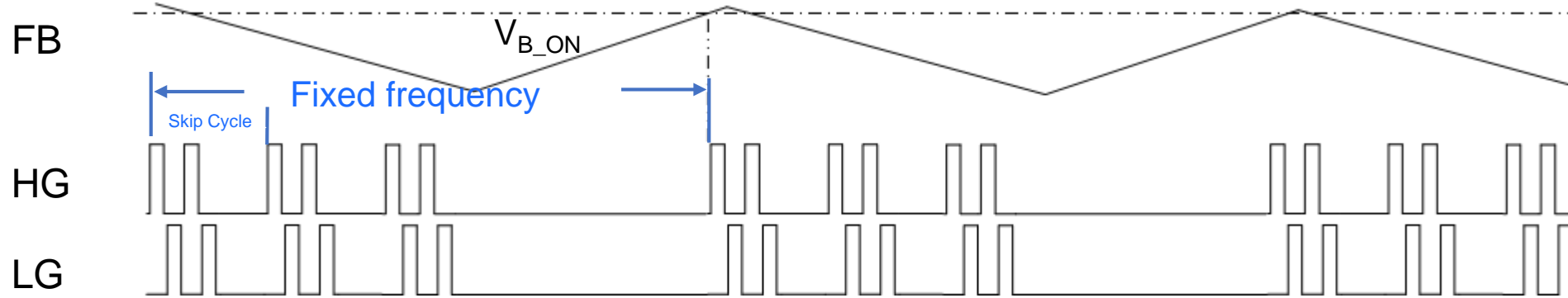


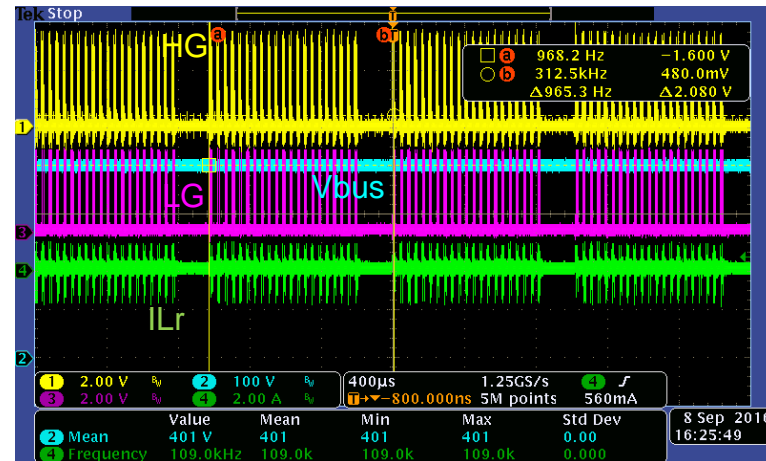- At very light load condition, HG & LG switch in skip mode and stops switching for a long time which determined by VFBL touching the burst-on threshold ( $V_{B\_ON}$ )
- The burst frequency can be select to keep at  $f_s$  (programmable) for low audible noise




# HR1210-LLC digital control

## LLC Low Power Mode:

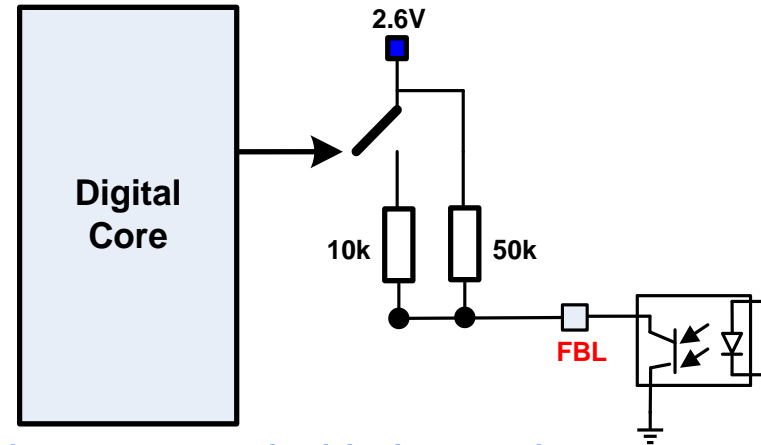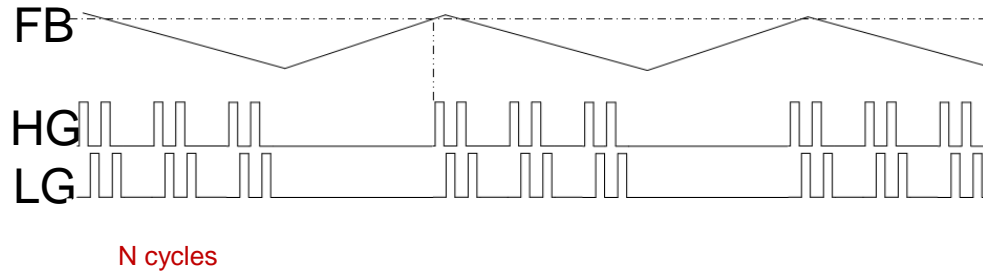

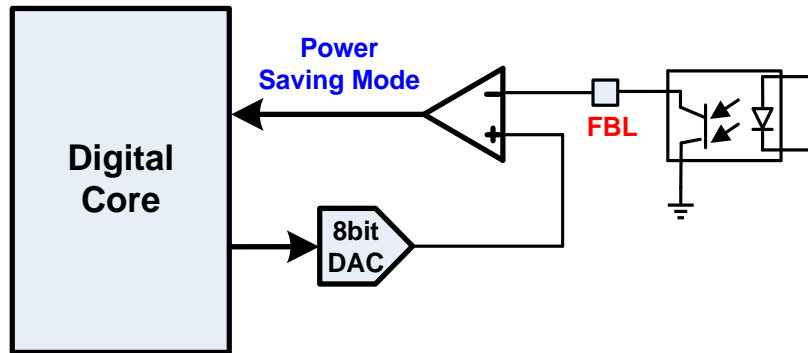- When the LLC switching cycles N during each burst-on period is lower than a preset value (defined by GUI), the digital core will switch the FBL pull up resistor from ~8kOhm to 50kOhm to pull down the opto current




- When VFBL voltage (during burst-off) is lower than a preset value (defined by GUI), the IC will enter
- In power saving mode, the IC will only active some necessary internal circuits, which help to decrease the

# HR1210-LLC digital control
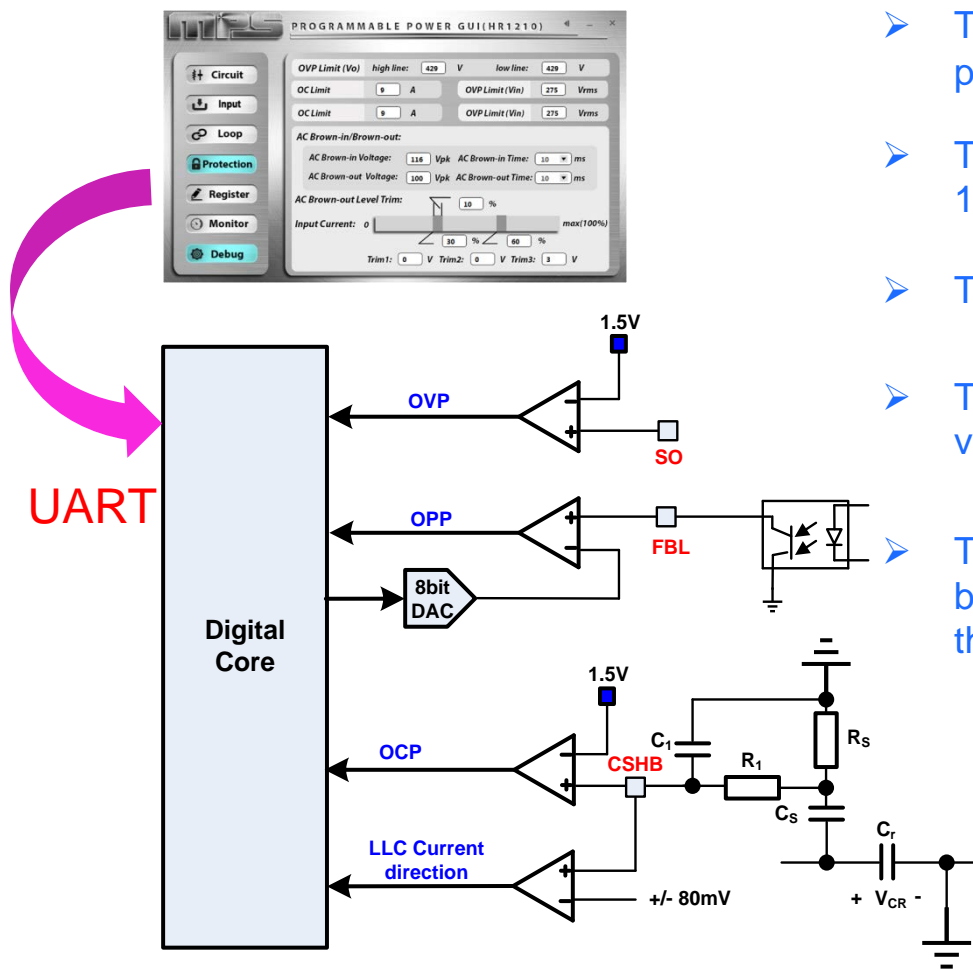
## LLC Protection:


- The digital core control the threshold for OPP protection for LLC.
- The OVP protection is achieved by SO pin with fixed 1.5V threshold
- The CSHB pin is used to sense the LLC current
- The OCP protection is achieved by compare current sense voltage on CSHB with 1.5V fixed threshold.
- The digital core also sense the current direction of LLC by comparing the CSHB voltage with fixed +/- 80mV threshold (This used for CMP of LLC, see next page)



# HR1210-LLC digital control


## CMP (Capacitive Mode Protection):

Without CMP

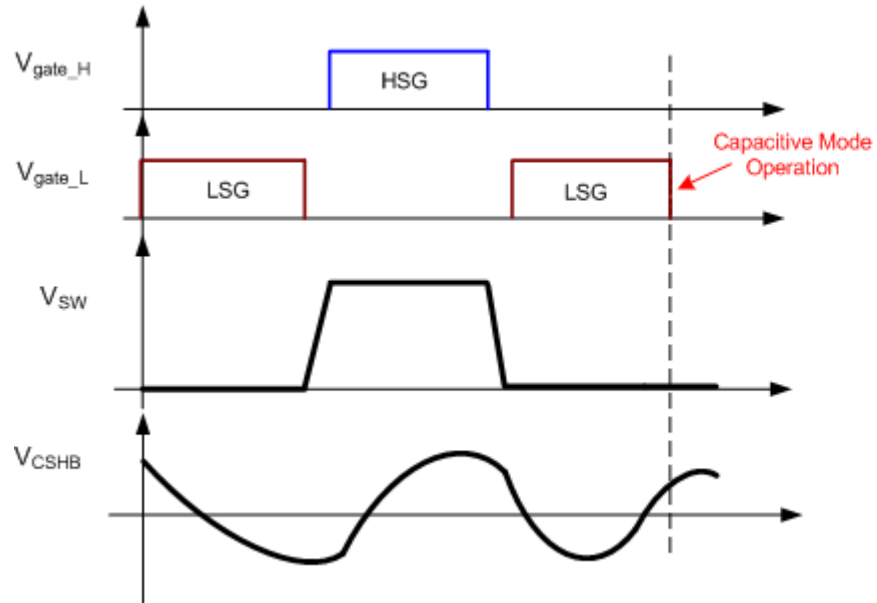

Capacitive Mode operation:  
HG turned off at  $I_r < 0$  ( $V_{CSHB} < 0$ );  
LG turned off at  $I_r > 0$  ( $V_{CSHB} > 0$ );

HR1210 with CMP

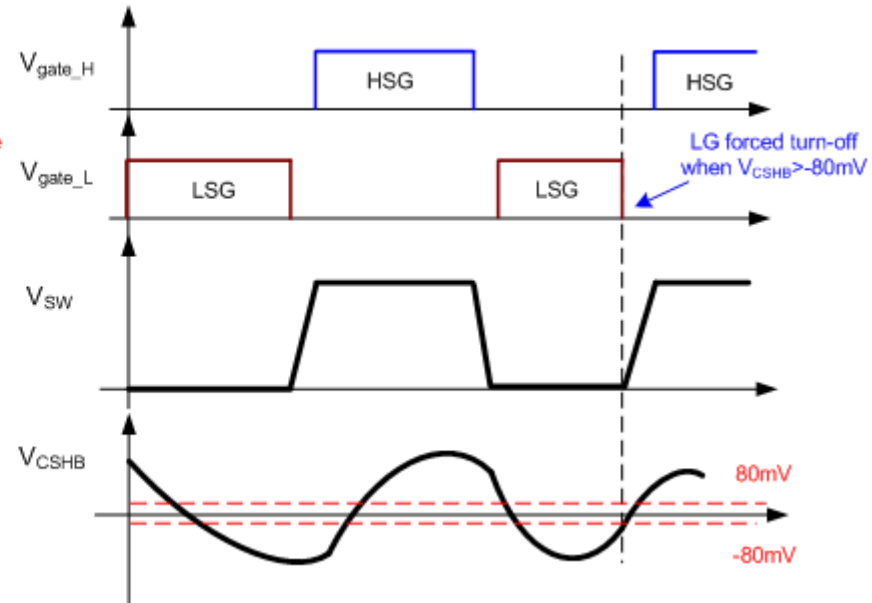

In HR1210  
HG will be forced off when  $V_{CSHB} > -80mV$   
LG will be forced off when  $V_{CSHB} < 80mV$

# HR1210 key features

## Enhanced Surge Immunity





**Issue**




**System shutdown & output drops when surge occur:**

- Surge noise lead the digital IC restart.
- Surge noise trigger LLC OVP on SO pin
- Surge noise trigger LLC SCP on CSHB pin


**HR1210**

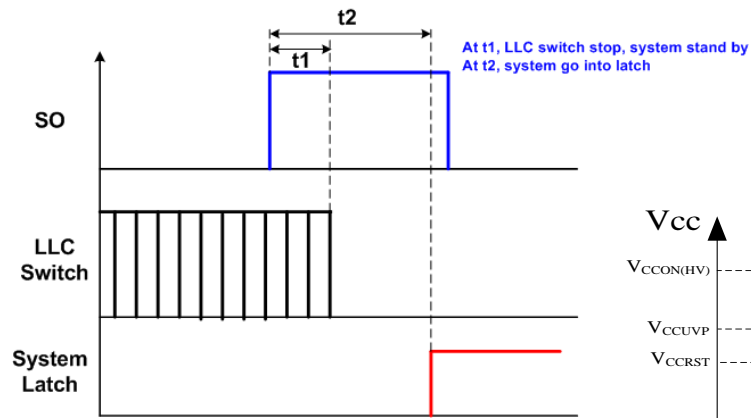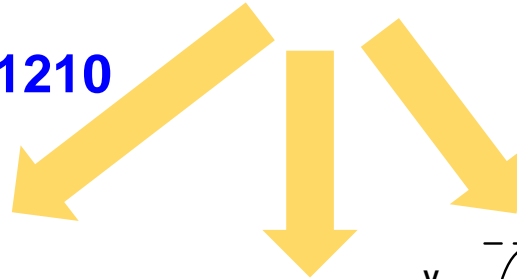

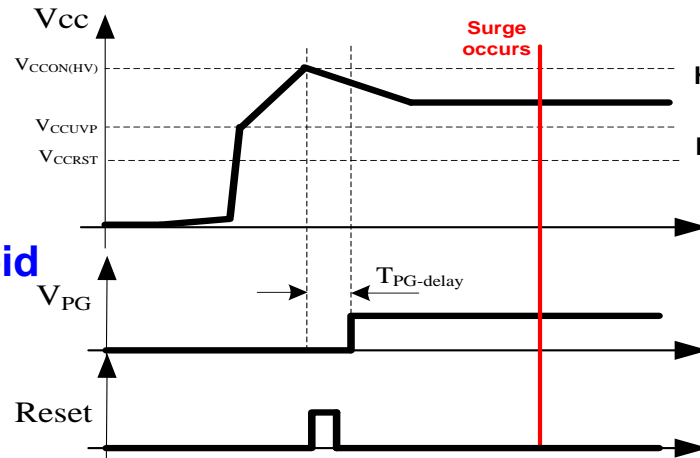**A digital filter on SO to avoid error trigger**





**PG signal to indicate a real restart**

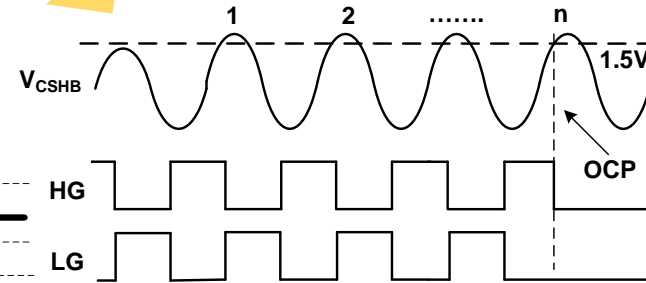


**CSHB Counter to filter noise**

# HR1210 key features

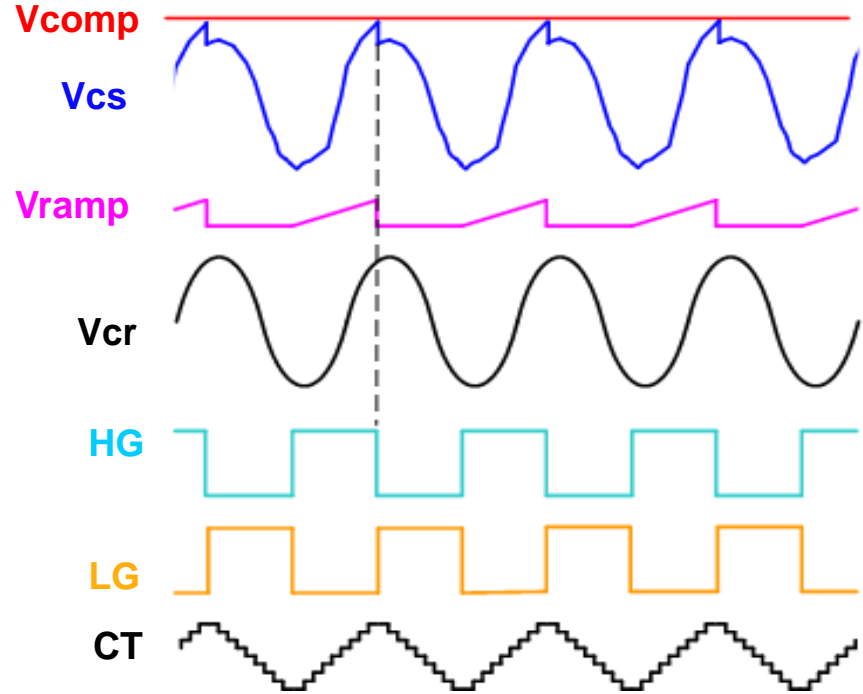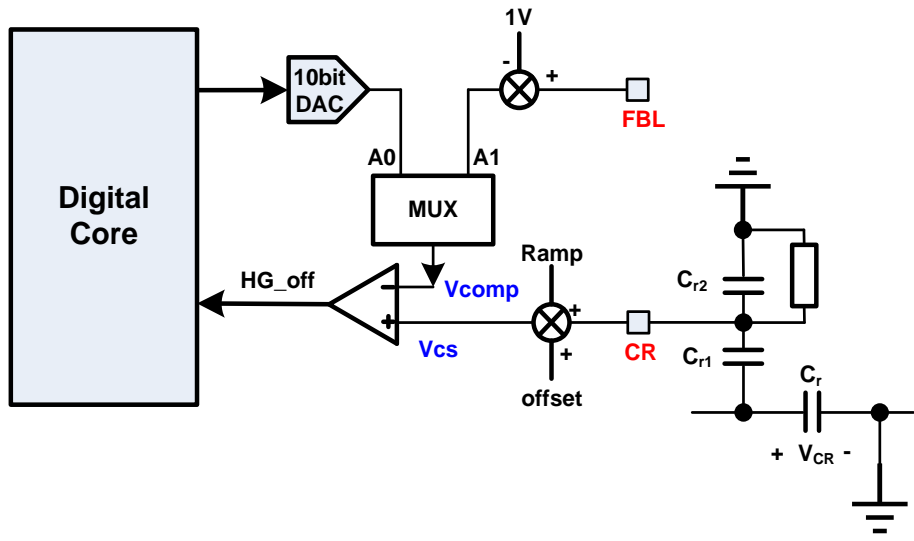
## Current Mode Control LLC with better loop response



LLC\_Voltage Mode Control


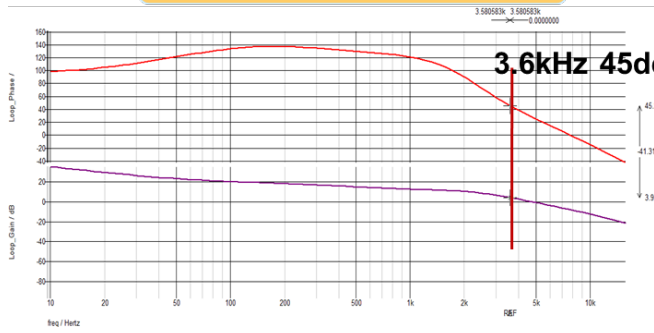


LLC\_Current Mode Control

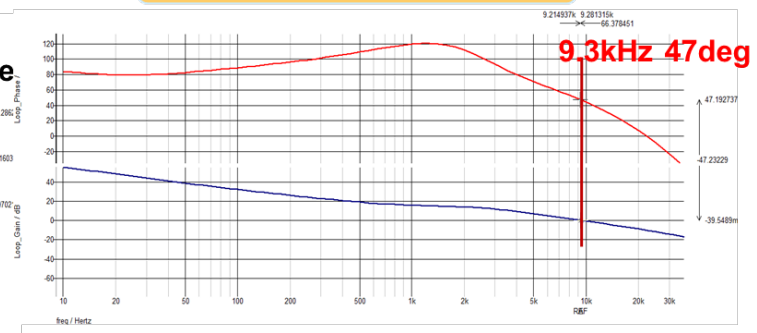



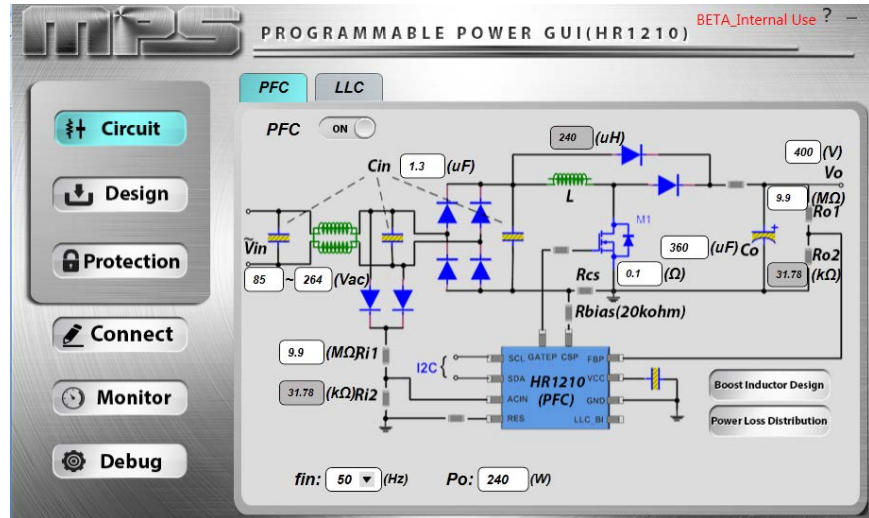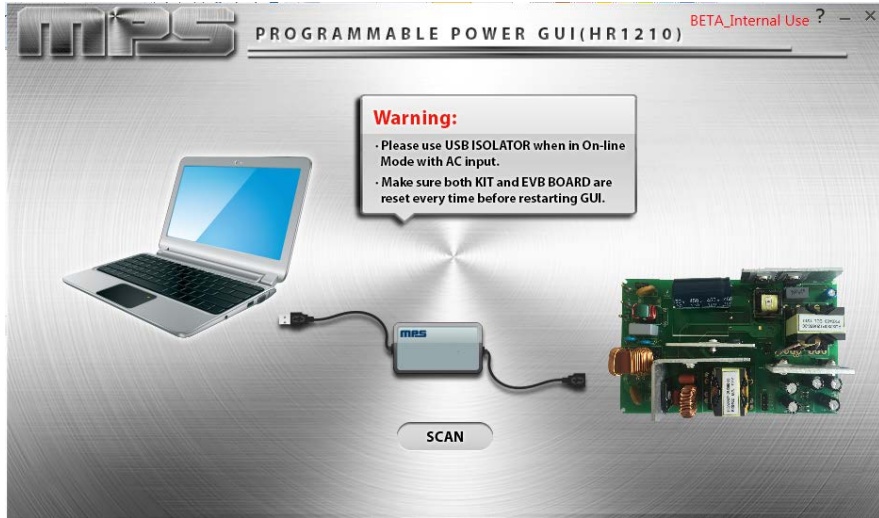
# HR1210 User GUI for Parameters Configuration




## Step1: Connection Kits

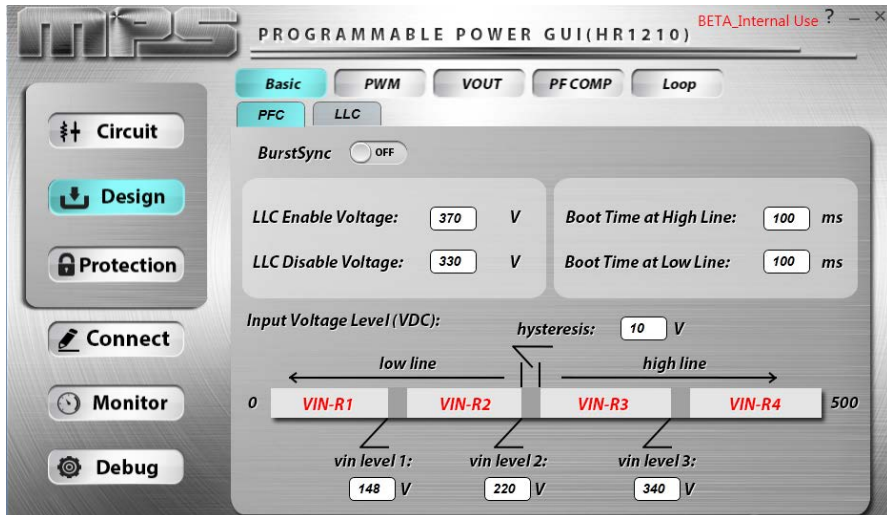

Input PFC & LLC Design Parameters

## Step2: Configuration Parameters

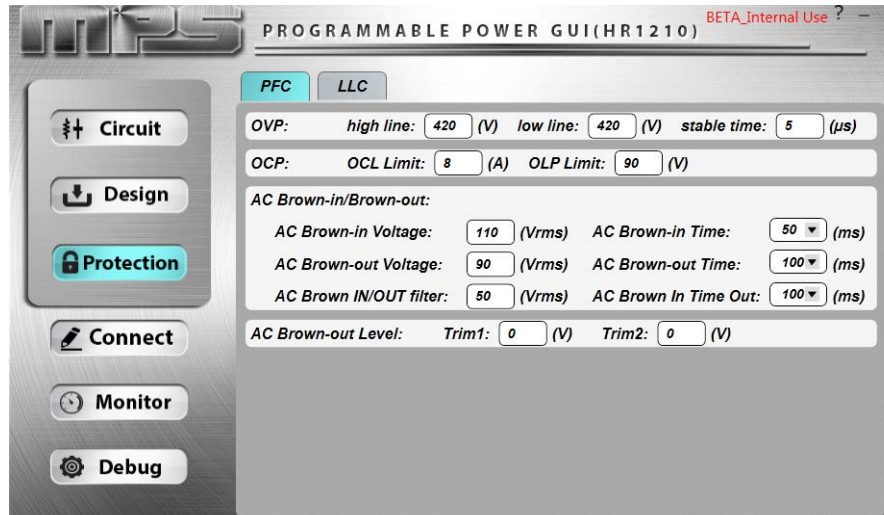

Input PFC & LLC Protection Parameters

# HR1210 User GUI for Parameters Configuration

Use GUI for Parameters Configuration :

The screenshot displays the 'PROGRAMMABLE POWER GUI(HR1210)' interface. On the left, there is a vertical menu with buttons for 'Circuit', 'Design', 'Protection', 'Connect', 'Monitor', and 'Debug'. The 'Connect' button is highlighted in blue. The main area features a table with three columns: 'Command code', 'Command name', and 'Register value'. To the right of the table are three buttons: 'Program', 'Export', and 'Import'. The window title bar includes the 'MPS' logo, the text 'PROGRAMMABLE POWER GUI(HR1210)', and a red 'BETA\_Internal Use ?' label.

| Command code | Command name                  | Register value |
|--------------|-------------------------------|----------------|
| 02H          | Manufacturer and Project code | 0001           |
| 03H          | VBUS_CMD_H1                   | 031E           |
| 04H          | VBUS_CMD_H2                   | 031E           |
| 05H          | VBUS_CMD_H3                   | 031E           |
| 06H          | VBUS_CMD_H4                   | 031E           |
| 07H          | VBUS_CMD_L1                   | 031E           |
| 08H          | VBUS_CMD_L2                   | 031E           |
| 09H          | VBUS_CMD_L3                   | 031E           |
| 0AH          | VBUS_CMD_L4                   | 031E           |
| 0BH          | AUTO_VBUS_VCOMP1              | 07AA           |
| 0CH          | AUTO_VBUS_VCOMP2              | 0311           |
| 0DH          | AUTO_VBUS_VCOMP3              | 013A           |
| 0EH          | AUTO_VBUS_VCOMP PHYS          | 00C4           |
| 0FH          | PFC_TS_MIN1                   | 03E8           |
| 10H          | PFC_TS_MIN2                   | 03E8           |

Import & Export Register List

# HR1210 User GUI for Parameters Configuration

## Design Optimization with Labview:

The screenshot shows the HR1210 Labview GUI with several callouts pointing to specific features:

- Import ConfigFile**: Points to the 'Load' button in the top toolbar.
- Export File**: Points to the 'Save' button in the top toolbar.
- Start/Stop**: Points to the 'Run' button in the top toolbar.
- Print Curve Data**: Points to the 'Print' button in the top toolbar.
- About**: Points to the 'Help' button in the top toolbar.
- Exit**: Points to the 'Exit' button in the top toolbar.
- Version Information**: Points to the 'Version 0.1.6771.0 internal use' text in the top right corner.
- Efficiency**: Points to the 'Efficiency' tab in the 'Test Object' section.
- Test Conditions**: Points to the 'Test Conditions' section, which includes a table of parameters.
- Check USB Connect**: Points to the 'USB UART is disconnected' status bar.
- WriteWord Times**: Points to the 'Chip register written 16 times' status bar.
- Reset Times = 0**: Points to the 'Reset' button in the status bar.
- Result**: Points to the 'Efficiency' graph in the 'Result side'.

| Item | Value | Unit | Steps |
|------|-------|------|-------|
| Min  | 1.005 | V    | 4     |
| Max  | 1.205 | V    |       |
| Min  |       | V    | 5     |
| Max  |       | V    |       |
| Min  |       | V    | 5     |
| Max  |       | V    |       |
| Min  | 0.2   | V    | 8     |
| Max  | 1     | V    |       |

Use labview to get optimized parameters to improve the design


## Appendix




# HR1210-Demo board and test results

HR1210 Demo Board (12V/33.3A):

TOP VIEW

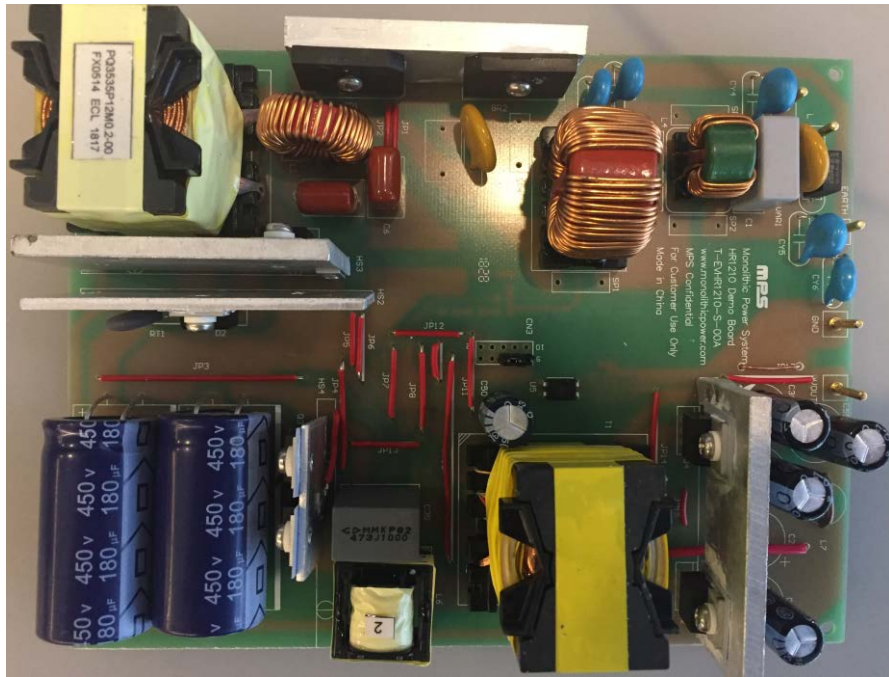


BOTTOM VIEW

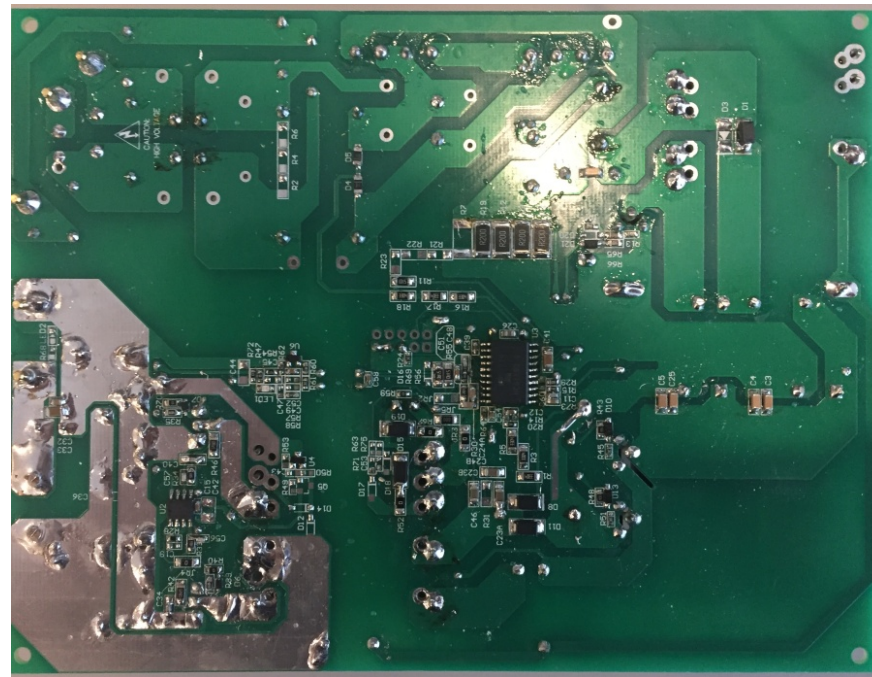




# HR1210-Demo board and test results
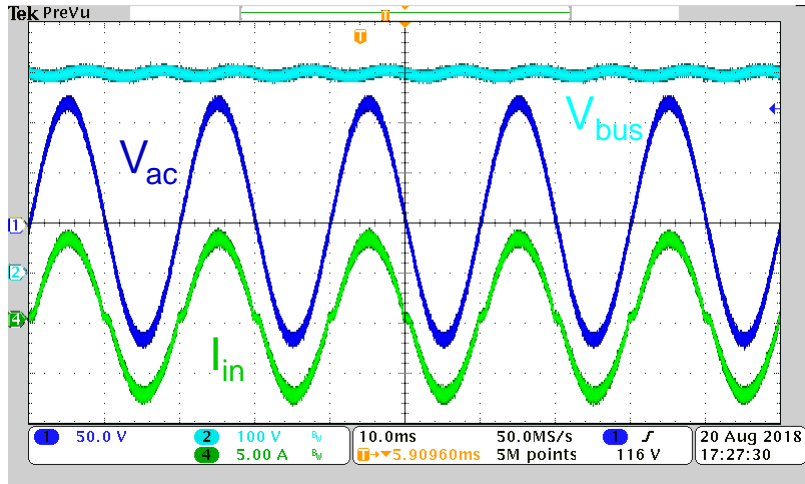
## Steady State Waveform (PFC):

Test Condition:  $V_{in}=85V_{ac}$ , Full Load



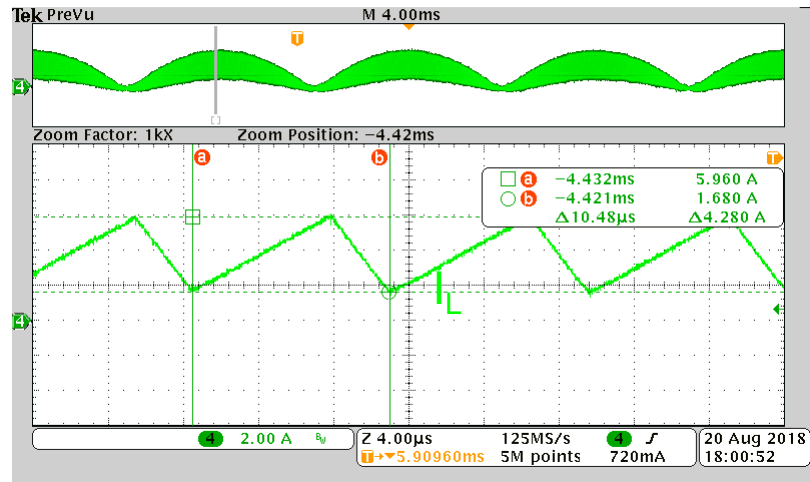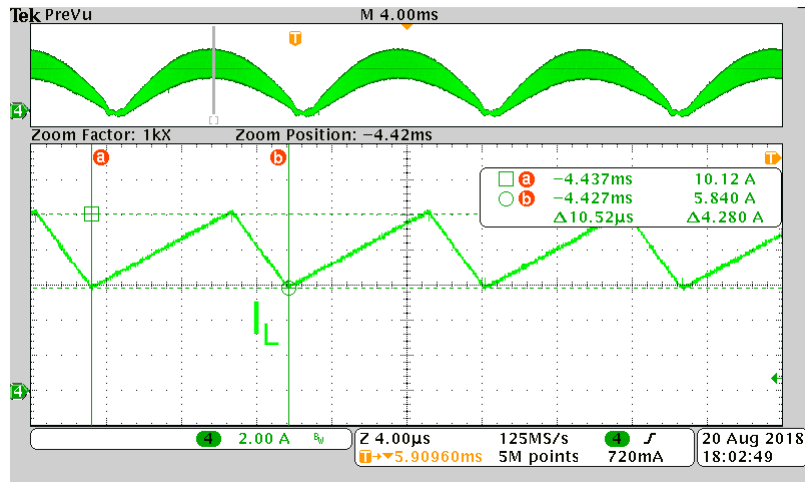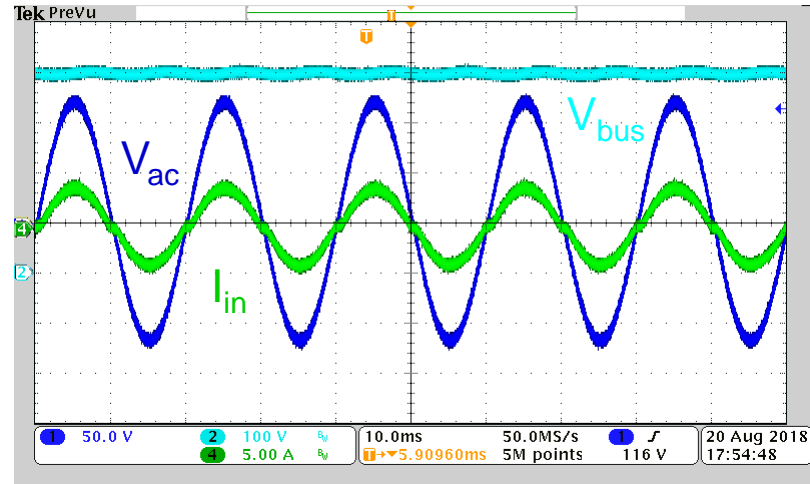
Test Condition:  $V_{in}=85V_{ac}$ , 50% Load






# HR1210-Demo board and test results
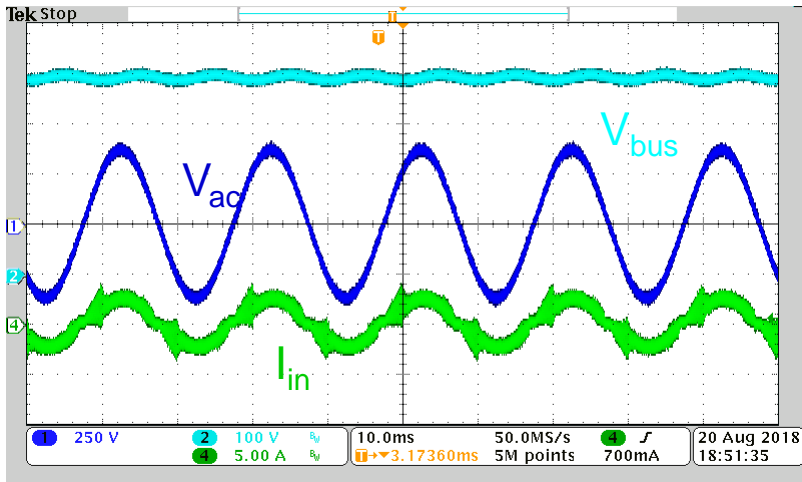
## Steady State Waveform (PFC):

Test Condition:  $V_{in}=265V_{ac}$ , Full Load



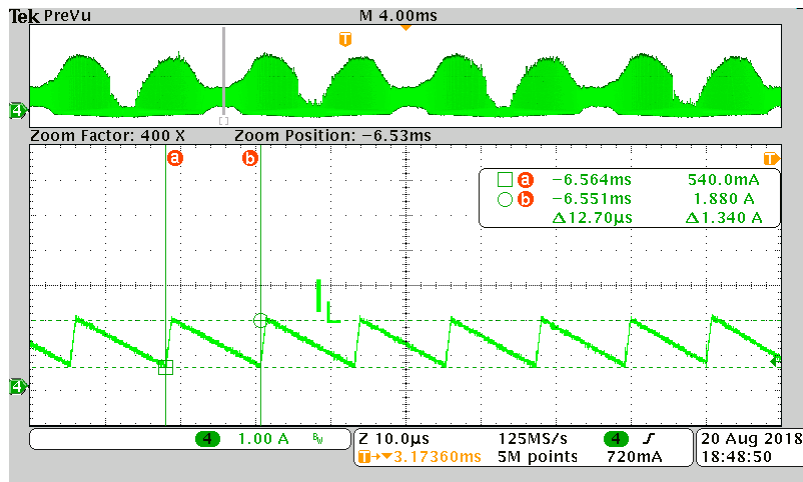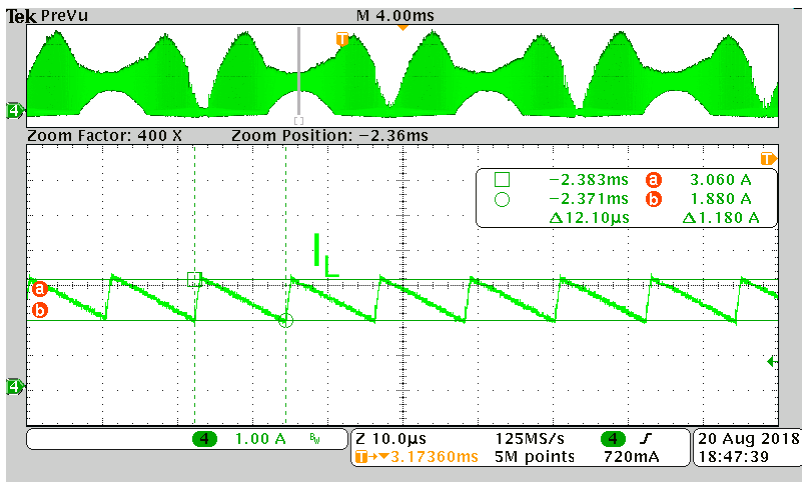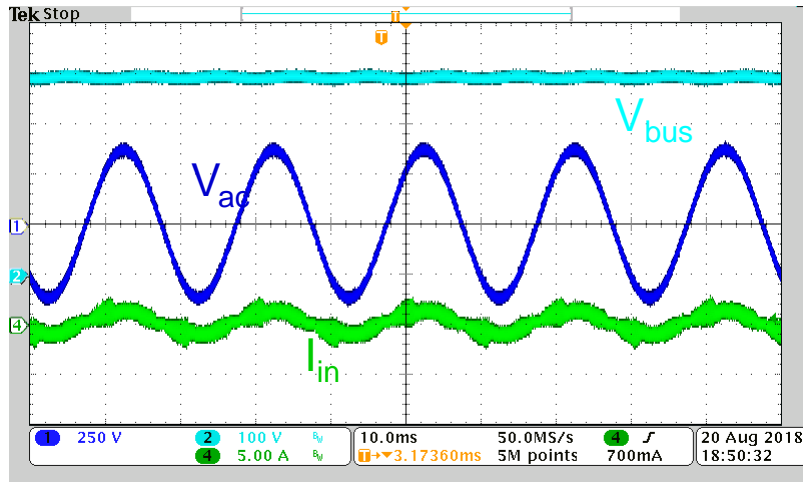Test Condition:  $V_{in}=265V_{ac}$ , 50% Load




# HR1210-Demo board and test results

## Steady State Waveform (LLC):


Test Condition:  $V_{in}=220V_{rms}$ ,  $I_o=20A$

Test Condition:  $V_{in}=220V_{rms}$ ,  $I_o=10A$

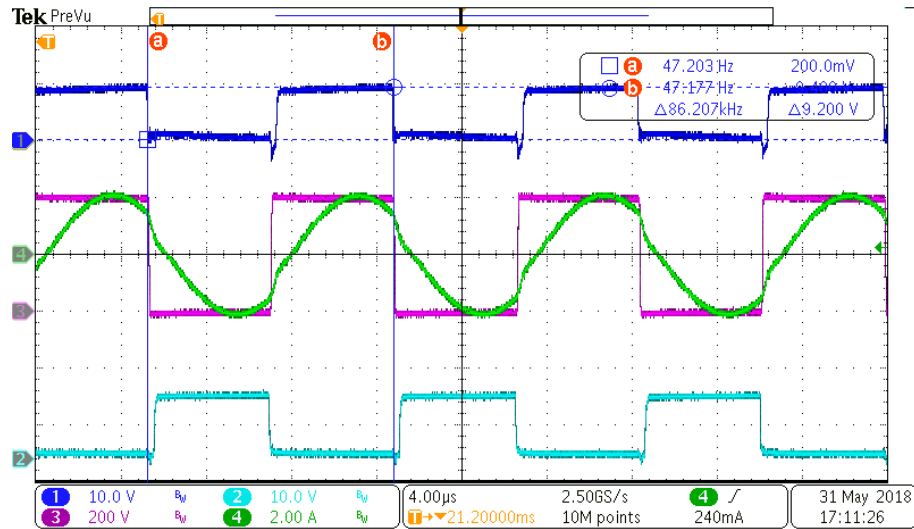

CH1:HSG

CH:LSG

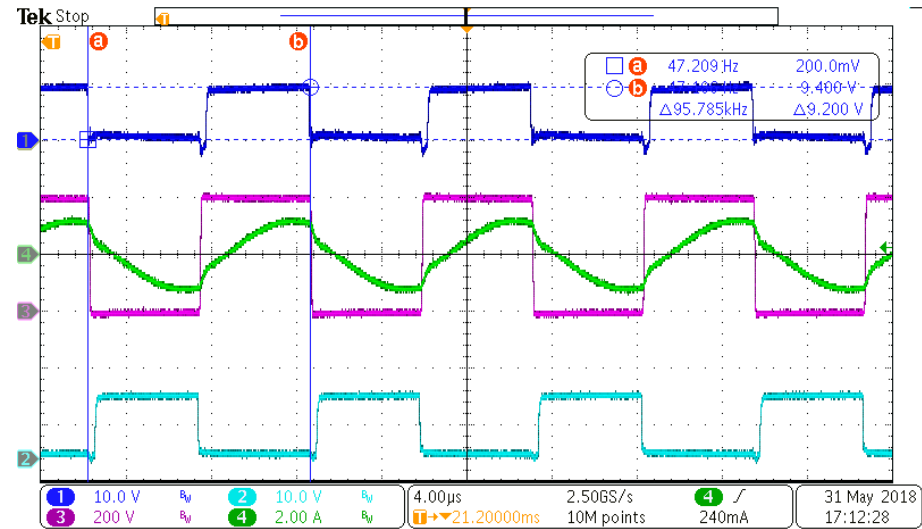

CH3:SW


CH4:Ir



# HR1210-Demo board and test results

## Steady State Waveform (LLC):


Test Condition:  $V_{in}=220V_{rms}$ ,  $I_o=5A$

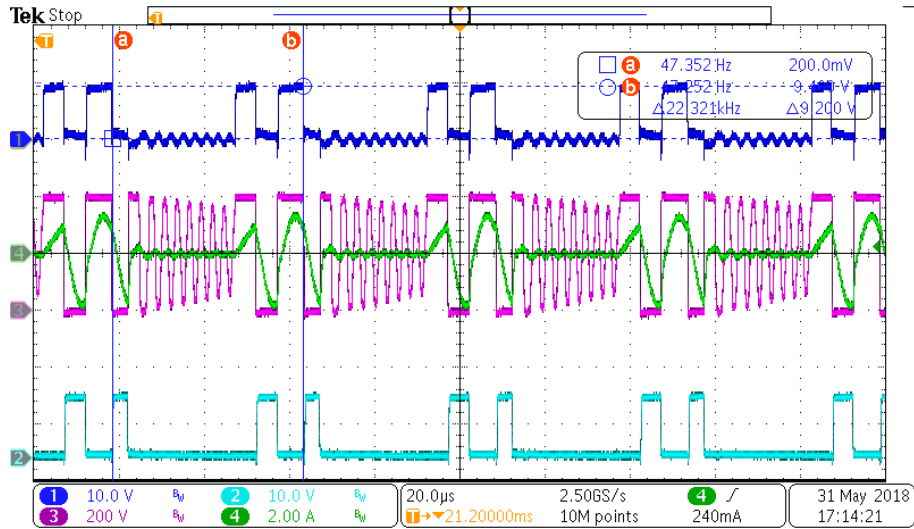

CH1:HSG

CH2:LSG

Test Condition:  $V_{in}=220V_{rms}$ ,  $I_o=0A$

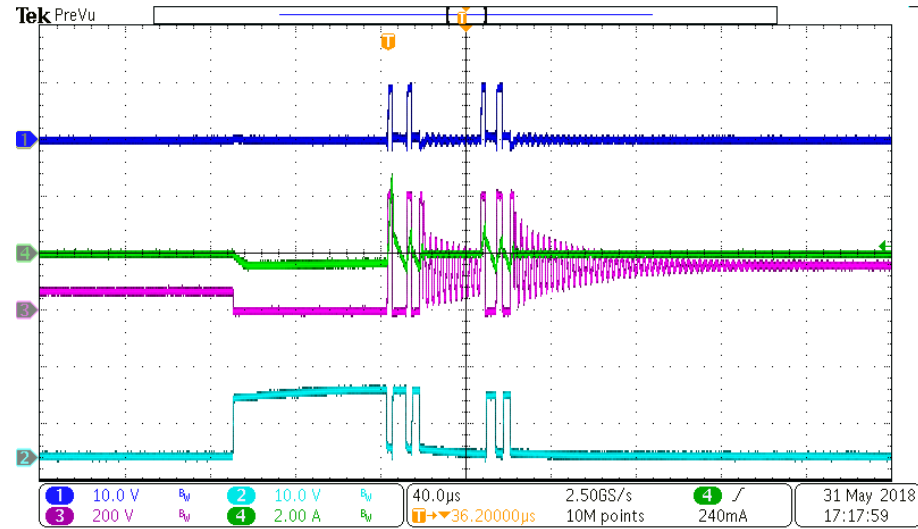


CH3:SW

CH4:Ir

# HR1210-Demo board and test results


## No Load Power Consumption:

| Vin                 | 85Vac   | 115Vac  | 230Vac  | 265Vac  |
|---------------------|---------|---------|---------|---------|
| No load consumption | 93.79mW | 94.30mW | 97.18mW | 99.47mW |

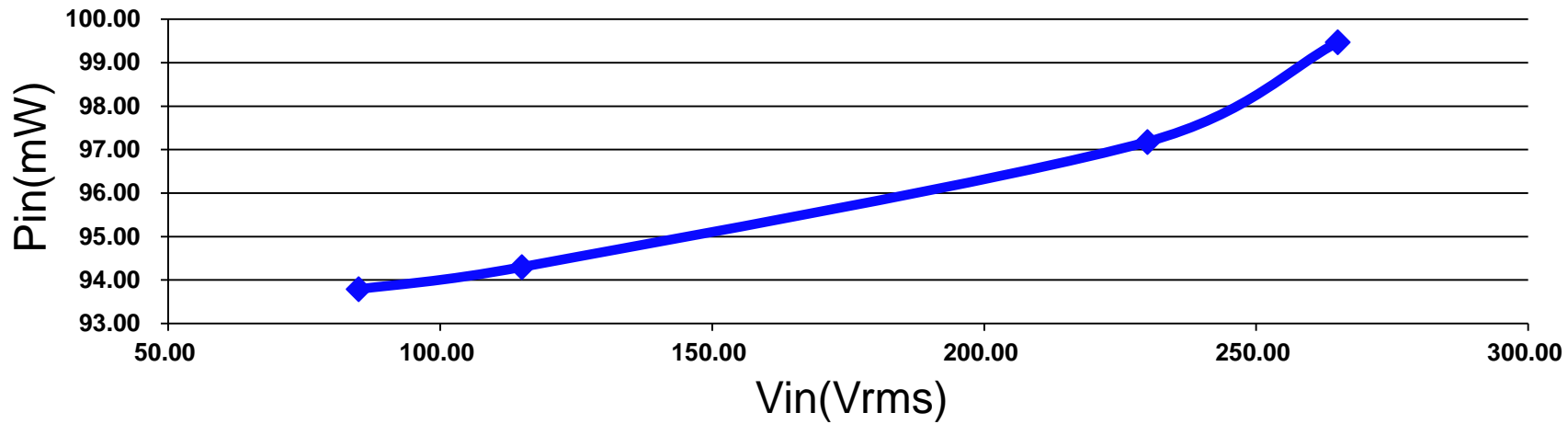

# HR1210-Demo board and test results

Total Efficiency:

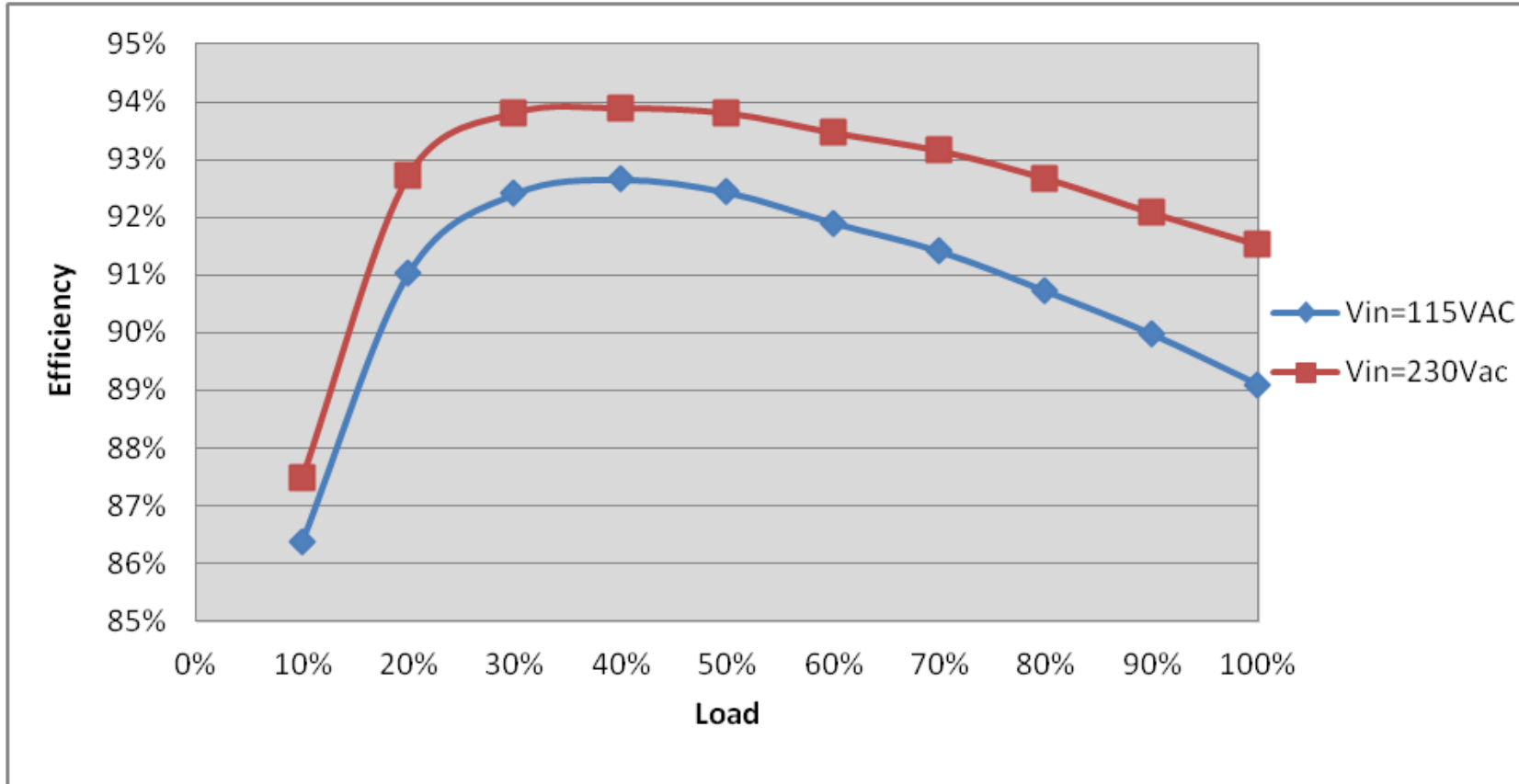


# Full Features Flyback Solution-HF500-X

## Features

- 700V FET integrated
- Fixed-frequency current mode control operation with built-in slope compensation
- Frequency Foldback down to 25kHz at light load condition
- Burst Mode for low standby power consumption
- Frequency jittering for a reduced EMI signature
- Over power compensation
- Internal high voltage current source
- VCC UVLO
- Programmable input B/O and OVP
- Over Load Protection with programmable delay
- Latch-off protection on TIMER pin
- OVP, OTP, SCP
- Programmable soft start

## Typical application

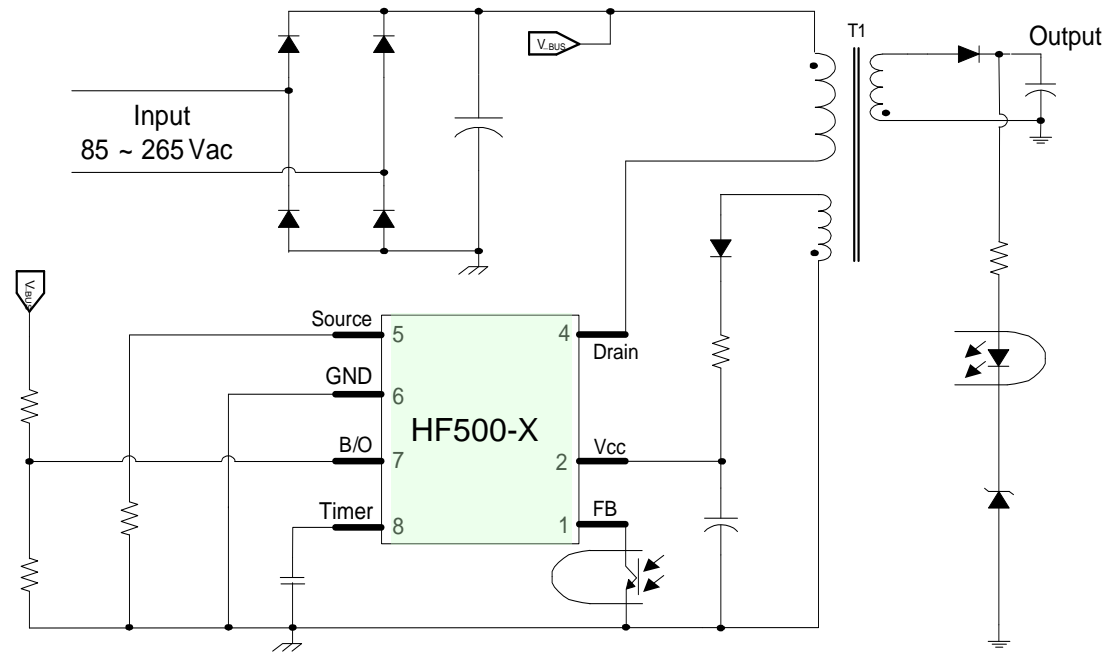

# Full Features Flyback Solution-HF500-X


## HF500-X Family

| Part No               | HF500-7  | HF500-15  | HF500-30  | HF500-40  |
|-----------------------|----------|-----------|-----------|-----------|
| Package               | SOIC8-7  | SOIC8-7   | DIP8-7    | DIP8-7    |
| Integrated Mosfet Ron | 12Ω/700V | 4.5Ω/700V | 1.4Ω/700V | 1.0Ω/700V |
| Power Rating Target   | 5-7W     | 7-15W     | 25-30W    | 35-40W    |


All parts released

# Full Features Flyback Solution-HF500-X

## ➤ Over Power Compensation

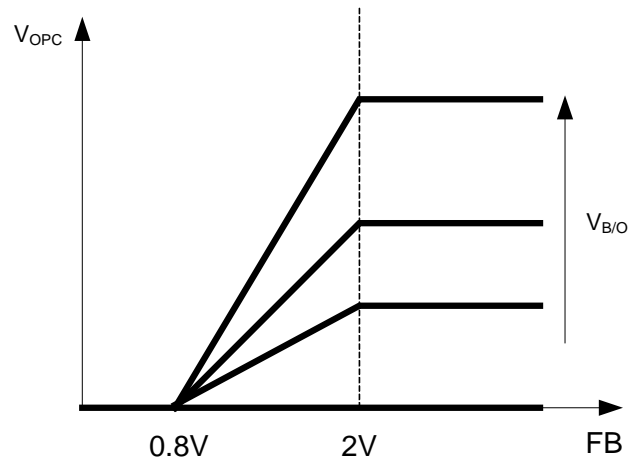

$$V_{OPC} = 94mV \cdot (V_{B/O} - 1.1)$$

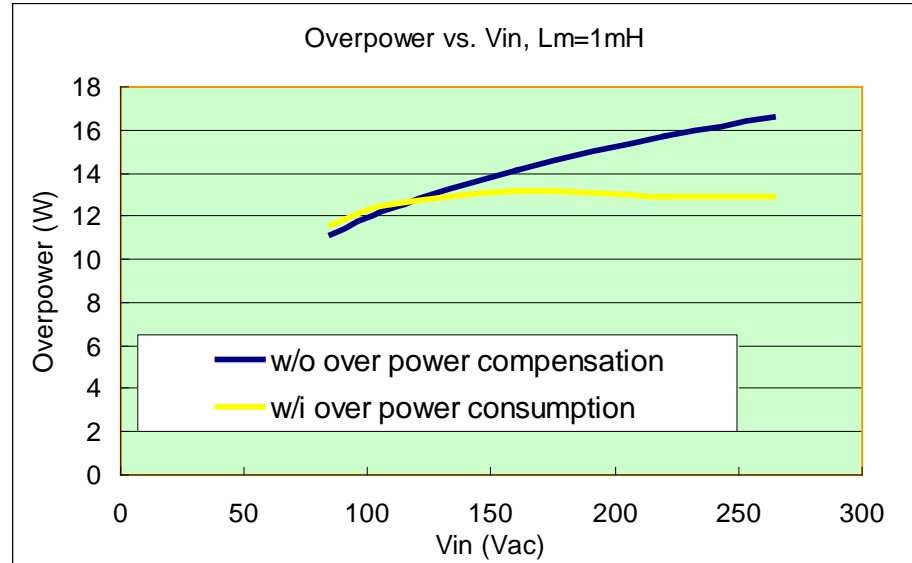


Based on 10W output design

The over power point can be kept similar both in low line and high line.

# Full Features Flyback Solution-HF500-X


## ➤ Frequency Foldback

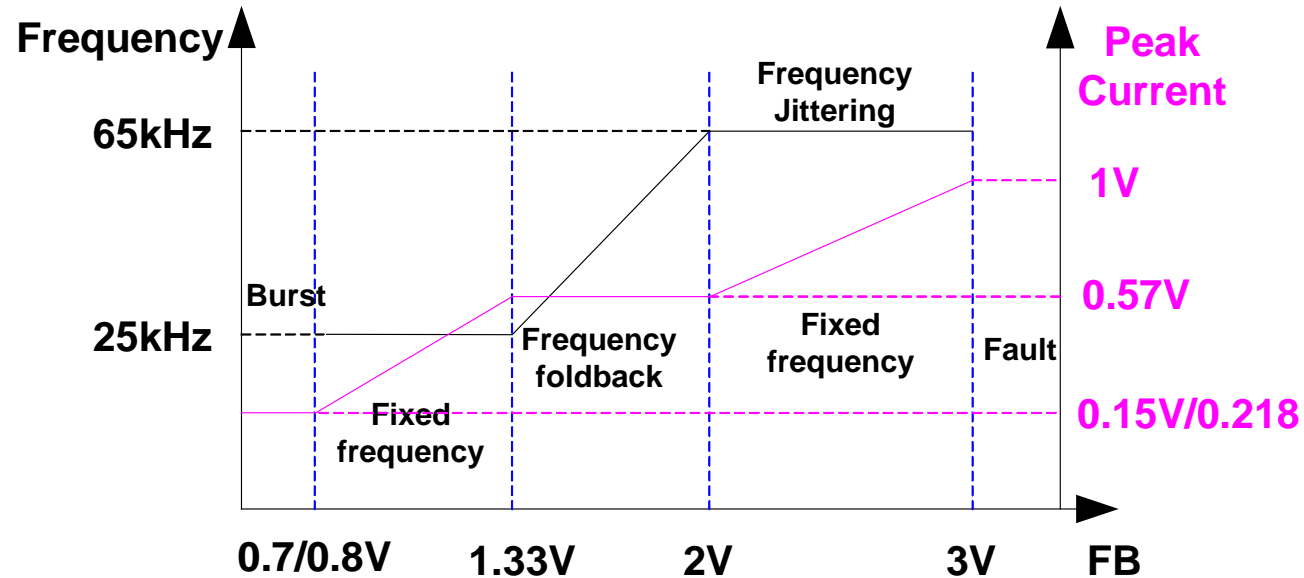

Frequency foldback at light load condition for higher efficiency and low no load power consumption.

# Full Features Flyback Solution-HF500-X

## ➤ Internal Slope Compensation

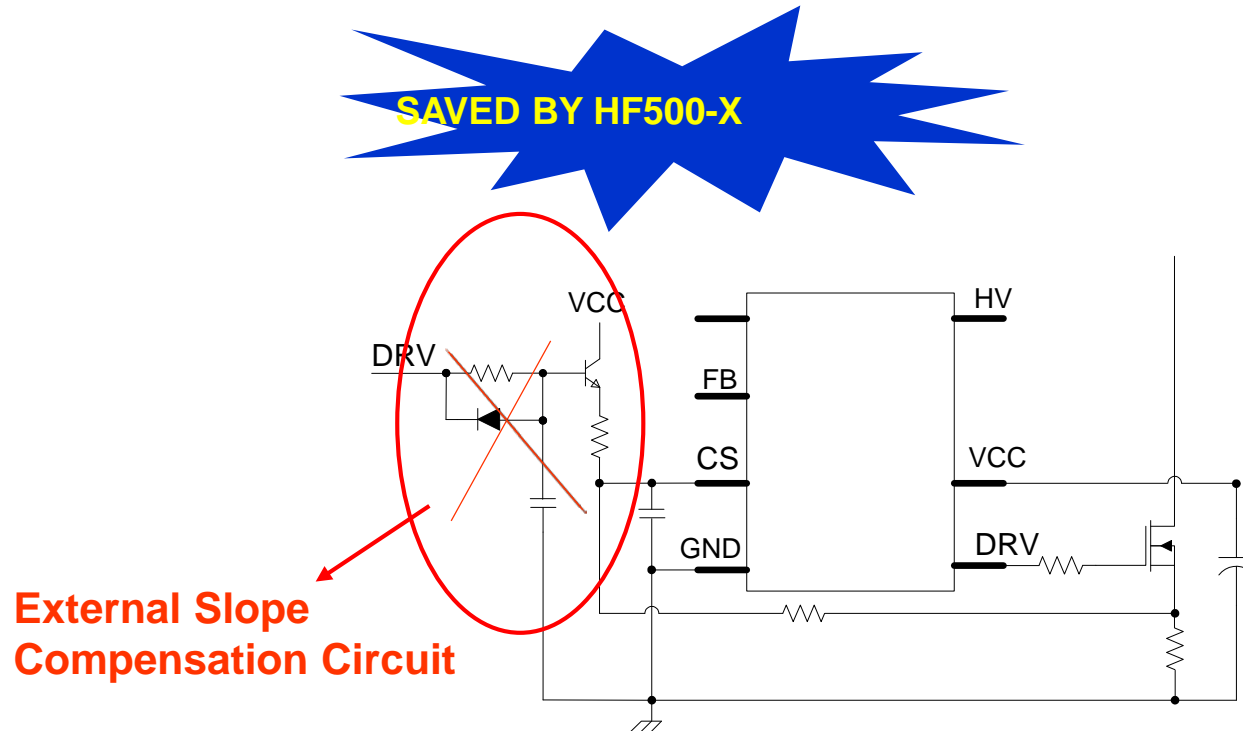


Converter keeps stable when duty cycle is larger than 0.5 in CCM.



# Full Features Flyback Solution-HF500-X

## ➤ Frequency Jittering


With Jittering

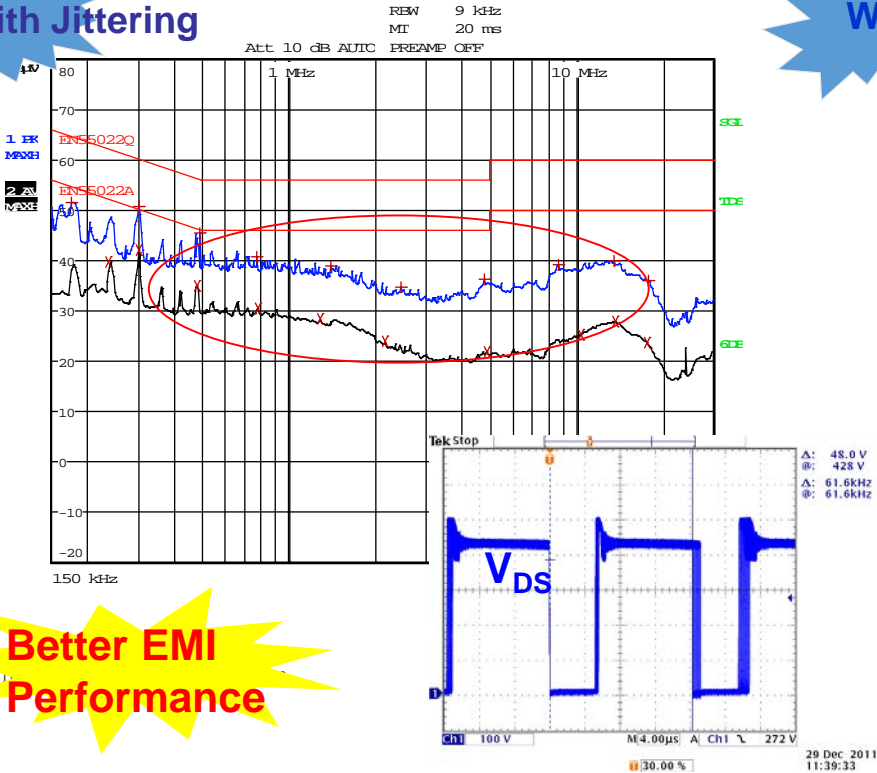

Better EMI Performance

65kHz±6.5%


Without Jittering

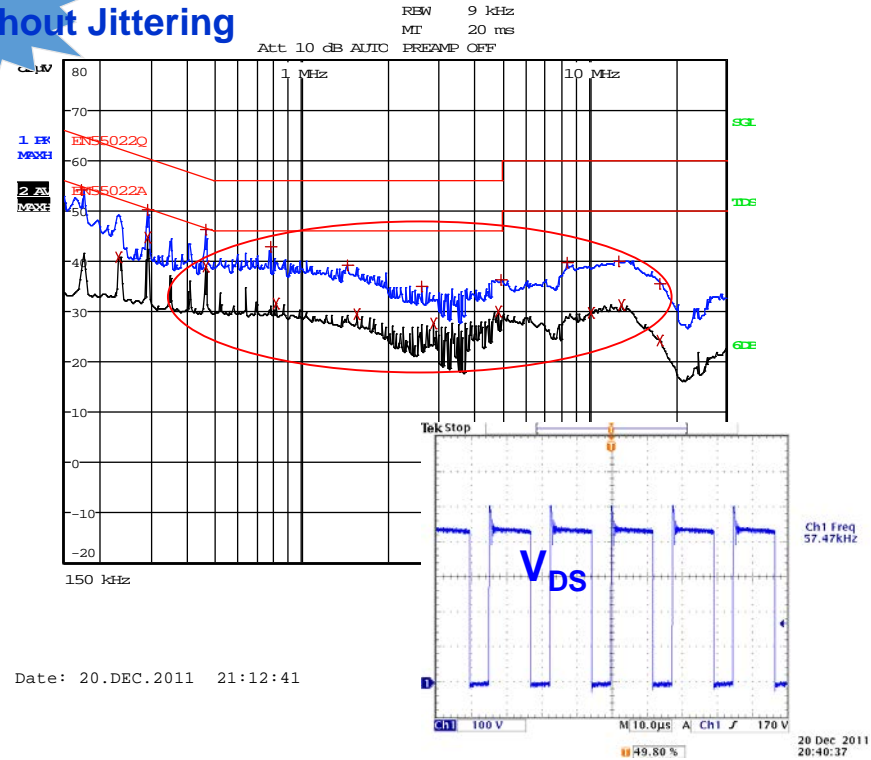

Frequency jittering which leads to better EMI performance.

# Full Features Flyback Solution-HF500-X

## ➤ Input Brown Out and OVP Function

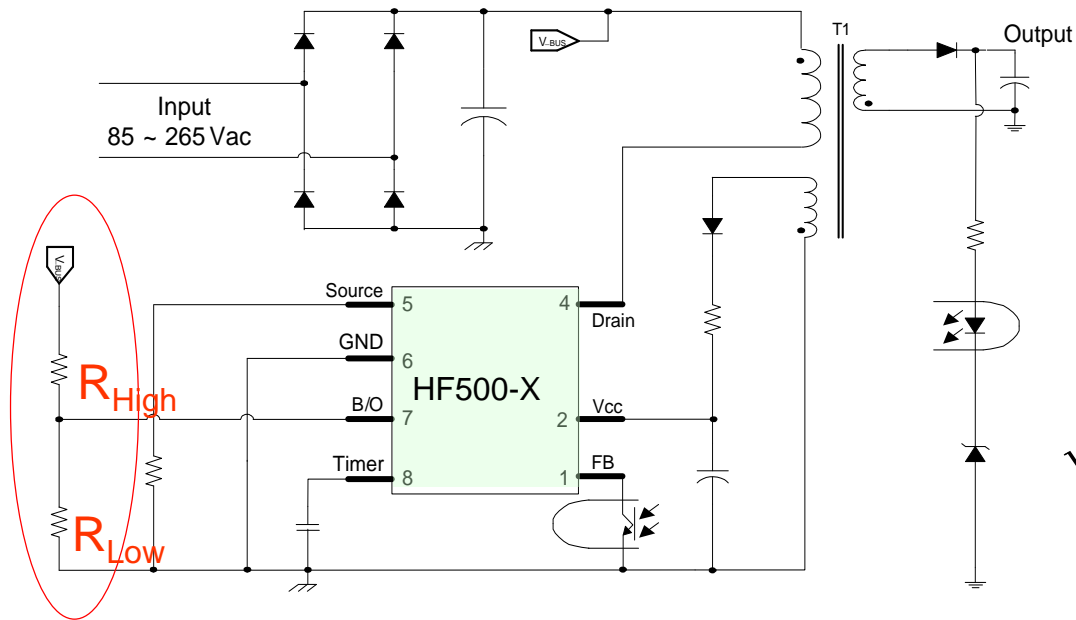

$$\sqrt{2} \cdot V_{AC\_Min} \cdot \frac{R_{Low}}{R_{Low} + R_{High}} > V_{B/O\_In}$$

$$\sqrt{2} \cdot V_{AC\_Max} \cdot \frac{R_{Low}}{R_{Low} + R_{High}} < V_{\_OVP_{B/O}}$$

By selecting the proper resistor divider, the input B/O and OVP can be realized by B/O pin.