

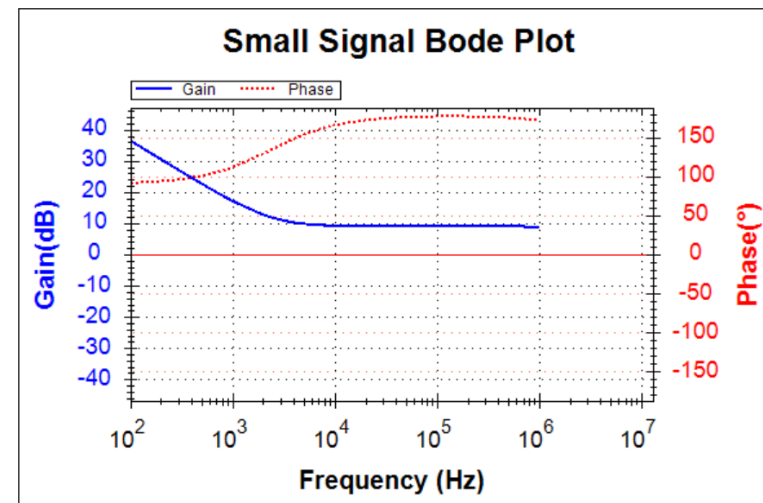
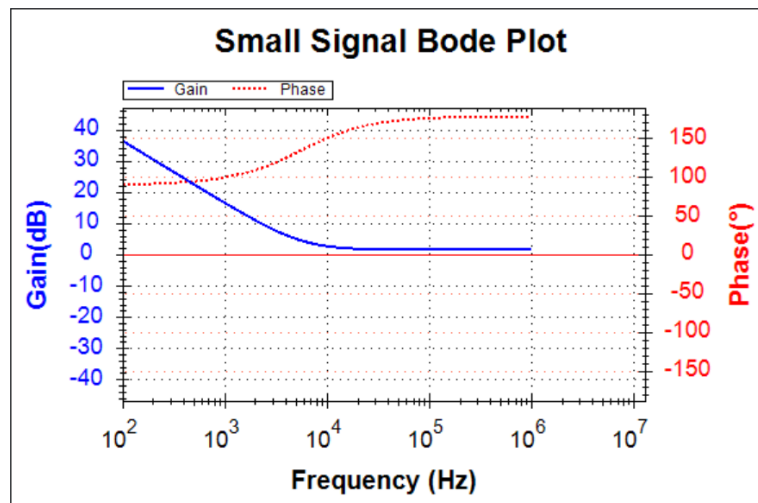
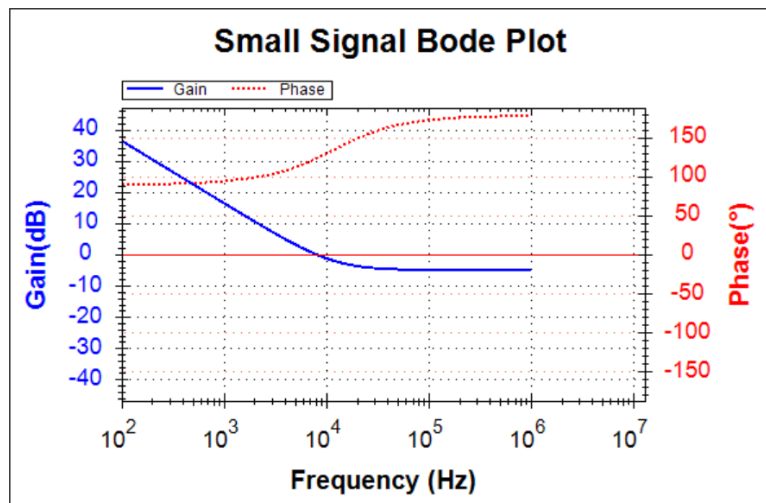
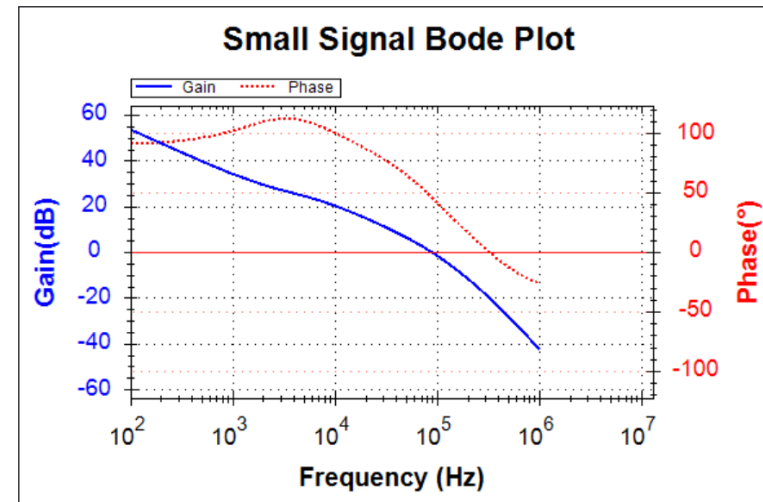


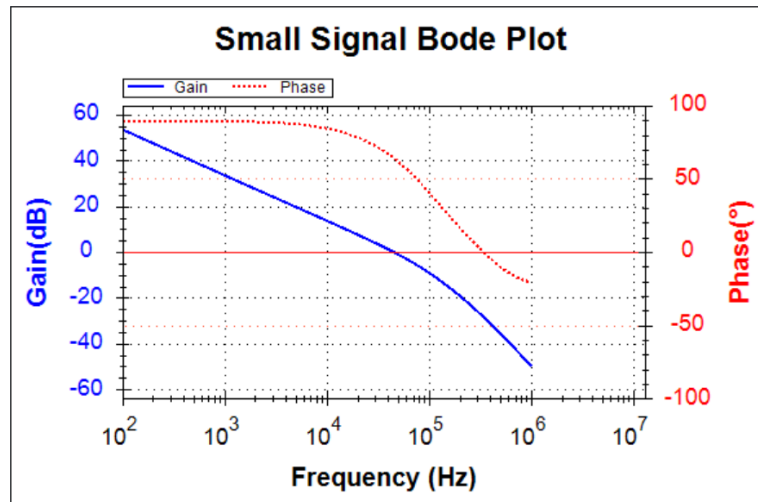

利用MPS在线仿真软件轻松掌握电源环路参数设计







2025

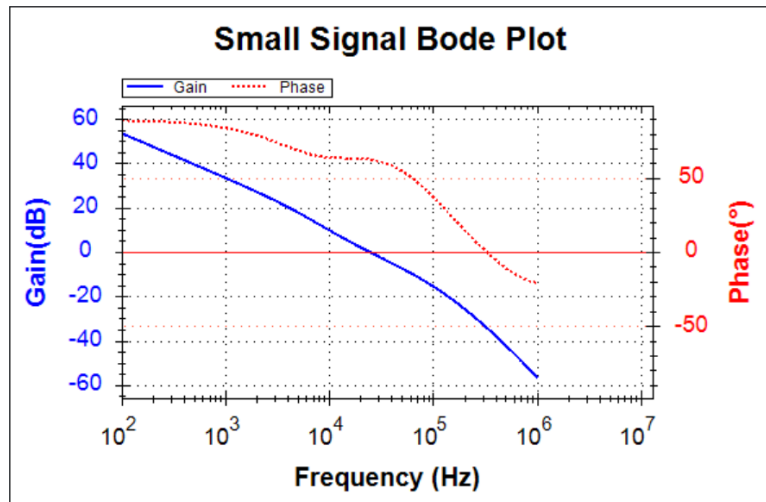

$R5 = 20k$

$R5 = 42.2k$







$R5 = 100k$

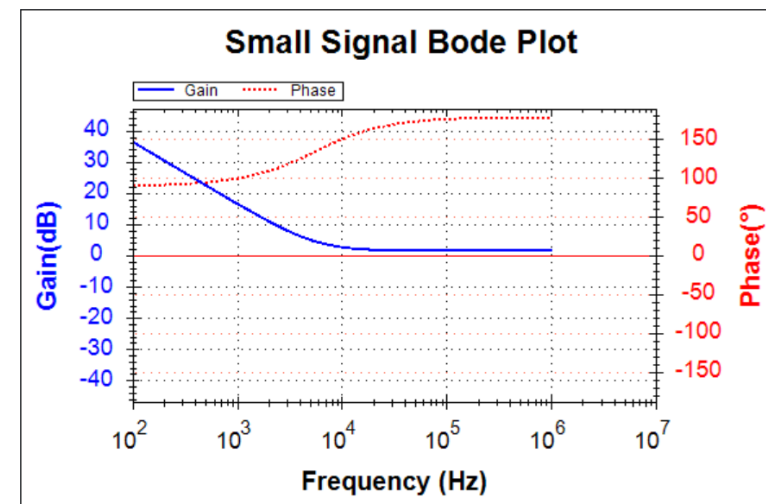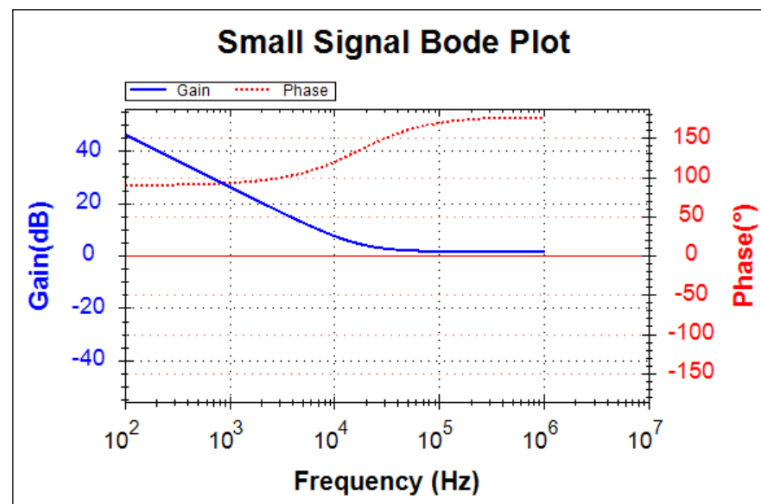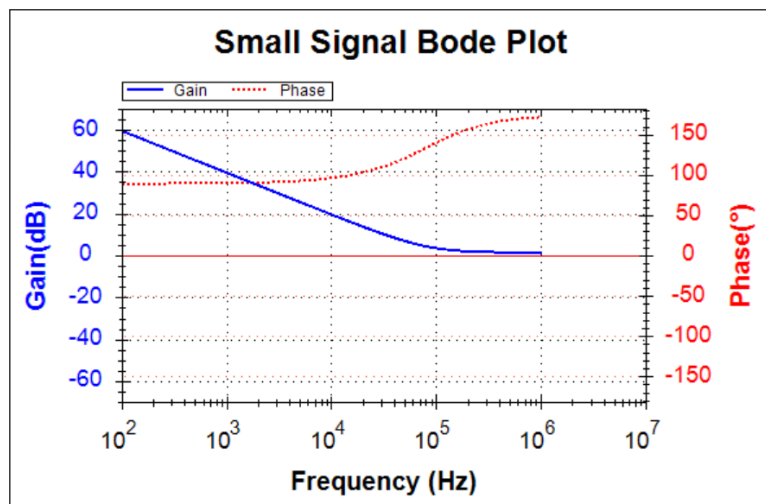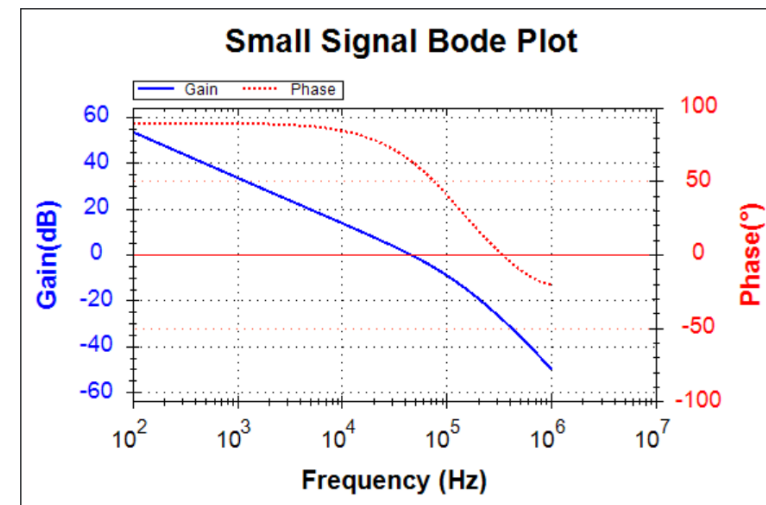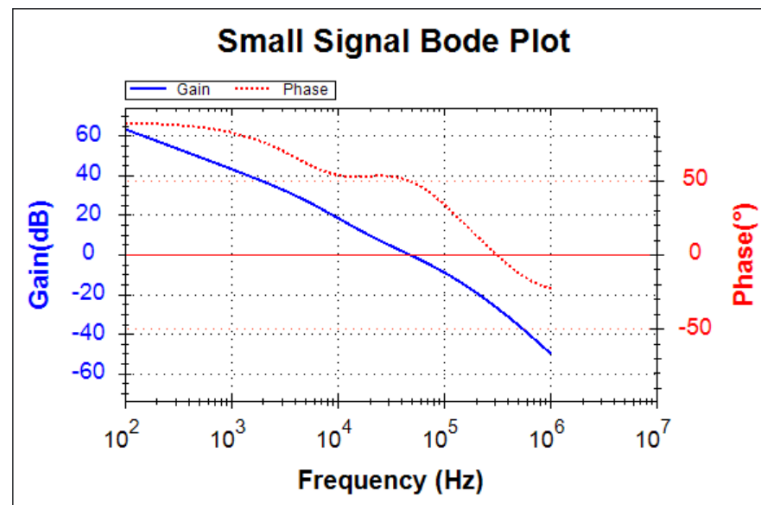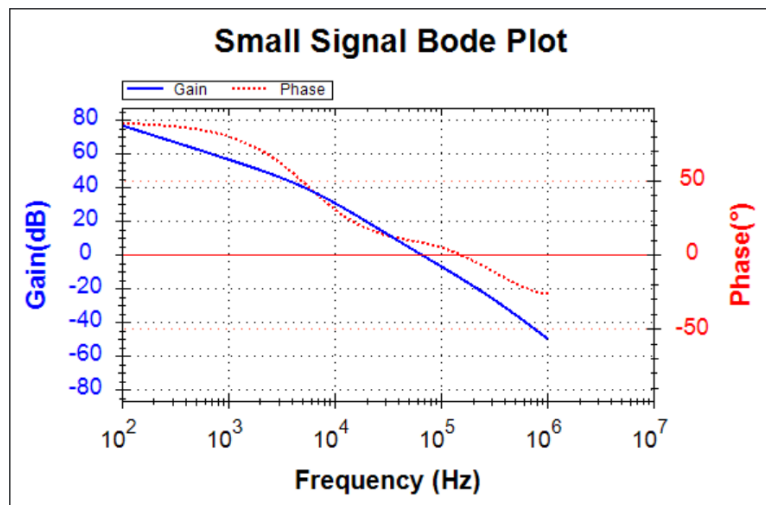

C7=47pF

C7=220pF

C7=680pF

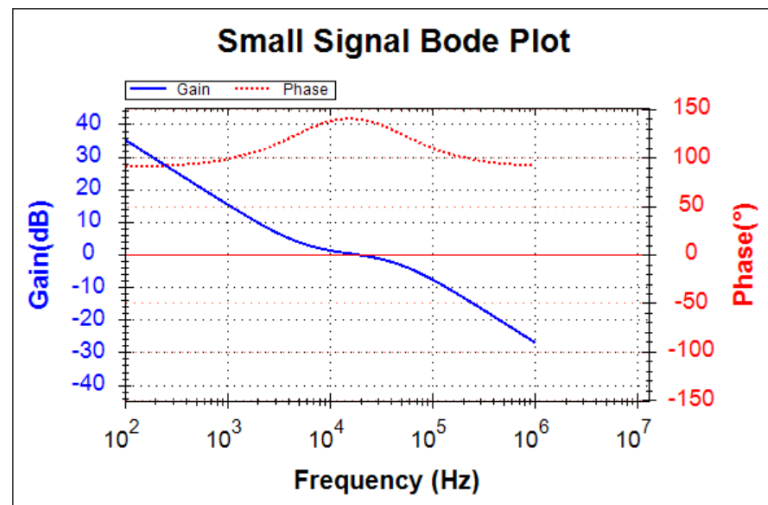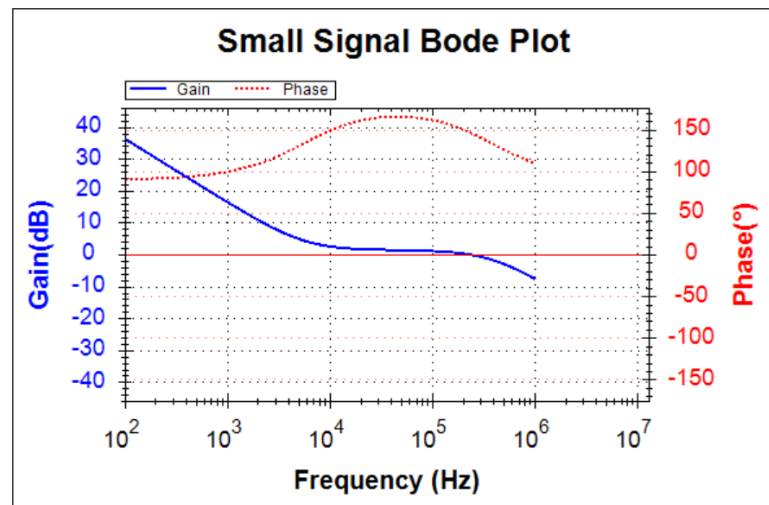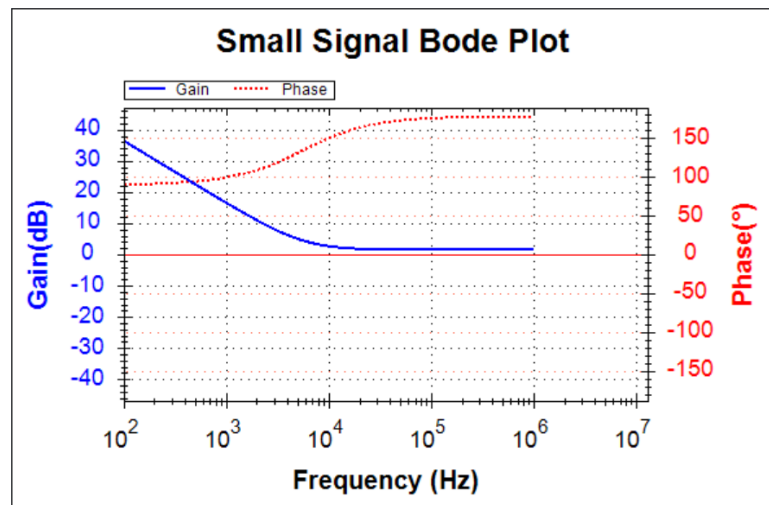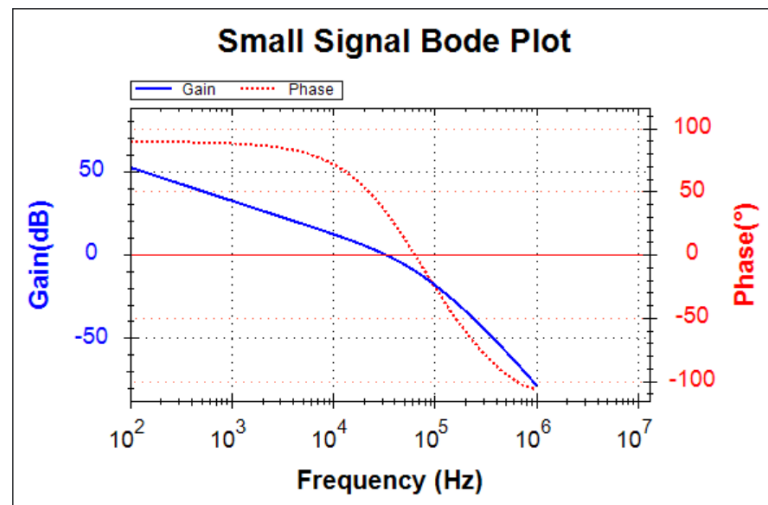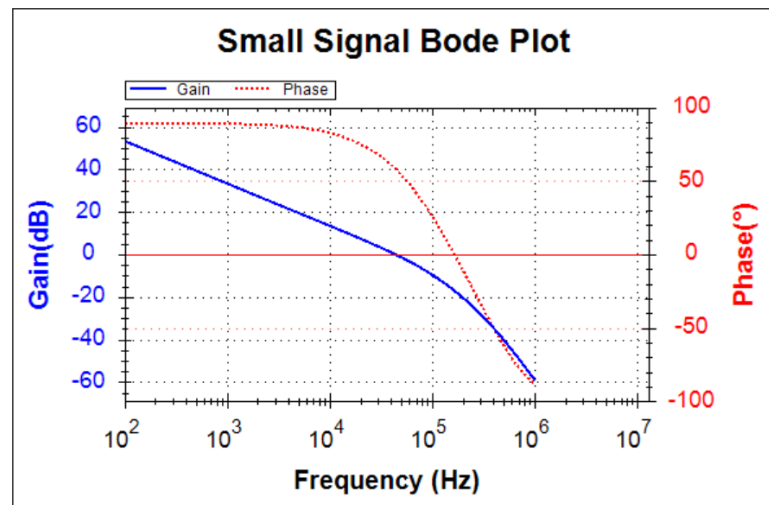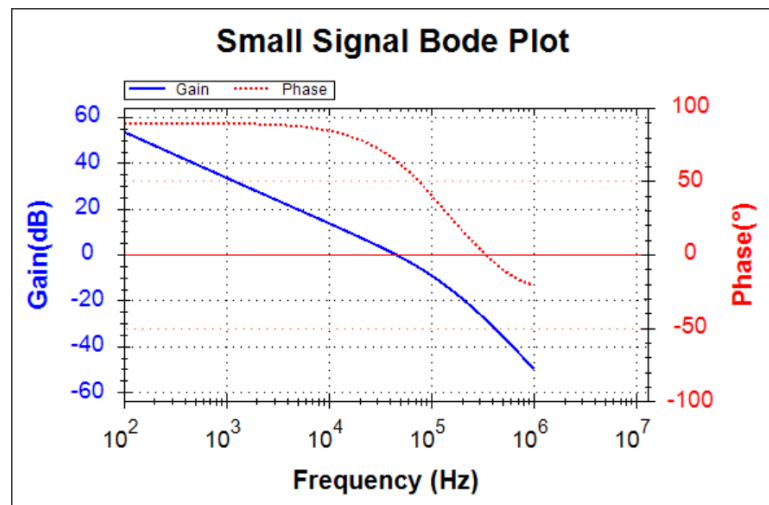

不加C8

C8=10pF

C8=100pF

Thank You !