

Introduction

Modern vehicles using 12V battery systems are subjected to a number of transient conditions. Some transients involve high-voltage pulses, while others may be under low-voltage conditions. Crank transients are low-voltage conditions that occur when a car engine starts, and the car battery drops several volts below its normal operating range for a brief time.

The requirements to maintain normal vehicle operation during crank conditions have become more stringent in recent years, and the need for more robust power solutions has become evident. Depending on the crank waveform — and the load that must be supplied by a specific supply rail — designing a system to meet these requirements can pose challenges to the designer. This article will explore a robust DC/DC converter that can sustain a wide range of automotive crank transients.

Designing for Extreme Starting Conditions

Extreme starting conditions must be considered when designing for 12V car systems (see Figure 1). Standards such as ISO 16750-2, ISO 7637-2, and Test Pulse 4 define a number of starting profiles for vehicles, including those that pertain to cold-crank conditions, warm-crank conditions, and similar waveforms.

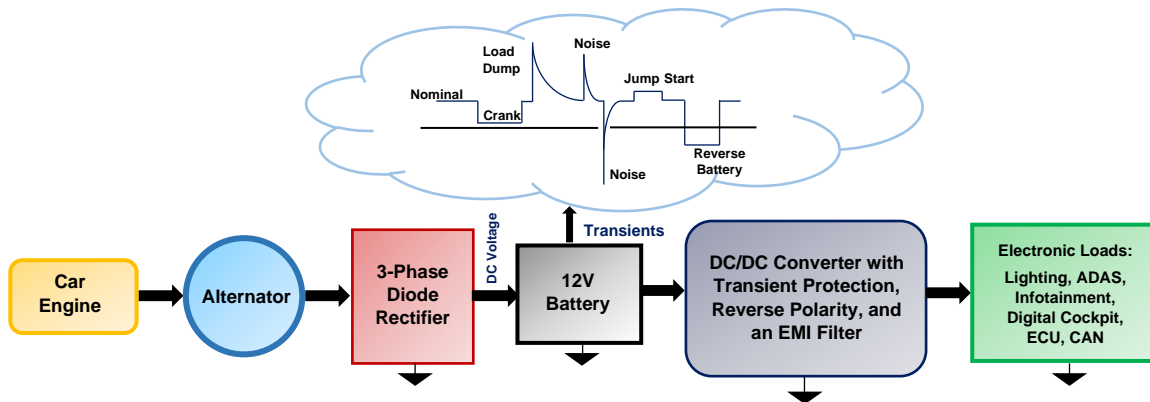


Figure 1: Typical Automotive Electrical System

Figure 2 shows an example of a cold-crank waveform with a starting profile defined by the ISO standards.

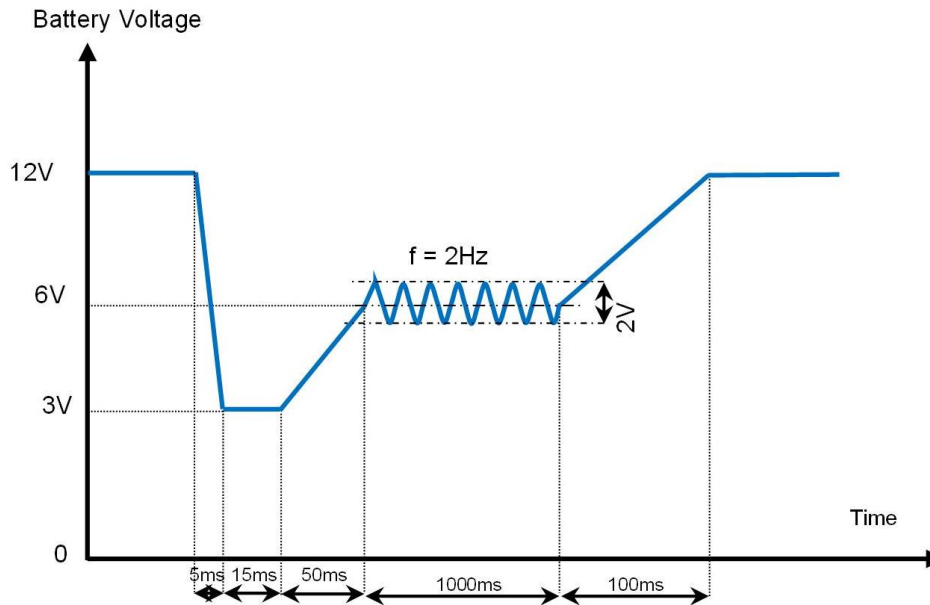


Figure 2: Example of Starting Profile for Cold Crank

The most challenging starting behavior for a vehicle is likely to occur during cold weather, when both the car battery and engine have been subjected to cold temperatures for a significant period of time. In this scenario, a high amount of battery current is needed to start the vehicle engine. A “cold-crank” condition describes when the battery voltage (V_{BATT}) drops very low after the starter draws a high current to turn on a cold engine. Under cold-crank conditions, V_{BATT} can drop to as low as 3V or 4.5V (depending on the vehicle’s electrical system) for 15ms to 50ms. During this event, there may be challenges if the power supply is required to regulate a particular voltage exceeding the input V_{BATT} . For example, a 5V or 10V supply cannot be stepped down, so it must be boosted from V_{BATT} during cold-crank conditions.

During a warm-crank condition, V_{BATT} also drops, though typically the drop is less severe than cold cranks. In general, a warm crank waveform may drop to as low as 6V or 7V, and it does not last as long as a cold crank. This is because the engine and battery are both at a relatively warm temperature, so the starter pulls less battery current to start the vehicle. Therefore, the battery’s overall voltage drop is lower since less current is pulled.

It is common for modern vehicles to support start/stop (or stop/start) to improve fuel economy. Start/stop is a warm-crank condition that occurs while driving, when the engine is warm. If the vehicle comes to a complete stop while the brake pedal is depressed, the engine shuts off. When the brake pedal is released, the engine is restarted. During a start/stop, critical modules in the vehicle must continue to operate without any change in performance.

Consider the example of a display control module (DCM) providing power and control to a display panel (see Figure 3).

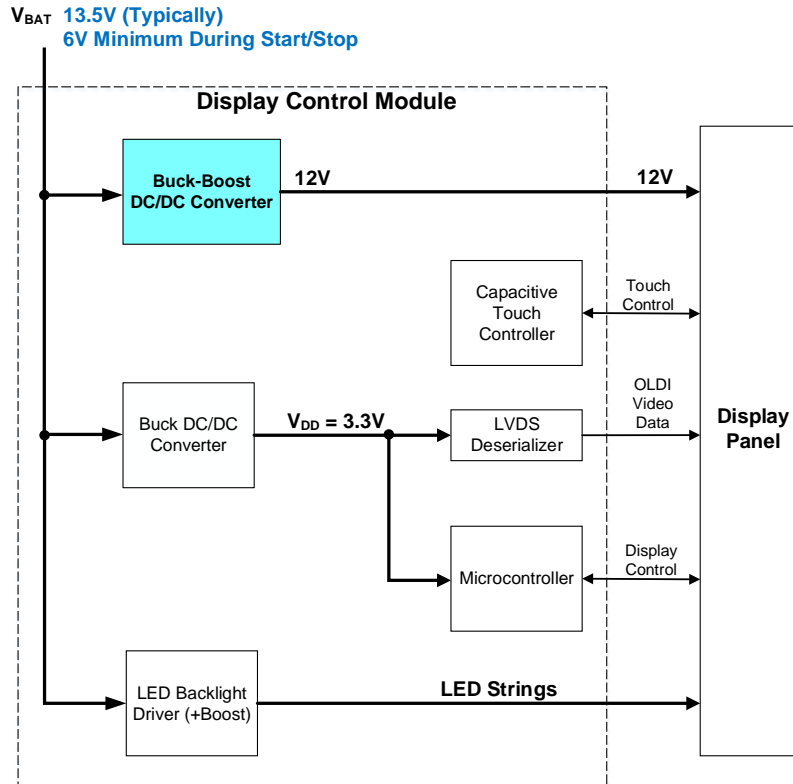


Figure 3: Display Control Module

The display panel could be a center stack display, rear seat display, or other display found in a modern vehicle. From a power standpoint, the DCM must always provide a regulated 12V supply to the display panel when the vehicle is running. 12V must also be supplied during start/stop, as the display panel cannot flicker, lose video, or stop functioning. During normal battery conditions, V_{BATT} is between 13V and 14V. However, during a warm crank start/stop, V_{BATT} drops to as low as 6V. To provide a constant 12V during these different conditions, a DC/DC converter must be selected that can step down (buck) a higher V_{BATT} , as well as step up (boost) V_{BATT} when it drops very low. To accomplish this, a [buck-boost DC/DC converter](#) is an excellent candidate to meet these requirements.

Closer Look at a Buck/Boost Converter During Crank Conditions

The [MPQ8875A-AEC1](#) is a 4-switch buck-boost converter that is capable of meeting automotive crank waveform requirements. It supports a wide 2.2V to 36V (up to 42V load dump) input voltage (V_{IN}) range, and has four integrated power MOSFETs. Figure 4 shows an application circuit when the MPQ8875A-AEC1 is configured to provide 12V of output at a 3A load. When V_{IN} exceeds the output voltage (V_{OUT}), the device operates in buck mode. When $V_{IN} < V_{OUT}$, the device operates in boost mode. When V_{IN} is almost equal to V_{OUT} , the device operates in buck-boost mode, and all of the switches commutate to provide 12V. For all modes, only a single inductor is required on the output to provide 12V regulation.

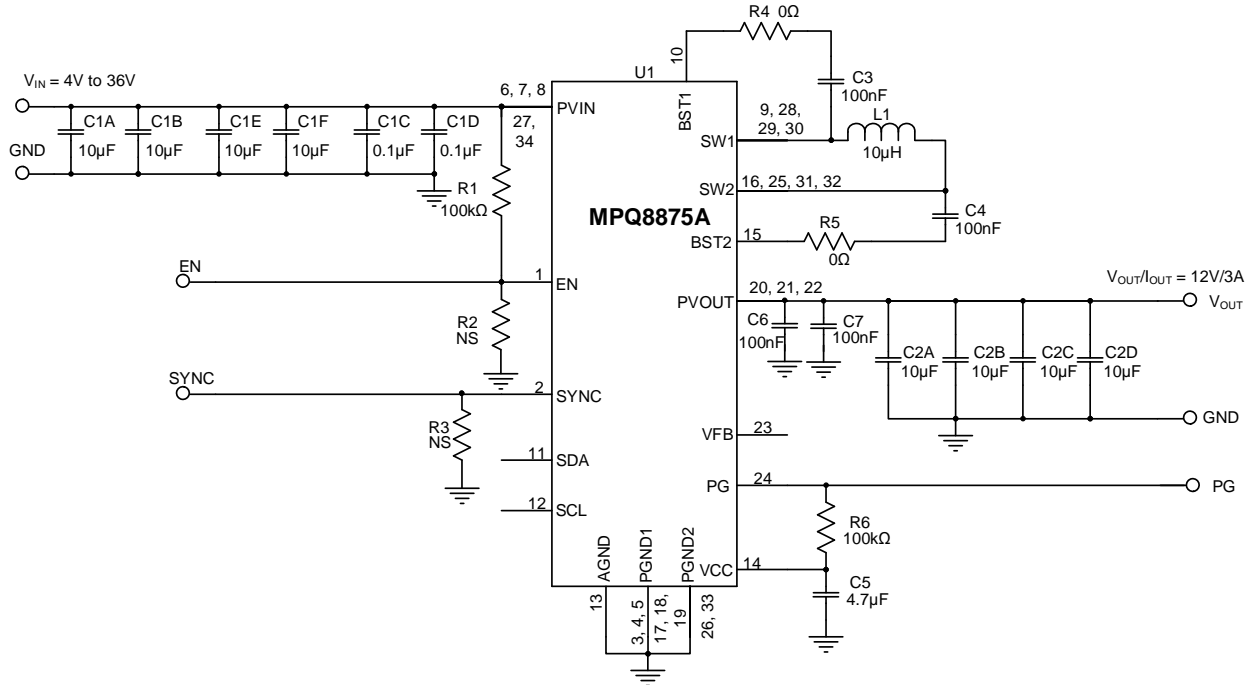


Figure 4: The MPQ8875A Provides 12V for Different V_{IN} Conditions

A DCM was designed using the MPQ8875A-AEC1, and it was tested for start/stop (or warm crank) using a starting profile defined by ISO 16750-2, Level IV for 12V systems. Figure 5 shows its behavior during this transient event, with waveforms for V_{IN} (in blue), V_{OUT} (in magenta), and the inductor current (I_L , in yellow). V_{IN} is the measured V_{BATT} input to the supply connector, which is subjected to a start/stop condition. V_{OUT} is the measured 12V regulated output, and I_L shows the measured inductor current. The load current for this test is 3A.

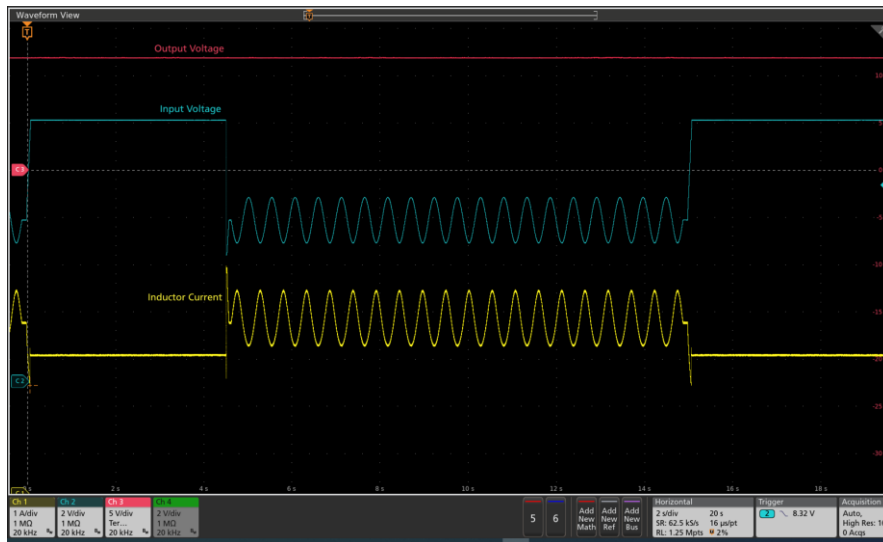


Figure 5: V_{IN} , V_{OUT} , and I_L Waveforms for the MPQ8875A During a Start/Stop Transient Condition

During warm-crank conditions, V_{IN} falls rapidly to 6V, where it remains for about 15ms. Then a low-frequency sinusoidal waveform, which represents an alternator ripple, occurs for several seconds; afterward, V_{IN} returns to its nominal voltage of about 13.5V. During this condition, the MPQ8875A-AEC1 continues to regulate its 12V output without any dropout. I_L increases sharply as V_{IN} falls, and creates a 4.9A peak current that lasts for about 15ms. I_L then fluctuates between 3.3A and 4.5A for about 10s. Finally, I_L drops to a nominal value of 3A when V_{IN} reaches the nominal V_{BATT} voltage.

Selecting an inductor (L1) with a proper current rating is crucial to proper operation, as it must meet not only the peak current during a warm crank, but also the peak current during cold-crank conditions. A soft saturating inductor is an excellent choice, and it should be able to handle peak currents for the duration of the initial voltage drop of the crank waveform, as well as peaks during the sinusoidal portion. In this situation, an inductor with a minimum saturation rating between 5A and 6A range is a great start. Measuring the inductor current's behavior during this test is a critical step in verifying that the inductor is sized appropriately. Do not overlook this step.

Conclusion

This article introduced some of the challenges when designing for automotive 12V battery transient conditions. Considerations for designing for extreme engine starting conditions, including cold cranks and warm cranks, were discussed. The [MPQ8875A-AEC1](#) was used as an example to design a buck-boost circuit, and it was able to withstand typical cranking waveforms while providing a stable, regulated V_{OUT} . In particular, the MOSFET and inductor current ratings are critical, especially when V_{IN} briefly drops much lower than normal conditions. As part of the circuit design and validation, V_{IN} , V_{OUT} , and the inductor current should always be measured to verify proper circuit operation for all input conditions.

Additional [automotive buck-boost](#) and [boost converter](#) solutions can be found on the [MPS website](#).