

Automotive EMI Demystified: Part 2

Pursuing an Ideal Power Supply Layout

Jens Hedrich

Senior FAE, Central Europe

December 2018



Jens Hedrich – Senior FAE, Central Europe



2010 – Present

- MPS Senior FAE since 2010, working with industrial and automotive customers on power supply design.
- Particular specialty focus on layout and EMC topics, including frequently visiting automotive EMC lab for EVB testing / optimization and improving MPS automotive/industrial EVB's EMC performance

1999 – 2010 FAE at Linear Technology

- Support industrial and automotive customers; Support LTC's EMC clean EV-Board DC1212 (LT3480/LT3685)

1995 – 1998

- Hardware design engineer at Nokia Mobile Phones; Worked on early automotive Telematic solution with e-call and emergency battery; EMC support

Agenda

The Motivation

Initial PCB Real Estate Planning

How Best to Utilize Each Layer in the PCB

Copper Under the Inductor or Not: the Classic Debate


EMI-Optimized Schematic and Layout Case Study

Frequently Asked Questions About Layout for EMI


Open Q&A

Our Motivation: Avoiding This Result

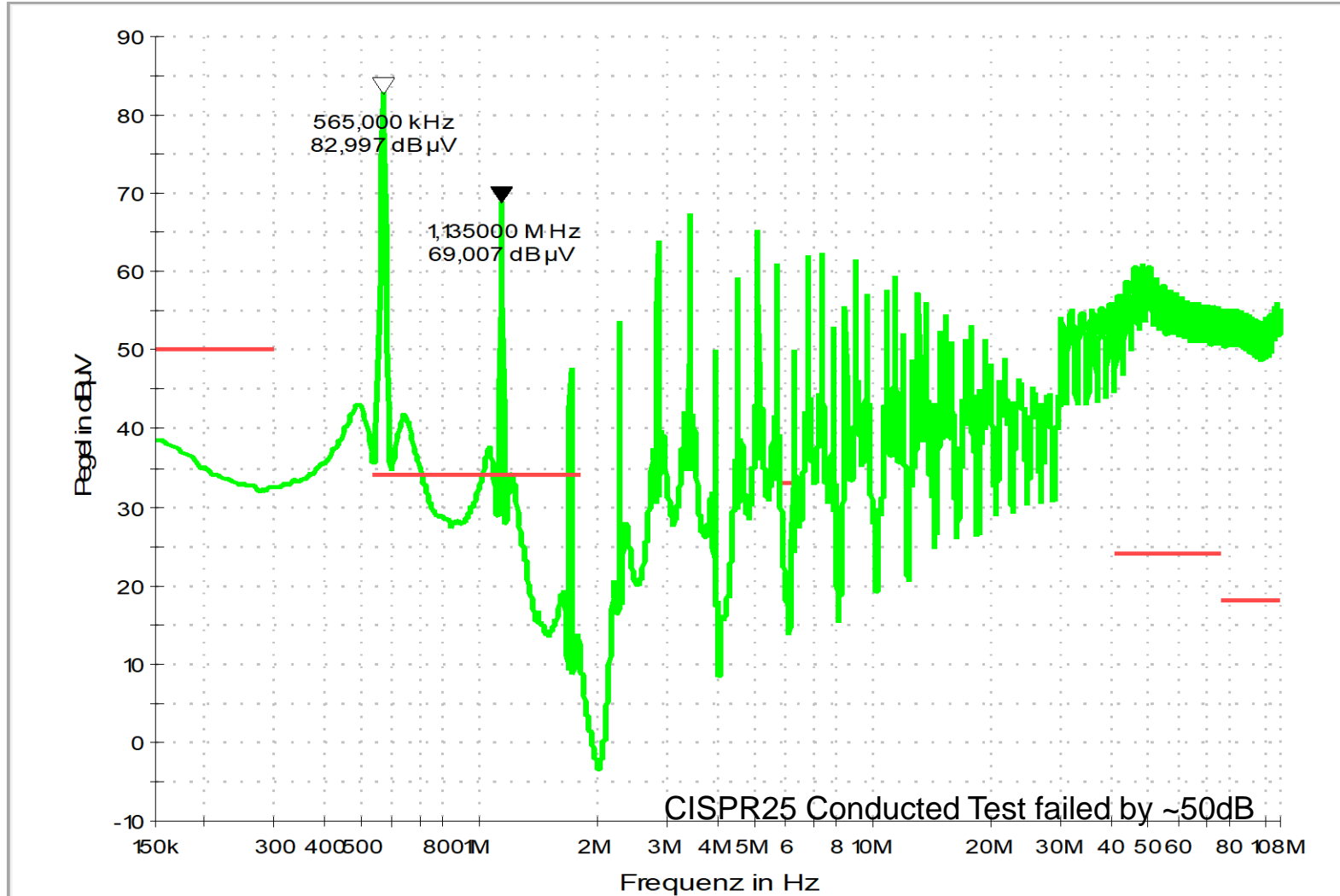EMC Test Result of a Bad* PCB Without Filter





 30V / 7A Sync. Buck Board Optimized for Thermal Performance but not EMC



- Large SW area
- No solid GND plane
- Only two Layer
- NO EMC Filter

A Much Better Board with EMC Filter

 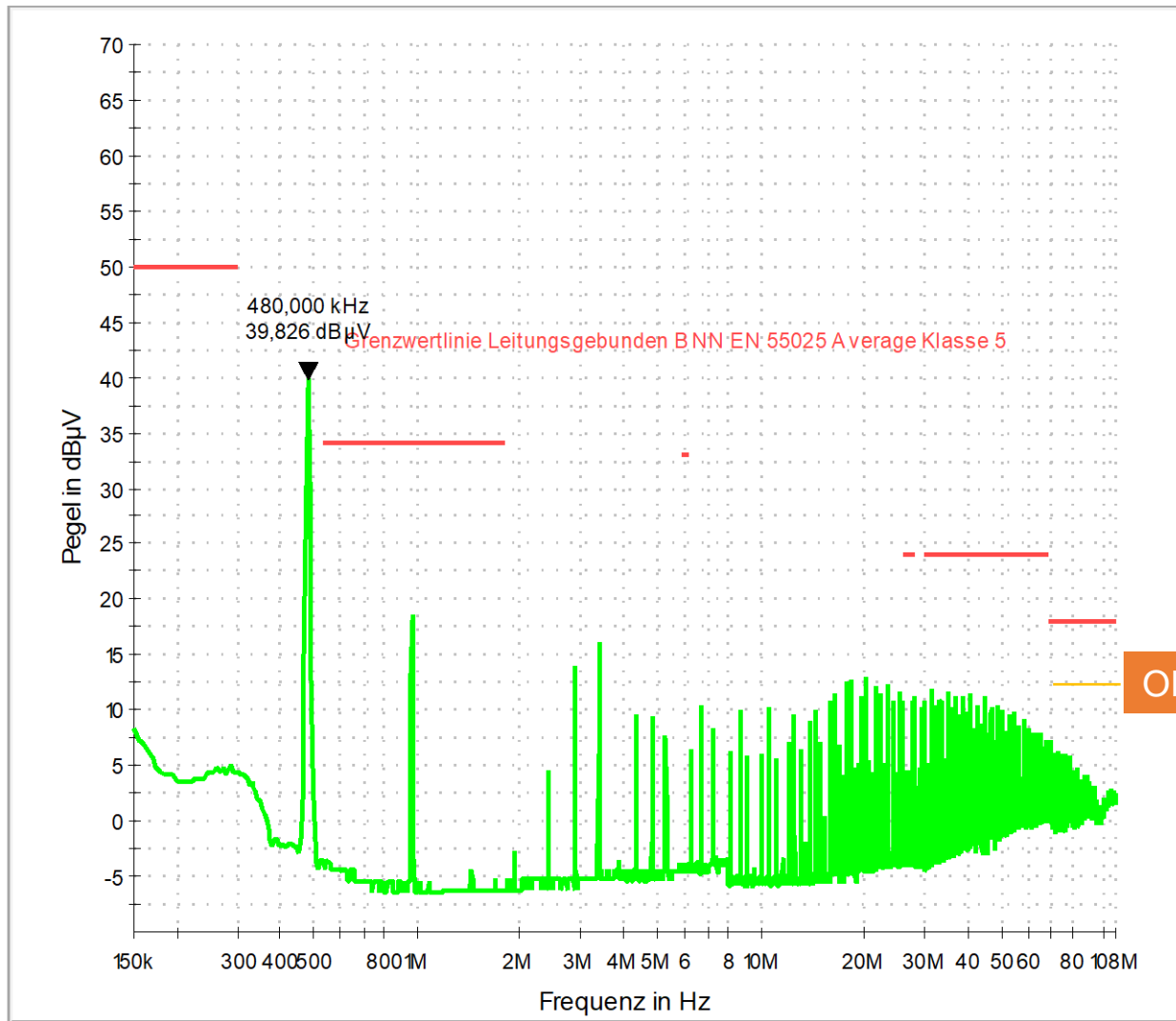


Input EMC Filter on Bottom side of PCB

Single stage filter with 10µH 5x5x5 and 10µF 1210




A Much, *Much* Better Board

100kHz to 30MHz 9kHz RBW

 


30MHz to 108MHz 120kHz RBW

 

EVQ4430-00A 480kHz Spread Spectrum



Learn how to get to this level

 


Filter on bottom side

Two stage filter with small components



Reminder From Last Webinar: Magnetic Antennas

 
On AC current loops like hot loops, there is still an increased current density at the outside boundary of the loop



Good EMC Design Starts with Initial PCB Real Estate Plan

Initial PCB Real Estate Plan

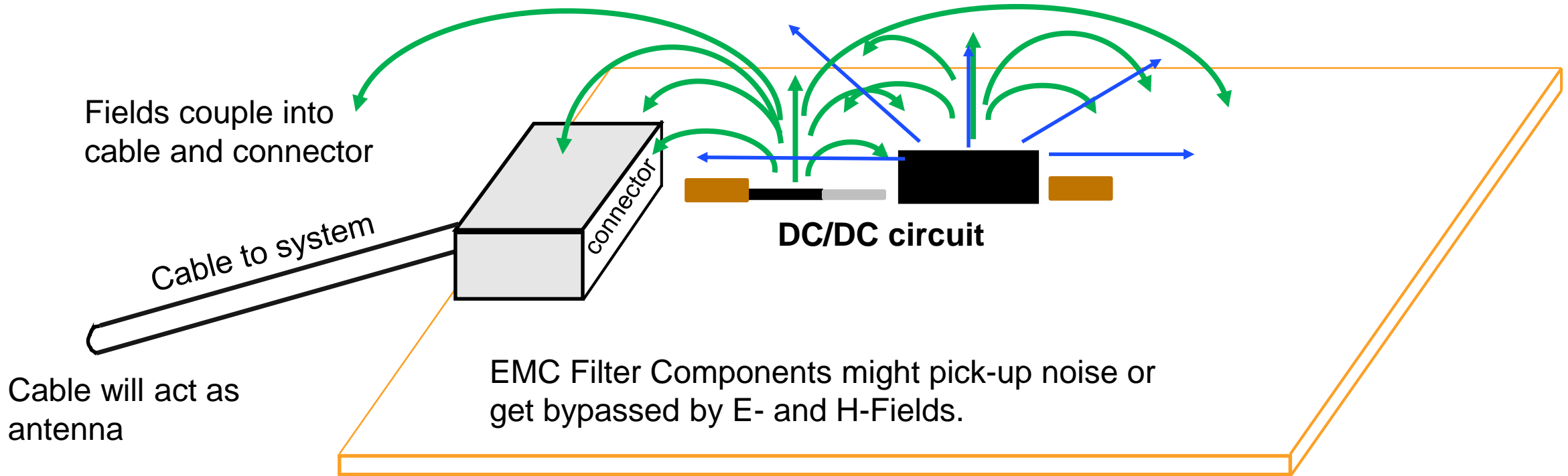
H- and E-stray fields from DC/DC (simplified)



EMC Problem


Initial PCB Real Estate Plan: Where to Place the DC/DC?

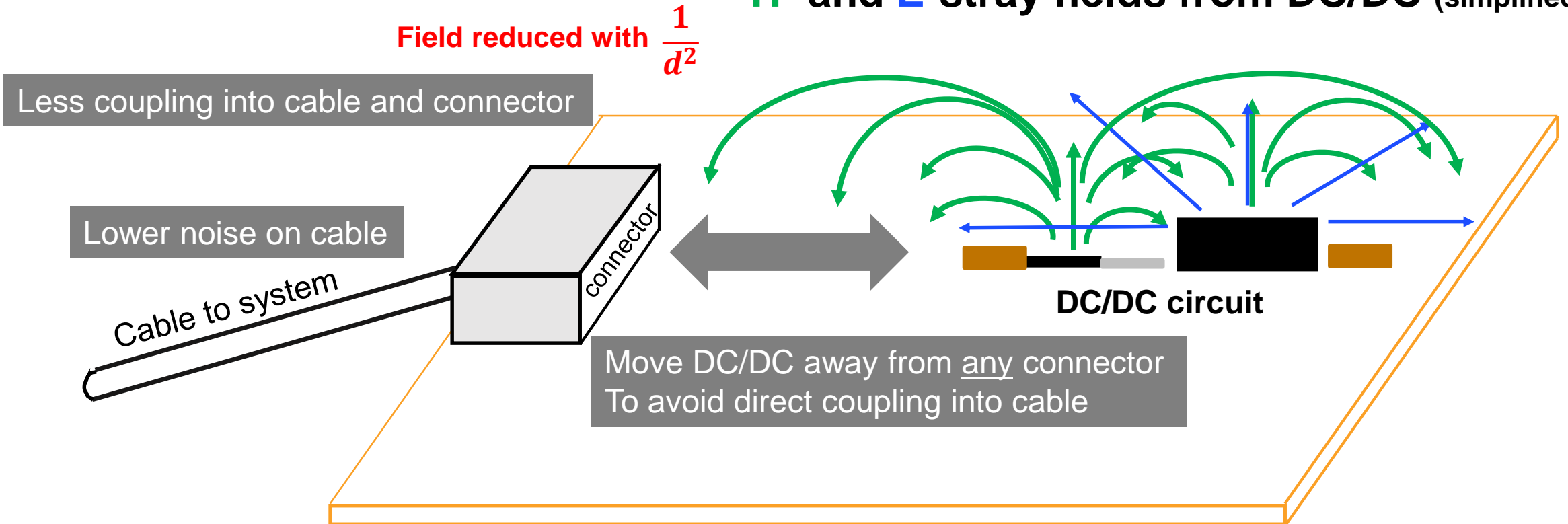H- and E-stray fields from DC/DC (simplified)



- EMC filter components must be placed close to connector
- In case of two side assembly, EMC filter on opposite side with respect to DC/DC Converter gives best results

 
Coupling From SW-Node Into Other Circuits: Single Side Assembly




Single Side Assembly : Placing a Shield



A Heat-Sink can also act as a Shield

 


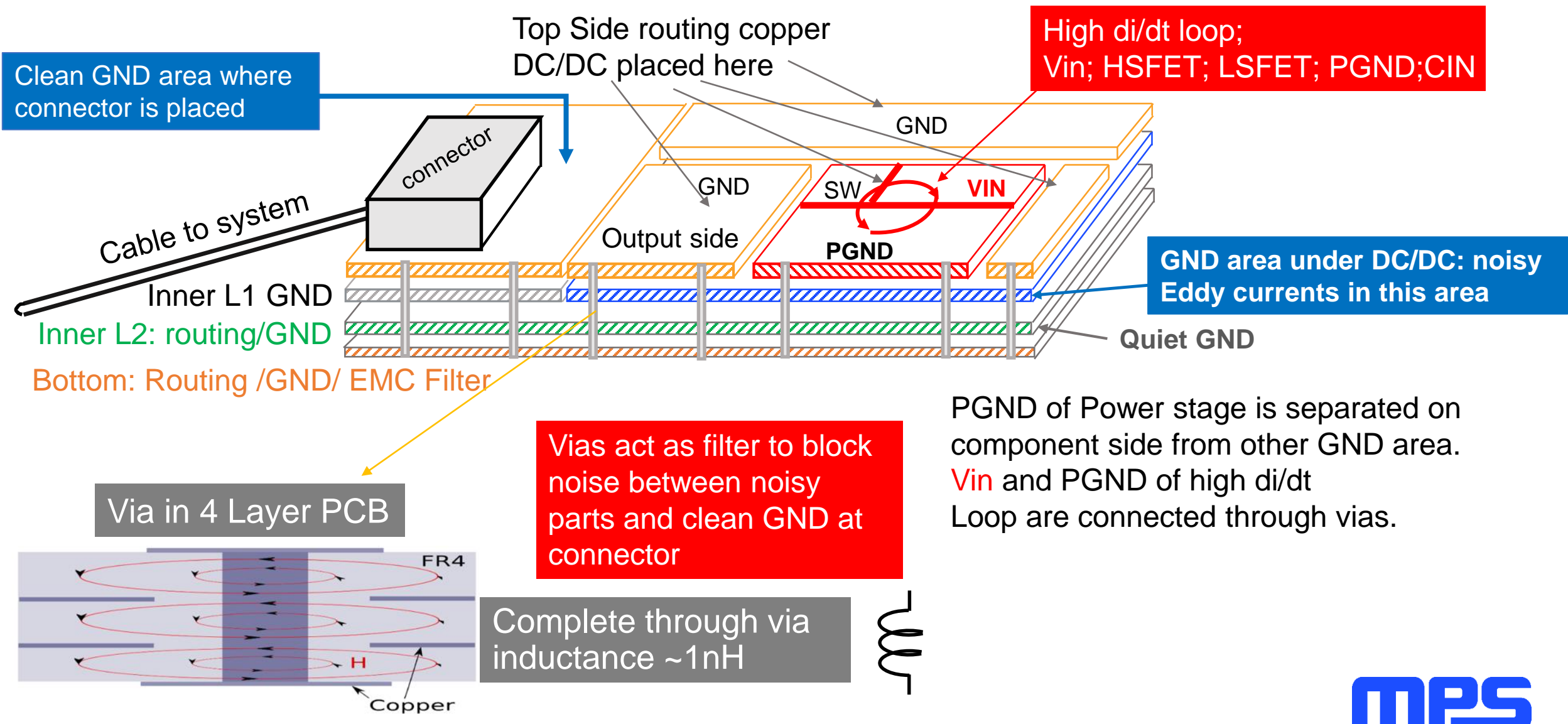How to Utilize a Multi-Layer PCB for Best EMC Performance?



Look at the PCB In 3-Dimensions: Simplified Equivalent Representation

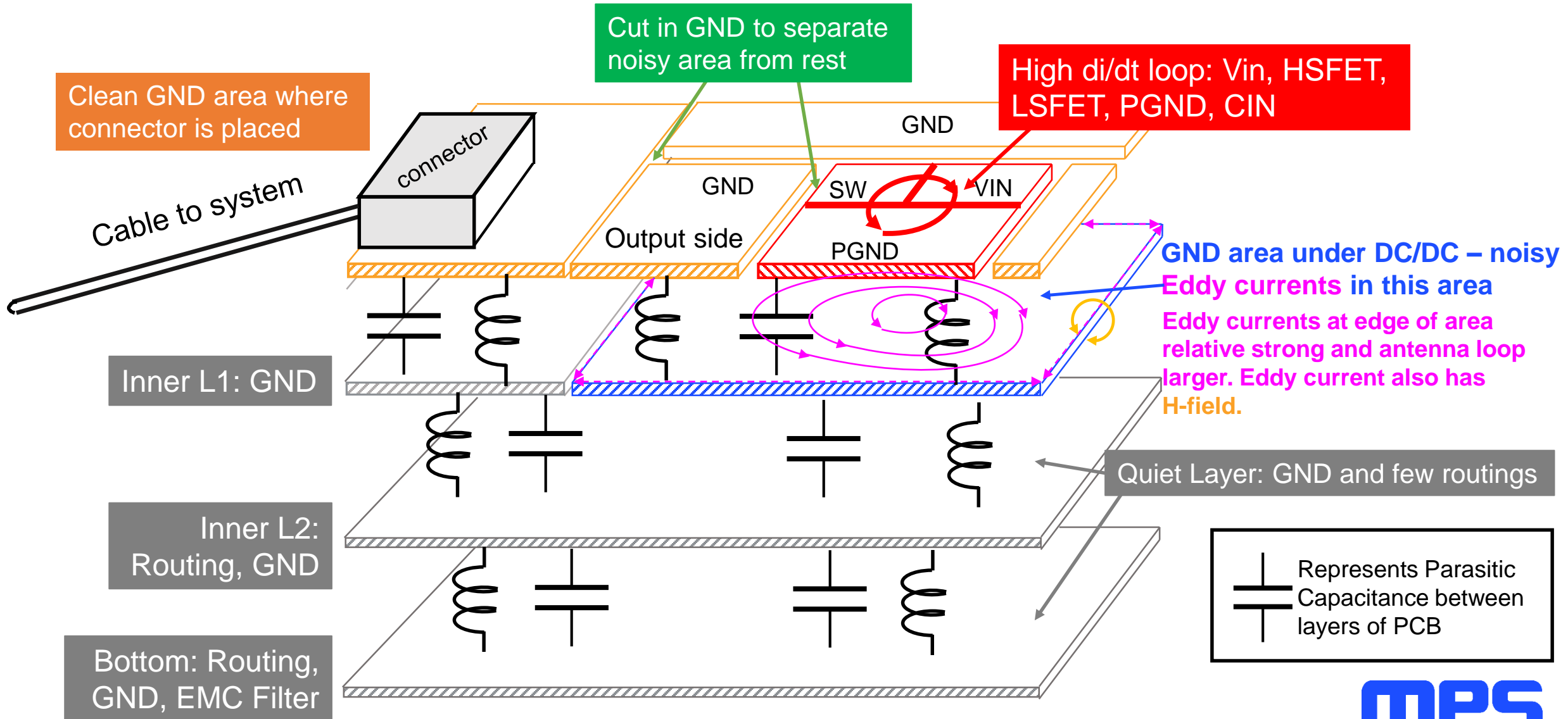Use parasitic elements of the layout to your advantage. A via is a small inductor 



Place Copper Under Inductor?

Opinion A:

“No! AC magnetic field from coil will create Eddy currents in copper under inductor. This will reduce effective inductance and create additional losses!”

Opinion B:


“Yes! Directly on top side of PCB to avoid magnetic fields disturbing other layers of the PCB!”

Which opinion is right?

Example 1: No Copper Under Coil in all Layers

Magnetic field lines close around PCB (sketch)

Very Bad for EMC

 

Magnetic field from Eddy currents on top of copper, field from Eddy currents cancels original AC magnetic field

Eddy currents also have **H-field**


- + No eddy currents under coil
- + No reduction of effective inductance

- Magnetic field couples in other components
- Magnetic field couples directly in cable
- Possible coupling in adjacent PCBs
- Eddy currents at edge of hole in all layers


NO "quiet" position on PCB for EMC filter

Detailed Look on a PCB with a hole, exposed to AC magnetic field

Simplified sketch for illustration!

 


Example 2: Copper Under Coil in Layer 4

 

++ much lower magnetic field around PCB
+ less direct coupling into cable

- Losses in Cu due to Eddy currents
- Reduced effective inductance
- Eddy currents at edge of hole in L1-L3
- Bottom side of PCB much cleaner, but not completely clean
- Eddy currents flowing in L4 will create voltage drops across layer-impedance.
- Layer impedance is further increased by any holes or routings
- EMC filter components are referred to a noisy GND and therefore will not be fully effective

 Example 3: Copper Under Coil in all Layers



- + No AC magnetic field on bottom side of PCB
- + No magnetic coupling into bottom side components
- + Reduced Magnetic field coupling in cable
- + Reduced coupling in adjacent PCBs
- + AC Magnetic fields only on top side of PCB
- + inner layer should be clean

- Losses in Cu due to Eddy currents
- Increased parasitic capacity of coil
- Reduced effective inductance
- Eddy currents under coil in L1 and at edge of Cu-area



- Bottom side of PCB CLEAN
- EMC filter can be placed effectively here

Place GND Copper Under SW-Node?

CON:

If copper is placed in the layer directly under SW-node, parasitic capacitance of SW is increased. An AC current will flow across that parasitic capacitor

Top side Layout Example EVQ4430

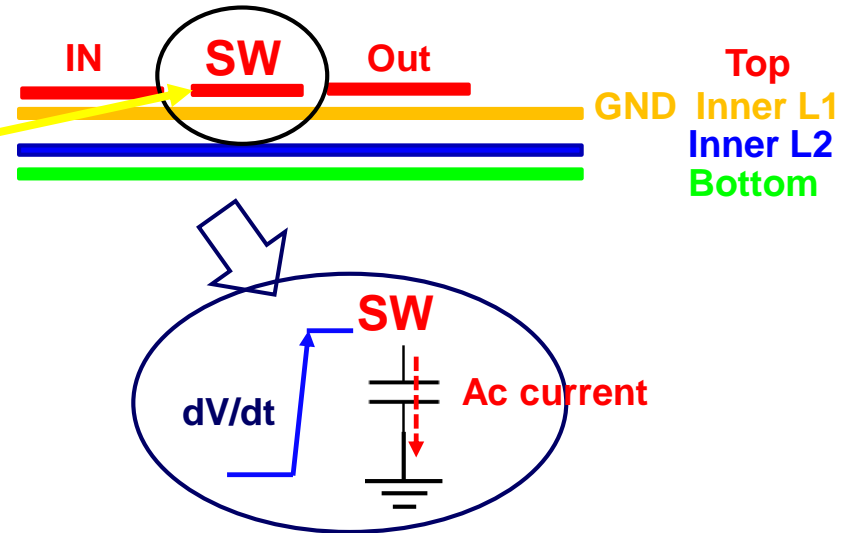 

PRO:


Solid GND under DC/DC will allow Eddy currents to mirror image the top side high di/dt current loop

- Parasitic Capacitor from SW to GND:
 $C_{sw} = 17\text{mm}^2 / 0.1\text{mm} * 4 * 8.85\text{pF/m} = 102\text{pF}$
- Low-Side-Power FET: $C_{oss} \sim 3\text{nF to } 7\text{nF}$
this is around 30 times higher

Parasitic capacitance is negligibly small


Buck EMC Optimized Schematic

MPQ4430 Family: P2P 1A to 3.5A

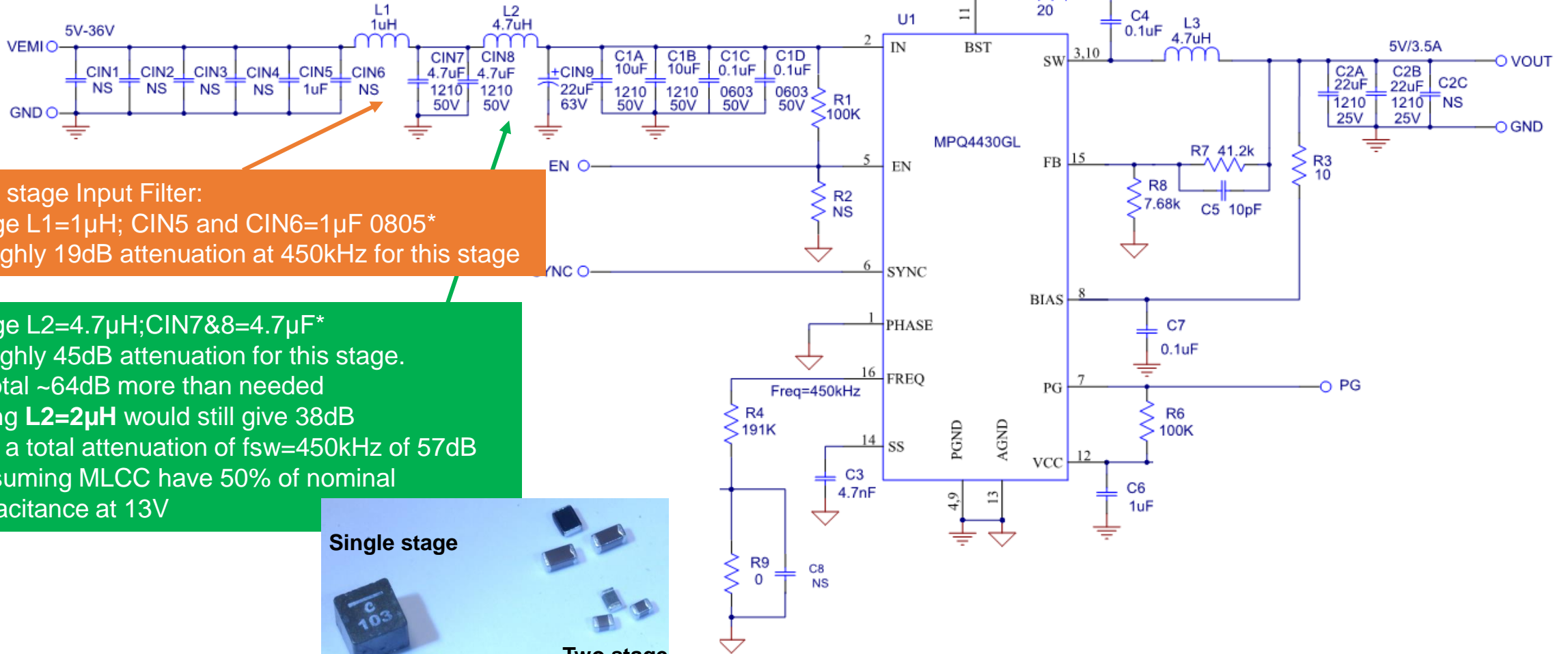

Two stage Input Filter:
 Stage L1=1µH; CIN5 and CIN6=1µF 0805*
 Roughly 19dB attenuation at 450kHz for this stage

 Stage L2=4.7µH; CIN7&8=4.7µF*
 Roughly 45dB attenuation for this stage.
 In total ~64dB more than needed
 Using L2=2µH would still give 38dB
 And a total attenuation of fsw=450kHz of 57dB
 *assuming MLCC have 50% of nominal capacitance at 13V



T-EVQ4431-L-00A Top Side



Cuts in Top GND to separate noisy PGND from clean GND

Two Cout are placed on both sides of coil

This shields part of E-Field radiation

Symmetric Cin arrangement


T-EVQ4431-L-00A Bottom Side

To avoid coupling with DC/DC fields, two stage input filter is placed on bottom side. Distance between stages to avoid coupling.

Small cap directly at load connector


CIN5 and CIN6 for $f_{sw}=470\text{kHz}$: use 0805 1 μF

 Symmetric capacitor arrangement to cancel magnetic field of AC-current




555 circuit

T-EVQ4431-L-00A Top Side Detail

 

T-EVQ4431-L-00A Inner Layer 1 Detail


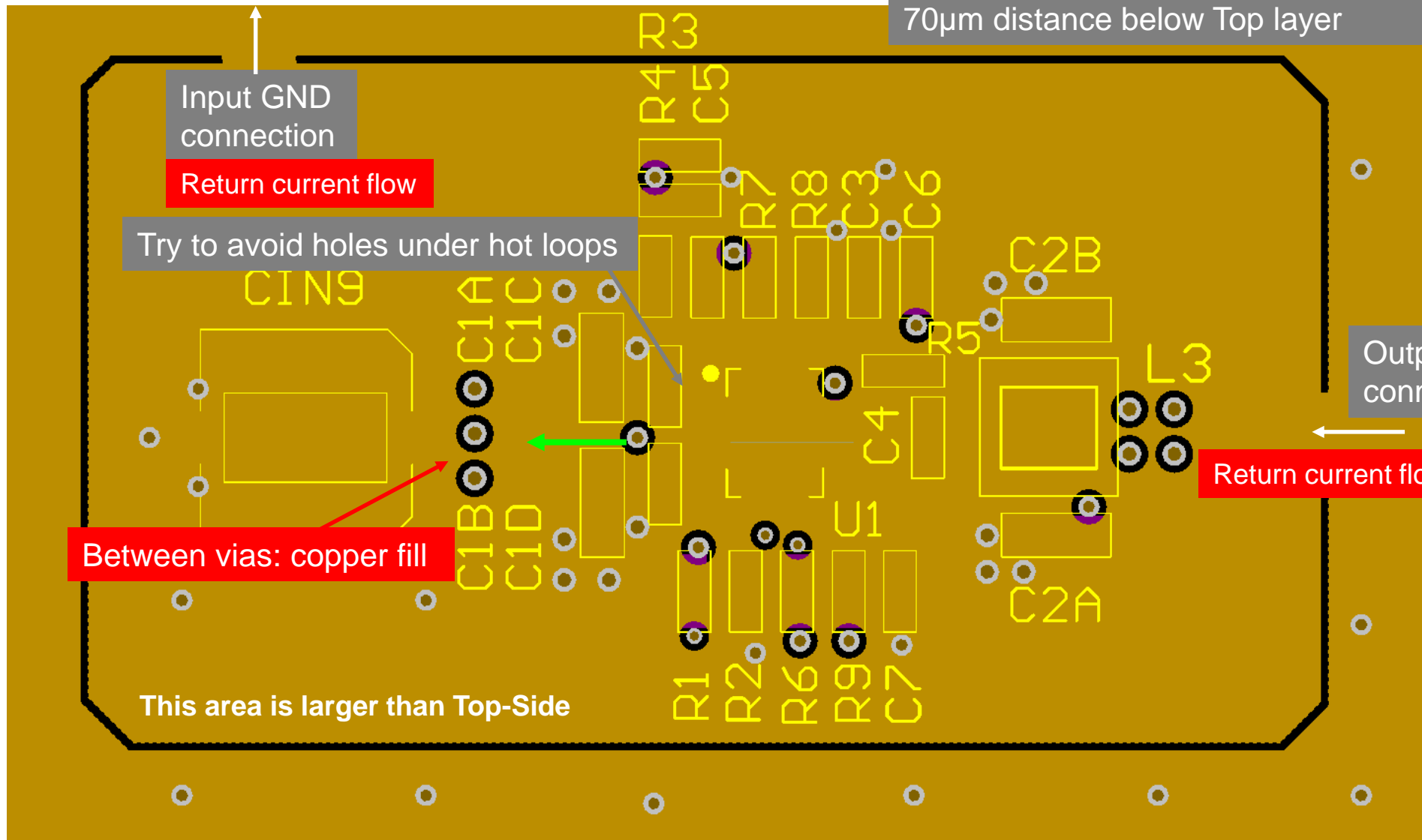
Ground area for return and eddy currents
70µm distance below Top layer




T-EVQ4431-L-00A Inner Layer 2 Detail

Inner L2 has 70µm distance to bottom layer

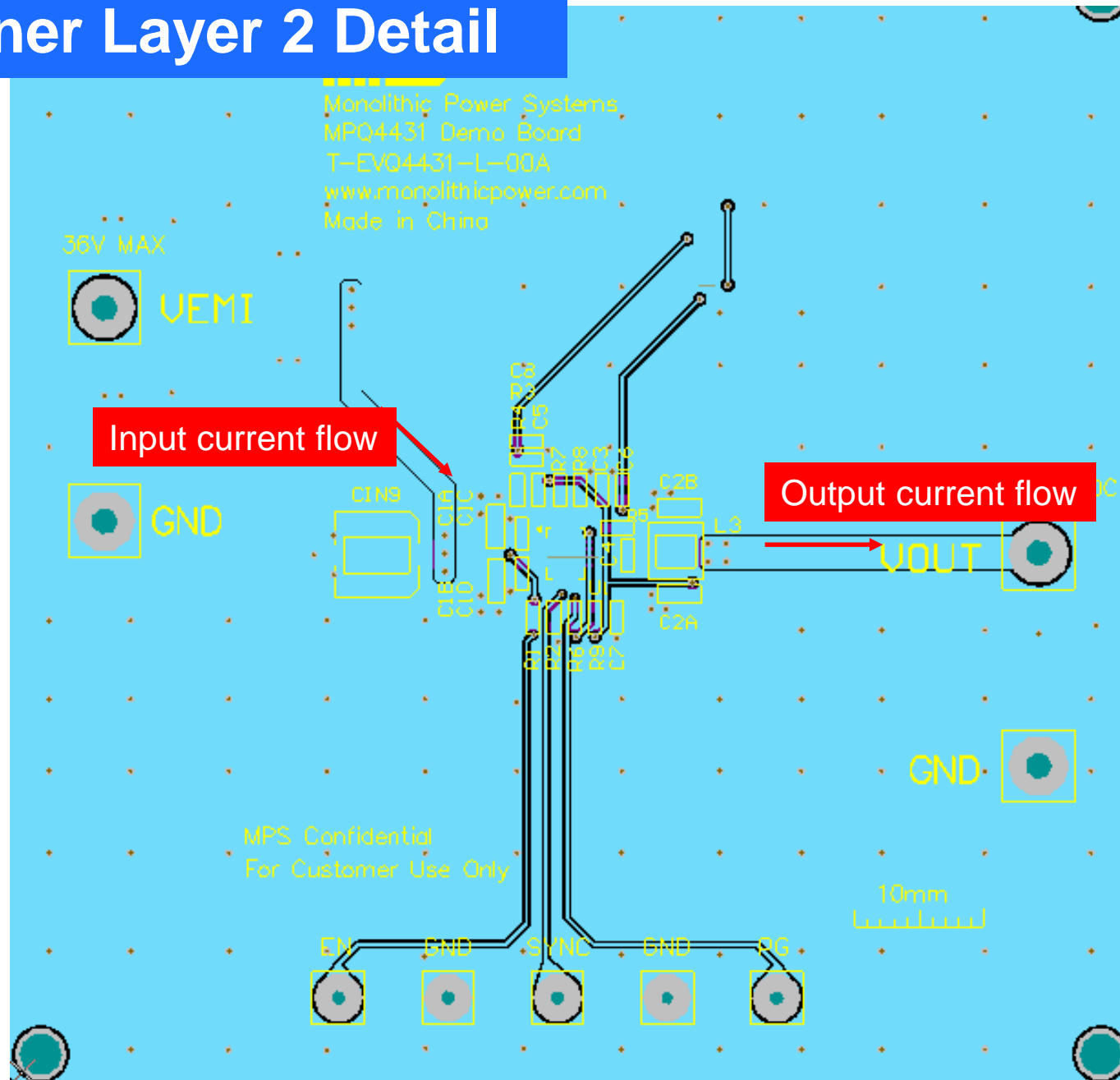 Input and Output are routed together with return



T-EVQ4431-L-00A Bottom Layer Detail

 

Between vias: copper fill




Small cap at pin

Solid GND except at input filter and the 555

A Good Design





  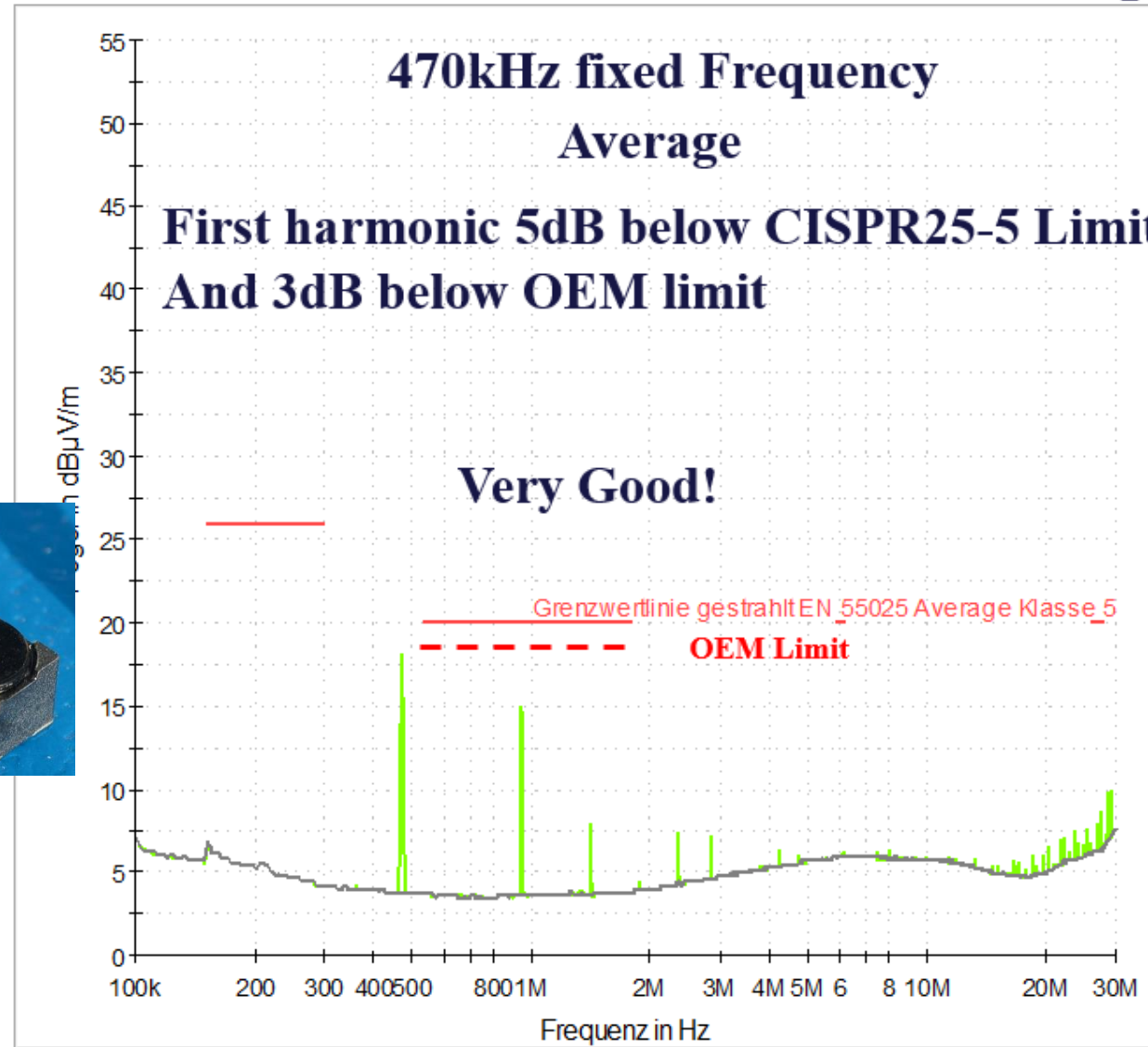Radiated Emissions – 100kHz – 30MHz Monopole




Conducted Emission Test Results

EVQ4430-00A 480kHz Spread Spectrum

  


CE Test (avg) of 3A part with different 6x6mm coils

EVQ4430-01A 2MHz Spread Spectrum

 

Radiated Emissions 30MHz to 200MHz

 

Some Frequently Asked Questions About Layout for EMC

1. Why Al-Elco at Vin?
2. Is there any difference in output filtering for buck and boost topology? How about 4 switch buck boost?
3. Shall I connect AGND and PGND at the power IC or somewhere else?
4. When do you go for more than 4 layers?
5. Should you keep areas free of copper?
6. What to do with isolated copper islands?
7. Does the input connector shape / elevation above the board has any influence on EMI?
8. How to treat NC pins and thermal pad of the IC?
9. Optimum number/spacing of via holes to connect top layer ground to internal ground?

Thank You – Q&A

AUTOMOTIVE POWER MANAGEMENT

AEC-Q100 Solutions
• • •



MPS
MonolithicPower.com


For more information, contact:
automotive@monolithicpower.com

Check out our AEC-Q100 Power
Management Solutions at
MonolithicPower.com

MPS

Backup Slides

How About A Two Layer Board?

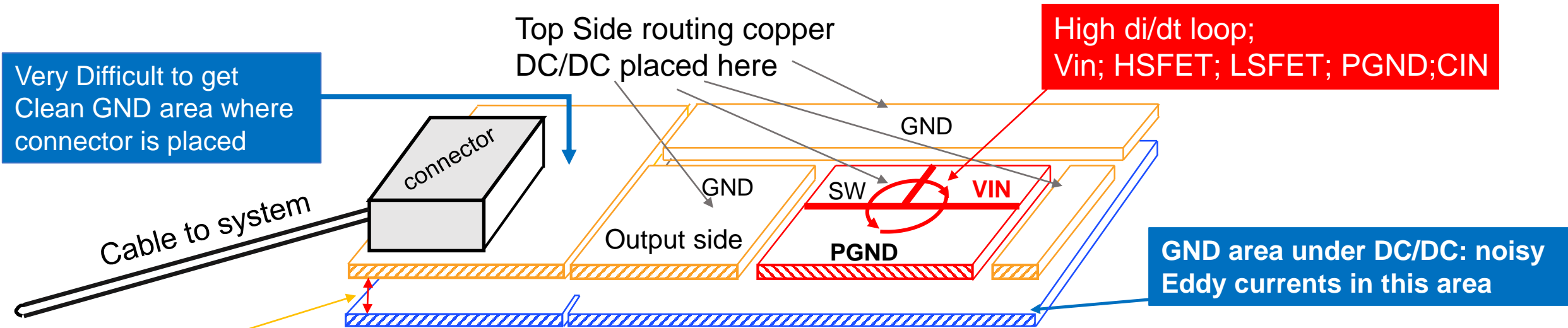

Very Difficult to get Clean GND area where connector is placed

High di/dt loop;
Vin; HSFET; LSFET; PGND; CIN

GND area under DC/DC: noisy
Eddy currents in this area


Distance >1.0mm...1.6mm
More than 10x than in a good 4-layer
Larger distance, Eddy current cancelation works **15dB to 20dB worse!**

A) With two layer PCB it is difficult to provide solid GND area under the DC/DC circuit, as Bottom side is also for routing.

 B) Compromise system reference GND vs. separation of noisy GND and clean GND. No clean Reference point!

Magnetic Antennas



On AC current loops like hot loops, there is still an increased current density at the outside boundary of the loop



Magnetic Antennas

Cut around PGND to prevent AC current to disturb to layer

Still significant AC current here

 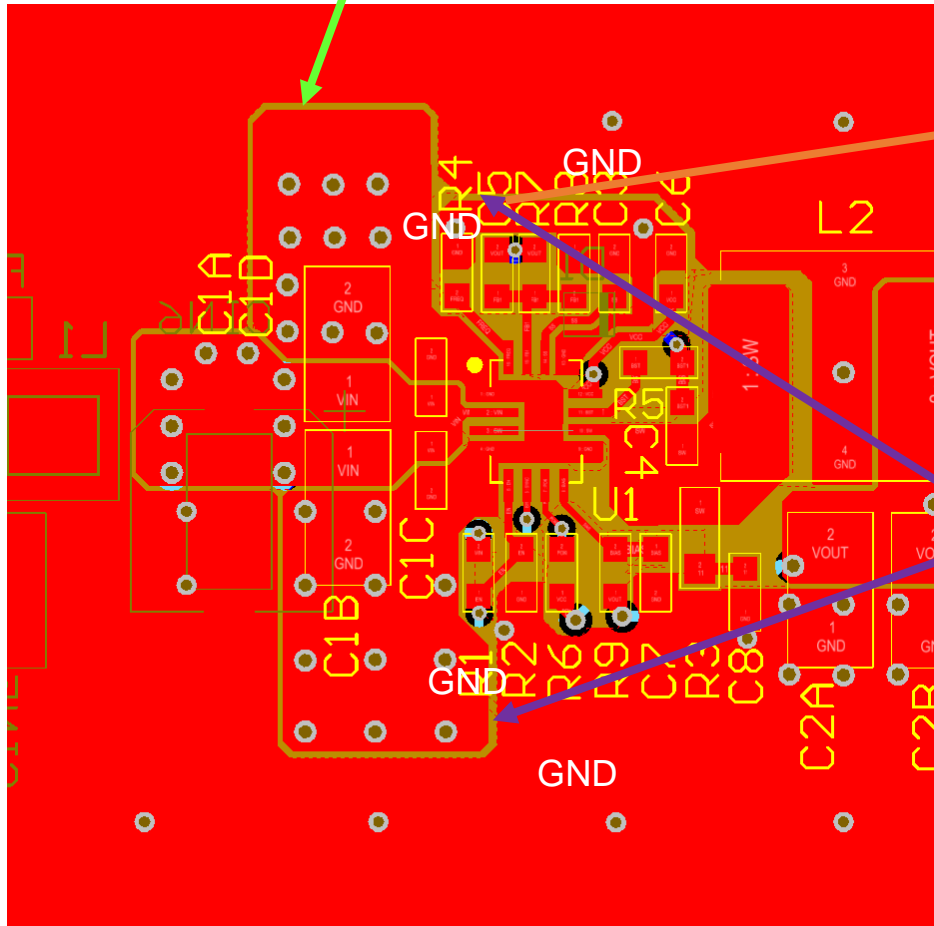

That's the reason you might cut even the GND of the hot loop on the top side.

Otherwise there will still be some current density left at the edge of your PCB where it will radiate, and eddy current shielding is less effective