

How to Estimate Motor Driver Power Dissipation


Emmanuel Granatello – Technical Marketing Engineer
Christophe Vaucourt – Sr. Technical Marketing Engineer

Webinar will begin at 10:00AM CET | 2:00 AM PDT | 5:00 AM EDT

Agenda


- Introduction
 - Motor current profile including stall current and application mission profile
 - Motor driver thermal challenges requiring accurate loss estimation
- Motor driver power stage basics
 - Topology (B2, B4, B6 bridges)
 - Switching waveforms
 - EMC trade-offs
 - Power stage losses introduction
- Motor driver power dissipation estimations
 - SPICE simulation
 - Lab measurements
- Conclusions

Motor Load Current Mission Profile

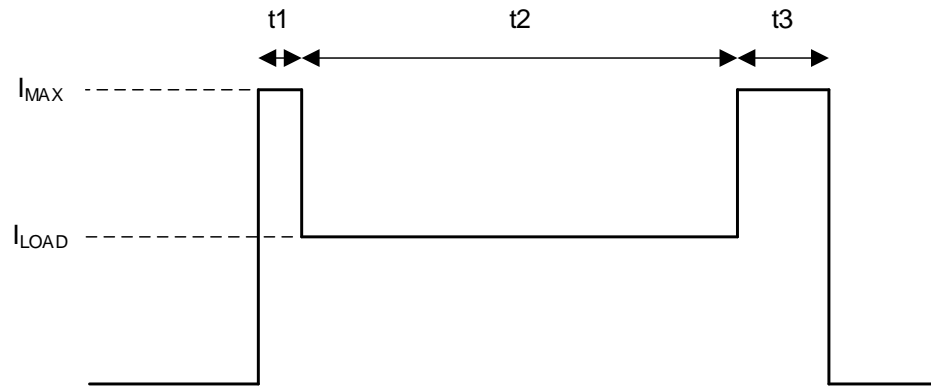


Timing	Duration (ms)
t1 (inrush current)	10 to 50 (30)
t2 (load current)	2000 to 30000 (up to ∞)
t3 (stall current)	100 to 1000

Current	
I_{LOAD}	25% to 75% I_{MAX} (30%, 50%)

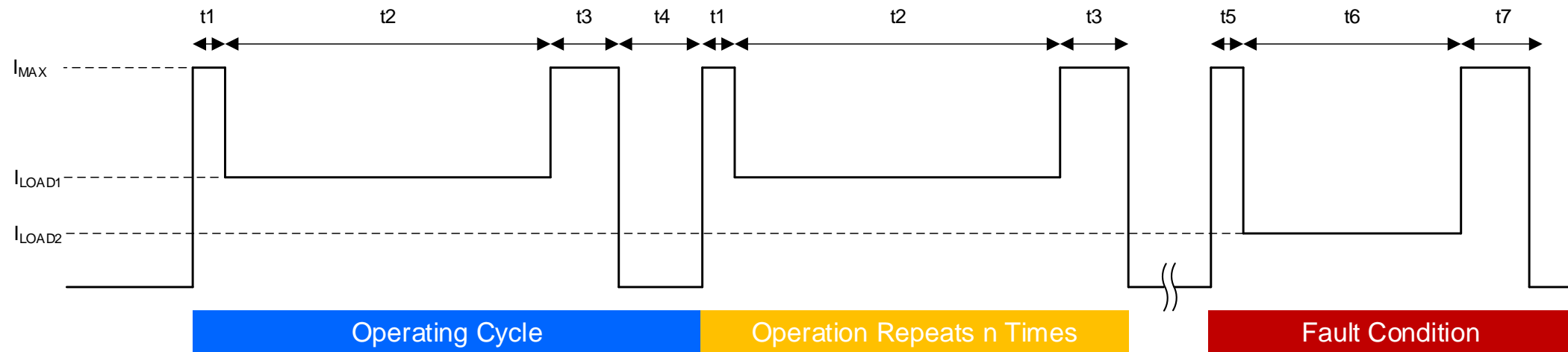

Thermals and Losses Under Pulsed Operation

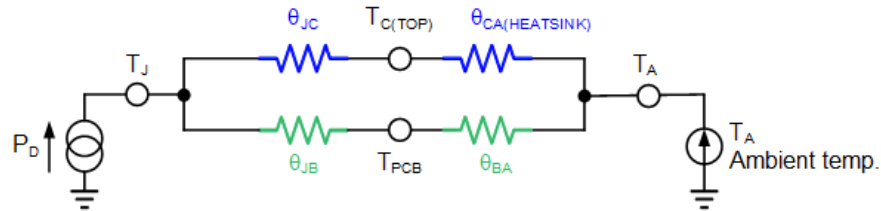Under pulsed load operation, higher peak power dissipation can be tolerable. The critical junction temperature is not reached instantaneously, even when excessive power is being dissipated in the device.




Package specific Not part of the package

θ_{JB} : Thermal impedance from the die to the board. θ_{JB} includes some of the board characteristics and their coupling with the package.


Thermal capacitance (C_{TH}) is a measure of the capability to accumulate heat and it depends on the specific heat capacity (c), volume (V), and density (ρ):
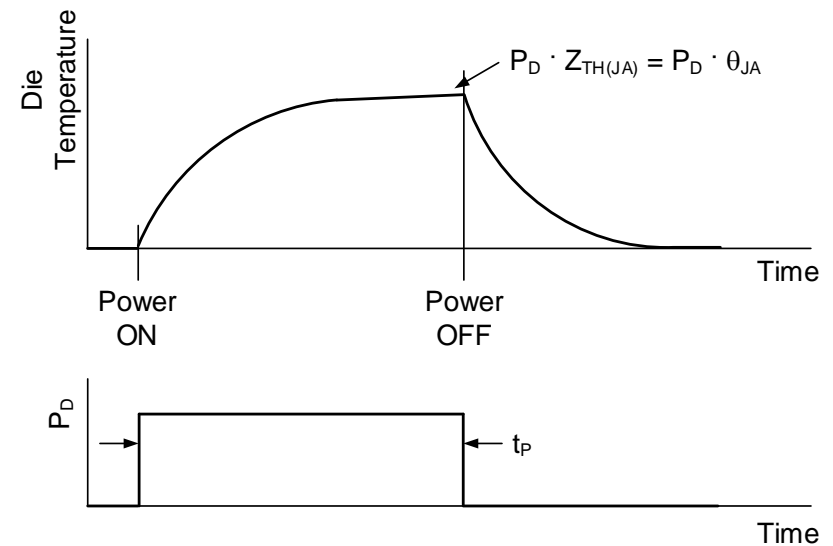
$$C_{TH} = c \cdot \rho \cdot V \quad \text{expressed in J/K}$$



Thermal Modeling


Transient Measurements

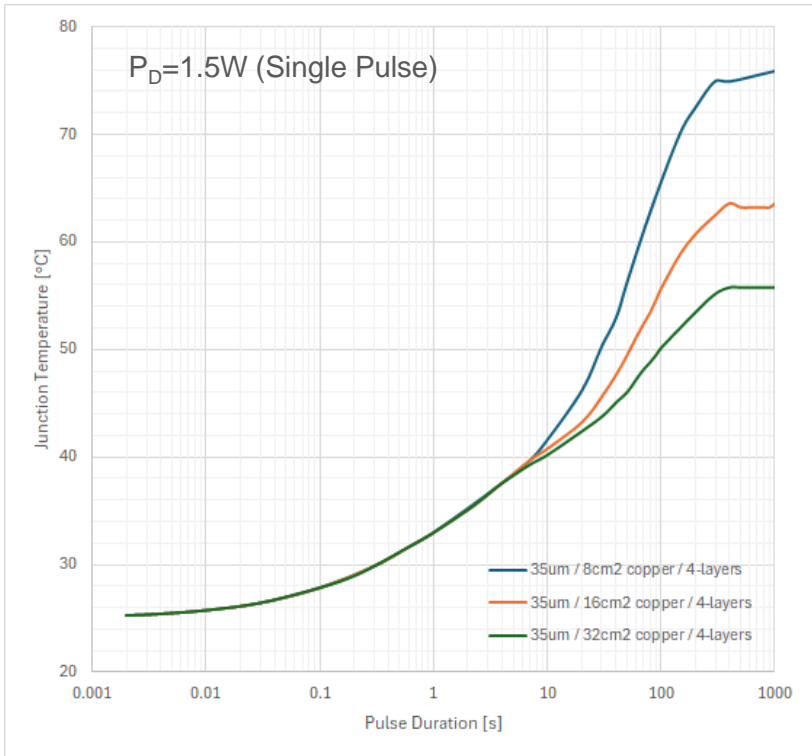

$$T_j(t) = T_J(0) + f(t)$$

$T_j(t)$ can be found using curve fitting techniques

Model

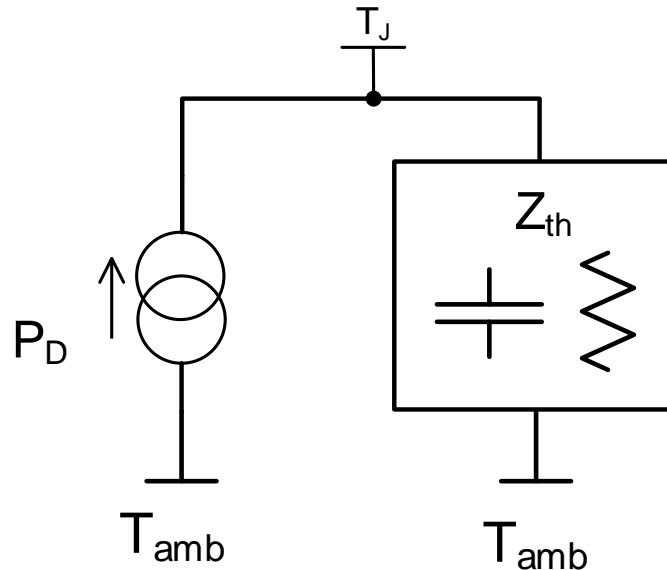

$$T_j(t) = \underbrace{T_{amb}}_{T(0)} + PD(t) * \underbrace{Z_{th}(t)}_{f(t)}$$

$\mathcal{L} \downarrow$

$$\mathcal{L}\{T_j(t) - T_J(0)\} = PD(s) Z_{th}(s)$$




$$Z_{th}(s) = \frac{\mathcal{L}\{T_j(t) - T_J(0)\}}{P_D(s)}$$

To know $Z_{th}(s)$ one needs:

- $T_j(t)$ time response (i.e. to step or impulse power dissipation stimuli)
- resting condition $T_J(0)$ (temp. when no power dissipation is applied)
- stimuli function (i.e. step or impulse and its amplitude)


Thermal Modeling (Cont'd)

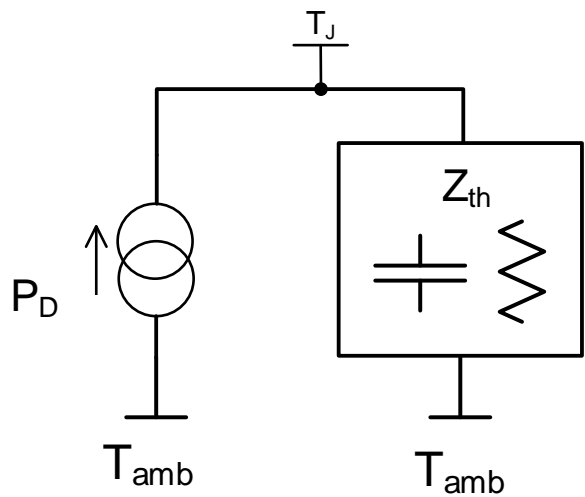Any $Z_{th}(s)$ impedance can be synthesized in a passive network using the Cauer or Foster algorithm. For thermal models, RC networks result quite handy and representative of the reality.



$$Z_{th}(s) = \frac{N_{th}(s)}{D_{th}(s)}$$

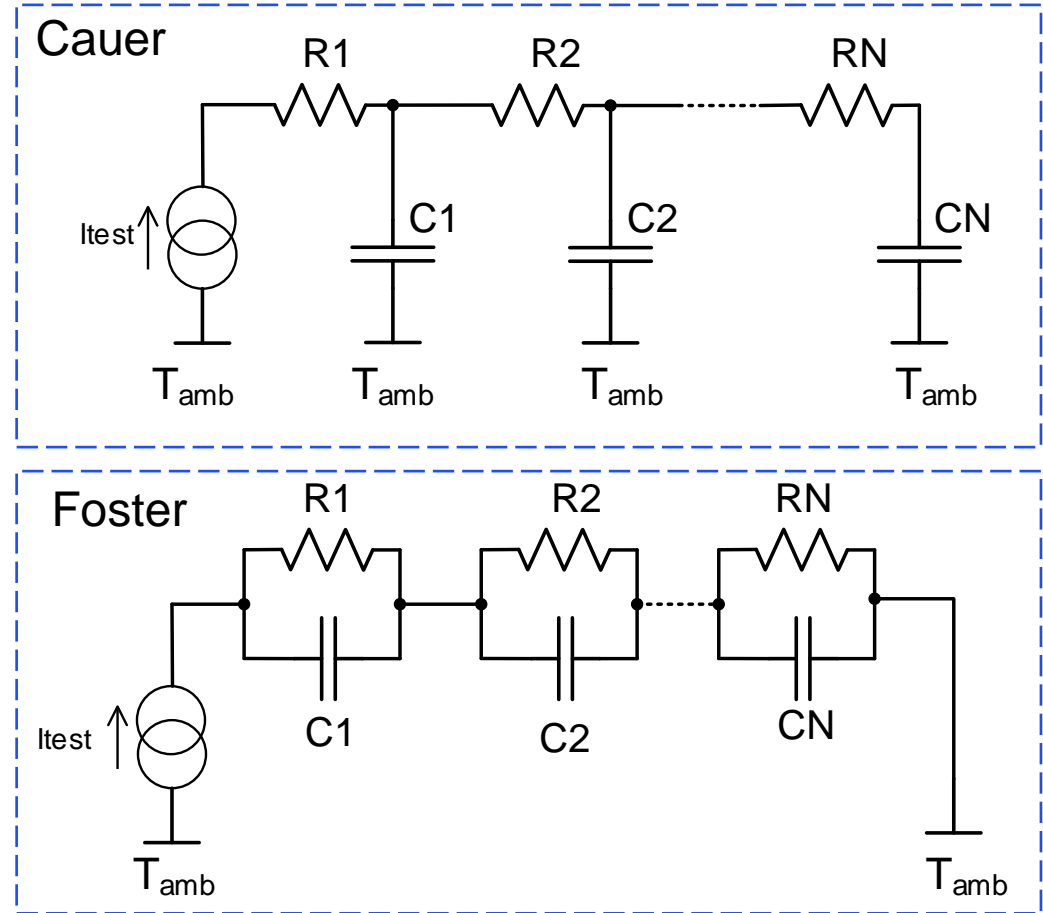
RC network extraction from $Z_{th}(s)$:
Cauer or Foster representation



Basic DC Motor Driver Topologies


Half-Bridge

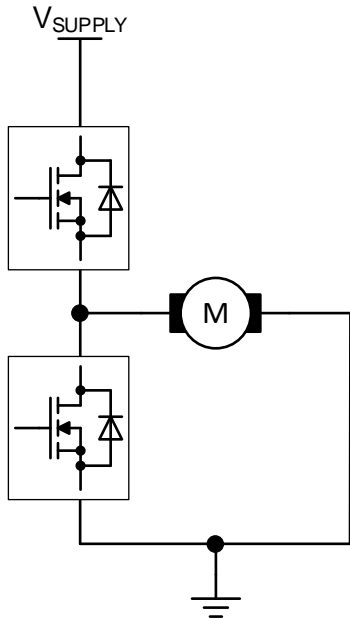- 1-direction Brushed DC motor
- Three modes: Run, Coasting and Braking



H-Bridge (B4)

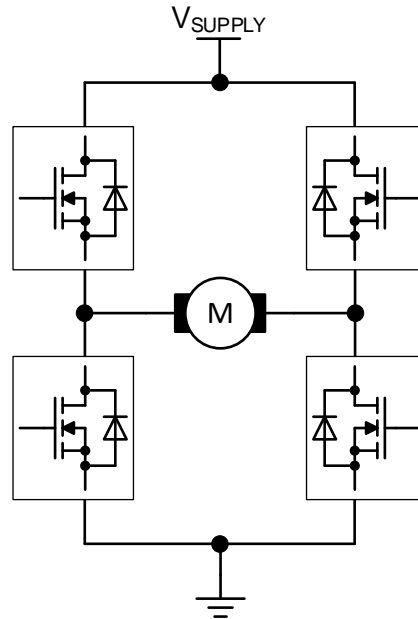
- 2-Direction Brushed DC motor
- Four modes: Run, Reverse, Coasting and Braking





Also 2 H-bridge for **stepper**

B6-Bridge


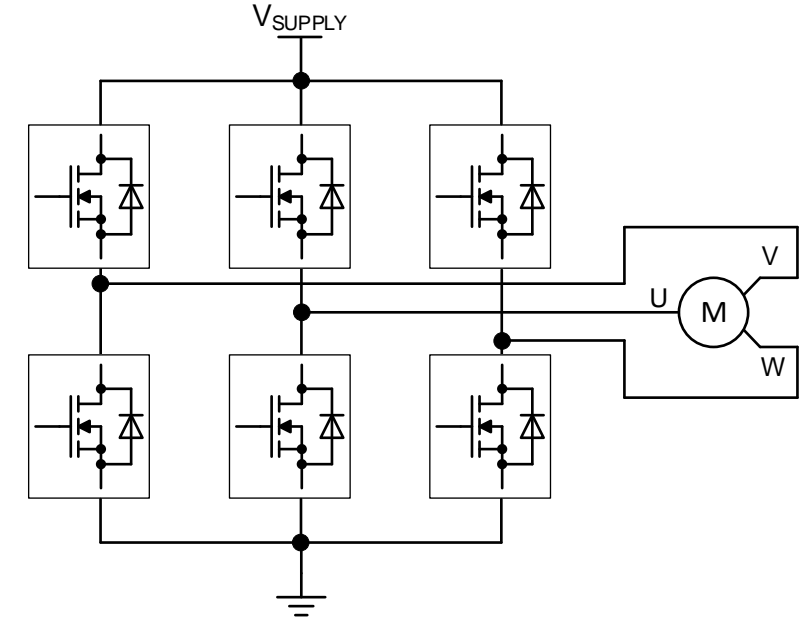
- BLDC motor – electrically commutated.
- Four modes: Run, Reverse, Coasting and Braking



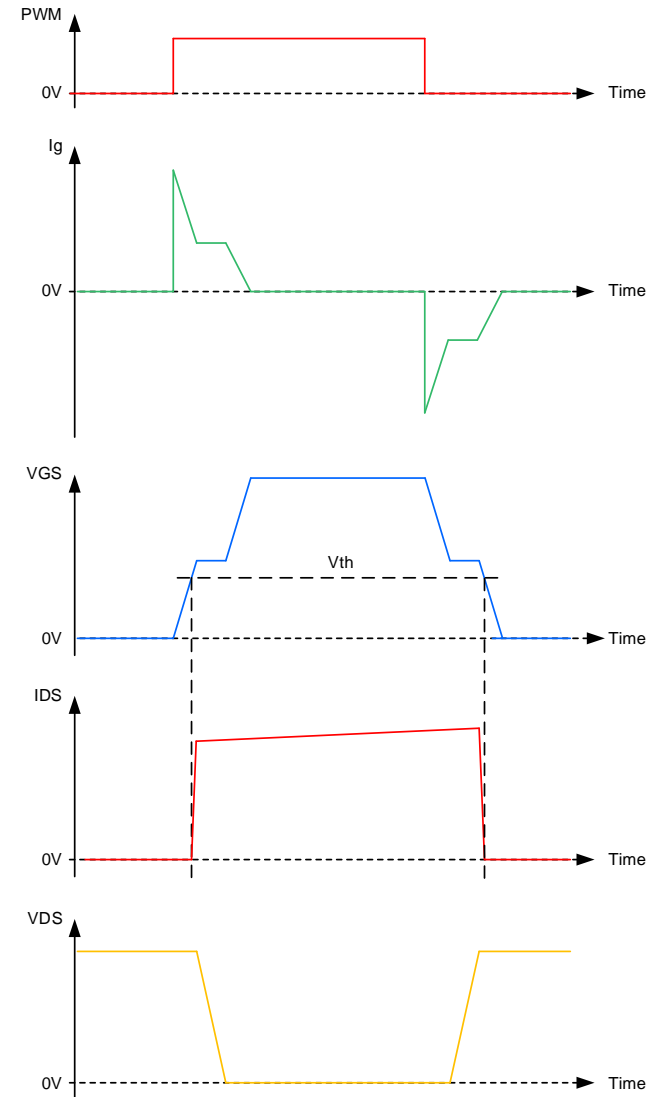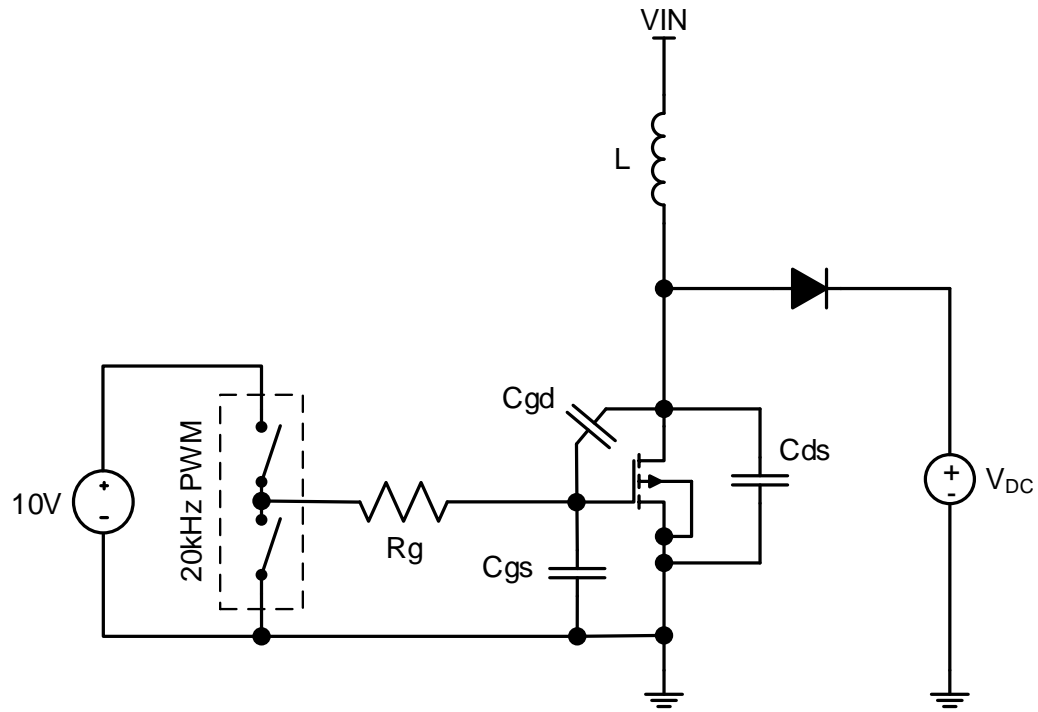
Understanding MOSFET Basic Switching (Inductive Load)




Half-Bridge Switching Waveforms

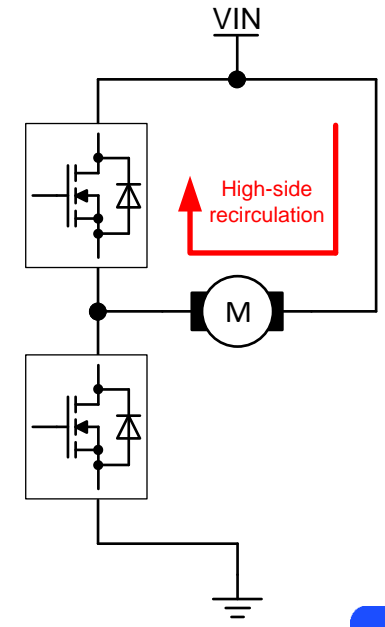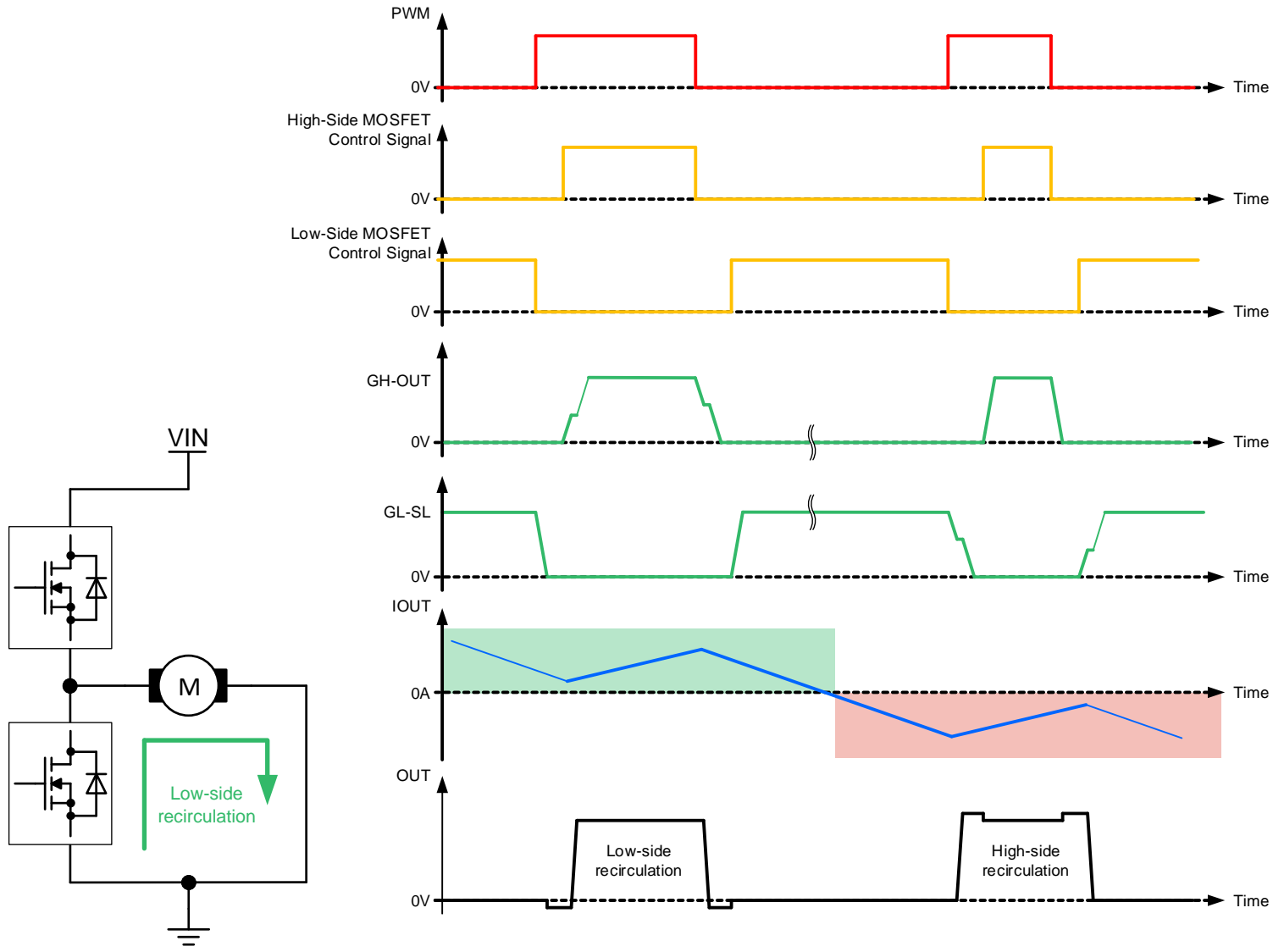

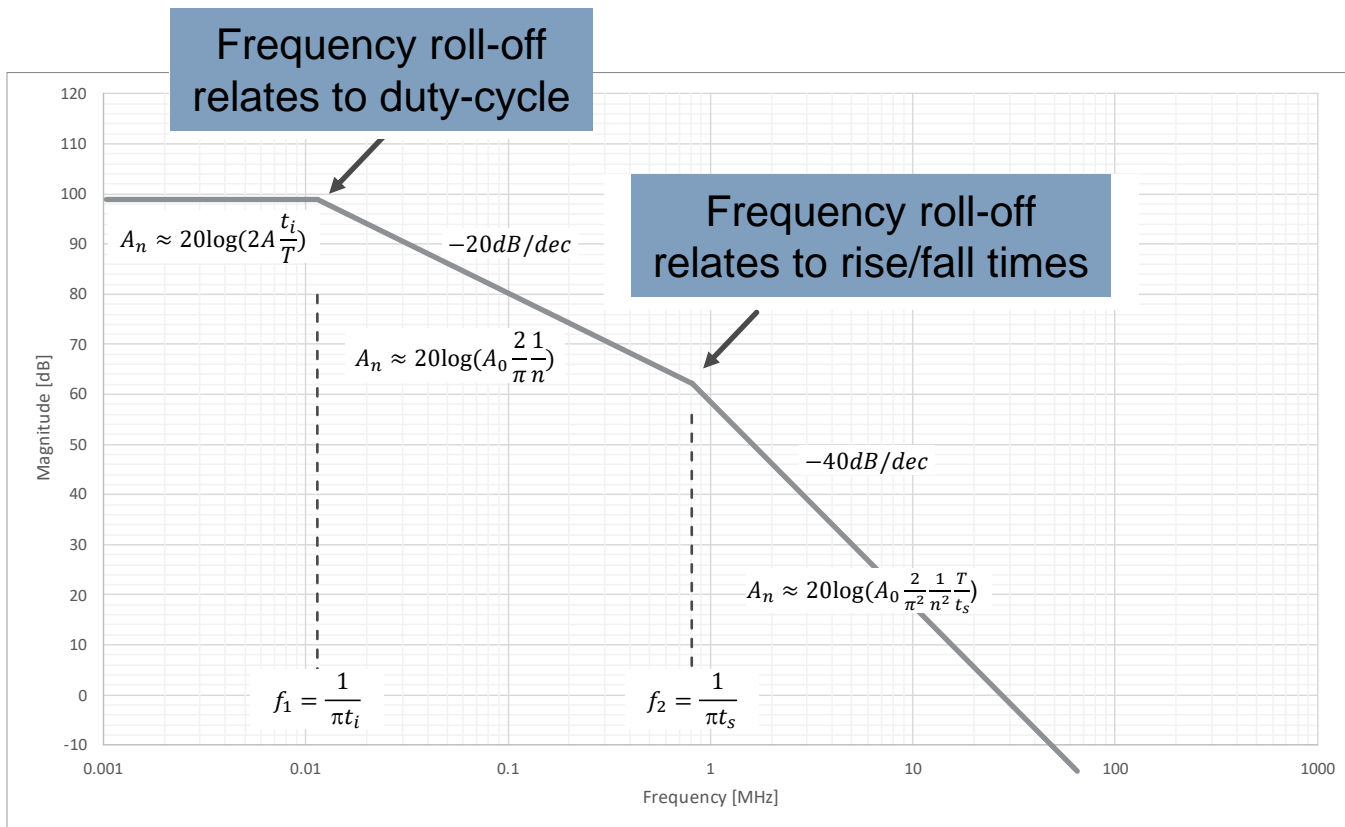Conducted Emission Spectrum – Trapezoidal Signal



Time domain signal

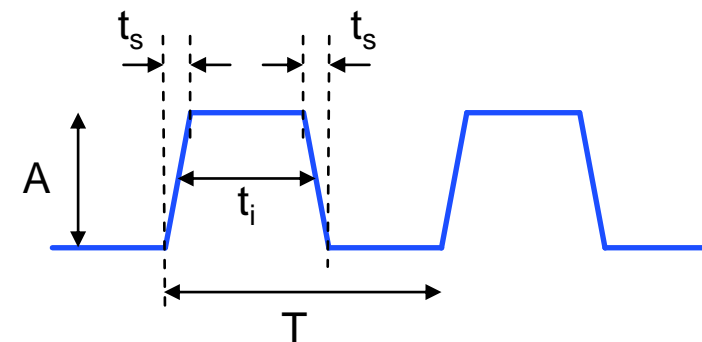

Frequency roll-off vs. rise/fall times

Rise/Fall Times t_s (ns)	Roll-Off Freq. f_2 (MHz)
100	3.2
150	2.1
500	0.65
1000	0.33
1500	0.21

Half-Bridge Power Losses: 1st Order Estimation

MOSFET Turn-On Losses

$$P_D = \frac{V_{IN}}{2} \times I_{MOTOR} \times \frac{t_{RISE}}{T_{PWM}}$$

MOSFET Turn-Off Losses

$$P_D = \frac{V_{IN}}{2} \times I_{MOTOR} \times \frac{t_{FALL}}{T_{PWM}}$$

$t_{RISE} = t_{FALL}$ (VDS transition)

MOSFET Switching Losses

$$P_{SW} = V_{IN}^2 \times I_{MOTOR} \times f_{PWM} \times \frac{1}{SR}$$

Where I_{MOTOR} is assumed to have a very low ripple

MOSFET Conduction Losses



$$P_{COND} = R_{DS(ON)} \times I^2_{(RMS)} \quad I_{RMS} = I_{MOTOR} \times \sqrt{D}$$

$$P_{COND} = R_{DS(ON)} \times I^2_{MOTOR} \times D$$

MOSFET Back-Gate Diode Losses


$$P_{BG} = 2 \times V_F \times I_{MOTOR} \times t_{BG_TIME} \times f_{PWM}$$

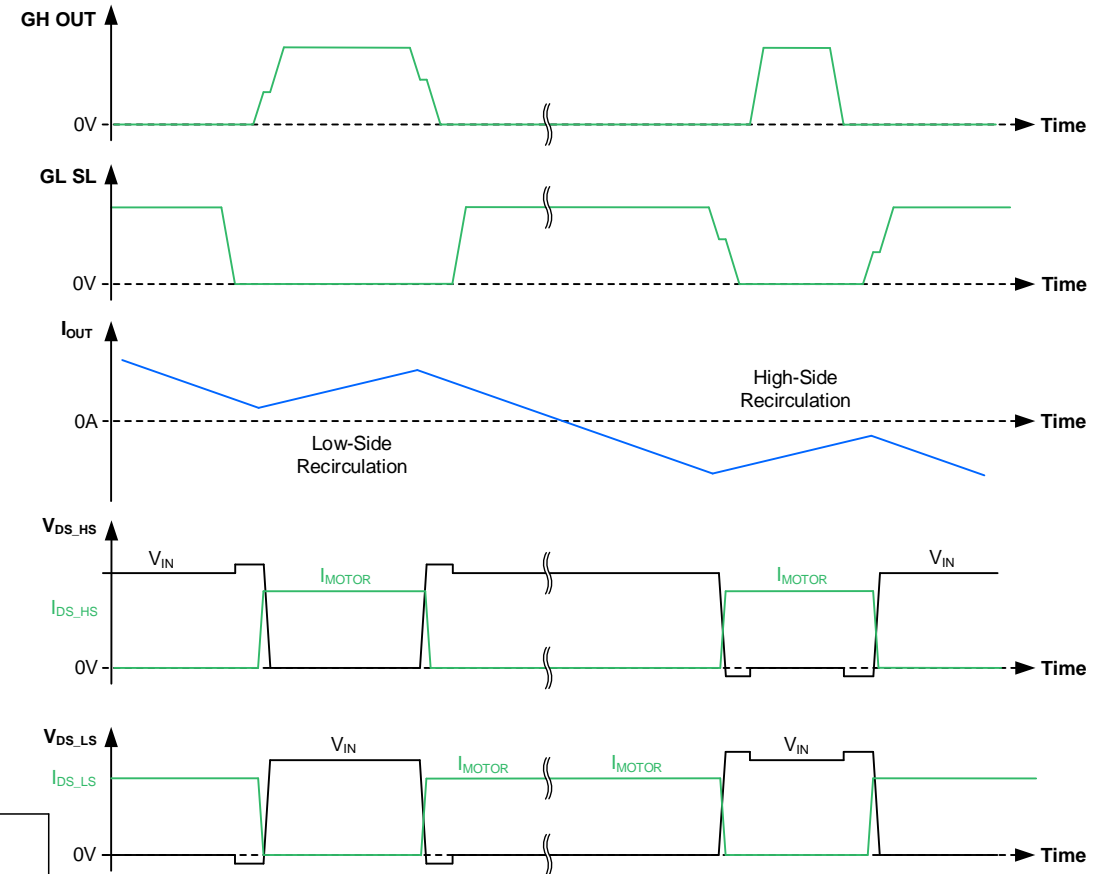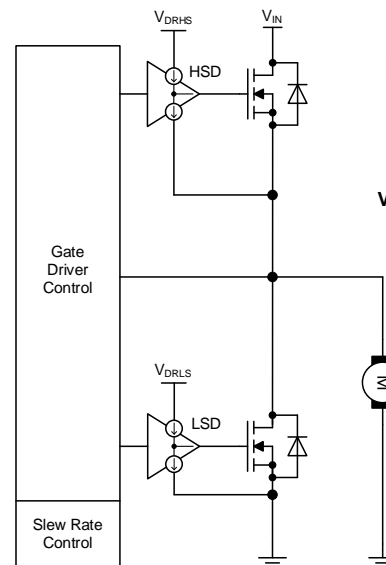Where the I_{DS} transition is assumed to be negligible





IPP80CN10N SPICE Model Level 0

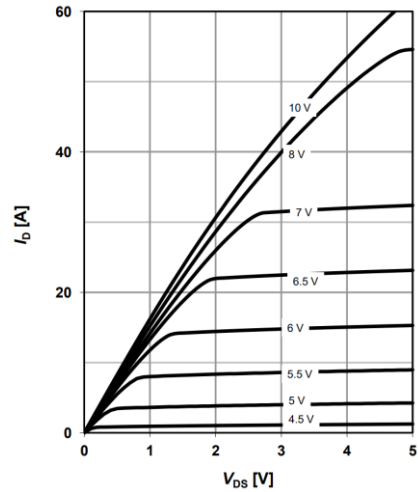MOSFET Drain-Source On-State Resistance Datasheet Parameter



Drain-source on-state resistance	$R_{DS(on)}$	$V_{GS}=10\text{ V}, I_D=13\text{ A},$ (TO252)	-	59	78	mΩ
----------------------------------	--------------	---	---	----	----	----

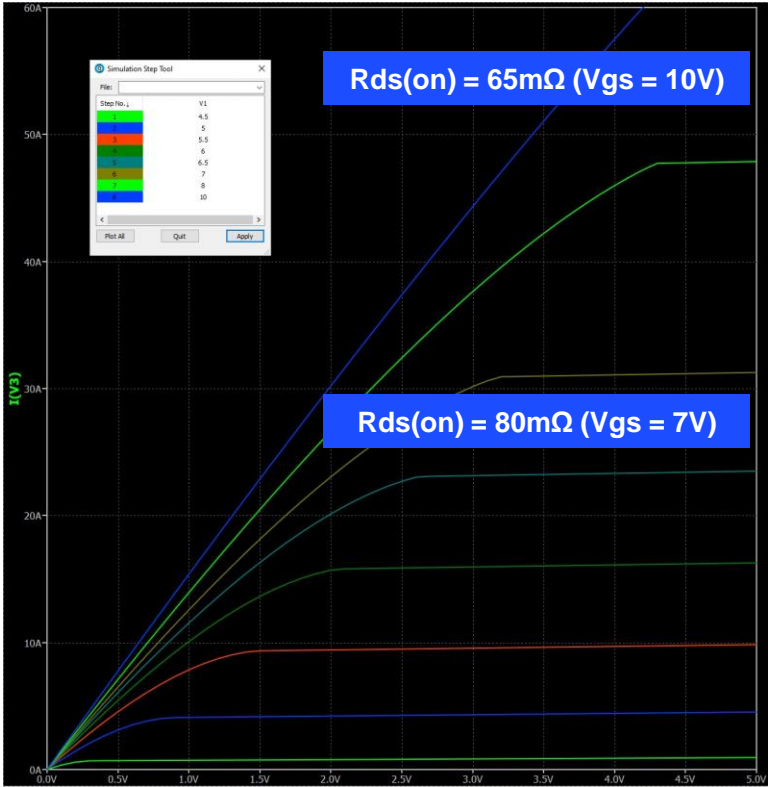
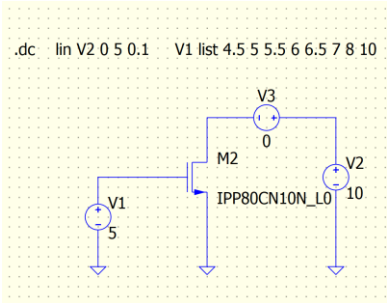
MOSFET Drain-Source On-State Resistance Model Verification





IPP80CN10N SPICE Model Level 0 (Cont'd)

MOSFET Gate Charge Datasheet Parameters

Gate to source charge	Q_{gs}	$V_{DD}=50\text{ V}, I_D=13\text{ A},$ $V_{GS}=0\text{ to }10\text{ V}$	-	3	4	nC
Gate to drain charge	Q_{gd}		-	2	3	
Switching charge	Q_{sw}		-	3	5	
Gate charge total	Q_g		-	8	11	
Gate plateau voltage	$V_{plateau}$		-	5.7	-	

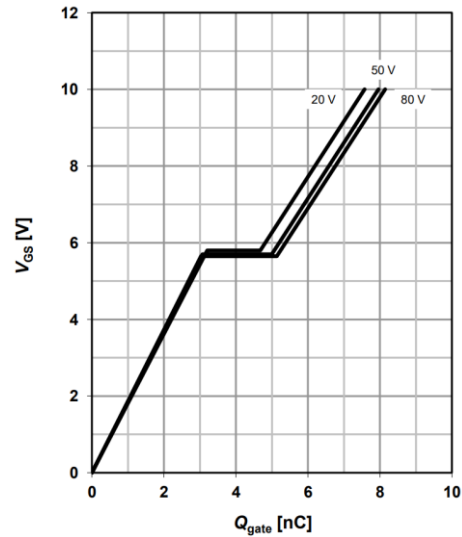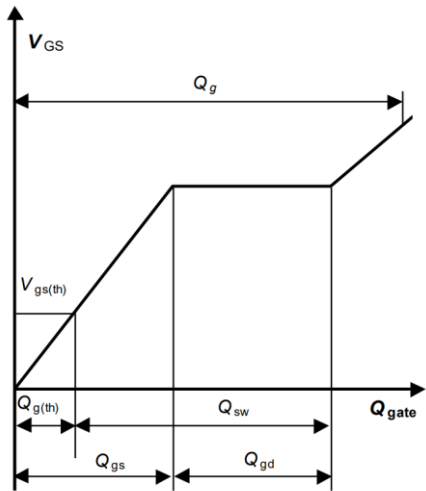

MOSFET Gate Charge Model Verification

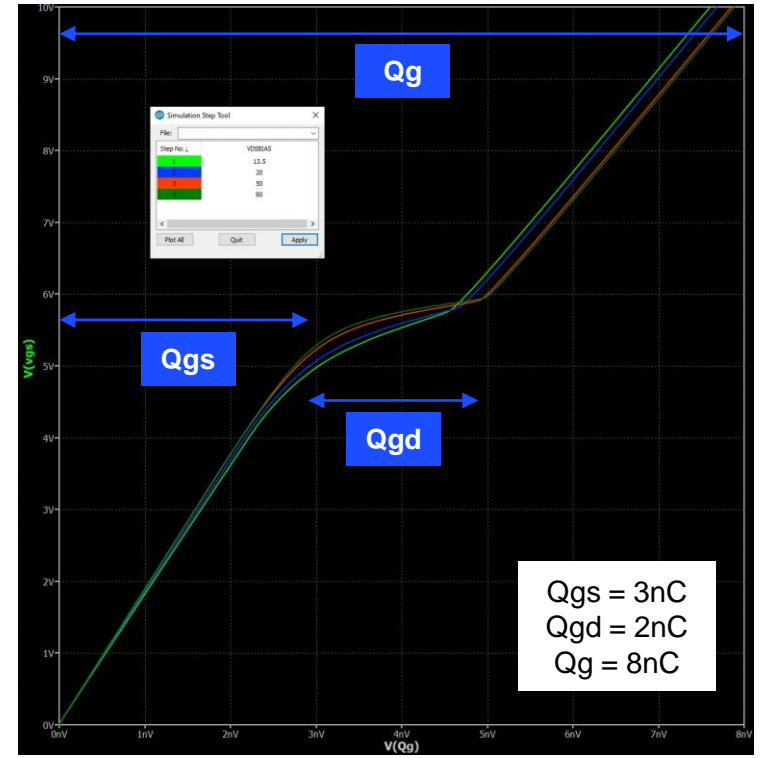
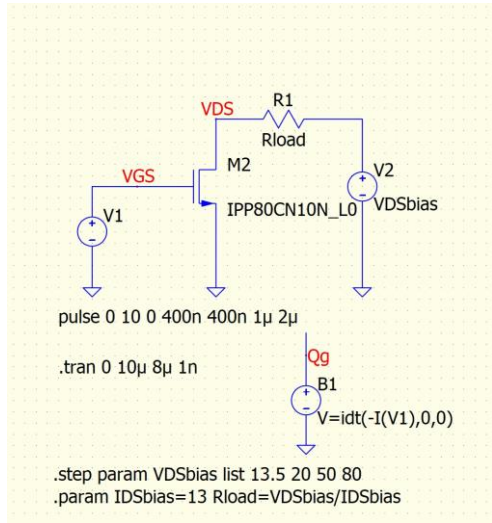


IPP80CN10N SPICE Model Level 0 (Cont'd)

MOSFET Output Charge Datasheet Parameters

Output charge	Q_{oss}	$V_{DD}=50\text{ V}, V_{GS}=0\text{ V}$	-	8	10	nC
---------------	-----------	---	---	---	----	----


MOSFET Output Charge Model Verification

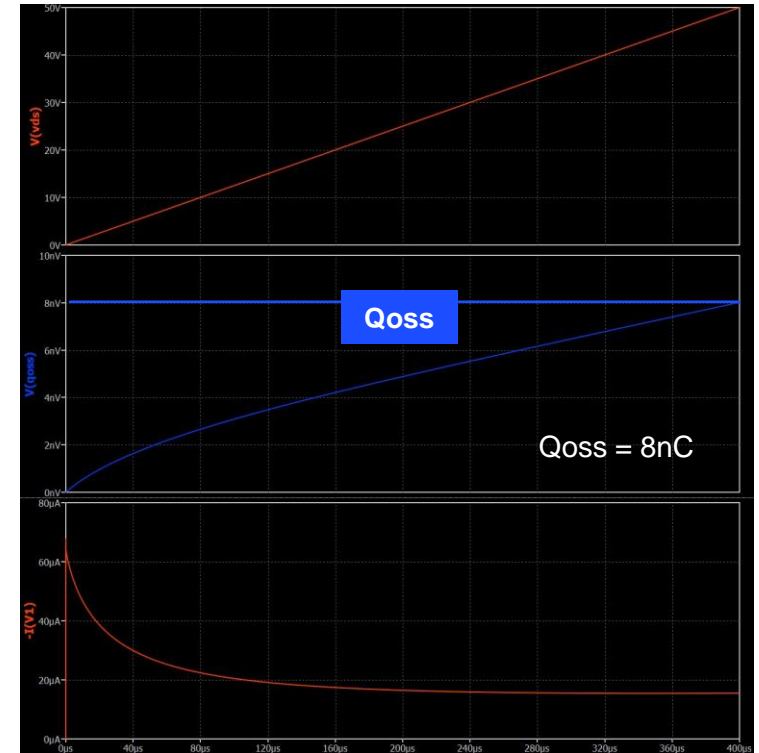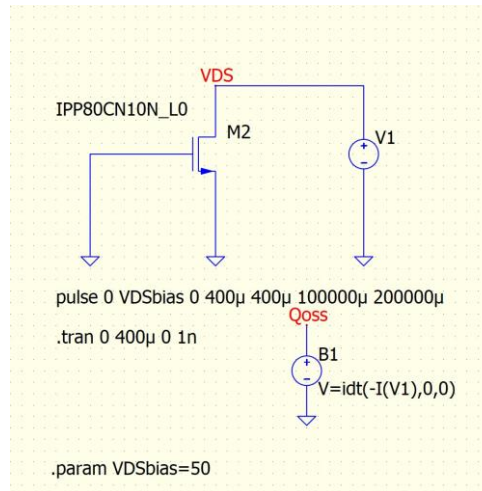

Simple Switching MOSFET SPICE Model

Testbench
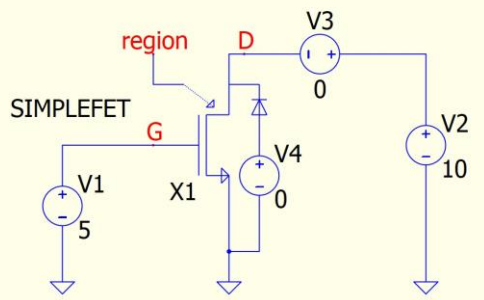
```
.dc lin V2 0 5 0.1 V1 list 4.5 5 5.5 6 6.5 7 8 10
```




```

1 .subckt simpleFET G Drain Source Dp region
2
3 *External resistances
4 R2 Drain D Rdrain
5 R3 Source S Rsource
6 R1 G S 10Meg
7
8 *Body diode model
9 D1 DR D Diode
10 R4 Dp DR RDon
11 .model Diode D(Ron=Rdiode Roff=RDoff Vfwd=VD Vrev=VBD EPSILON=0)
12
13 *Mosfet current
14 *Mosfet current
15 B1 D S I=if(V(G,S)<VTH, 0, if(V(G,S)-VTH>=abs(V(D,S)),
16 + Kp*(V(G,S)-VTH-abs(V(D,S))/2)*V(D,S),Kp/2*((V(G,S)-VTH)**2) ) ) +
17 + if(V(D,S)>0 & V(G,S)>VTH,V(D,S)*lambda,0)
18
19 *Mosfet operating region
20 B2 region 0 V=if(V(G,S)<VTH, 0, if(V(G,S)-VTH>=V(D,S),1,2) )
21
22 *Mosfet parameter extraction
23 .param Kp=Kp_lin
24 .param Kp_lin=IDSx/(VGSx-VTHx-VDSx/2)/VDSx
25 .param Kp_sat=IDSx*2/((VGSplx-VTHx)^2)
26 .param VDSx=(Rdsx-Rdrain-Rsource)*IDSx
27 .param VTH=VTHx
28
29 *Mosfet parameters
30 .param RDStgt=64m
31 .param Rdrain=1u Rsource=1u
32 .param lambda=1/235
33 .param Rdsx=RDStgt RdsOff=10Meg
34 .param VGSx=10 IDSx=13 VTHx=4 VGSplx=5.7
35
36 *Diode parameters
37 .param RDon=10m Rdiode=1u RDoff=10Meg VD=0.7 VBD=1Meg
38 .ends simpleFET
    
```

Drain-source on-state resistance	$R_{DS(on)}$	$V_{GS}=10V, I_D=13A, (10Z5Z)$	-	59	78	mΩ
Gate threshold voltage	$V_{GS(th)}$	$V_{DS}=V_{GS}, I_D=12\mu A$	2	3	4	V
Gate plateau voltage	$V_{plateau}$		-	5.7	-	V


No body-diode reverse recovery modeling (Qrr)
No gate charge modeling

Model Verification

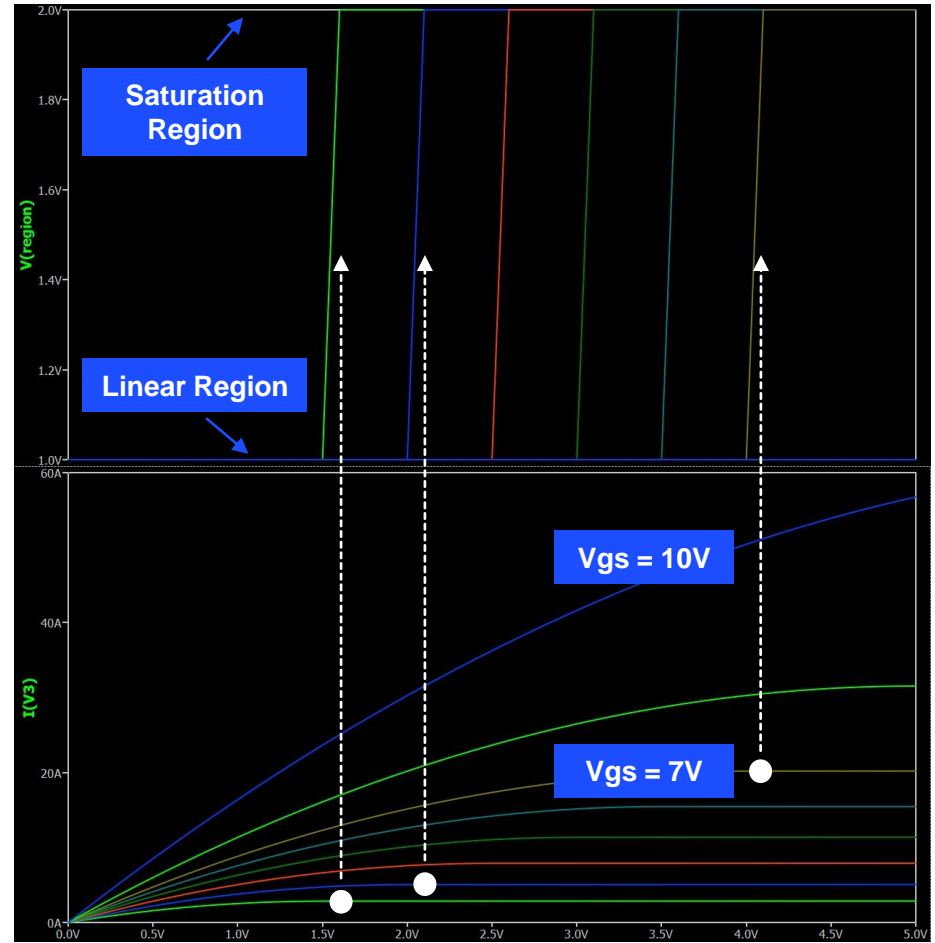


Testbench Comparison (MOSFET Level 0 Model vs. Simple MOSFET)

MOSFET Model Level 0 Testbench

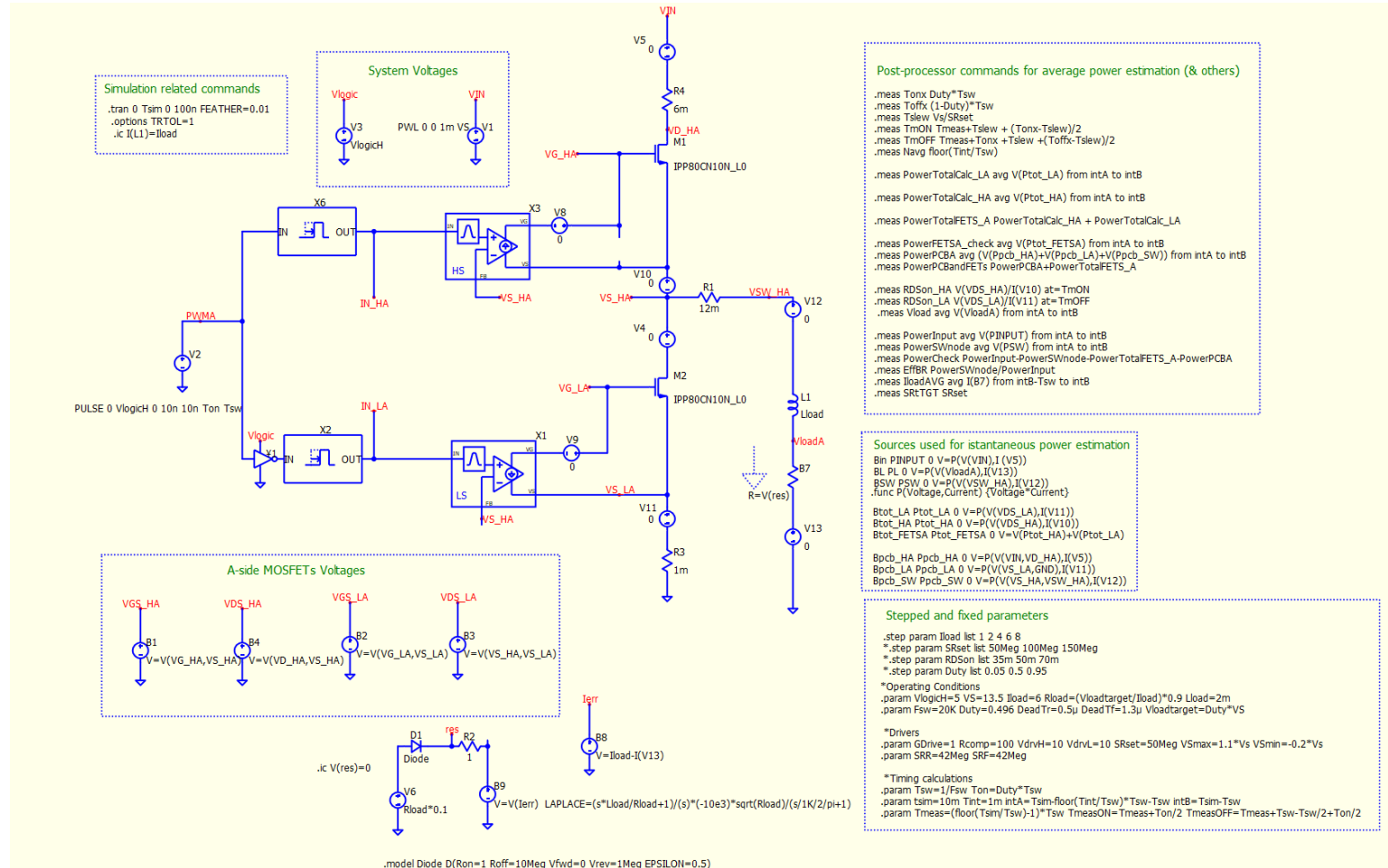


Testbench Comparison (Cont'd) (MOSFET Level 0 Model vs. Simple MOSFET)

Simple MOSFET Testbench

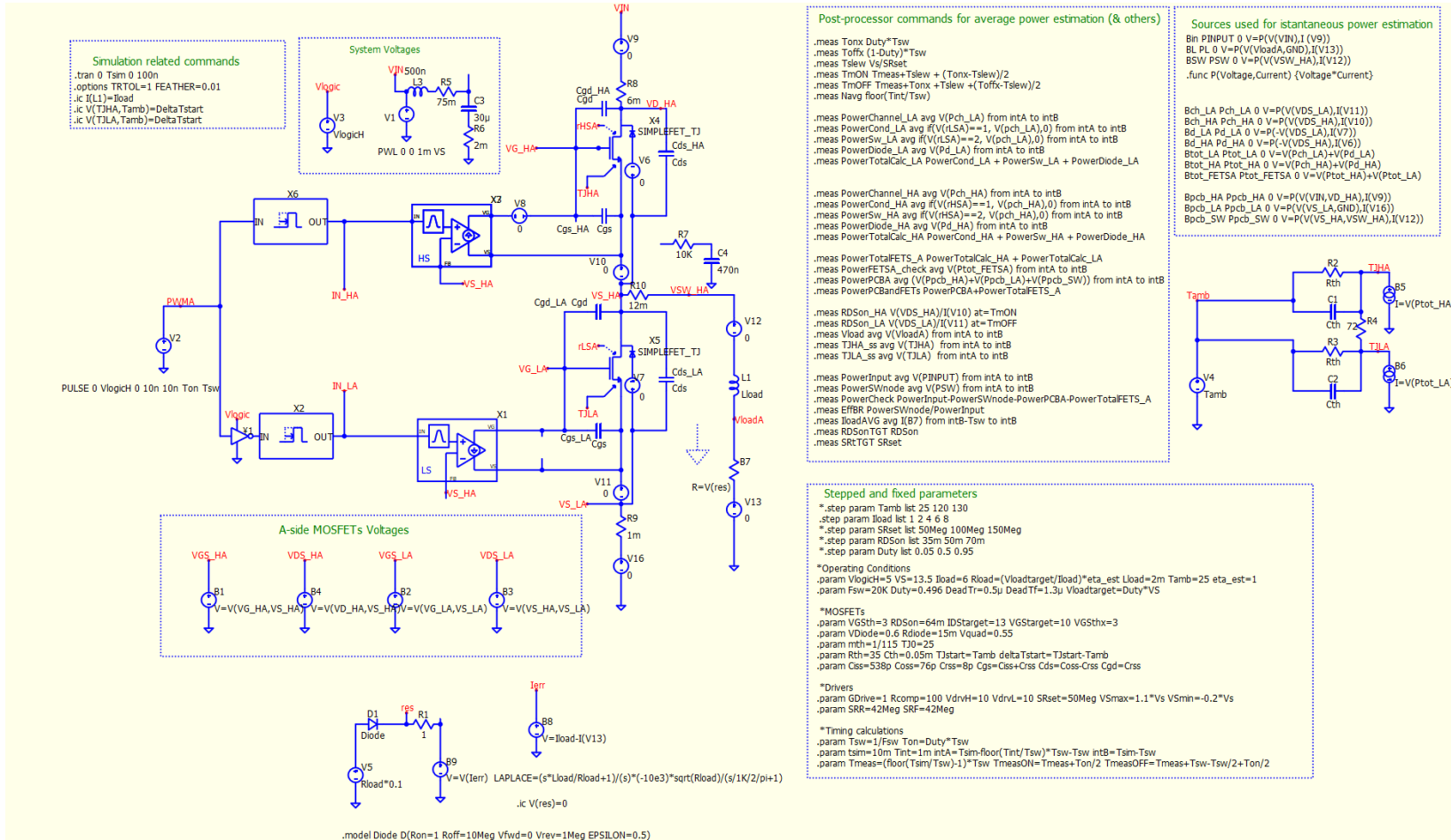


Testbench Comparison (MOSFET Level 0 Model vs. Simple MOSFET)

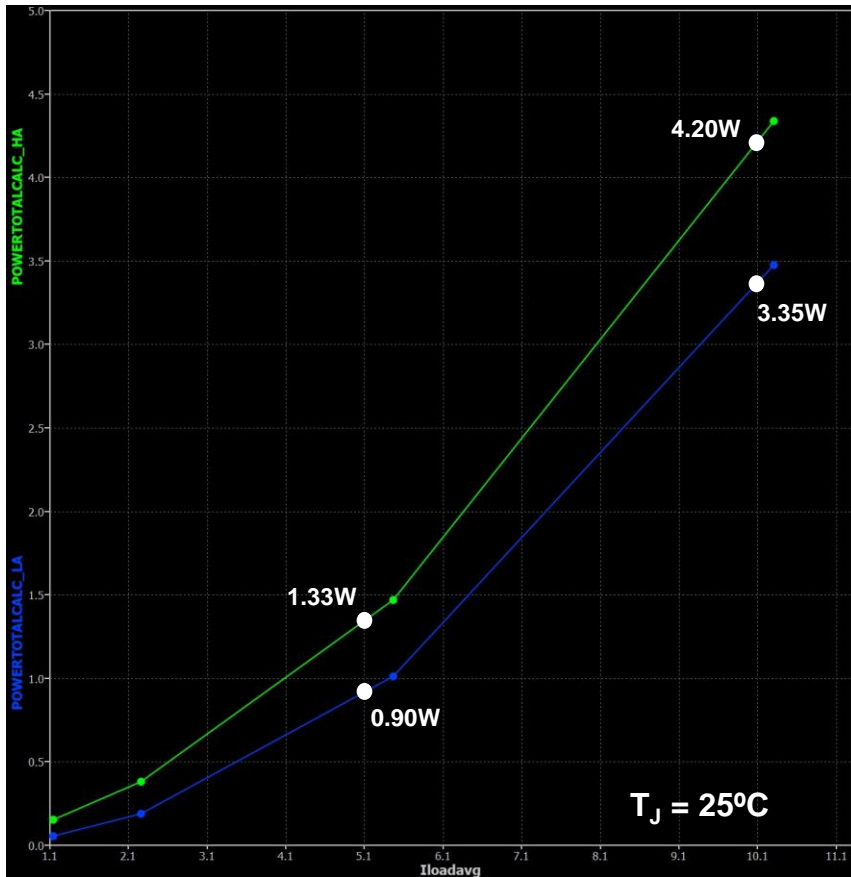MOSFET Model (From Vendor) Based Testbench







Simple MOSFET Testbench

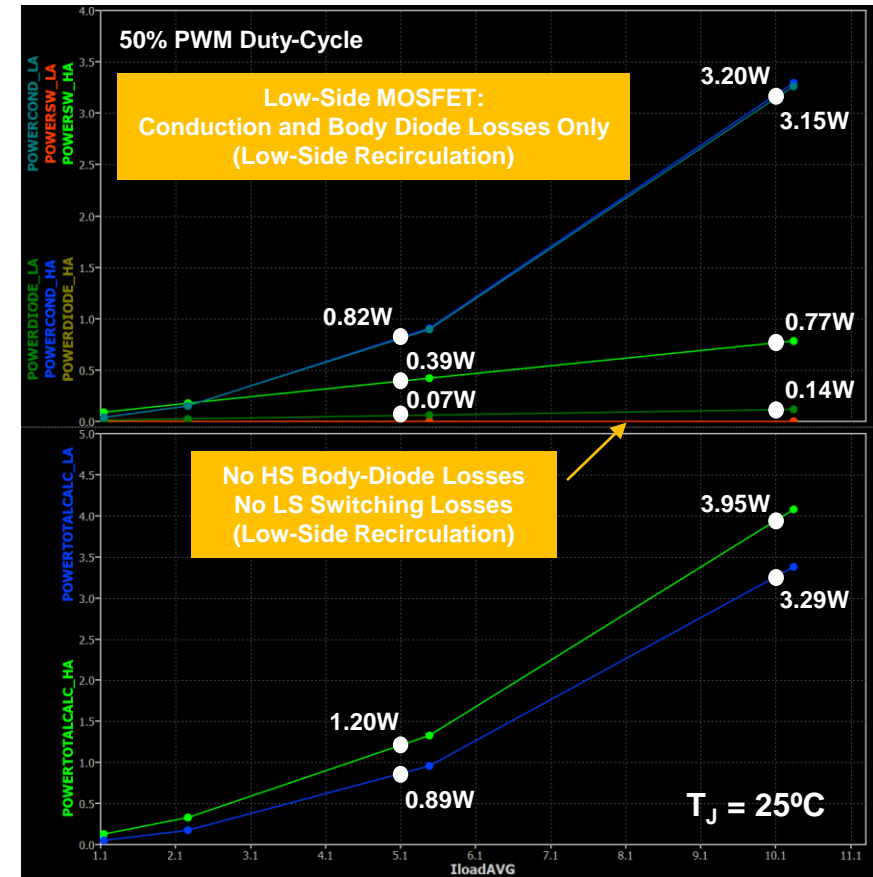

Validation Testbench

$$\langle P_D(t) \rangle = \frac{1}{T_{PWM}} \int_0^{T_{PWM}} v(t) \times i(t) dt$$

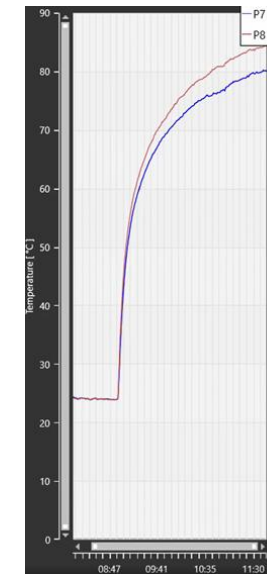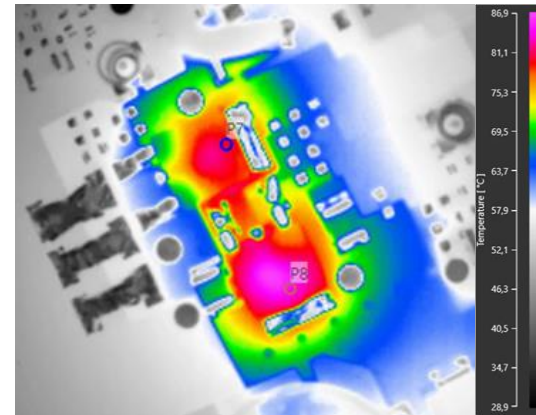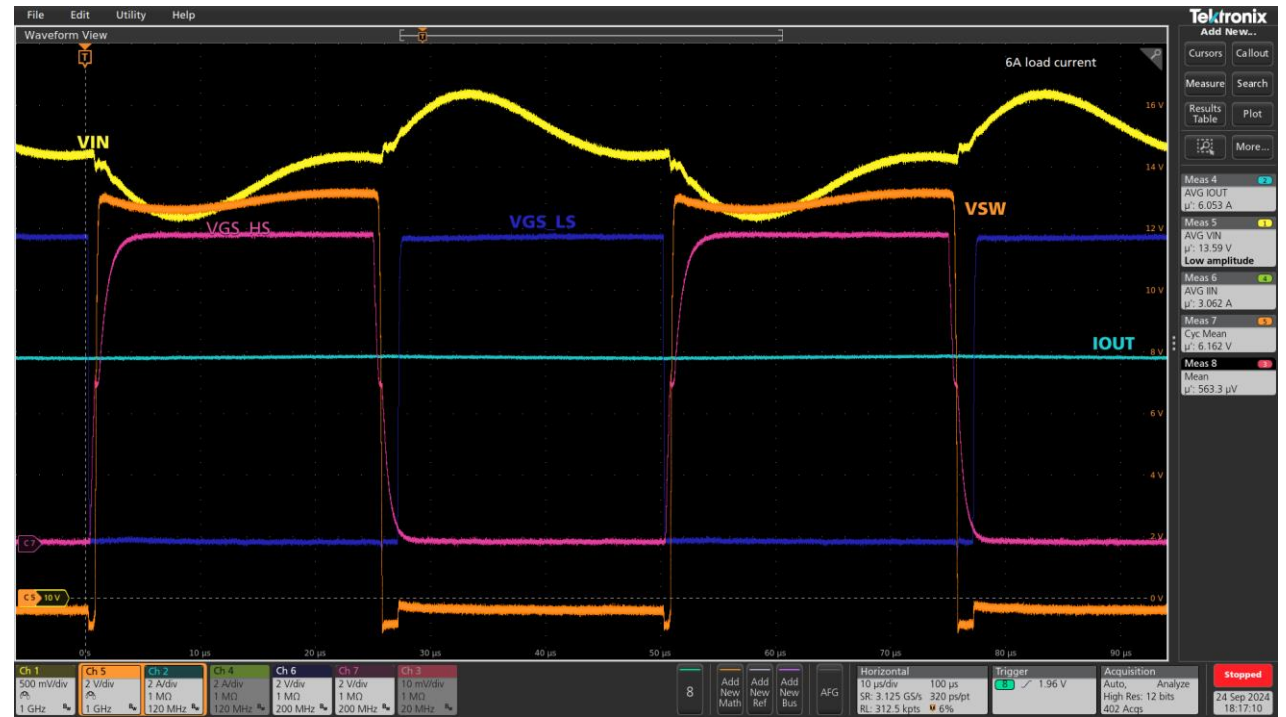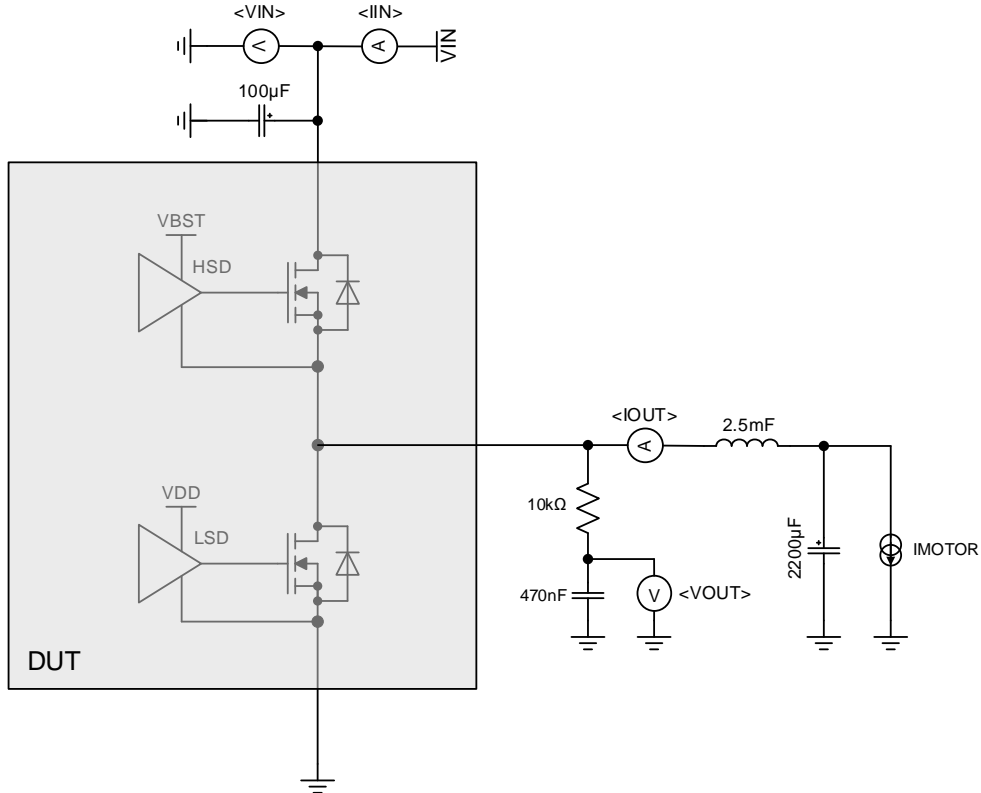Cycle mean value of the voltage x current product



Model Comparaison

Invalid assumption
 $R_{ds(on)}$ drop > BG diode V_F

	Average Motor Current [A]	High-Side MOSFET						Low-Side MOSFET				PCB	Low-Side + High-Side MOSFETs	MOSFETs + PCB	
		Conduction Losses [W]	Turn-On Switching Losses [W]	Turn-Off Switching Losses [W]	Switching Losses [W]	Back-Gate Diode Losses [W]	Total [W]	Conduction Losses [W]	Switching Losses [W]	Back-Gate Diode Losses [W]	Total [W]	Total copper losses [W]	Total losses [W]	Total losses [W]	
1 st order approximation	1	0.030	0.046	0.046	0.092	0	0.122	0.030	0	0.061	0.091	Not included	0.21		
	2	0.132	0.092	0.092	0.184	0	0.316	0.132	0	0.122	0.254		0.57		
	4	0.600	0.184	0.184	0.367	0	0.967	0.600	0	0.258	0.858		1.83		
	6	1.620	0.275	0.275	0.551	0	2.171	1.620	0	0.408	2.028		4.20		
	8	4.032	0.367	0.367	0.734	0	4.766	3.456	0	0.544	4.000		8.77		
IFX FET Spice Model Level 0 (T_j fixed at 25°C)	1	not available in the vendor model					0.143	not available in the vendor model					0.015	0.20	0.22
	2	not available in the vendor model					0.349	not available in the vendor model					0.062	0.53	0.59
	4	not available in the vendor model					0.940	not available in the vendor model					0.25	1.55	1.80
	6	not available in the vendor model					1.780	not available in the vendor model					0.56	3.07	3.63
	8	not available in the vendor model					2.880	not available in the vendor model					0.99	5.09	6.10
Simple FET Spice Model	1	0.030			0.093	0	0.123	0.029	0	0.026	0.055	0.015	0.18	0.20	
	2	0.120			0.190	0	0.310	0.120	0	0.056	0.176	0.062	0.49	0.55	
	4	0.580			0.370	0	0.950	0.540	0	0.120	0.660	0.25	1.61	1.86	
	6	1.650			0.540	0	2.190	1.500	0	0.190	1.690	0.56	3.89	4.45	
	8	4.390			0.690	0	5.080	1.700	0	0.950	2.650	0.99	7.73	8.72	
Lab Measurement	1	Not practical to measure experimentally						Not practical to measure experimentally					Not practical to measure experimentally	Not practical to measure experimentally	
	2	Not practical to measure experimentally						Not practical to measure experimentally						0.24	
	4	Not practical to measure experimentally						Not practical to measure experimentally						0.65	
	6	Not practical to measure experimentally						Not practical to measure experimentally						2.15	
	8	Not practical to measure experimentally						Not practical to measure experimentally						4.81	

<7.5% error

- Notes:
- 13.5V input voltage
 - 1A / 2A / 4A / 6 / 8A average motor current
 - 20kHz PWM operation
 - 50% duty-cycle
 - 2us back-gate diode time
 - 40V/us slew-rate (340ns rise time, 340ns fall time)
 - 65mOhm $R_{ds(on)}$, 0.85V back-gate diode voltage
 - ca 20mOhm PCB trace resistance

Low-side recirculation

High-side active switch (i.e. output slew-rate control)

Conclusion

- 1st order approximations are very handy to draw an initial picture of the power-stage losses
- Simple MOSFET model provides a powerful method to breakdown the losses
- Simple MOSFET model can be easily defined with datasheet parameters
- Fast simulation time
- Temperature dependencies help to improve first order estimates
- Good degree of accuracy: predicted power dissipation off by less than 10% vs. bench measurements
- Q_{rr} modeling is usually not required in motor driver applications switching at ca. 20kHz.
- Helpful to optimize the tradeoff conduction losses, switching losses and electromagnetic noise emissions
- Do not underestimate PCB copper losses

COMPLEMENTARY MATERIAL

MOSFET SPICE Level (sub) 0




$$g(V(D,S), V(G,S))$$



$$f(V(D,S), V(G,S))$$





Cut Off	$V_{GS} \leq V_T$	$I_{DS} = 0$
Linear	$V_{GS} > V_T, V_{DS} \leq V_{GS} - V_T$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})$
Saturation	$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$

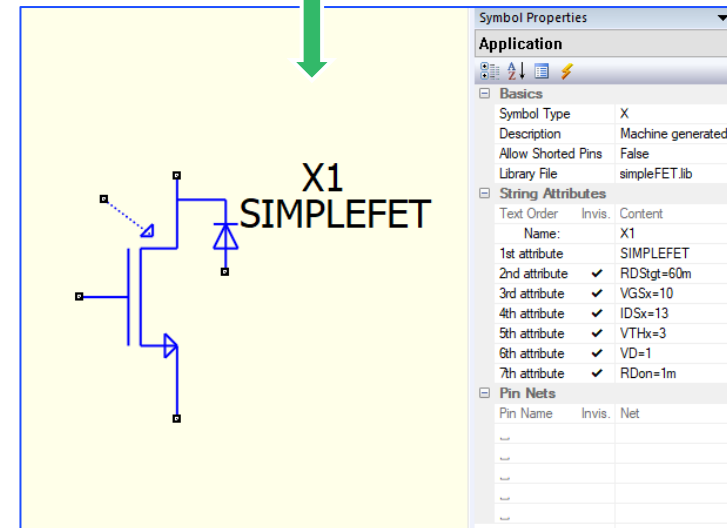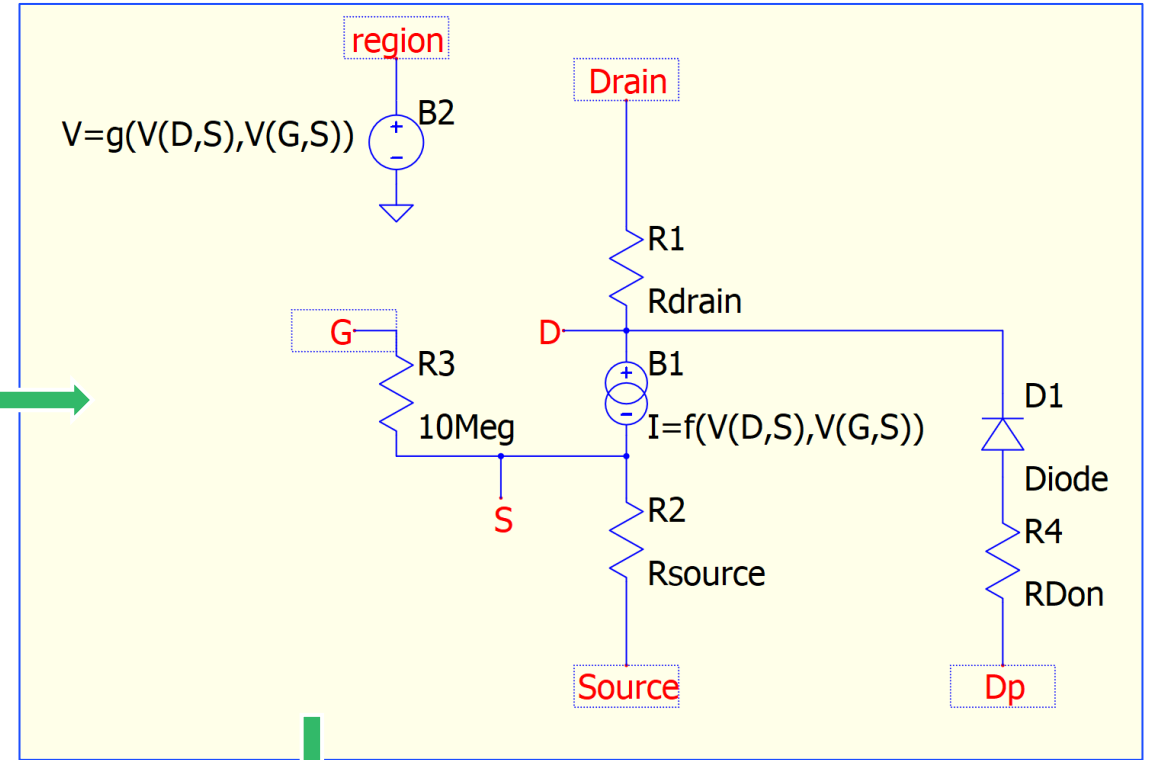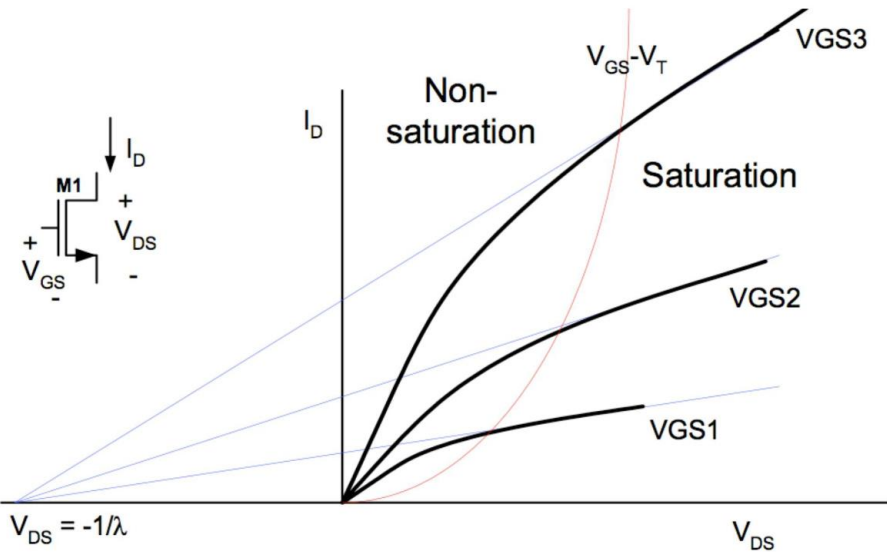

MOSFET SPICE Level (sub) 0

Cut Off	$V_{GS} \leq V_T$	$I_{DS} = 0$
Linear	$V_{GS} > V_T, V_{DS} \leq V_{GS} - V_T$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})$
Saturation	$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$

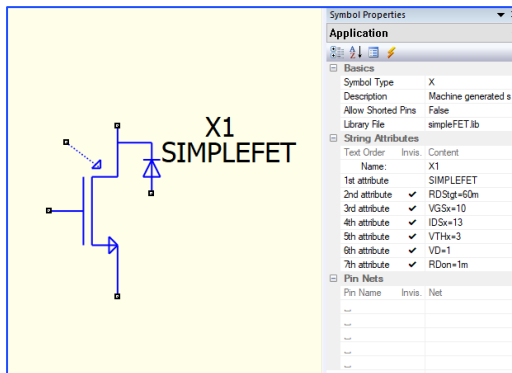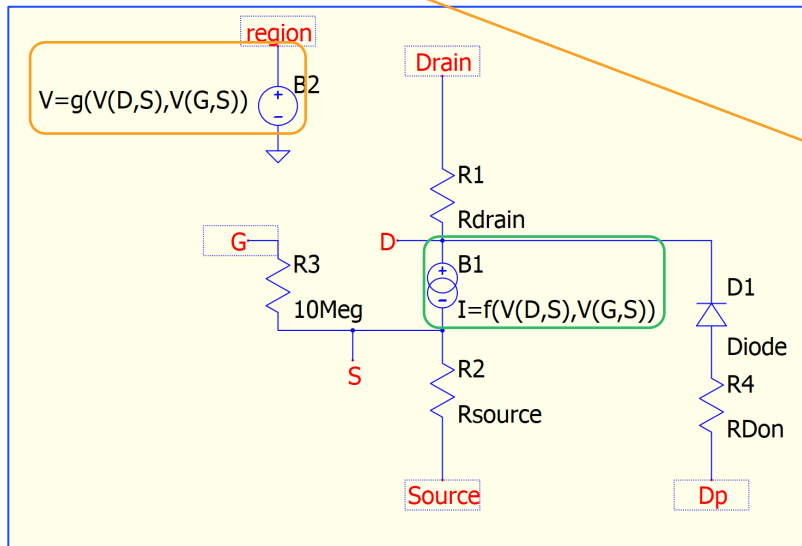

Params in subckt are overwritten when new values are passed through symbol

```
.subckt simpleFET G Drain Source Dp region
```

*External resistances

```
R2 Drain D Rdrain
R3 Source S Rsource
R1 G S 10Meg
```

*Body diode model

Simple PWL diode model

```
D1 DR D Diode
R4 Dp DR RDon
.model Diode D(Ron=Rdiode Roff=RDoff Vfwd=VD Vrev=VBD
EPSILON=quad)
```

*Mosfet current

```
B1 D S I=if(V(G,S)<VTH, 0, if(V(G,S)-VTH>=abs(V(D,S)),
+ Kp*(V(G,S)-VTH-abs(V(D,S))/2)*V(D,S), Kp/2*(V(G,S)-VTH)**2)
) +
+ if(V(D,S)>0 & V(G,S)>VTH,V(D,S)*lambda,0)
B2 region 0 V=if(V(G,S)<VTH, 0, if(V(G,S)-VTH>=V(D,S),1,2))
```

*Mosfet parameter extraction

```
.param Kp=Kp_lin
.param Kp_lin=IDSx/(VGSx-VTHx-VDSx/2)/VDSx
.param Kp_sat=IDSx*2/((VGSplx-VTHx)^2)
.param VDSx=(Rdsx-Rdrain-Rsource)*IDSx
.param VTH=VTHx
```

To be extracted from MOSFET datasheet

*Mosfet parameters

```
.param RDStgt=65m
.param Rdrain=1u Rsource=1u
.param lambda=1/235
.param Rdsx=RDStgt Rdsoff=10Meg
.param VGSx=10 IDSx=12 VTHx=4 VGSplx=5.7
```

*Diode parameters

```
.param RDon=7m Rdiode=1m RDoff=10Meg VD=10 VBD=1Meg quad=1
.ends simpleFET
```