

Maximizing the Power Density of DC Fast-Charging Systems with an LLC Power Supply

February 2023

Agenda

- Overview of Charging Infrastructure
- DC Fast-Charging Station Block Diagram
- MPS Solutions for Charging Infrastructure
- Designing a Resonant LLC Power Supply
- Conclusion

Overview of EV Charging Infrastructure

- L1 Charger:
 - L1 chargers charge at 3kW or less
 - Uses OBC inside a vehicle to charge the battery
- L2 Charger:
 - L2 chargers charge at 3kW to 22kW
 - Uses OBC inside a vehicle to charge the battery
- DC Fast Chargers (DCFC):
 - DCFC charge at 50kW to 400kW, and can charge 10% to 90% of an EV battery in as fast as 18 minutes




Charging Plug Standards Globally

AC

L1 (120V)
Power:1kW-3kW
L2 (208V-240V)
Power:3kW-19kW

China

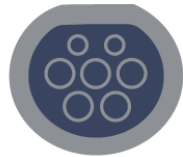

GB/T

EU

and rest of markets



Mennekes
(Type 2)

North America South Korea



J1772
(Type 1)

Japan



J1772
(Type 1)


All Markets

Tesla in EU uses CCS2




DC

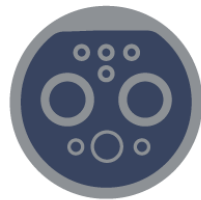
L3/DC Fast Charger
400V-800V
Power: 50kW-400kW



GB/T

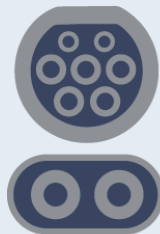

CCS2

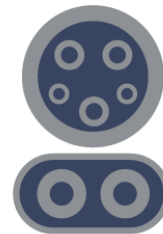

CCS1




CHAdeMO

Tesla

DC Fast-Charging System

DC Fast-Charging Station

- Converts a 3-phase AC voltage into a 250V to 800V DC voltage
- Contains several of the subunits on the right to get to a 350kW+ output
- Power factor correction (PFC) stage converts an AC voltage into an intermediate DC voltage
 - 3-phase, 3-level rectifier/inverter topology is typically used for the PFC stage
- Second stage converts the intermediate DC voltage into the target battery charging voltage

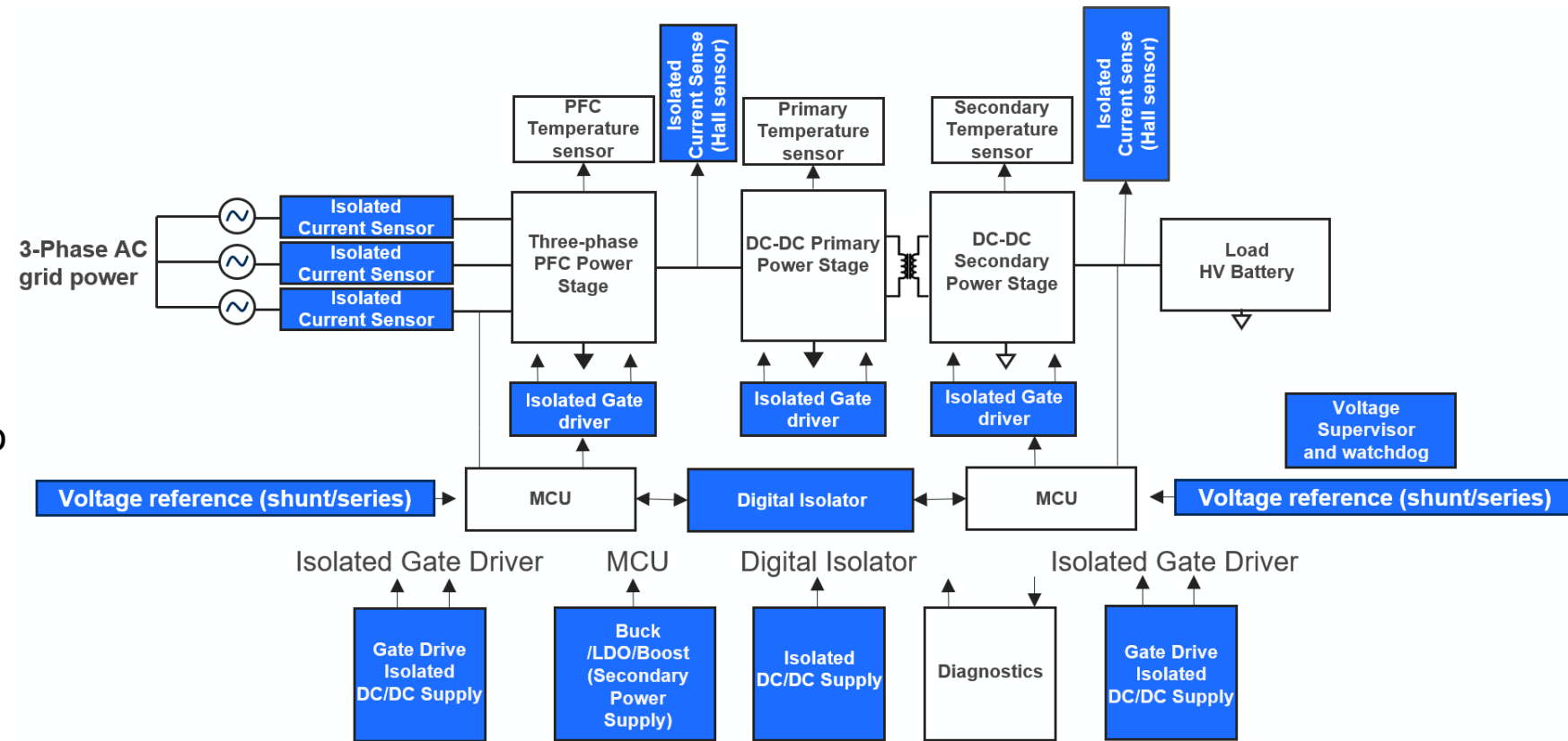

MPS Electrification – We Know What Drives You

✓ Electrification

Si Carbide

Compatible solutions

Integration

Low component count
Lower solution cost

800V Solutions

Enable high-voltage
charging solutions

✓ Technology

MPS
B C D Power | Analog

800+ SKUs

Broad portfolio with flexible,
scalable solutions

MPSafe™

Functional safety ready

✓ Experience

12 Years

Automotive industry

1.8 Billion

Automotive units shipped

✓ Quality

10x

Finer quality record vs.
industry standard

0.06 DPPM

Quality record



Run Cooler



Design Faster



Push Higher
Performance



Achieve EMC
Resilience



Capacitive
Isolation



Integrated
Solutions




Improve Quality



Extend Battery
Runtime

Automotive EV/MHEV Applications

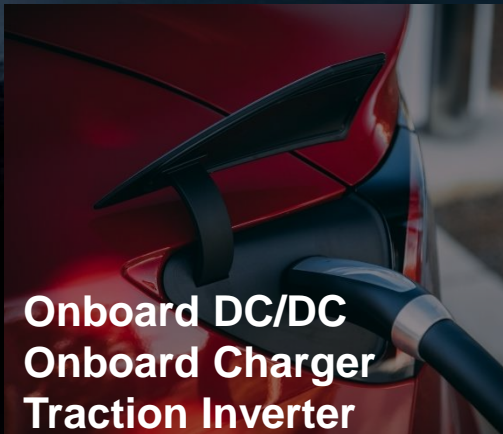

- Supports various isolation requirements to maximize system safety level
- Industry-leading performance
- Switching frequency up to 10MHz to minimize solution size


Isolated products compliant with different safety specifications:

- UL1577 – E322138
- VDE V 0884-11

AEC-Q100 Qualified Products

- Isolated Gate Drive
- Digital Signal Isolator
- Isolated Power
- Isolated Amplifier
- Half-Bridge GaN Driver

Digital Isolator/Power Supply Roadmap

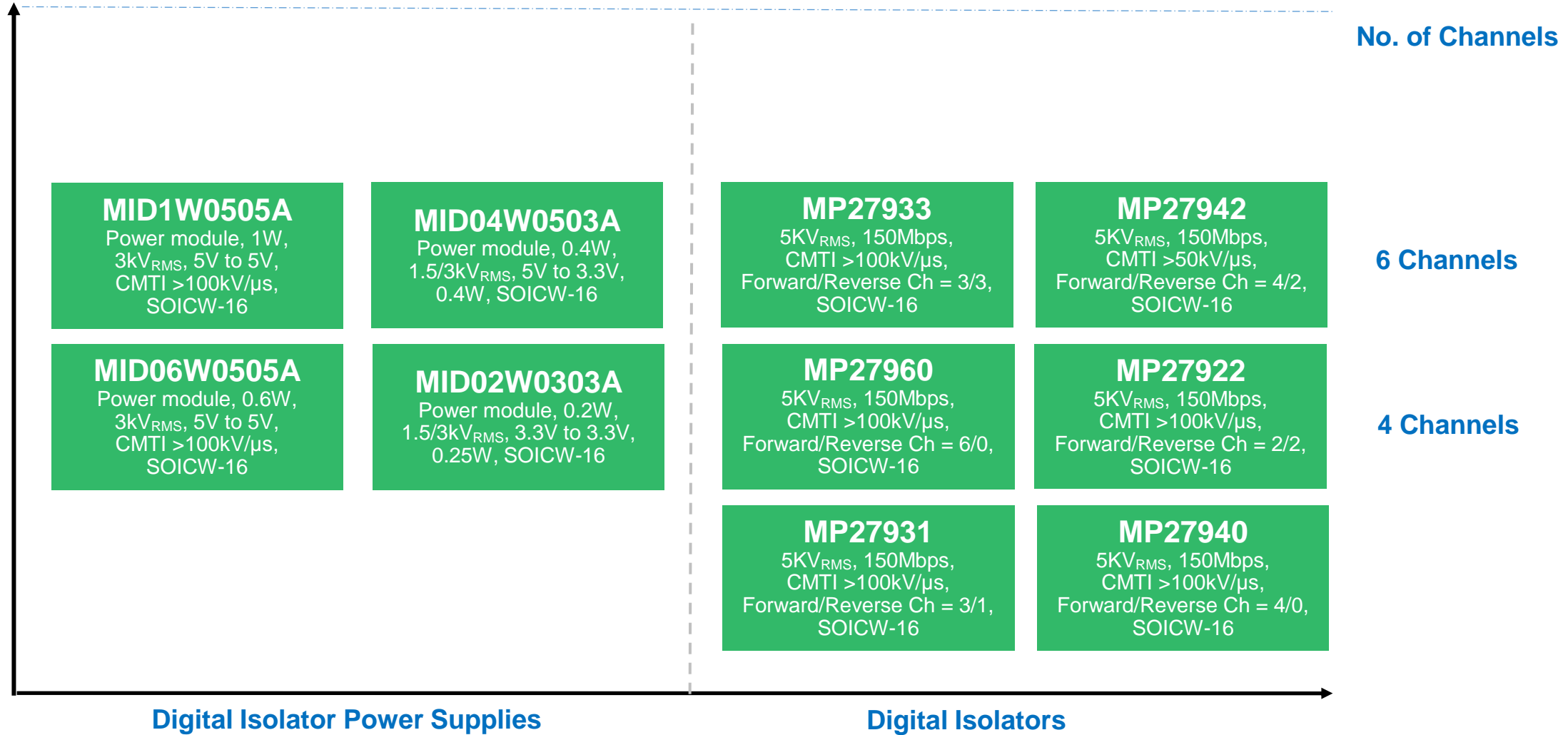

Newly Released


Sampling

MID1W0505A- 5V to 5V Isolated Module

Key Features:

- Input Range: 3V to 3.6V or 4.5V to 5.5V
- 3.3V/5V Output Voltage
- Excellent Load Transient Performance
- 0.5% Load Regulation, 1.5% Line Regulation
- Strong Magnetic Field Immunity
- 0.25W, 0.4W, 0.6W, 1W Output Rating Option
 - MID1: 1W, MID06: 0.6W
 - MID04: 0.4W, MID02: 0.2W
- SCP, OCP, and OTP
- 3kV_{RMS} Isolation
- 54% Efficiency
- Low Emission: Meets CISPR 32 Class B
- Small SOICW-16 Package

Typical Circuit

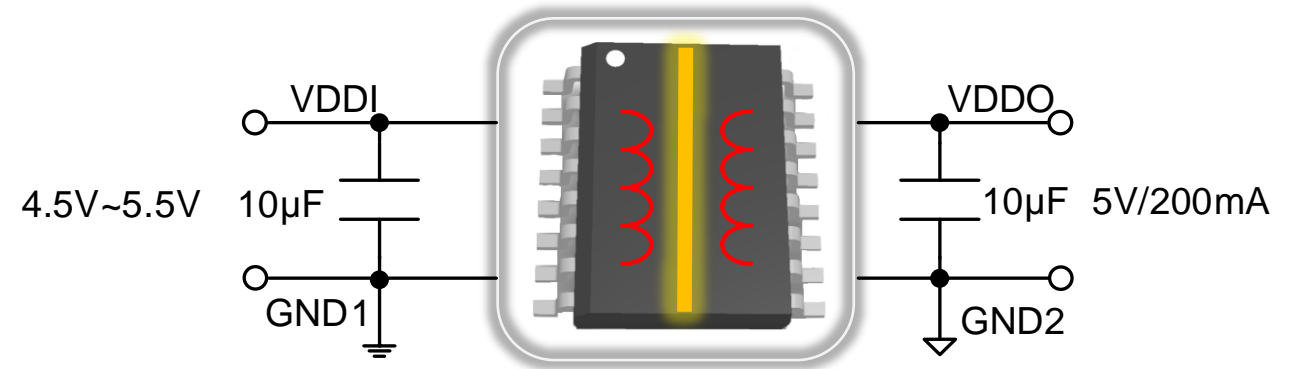

Applications

Industrial automation, PLC I/O modules
Grid protection relays
Isolated sensor power
Isolated bias for RS-485/CAN

MP(Q)279xx – 4~6 Channel digital isolator


Key Features

- Wide Input Range: 2.5V to 5.5V
- Up to 150Mbps Data Rate, 20Mbps Option
- MP279xx family (forward channels/reverse channels)
 - 4 channel 31 (3/1), 40 (4/1), 22(2/2)
 - 6 channel 33 (3/3), 42(4/2), 60(6/0)
- Ultra-Low Power Supply Current
- High Electromagnetic Immunity
- $>\pm 100\text{kV}/\mu\text{s}$ Common-Mode Transient Immunity
- 13ns Propagation Delay for 5V Operation
- 5kV_{RMS} Isolation, $2.5\text{kV}_{\text{RMS}}$ Option
- Selectable Channel Direction
- Selectable Output Default Value
- Available in SOICW-16


Applications

- E-Meters, Isolated ADCs/DACs, Motor Control, Industrial Automation, SPI Isolation

Typical Circuit

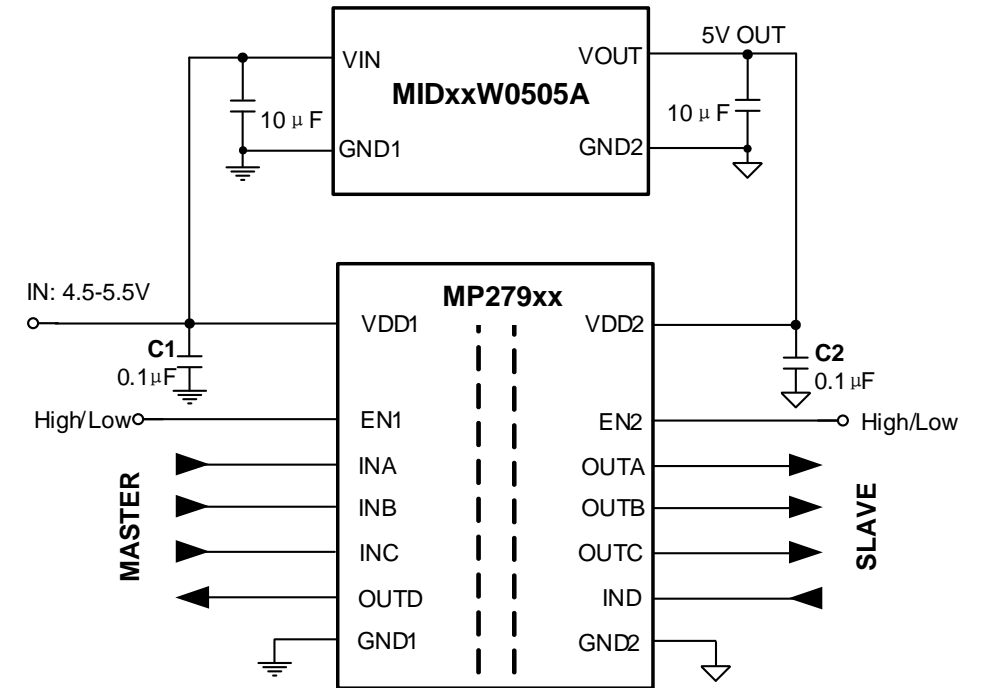

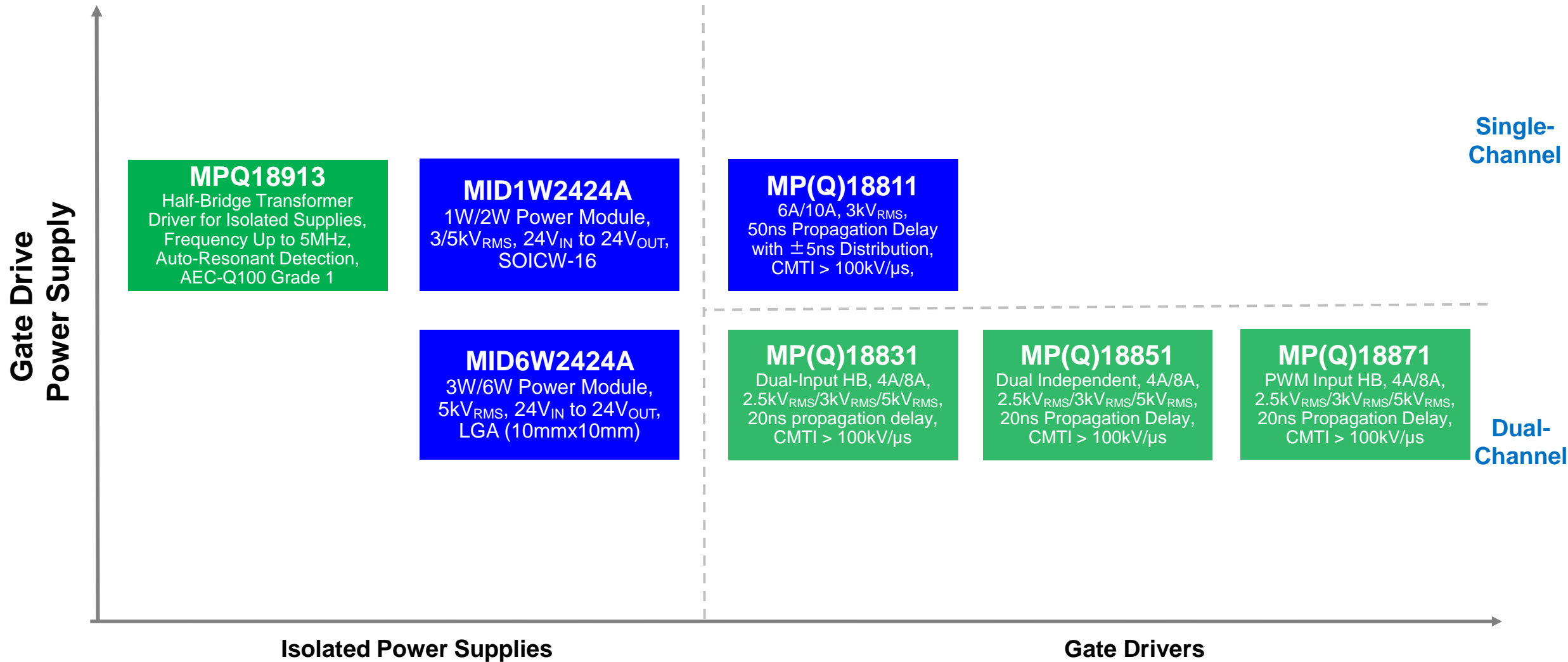Isolated Gate Driver/Power Supply Roadmap



Newly Released


Sampling



MP(Q)18811 – Isolated Single-Channel Gate Driver

FEATURES

- 5kV for SOIC-8 WB, 3kV_{RMS} Input to Output Isolation for SOIC-8 NB
- CMTI >100kV/μs
- TTL and CMOS Compatible Inputs
- Differential-Input Control
- Up to 30V Output Drive Supply with UVLO Options (5V/8V/10V/12V/15V)
- Output Configurations: Single-Output with Miller Clamp or Split Outputs
- 6A Source/10A Sink Peak Current Output
- 50ns Typical Propagation Delay
 - Tight ±5ns Distribution from Part to Part
- Active Miller Clamp
- Operating Junction Temperature Range –40°C to +150°C
- Packages: SOIC-8 NB, SOIC-8 WB
- AEC-Q100 Qualified (MPQ18811)

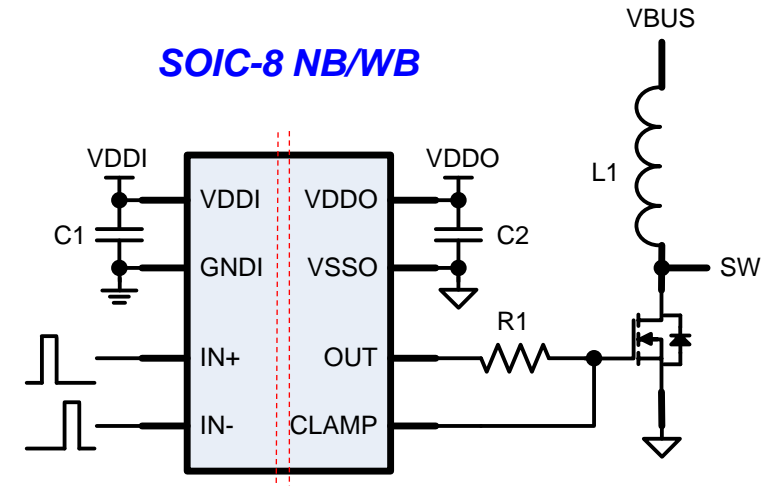

Applications


- SiC/IGBT Gate Drive Power Supply
- Industrial Automation, PLC I/O modules
- DC Fast Charger
- Grid protection relays

MP(Q)1883/5/71 - Isolated Dual-Channel Gate Driver


FEATURES

- Flexible Configuration: Rich Family, Independent Dual-Channel Driver, Dual-/PWM-Input Half-Bridge Driver
- Up to 5kV_{RMS} Isolation
- CMTI >100kV/μs
- TTL and CMOS Compatible Inputs
- 30V Output Drive Supply with UVLO Options (5V/8V/10V/12V/15V)
- 4A Source/ 8A Sink Peak Current Output
- 50ns Typical Propagation Delay
 - Tight ±10ns Distribution from Part to Part
- Standard Packages: Narrow Body SOIC-16; Wide Body SOIC-16, 5mm x 5mm LGA-13, **Wide Body SOIC-14 Packages (3.3mm creepage)**
- AEC-Q100 Qualified
- Operating Junction Temperature Range -40°C to +150°C


MPQ18831
Dual Input HB

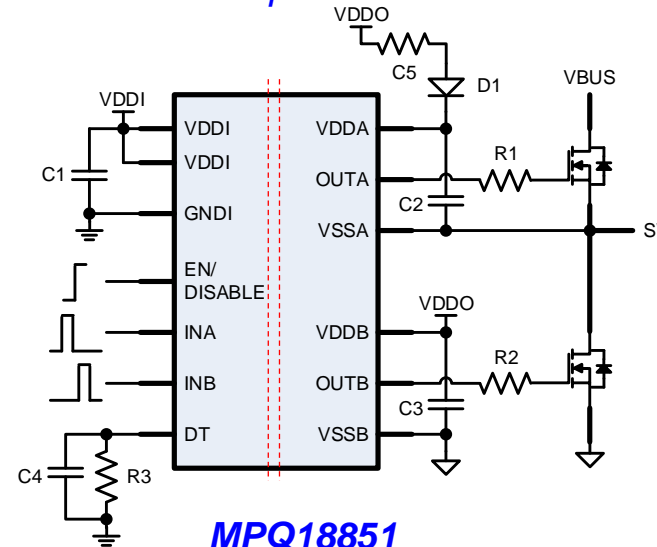


MPQ18851
Dual Independent Drivers

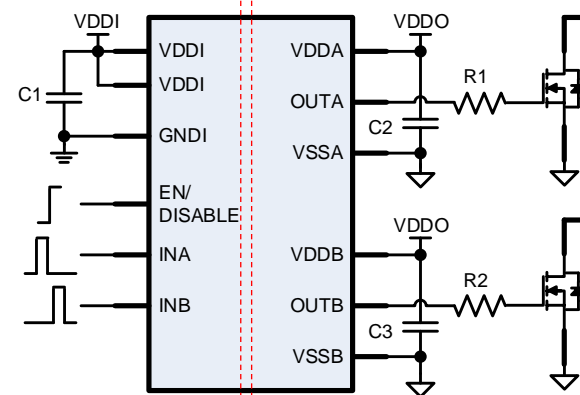

3.3mm creepage

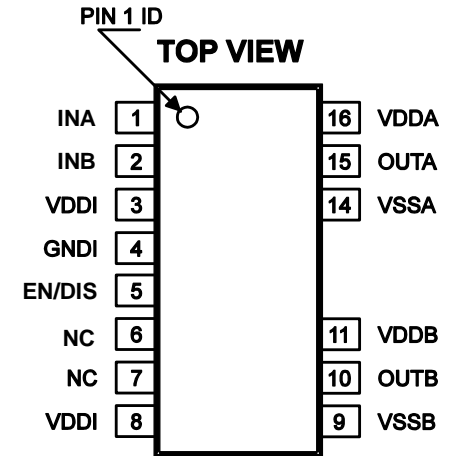


MPQ18871
PWM Input HB

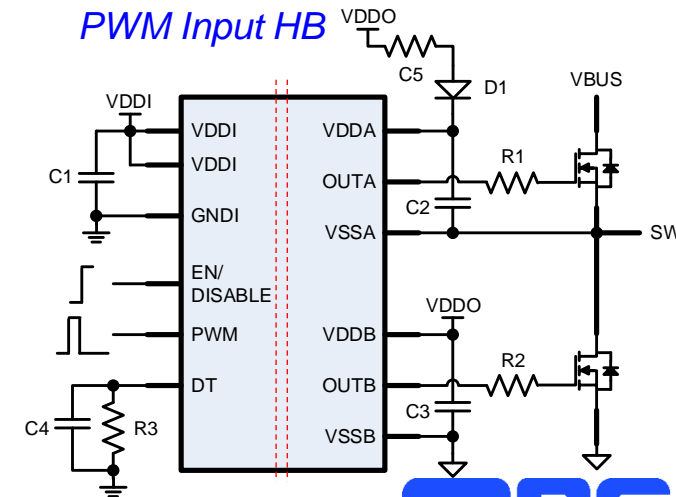


Isolation Voltage Rating with Different Packages


SOIC-16 WB

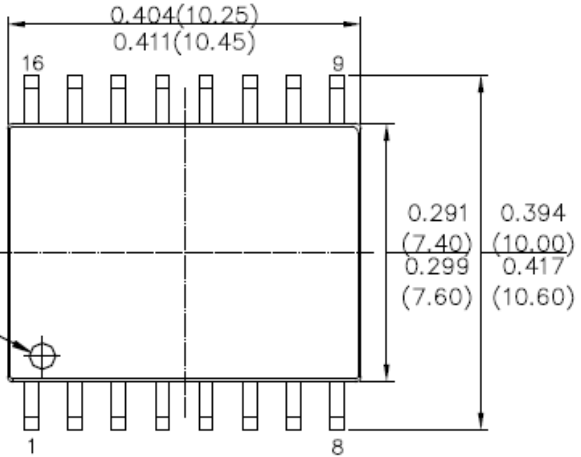


SOIC-14 WB

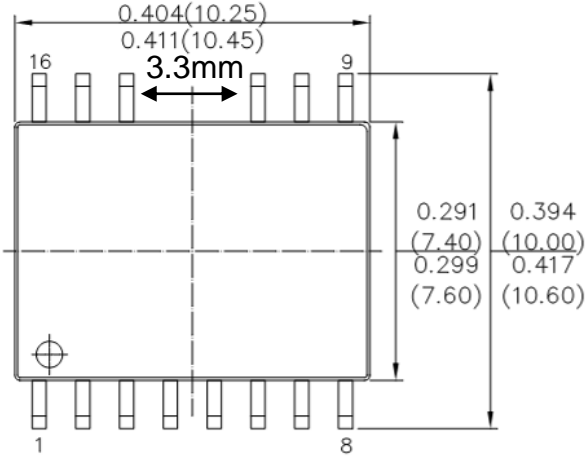

SOIC-16 NB

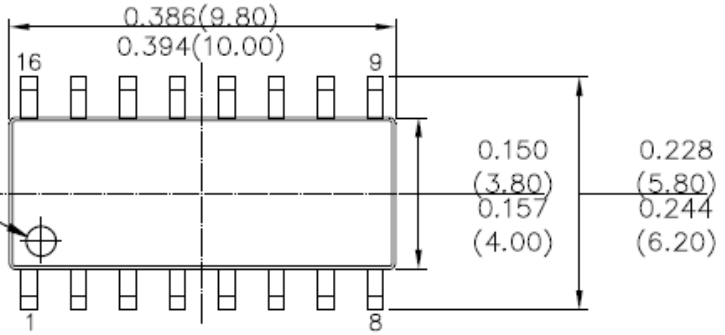

LGA-13

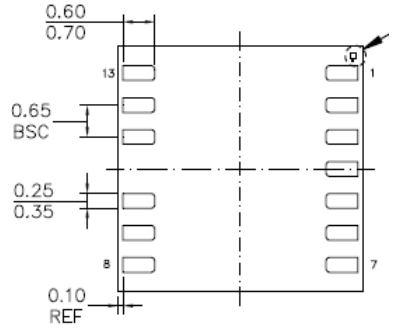

Package	Isolation Rating
SOIC-16 WB/SOIC-14 WB	5kV _{RMS}
SOIC-16 NB	3kV _{RMS}
LGA-13	2.5kV _{RMS}

MID6W2424A- 24V to 24V Isolated Module


Key Features:

- Input Range: 5V-30V (Typical: 24V \pm 10%)
- Power level 3W/6W, **87% peak efficiency**
- Transformer Turns ratio
 - MID6W1224/MID3W1224 1:2 turns ratio
 - MID6W1524/MID3W1524 1:1.6 turns ratio
 - MID6W2424/MID3W2424 1:1 turns ratio
- **Strong Magnetic Field Immunity**
- SCP, OCP, OTP Protection
- 5kVrms Isolation
- LGA 10x10mm package
- Operating Temperature -40C to 105C

Applications


- SiC/IGBT Gate Drive Power Supply
- Industrial Automation, PLC I/O modules,
- Grid protection relays

Typical Circuit

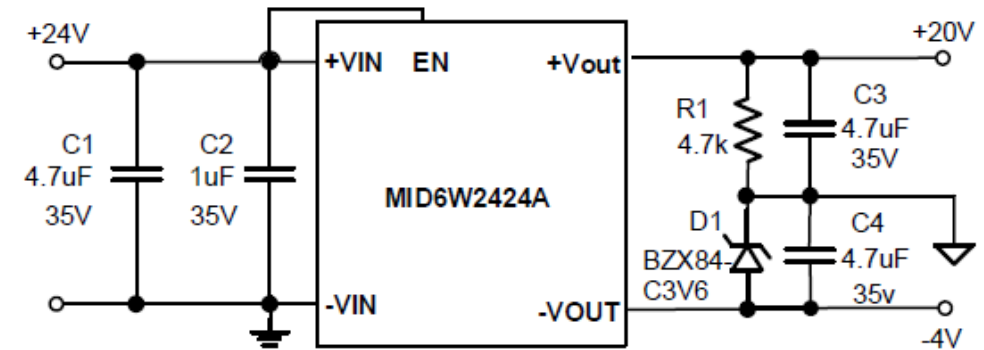



SiC Gate Drive Power Supply

PACKAGE REFERENCE

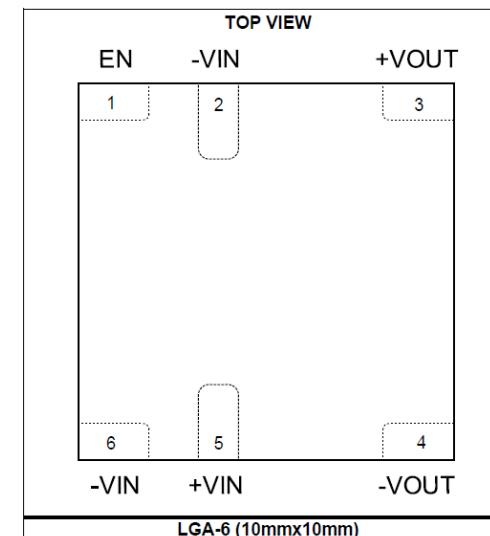

MID6W2424A performance

$V_{IN} = 24V$, $I_{out} = 0.25A$ (Full Load), $T_A = +25^{\circ}C$.

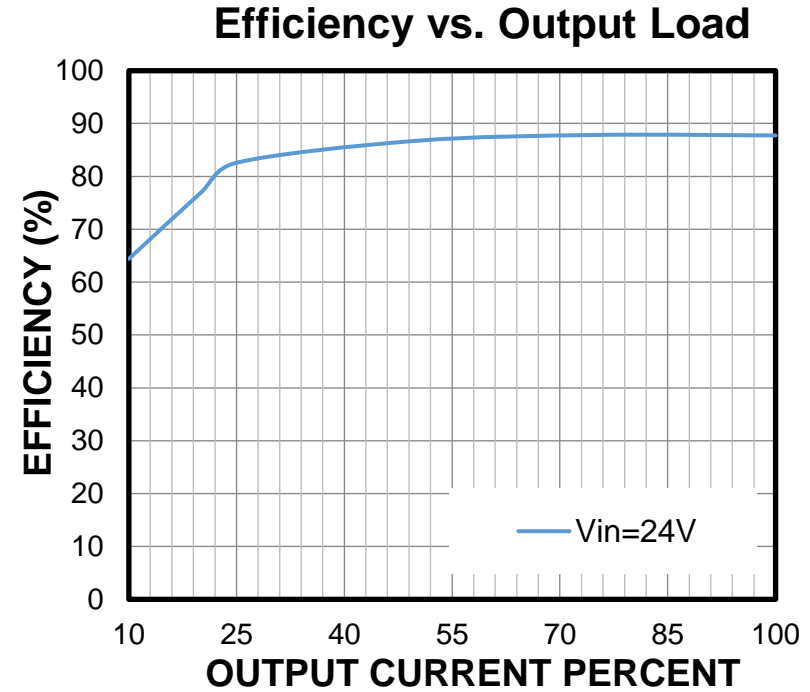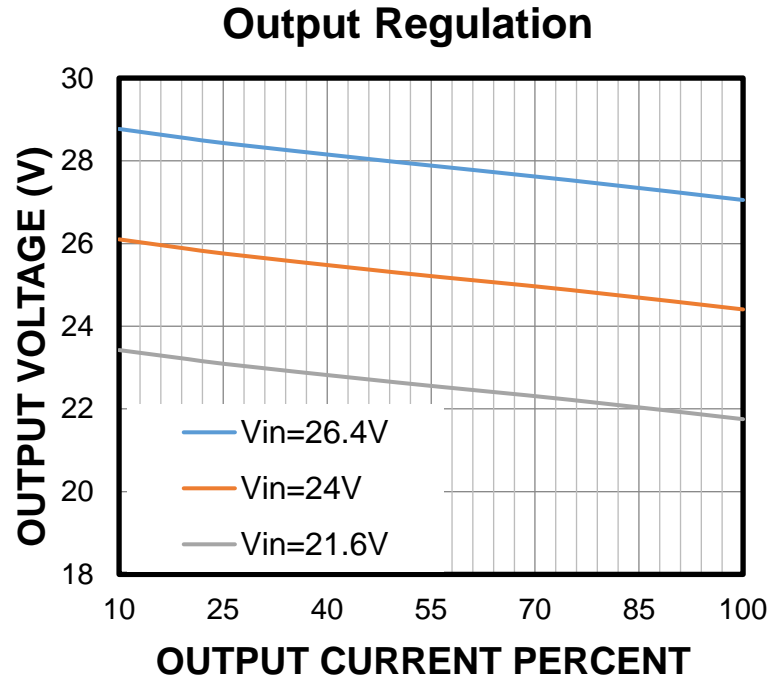



MPQ18913 – 30V, 0.5A LLC Transformer Driver for Isolated Bias Supplies

FEATURES

- 5V to 30V Input Voltage Range (50V Surge)
- Half-Bridge Transformer Driver for Isolated LLC Resonant Converters
- Configurable Frequency: 750kHz to 5MHz (913)
- Configurable Frequency: 750kHz to 10MHz (914)
- External Clock Input for Switching Synchronization
- Automatic Resonant Frequency Detection
- Optional Spread Spectrum for EMI Reduction
- Internal Soft Start
- OCP, SCP, OVP, OTP and FLT Reporting
- Supports Up to 5W
- Available in a QFN-10 (2mmx2.5mm) Package with Wettable Flanks

Applications

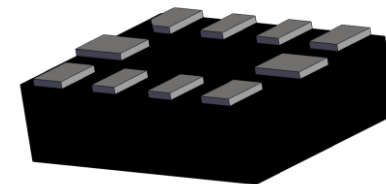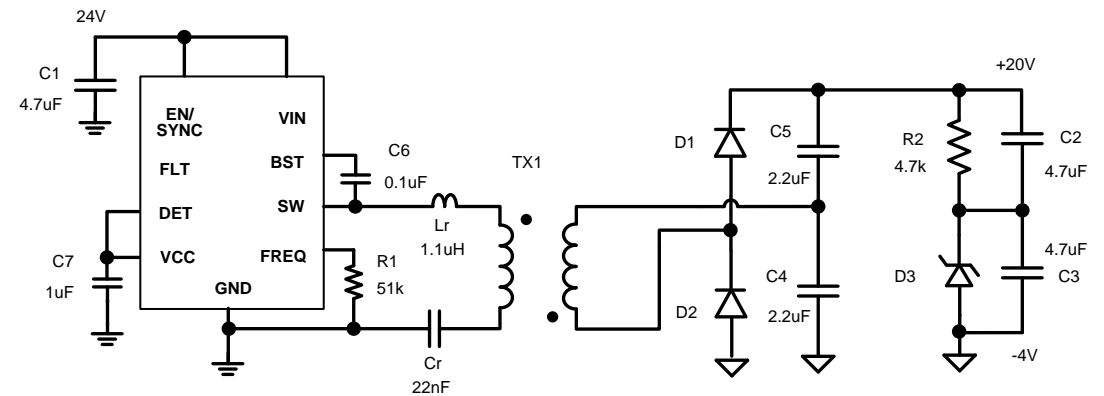- IGBT/SiC Gate Driver Bias
- EV DC Fast-Charging Stations
- EV Traction Inverters/Onboard Chargers




Available in a QFN-10 (2mmx2.5mm) Package

MPQ18913 Evaluation Board



EVQ18913-D-00A Evaluation Board

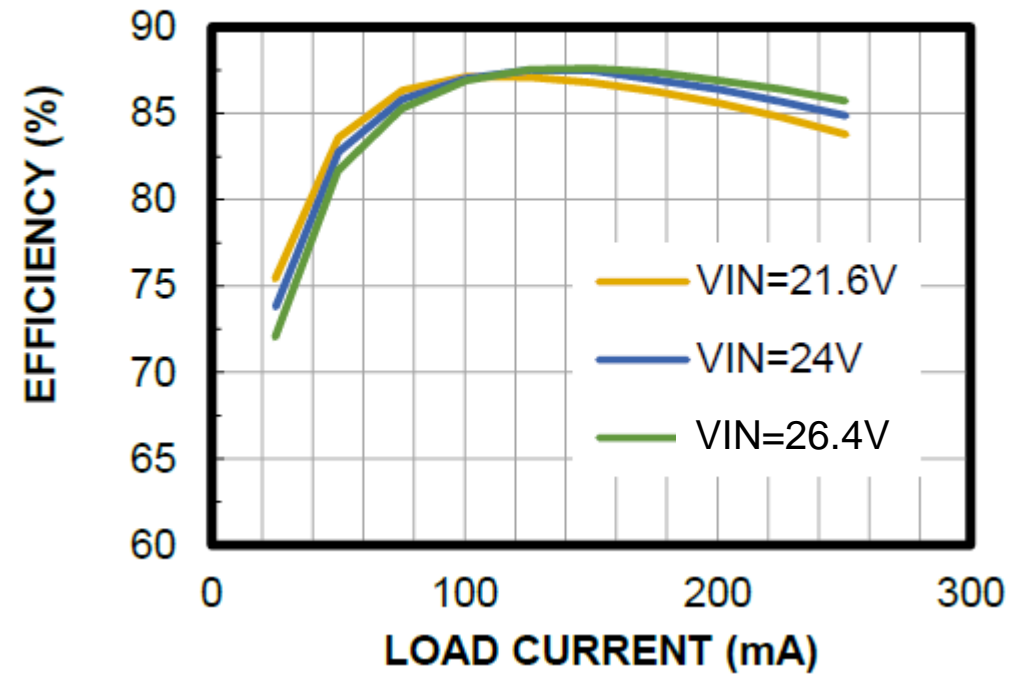
24V_{IN}, 24V_{OUT}, 1.33MHz
Efficiency vs. Load Current



MID1W2424A – 1W/2W, 24V Isolated Module

FEATURES


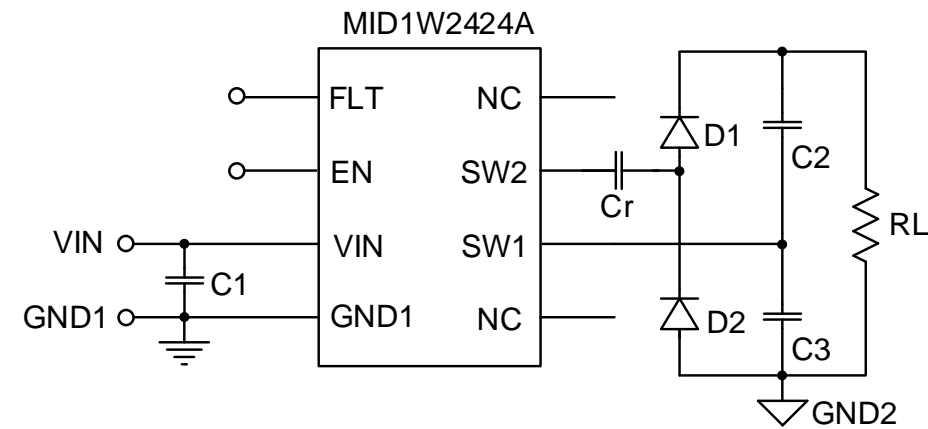
- 5V to 30V Input Voltage Operation Range
- 3kV_{RMS}, 5kV_{RMS} Isolation Voltage Options
- 1W, 2W Output Power Options
 - Integrated 1:1 Transformer
- 60% Efficiency with Full Load
- 100kV/ μ s CMTI
- 8pF Isolation Capacitance
- Soft Start, OCP, Input OVP, OTP, and FLT Indicator
- **AEC-Q100 Option**
- Operating Temperature -40°C to 125°C
- Available in an SOICW-16 Package



Applications



- IGBT/SiC Gate Driver Bias
- EV DC Fast-Charging Stations
- EV Traction Inverters/Onboard Chargers

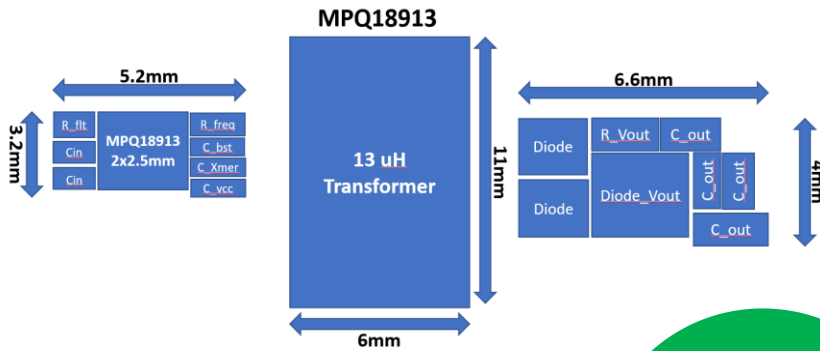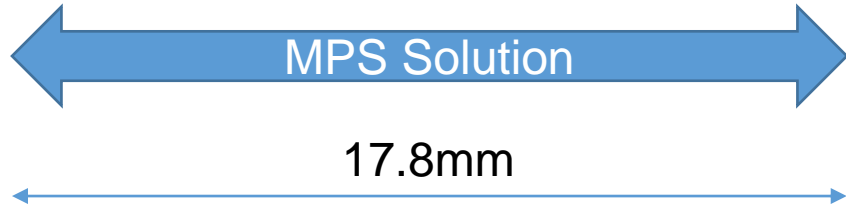PCB Footprint Analysis – Isolated Bias Supply



Solution Size: 109mm²
Total Area: 196mm²
Components: 21

**40%
Smaller
Solution
Size!**

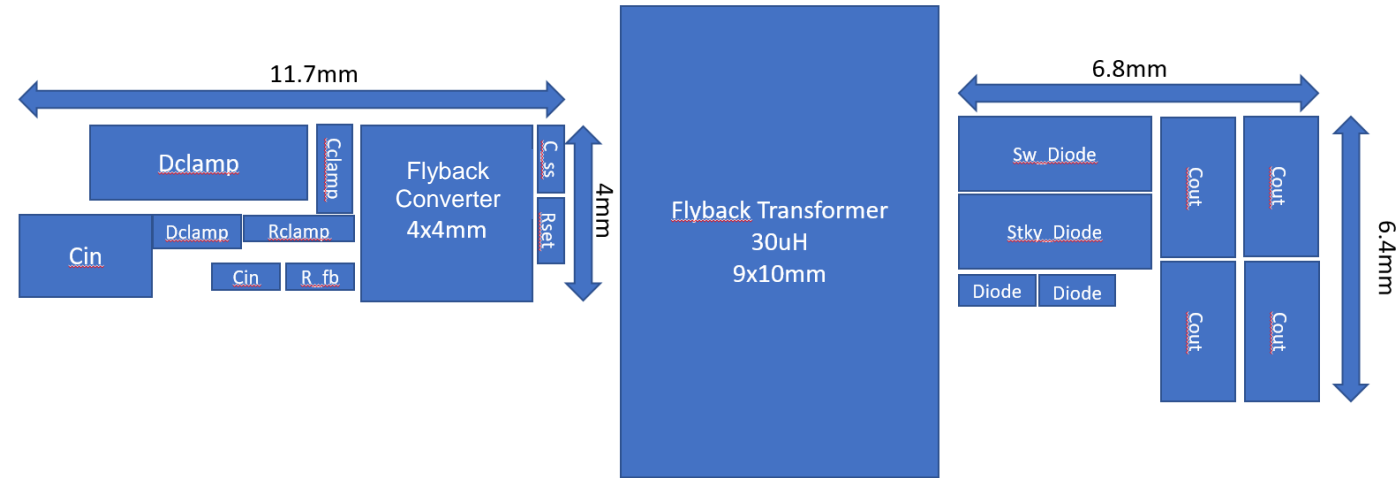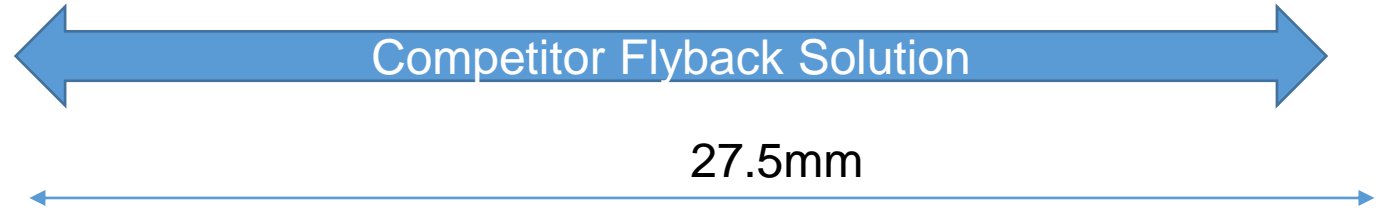

Solution Size: 180mm²
Total Area: 275mm²
Components: 26

MPQ18913 vs. Flyback BOM Cost Analysis

	MPQ18913 LLC Resonant Topology	PSR Flyback Converter Topology
HV Capacitor	11.6 μ F (= \$0.12)	4.7 μ F + 0.1 μ F (= \$0.05)
LV Capacitor	2 μ F (= \$0.01)	64 μ F + 47nF (= \$0.32)
Schottky Diode	2 (= \$0.08)	1 (= \$0.04)
Zener Diode	0	3 (= \$0.12)
Switching Diode	0	1 (= \$0.04)
Resistors	2 (= \$0.02)	3 (= \$0.03)
Transformer	13 μ H, 11x6mm (\$0.36)	30 μ H, 9mmx10mm (\$0.50)
IC	X	X
BOM Cost	= \$0.59 + X	= \$1.10 + X

**46%
Lower
BOM
Cost!**

LV capacitor assumed to be \$0.05/10 μ F
 HV capacitor assumed to be \$0.10/10 μ F

MPQ18913 vs. MID1W2424 BOM Size Comparison


	Discrete Solution MPQ18913	Module Solution MID1W2424
PCB Area for LV Size	25mm ²	120mm ²
Transformer Size	7 x 9 = 63mm ²	N/A
PCB Area for HV Size	30mm ²	30mm ²
Total Area	120mm ²	150mm ²
Max Height	9mm	2.65mm

- Transformer height is estimated by the creepage requirement of 7.1mm
- Discrete solution is smaller due to a small 63mm² transformer
- **The main advantage of module solutions are in the total height requirement from integrating the transformer**


MPQ18913 vs. Flyback Topology

	MPQ18913/4 LLC Resonant Topology	Competitor PSR Flyback Topology
Switching Frequency	High (Up to 10MHz)	Low (<400kHz)
Transformer Size	13 μ H (11mmx6mm)	30 μ H (10mmx10mm)
Leakage Inductance	Utilize leakage inductance as part of resonant tank	Leakage inductance induce voltage spike and extra loss
Isolation Voltage	High (up to 5kV)	Low (1.5kV)
Isolation Capacitance	Low (6pF)	High (13pF to 25pF)
EMI Emissions	Better	Worse
Package Size	2mmx2.5mm	4mmx4mm
Diodes (including Zener)	3	6
Solution Size	109mm ²	180mm ²
BOM Components	21 components	26 components


Isolated Power Supplies for Gate Drivers

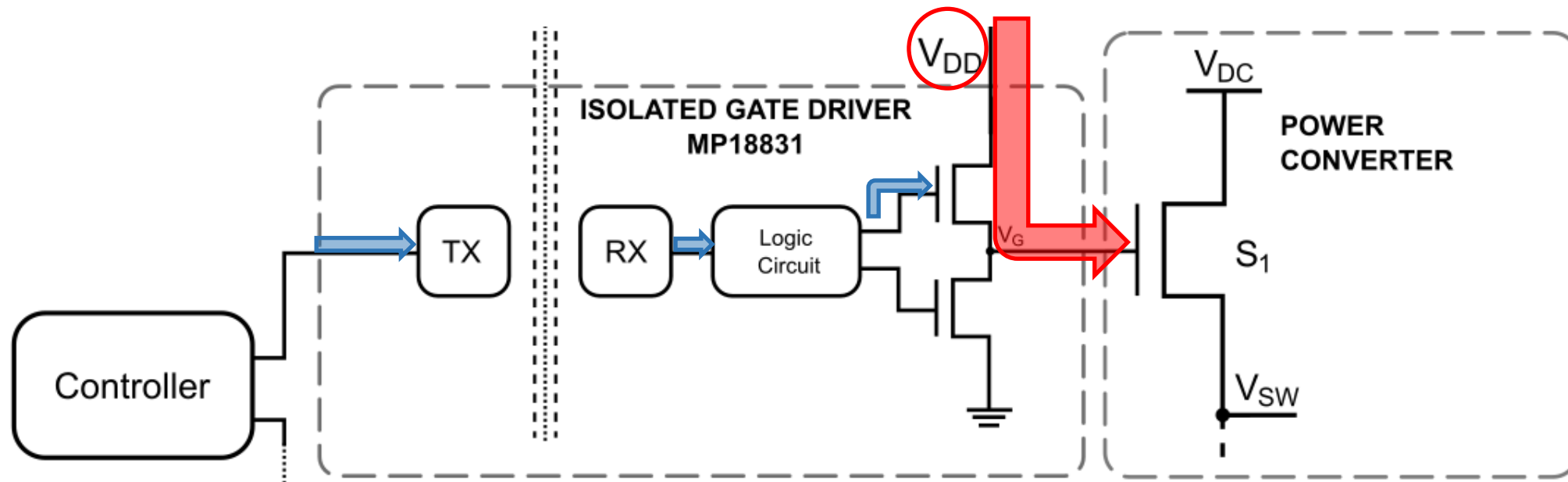

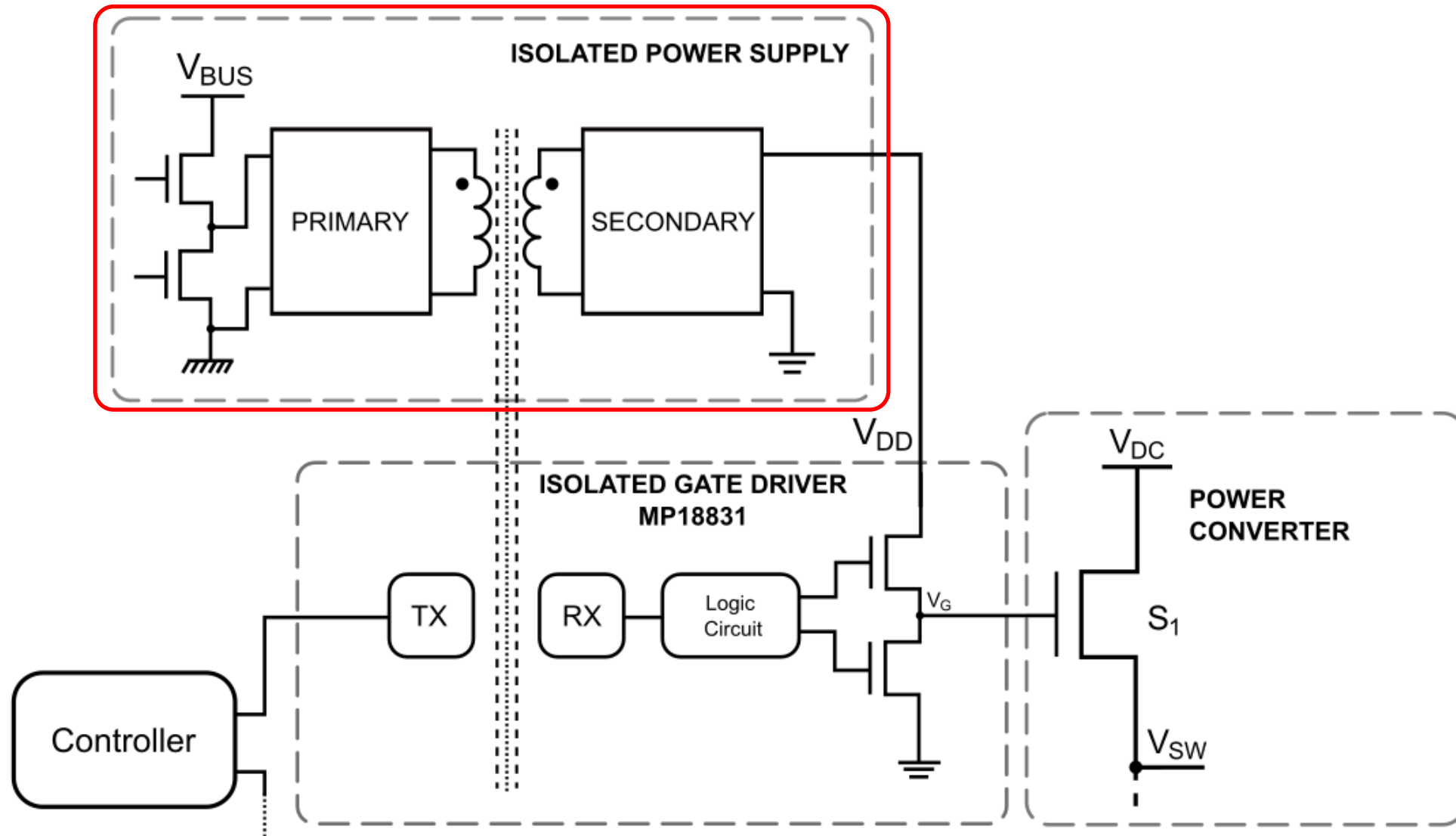Isolated Power Supplies for Gate Drivers (contd.)



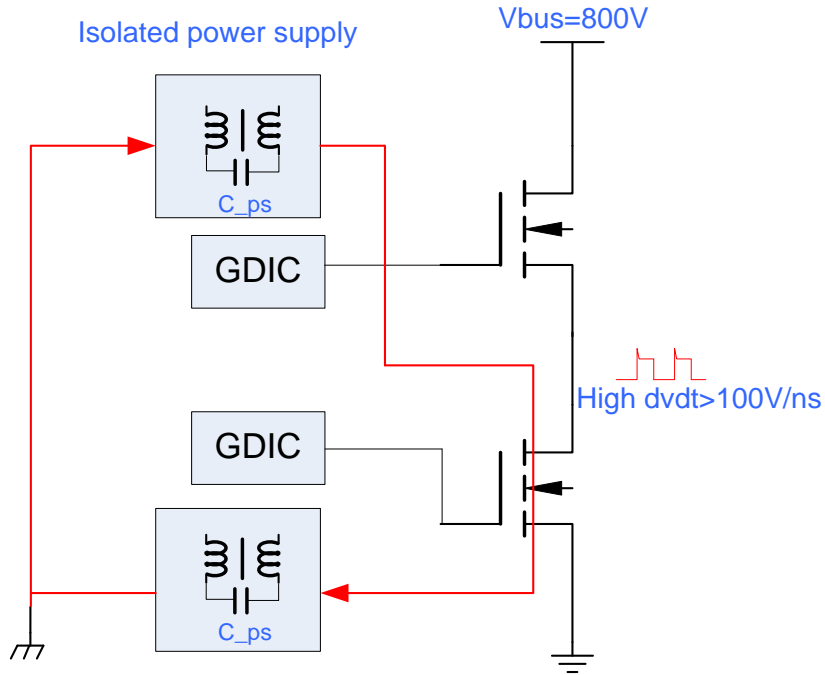Transformer Requirements for Gate Drive Power Supply





Trends on High-power Systems:

- Bus Voltage Increase → Higher Isolation Voltage Needed for Transformers
- Higher dV/dt → Requires Lower Interwinding Capacitance
 - Assuming 20pF Capacitor
 - $I_{CM} = 100V/ns \times 20pF / 2 = 1A$
 - I_{CM} is disruptive to the MCU, GDIC, and GDPS

Low-Capacitance Transformer Design

$$C_W = \frac{\epsilon_0 \epsilon_r A}{d}$$

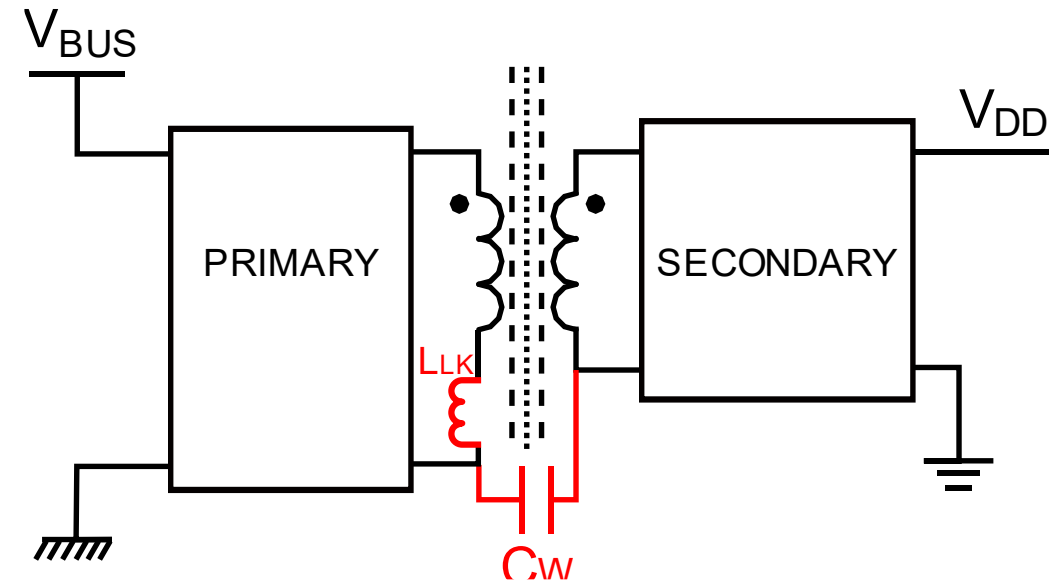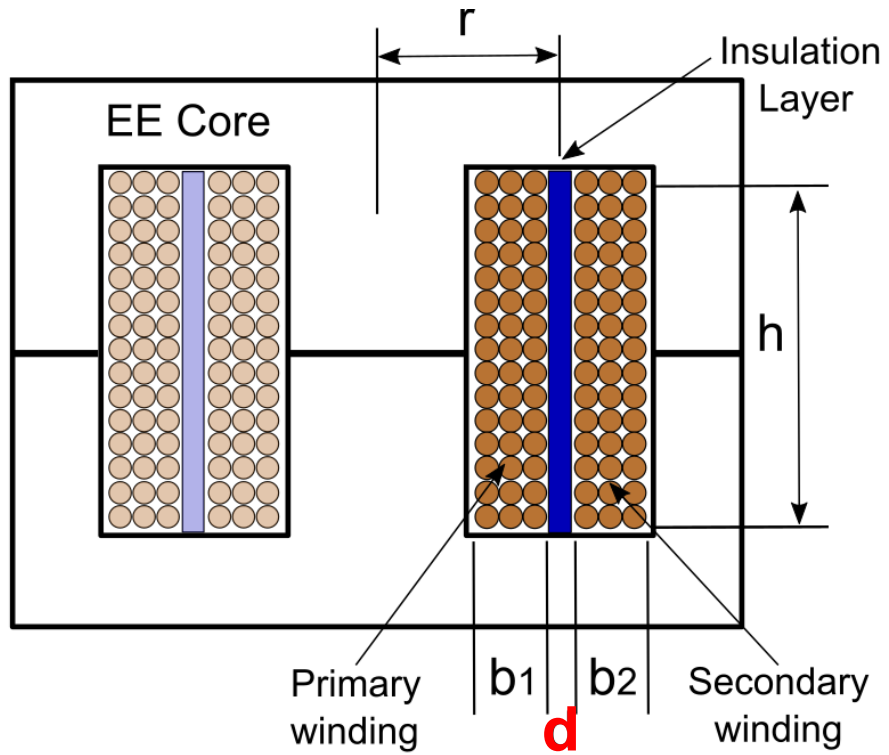To decrease $C_W \rightarrow$ Increase the distance between windings





Low-Capacitance Transformer Design


$$C_W = \frac{\epsilon_0 \epsilon_r A}{d}$$

To decrease $C_W \rightarrow$ Increase the distance between windings
 Increase the distance between windings \rightarrow Increase L_{LK}

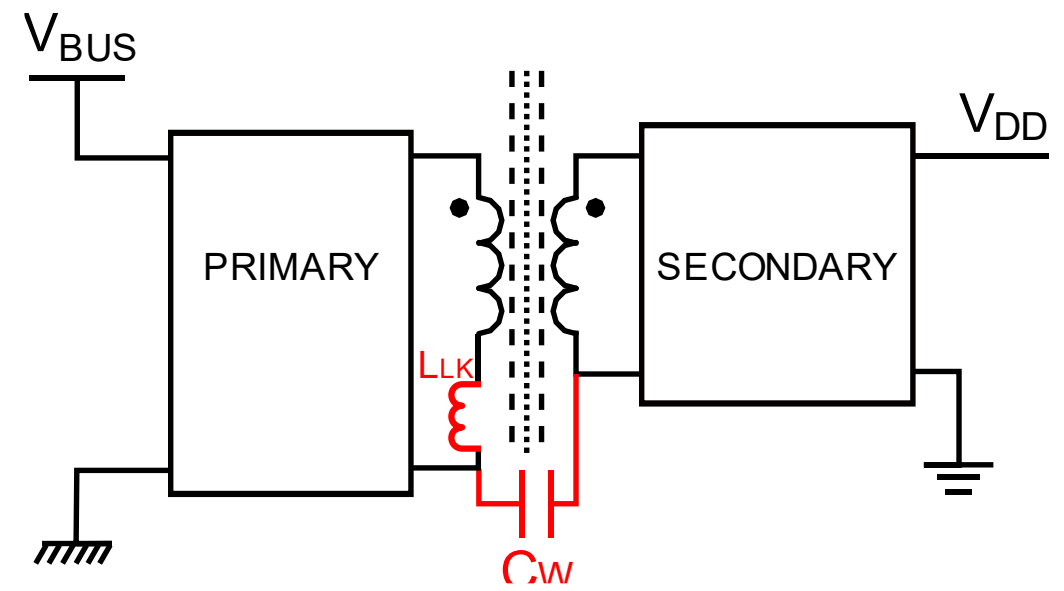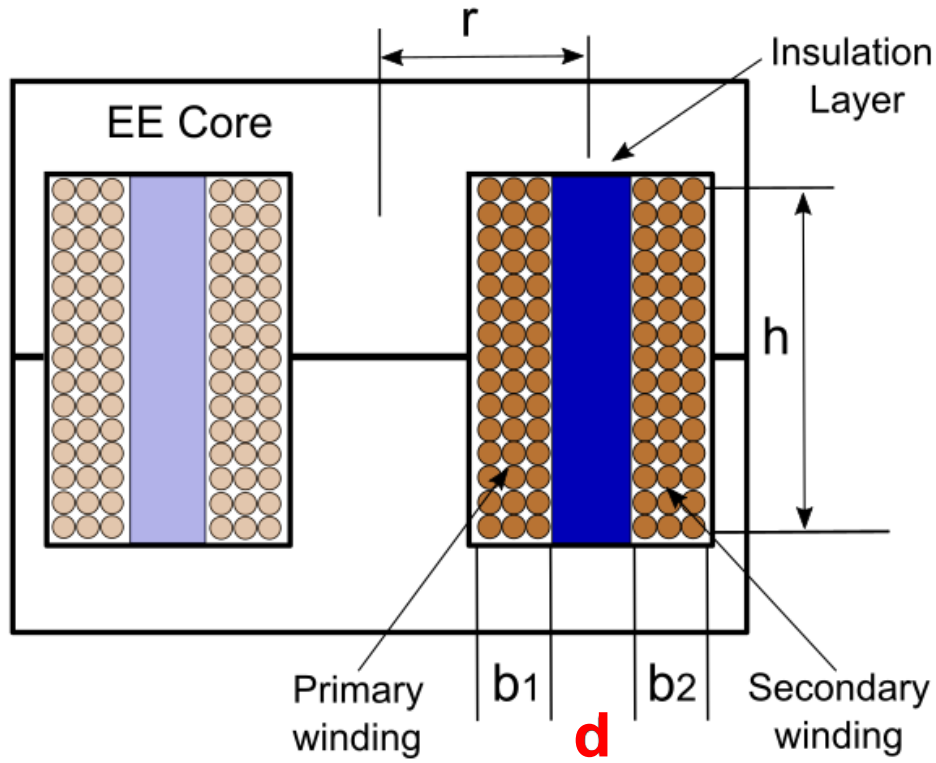
$$L_{LK} = \frac{8\pi^2 \times r \times N_P^2}{h} \left(d + \frac{b_1 + b_2}{3} \right)$$



Flyback Converter Operation with L_{LK}


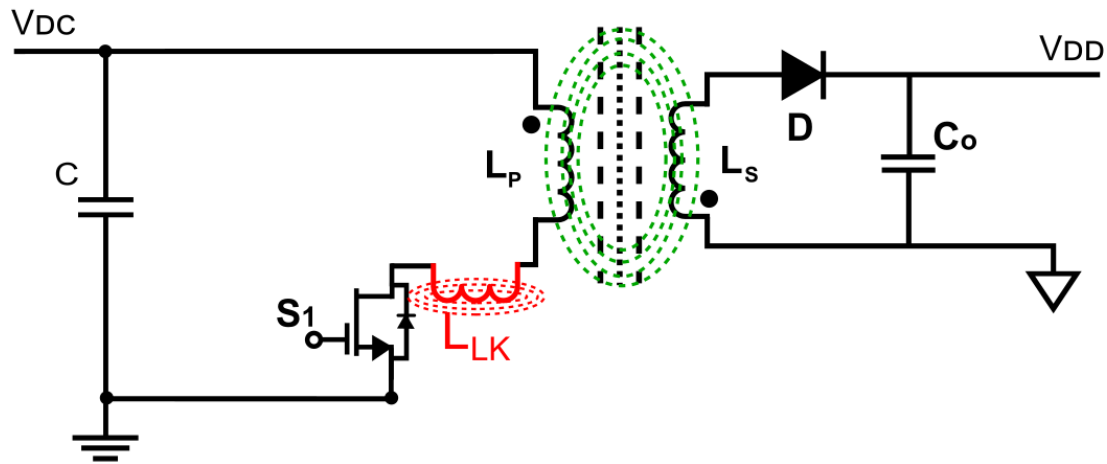


Flyback Converter

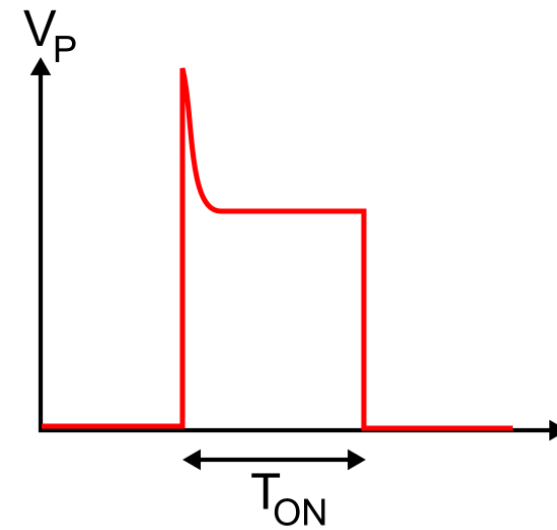


Voltage across Primary

Flyback Converter with Clamping Circuits

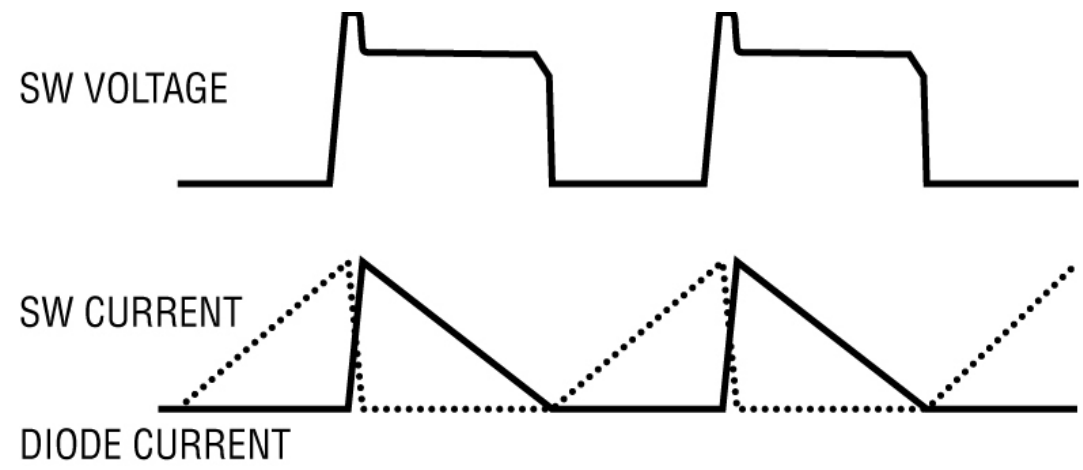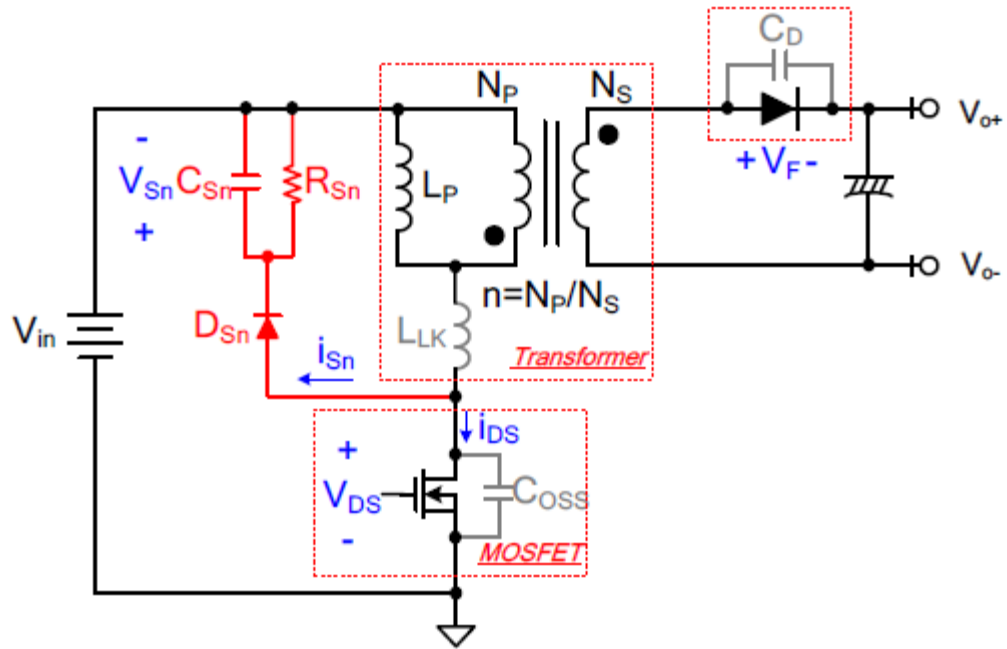

SW voltage spikes increase the device rating, complicate snubber design, generate loss and noise, and limit the max operating frequency. The larger the leakage, the worse the performance of the flyback

LLC Converter Operation with L_{LK}

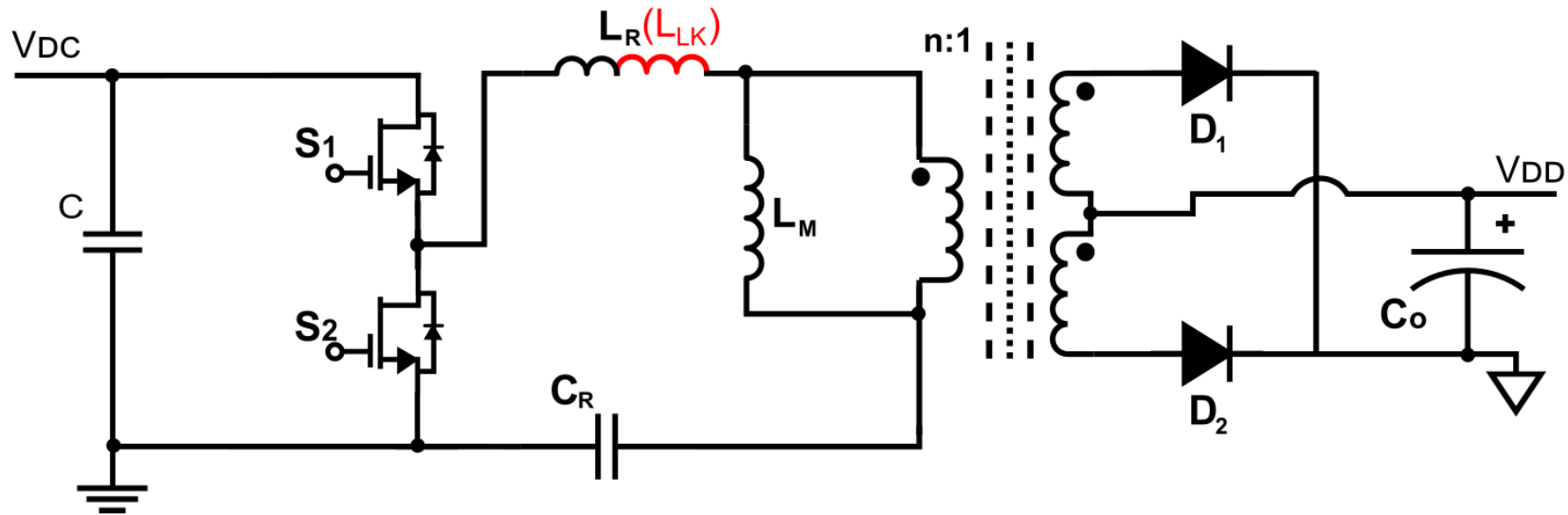


Soft Switching - ZVS → High Switching Frequency Achievable with LLC


Sample Design for Biasing SiC FETs

Multi-Output with the MPQ18913

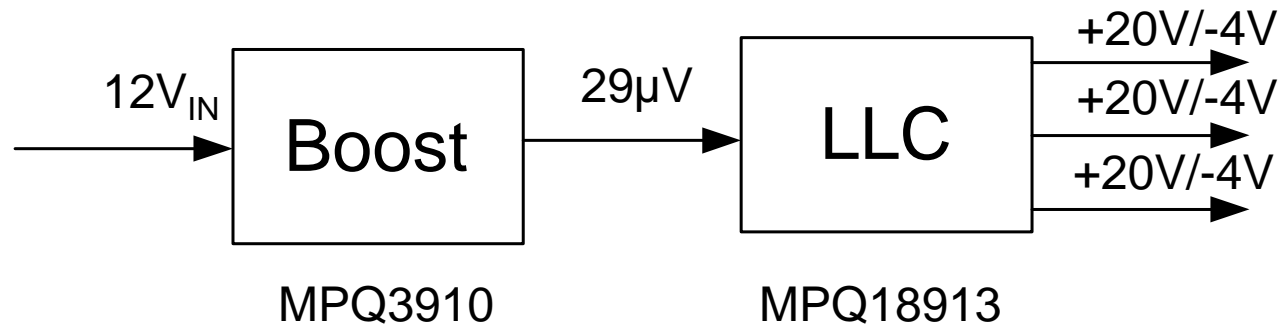
- 2 slots to separate the primary and secondary
- $C_{PS} < 1\text{pF}$, $L_M = 28\mu\text{H}$, $L_K = 5\mu\text{H}$



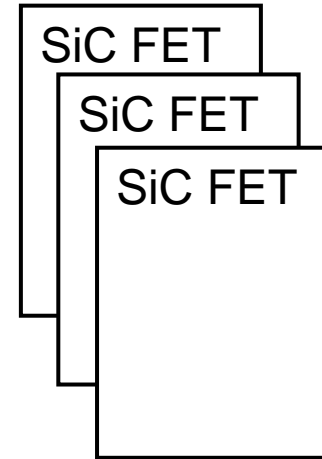Boost is optional if input comes from 12V vehicle battery



5kV Reinforced Isolation

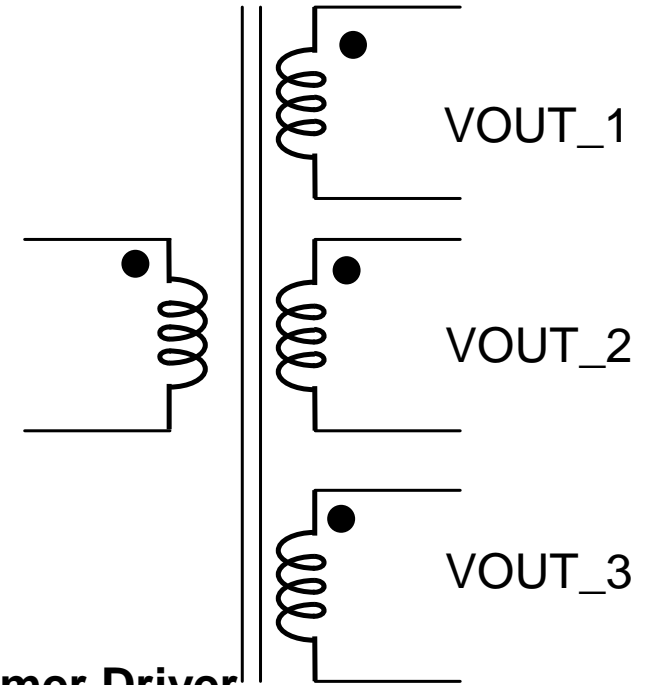

MPQ3910: 5V_{IN} to 35V_{IN} Boost Controller

Frequency 30kHz to 400kHz

1A MOSFET Gate Driver

Pulse-Skip Mode at Light Loads

Protection Features: OVP, SCP, OTP

MSOP-10 Package, AEC-Q100 Qualified

MPQ18913: 5V to 30V LLC Transformer Driver

Frequency 750kHz to 5MHz

Automatic Resonant Frequency Detection


Spread Spectrum

Supports Up to 6W


QFN-10 (2mmx2.5mm), AEC-Q100 Qualified

Performance with the MPQ3910 + MPQ18913

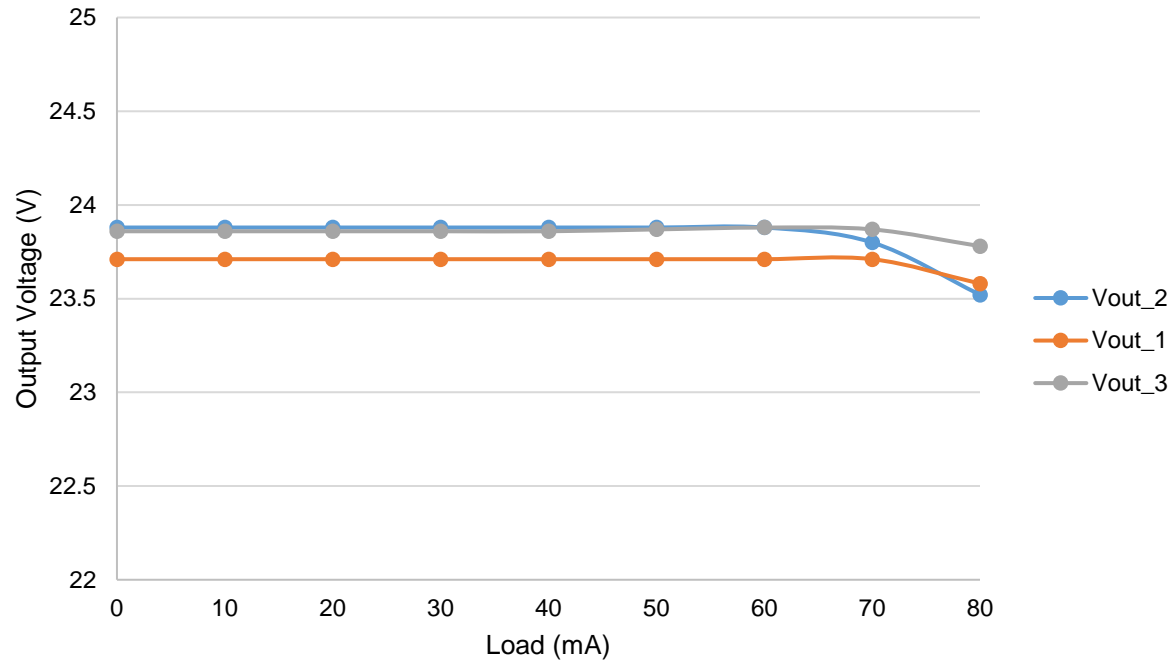Load Regulation of the MPQ3910 + MPQ18913




Efficiency of the MPQ3810 + MPQ18913

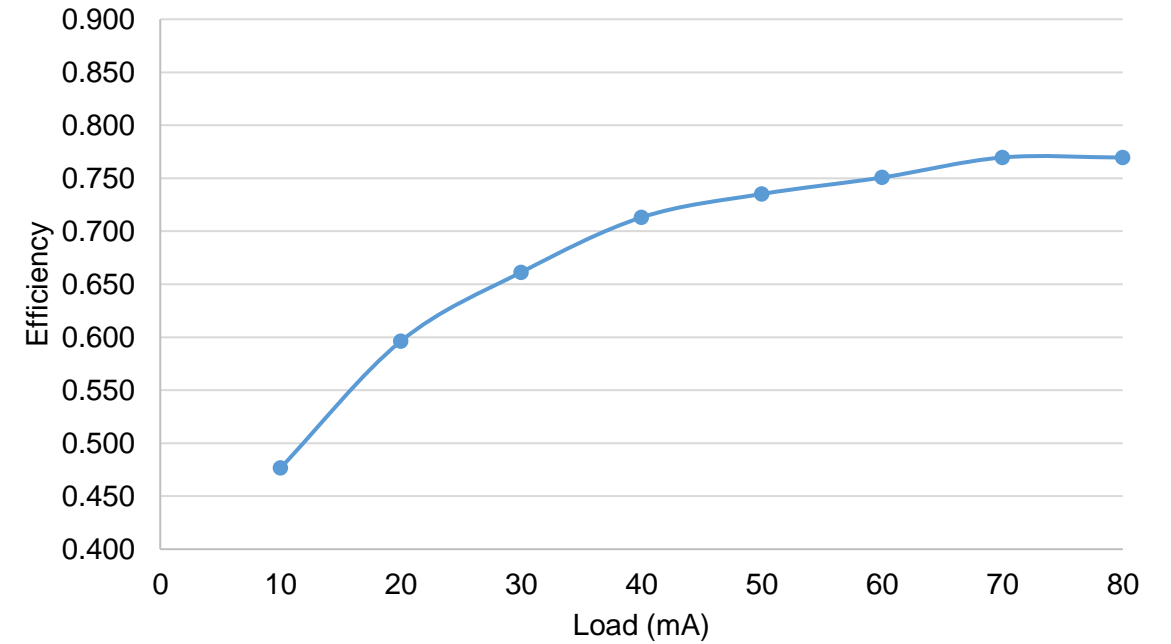


MPQ18913/4 vs. Flyback Topology

Ch2, SW
10V/div

Ch4, Ipri
500mA/div

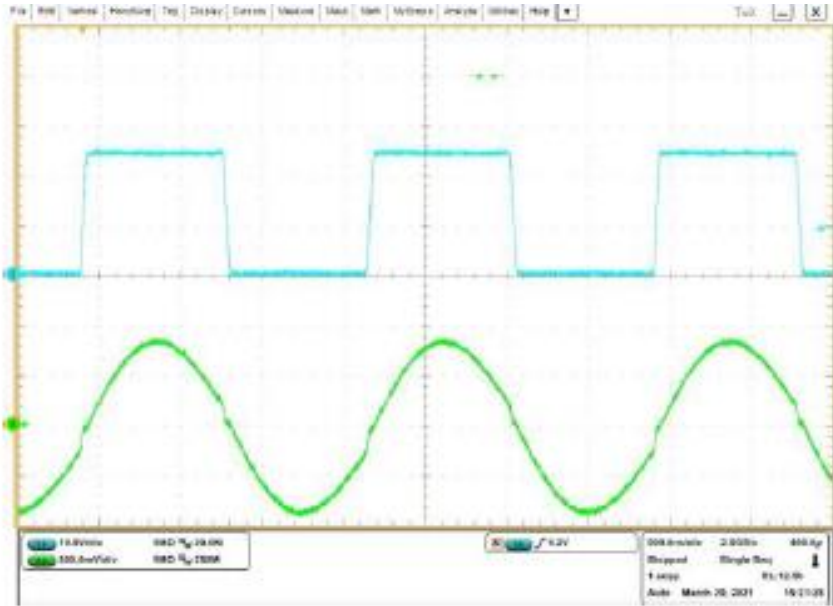


MPQ18913 SW Waveform (Top)

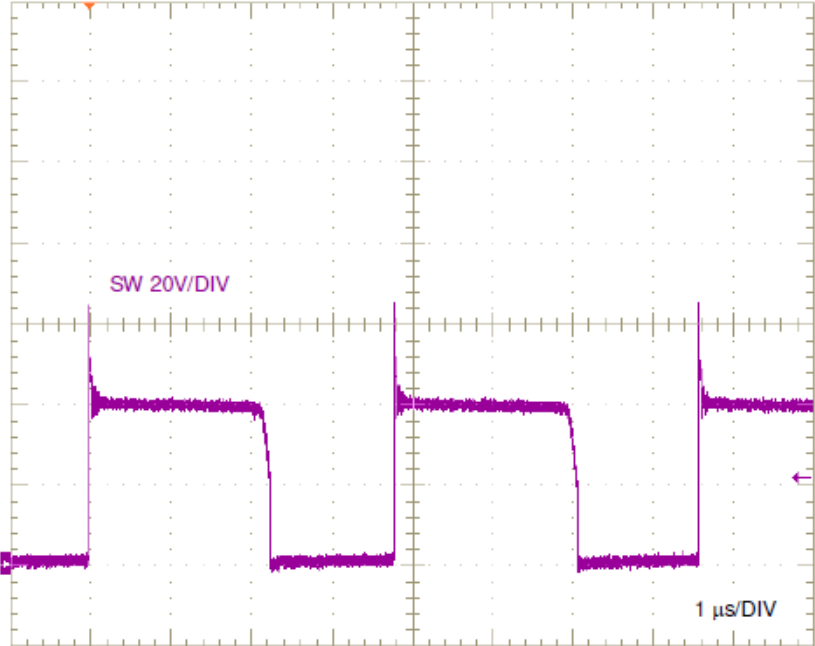


Competitor Flyback SW Waveform

MPQ18913/4 vs. Flyback Topology

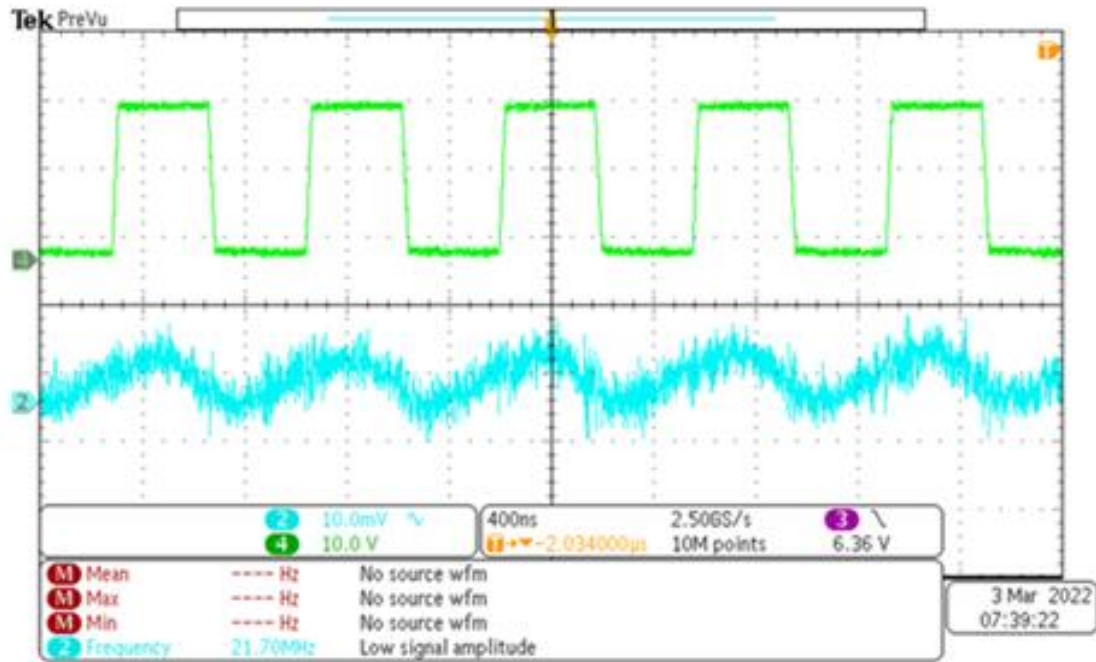The MPQ18913 uses a soft switching topology, resulting in better EMI performance compared to hard switching in a flyback that can couple switching noise to the input rail (circled in red)




MPQ18913 Input Voltage Waveform (Bottom)

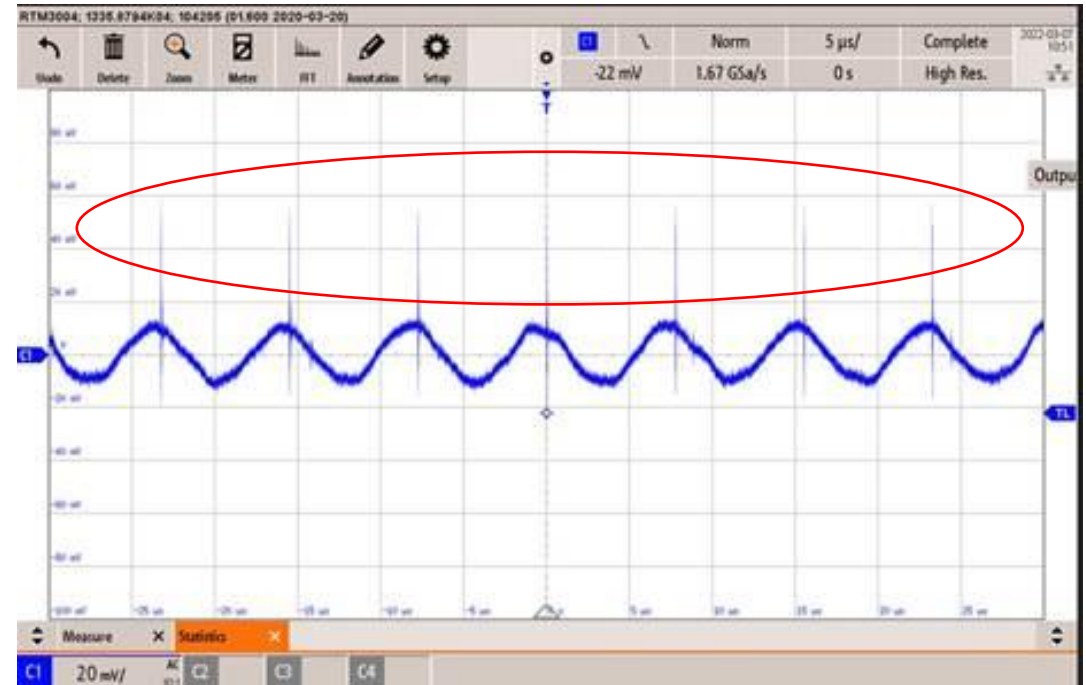

Competitor Flyback Input Voltage Waveform

Takeaways

- MPS is invested in the electrification market, with innovative solutions for onboard chargers, traction inverters, and charging stations
 - Digital Isolators
 - Low-Voltage Power Modules
 - Isolated Gate Drivers
 - LLC Gate Driver Power Supplies
- Resonant LLC supplies are a great way for biasing either IGBTs or SiC FETs to help increase power density in next-generation designs over a traditional flyback

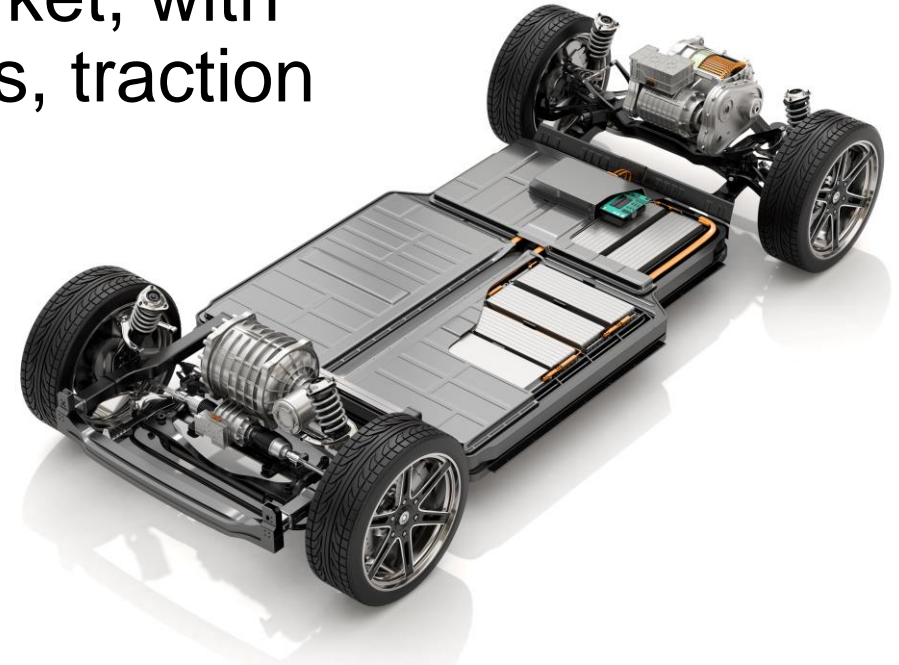

Thank You