

Introduction

One of the primary goals for the power supply industry is to bring higher power conversion efficiency and power density to power devices in applications such as [datacenters](#) and [5G](#). Integrating a driver circuit and power MOSFET (known as a [DrMOS](#)) into an IC increases power density and efficiency when compared to a conventional, discrete MOSFET with an individual driver IC. Moreover, the DrMOS's flip-chip technology further optimizes the [voltage regulator](#)'s performance by reducing response time and reducing the inductance between the die and package (see Figure 1).

 


Figure 1: Conventional Wire Bond vs. Flip-Chip Technology

However, parasitic inductance on the substrate and PCB significantly impacts the drain-to-source voltage (V_{DS}) spike, due to the resonant nature between parasitic inductance and the MOSFET's output capacitance (C_{OSS}). A high V_{DS} spike can cause a MOSFET avalanche, which leads to device degradation and reliability issues. To prevent an avalanche breakdown on the MOSFET, there are several methods to alleviate voltage stress.

The first method is to apply a higher-voltage, double-diffused MOSFET (DMOS) process on the DrMOS. If this process is adopted in the power MOSFET design, it results in a higher on resistance ($R_{DS(ON)}$) for the DrMOS due to a reduced number of paralleled DMOS within the same space.

The second method is to use a snubber circuit to suppress voltage spike. However, this method leads to extra loss on snubber circuit. Furthermore, adding a snubber circuit may not effectively lower the MOSFET's V_{DS} spike since the stray inductance that causes resonant behavior is mainly integrated in the DrMOS's package.

When trying to increase voltage regulator efficiency and reduce the MOSFET's voltage spikes, the tradeoffs described above can make it difficult to quantify and optimize the effects of parasitic inductance on the PCB and substrate. This article will first discuss parasitic inductance modeling. Next, the equivalent parasitic circuit model is applied in a SPICE simulation tool to predict the V_{DS} switching spike. Experimental results will be presented to verify the feasibility of the parasitic model. Lastly, this article will further analyze parasitic inductance optimization on a DrMOS.

Parasitic Inductance Modeling on a DrMOS

To model parasitic inductance, 3D structures of both the DrMOS and PCB were built for a simulation analysis (see Figure 2). Parameters such as the material, stack-up information, and PCB and package layer thickness are crucial for modeling accuracy.

After 3D-modeling the PCB and DrMOS, the parasitic inductance can be characterized and obtained via ANSYS Q3D. Since this article focuses on the MOSFET's V_{DS} spike, the main simulation settings of interest are the parasitic parameters on the power nets and driver nets.

 


Figure 2: 3D-Modeling Structure of DrMOS and PCB

When considering the parasitic component obtained from Q3D, the parasitic inductance matrix — including the self and mutual terms of each net on the DrMOS — can be selected under different frequency conditions. Since the resonant frequency for V_{DS} on the high-side MOSFET (HS-FET) and low-side MOSFET (LS-FET) is between 300MHz and 500MHz, the parasitic inductance matrix under 300MHz condition is adopted for further behavior model simulation.

Behavior Model Simulation on SPICE

After the equivalent parasitic component model is exported from Q3D, the effects of different types of decoupling capacitors on the PCB are taken into account. Due to the capacitance decay after applying a DC voltage on a multi-layer ceramic capacitor (MLCC), it is important to consider the equivalent circuit of each individual MLCC under certain DC voltage bias conditions. Each consideration should be based on the MLCC's operating voltage. Figure 3 shows the circuit configuration for the behavior model simulation on SPICE.

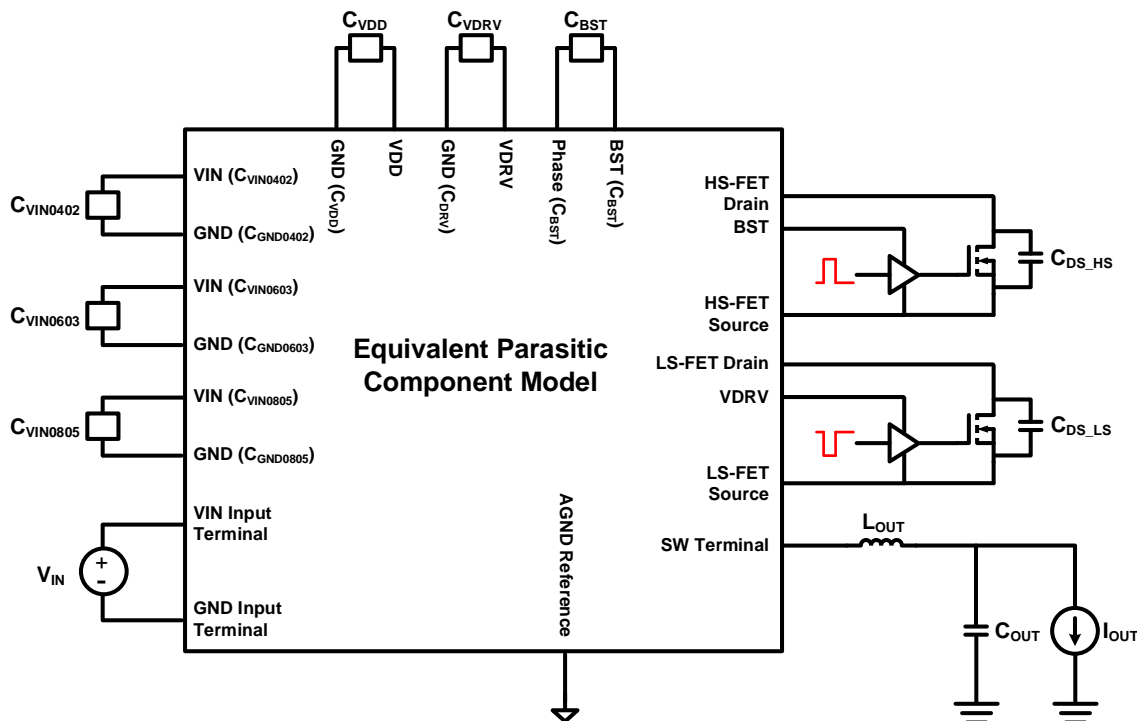


Figure 3: Circuit Configuration of Behavior Model Simulation

Table 1 shows the simulation and measurement conditions based on the schematic shown in Figure 3.

Table 1: Specification on Simulation Scheme and Experimental Test Bench

Parameters	Value
Input voltage (V_{IN})	12V
Output voltage (V_{OUT})	1.8V
Switching frequency (f_{SW})	800kHz
Output inductor	100nH
Load	50A
VDRV / VDD voltage	3.3V

DrMOS Solution with the MP87000-L

The [MP87000-L](#) is a 90A, monolithic half-bridge with built-in power MOSFETs and gate drivers for server core and graphic card core regulators applications. To suppress voltage ringing, the MP87000-L features Quiet Switcher™ technology, which is only achievable in monolithic architectures. This technology improves device reliability, lowers EMI, and reduces sensitivity to the PCB layout.

The MP87000-L is ideal for server applications where high efficiency and high power density are required, and it is available in a TLGA-41 (5mmx6mm) package.

Figure 4 uses the MP87000-L to show the simulation and experimental results for V_{DS} on the LS-FET.

 


Figure 4: Simulation and Experimental Results for V_{DS} (LS-FET)

Figure 5 uses the MP87000-L to show the simulation and experimental results for V_{DS} on the HS-FET.

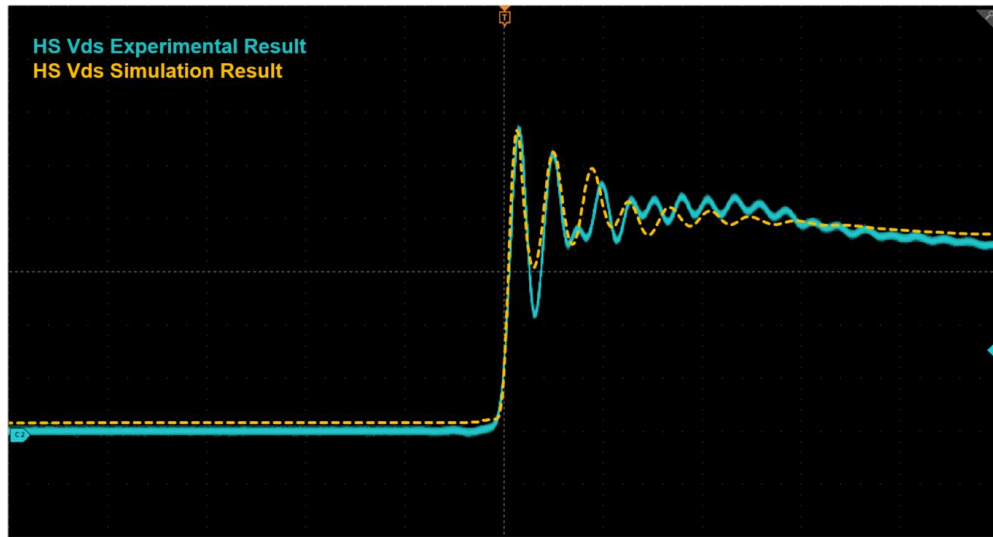


Figure 5: Simulation and Experimental Results for V_{DS} (HS-FET)

From Figure 4 and Figure 5, it can be concluded that the V_{DS} spike from the simulation results is almost equal to the experimental results. Table 2 shows additional simulation and experimental results under different load conditions.

Table 2: Simulation and Experimental Results under Different Load Conditions

Load	Simulated HS-FET V_{DS} Spike	Measured HS-FET V_{DS} Spike	Simulated LS-FET V_{DS} Spike	Measured LS-FET V_{DS} Spike
30A	14.4V	15.8V	12.4V	13.9V
40A	14.6V	15.4V	12.5V	13.5V
50A	17.1V	16.5V	13.4V	13.3V
60A	19.1V	19.2V	12.9V	13.1V
70A	21.4V	21.8V	13.5V	13V

Table 2 indicates that the simulated V_{DS} is congruent with the measured results. In other words, the V_{DS} spike predictions from the behavior model simulation can forecast potential avalanche breakdown on the MOSFET by conducting several optimization approaches that can lower parasitic inductance.

Optimizing Parasitic Inductance

To suppress the V_{DS} spike without compromising efficiency, it is vital to optimize parasitic inductance on the PCB and package. With advanced package technology, input capacitors can be integrated in the package to shorten the decoupling path (see Figure 6). Paralleling the embedded capacitors in the package can effectively reduce the equivalent parasitic inductance on the DrMOS.

 


Figure 6: 3D DrMOS Structure with Embedded Capacitors

Table 3 shows the equivalent parasitic inductance and V_{DS} spike when utilizing different decoupling capacitor configurations on the MP87000-L.

Table 3: Equivalent Parasitic Inductance and V_{DS} Spike with Different Capacitor Configurations

Capacitor Configuration	Equivalent Parasitic Inductance	Simulated HS-FET V_{DS} Spike (Load = 50A)	Simulated LS-FET V_{DS} Spike (Load = 50A)
3 embedded capacitors, 2 PCB 0402 capacitors, 3 PCB 0805 capacitors	157pH	17.1V	13.4V
2 embedded capacitors, 2 PCB 0402 capacitors, 3 PCB 0805 capacitors	180pH	18.2V	14.3V
1 embedded capacitors, 2 PCB 0402 capacitors, 3 PCB 0805 capacitors	206pH	21.5V	16.9V
2 PCB 0402 capacitors, 3 PCB 0805 capacitors	285pH	27.7V	20.6V

From the simulation results in Table 3, not only is the equivalent parasitic inductance lowered, but the V_{DS} spike on MOSFET is also suppressed. Moreover, thanks to the MLCC's low-ESR characteristics, no additional power loss is generated on the embedded input capacitors. Therefore, it is possible to add different embedded input capacitors to reduce parasitic inductance in DrMOS applications.

Conclusion

This article discusses the effect of parasitic inductance on the V_{DS} switching spike, as well as several methods to prevent an avalanche breakdown on the MOSFET due to the V_{DS} switching spike.

To quantify the effects of parasitic inductance on the V_{DS} switching spike, parasitic inductance modeling is first introduced, and behavior modeling on SPICE is proposed in this article. The results obtained via SPICE closely matched the experimental results for [DrMOS](#) solutions such as the [MP87000-L](#), which means the behavior model can accurately predict the risk of an avalanche breakdown on the MOSFET.

To effectively suppress the V_{DS} spike without any tradeoffs, embedded capacitors in the package were introduced. The behavior model simulation confirmed that these capacitors can reduce the equivalent parasitic inductance, and thus lower the V_{DS} spike without additional loss. MPS offers an extensive portfolio of [48V modules](#), [step-down converters](#), and [processor core power controllers](#) to complete your data center solution.