

Characterization and Design of Filter Inductors and Capacitors to Suppress the Radiated EMI in A Power Converter

Shuo Wang, Ph. D



Power Electronics and Electrical Power Research Lab

University of Florida

July, 2022

Power Converter's Radiated EMI Model


(A Dual Active Bridge Converter Example)

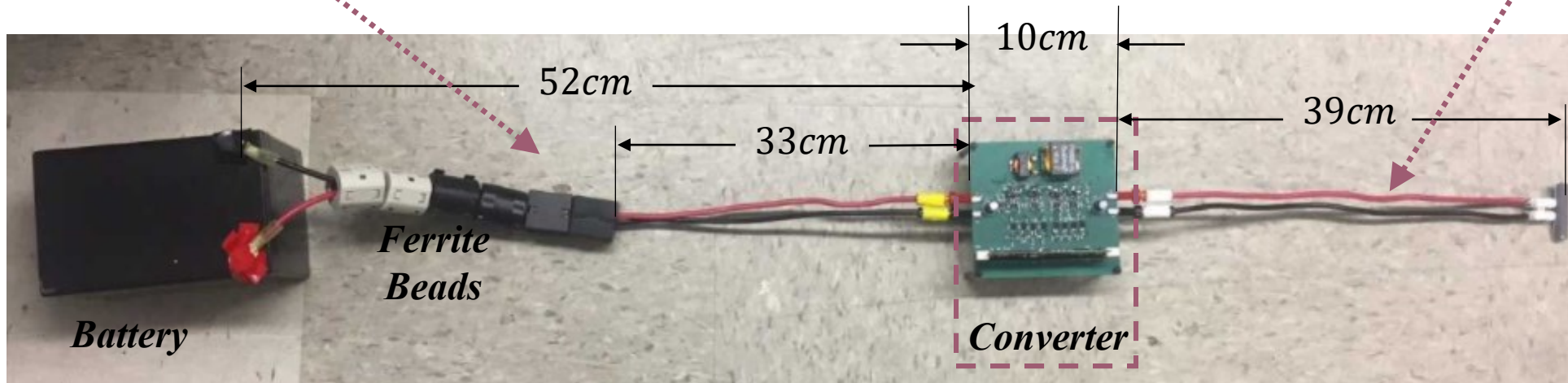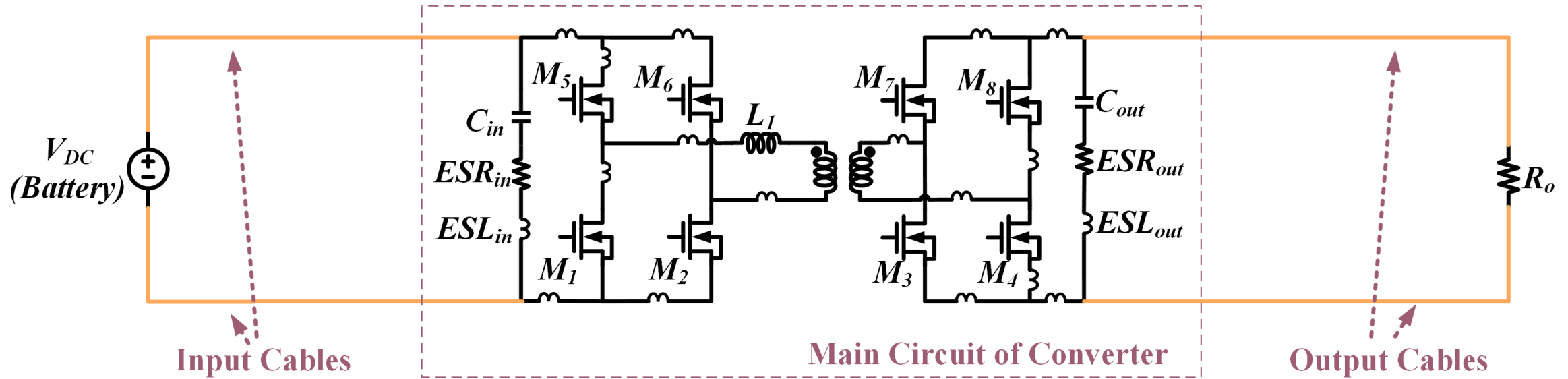


Power Converter's Radiated EMI Model

(A Dual Active Bridge Converter Example)


Cable antenna model:

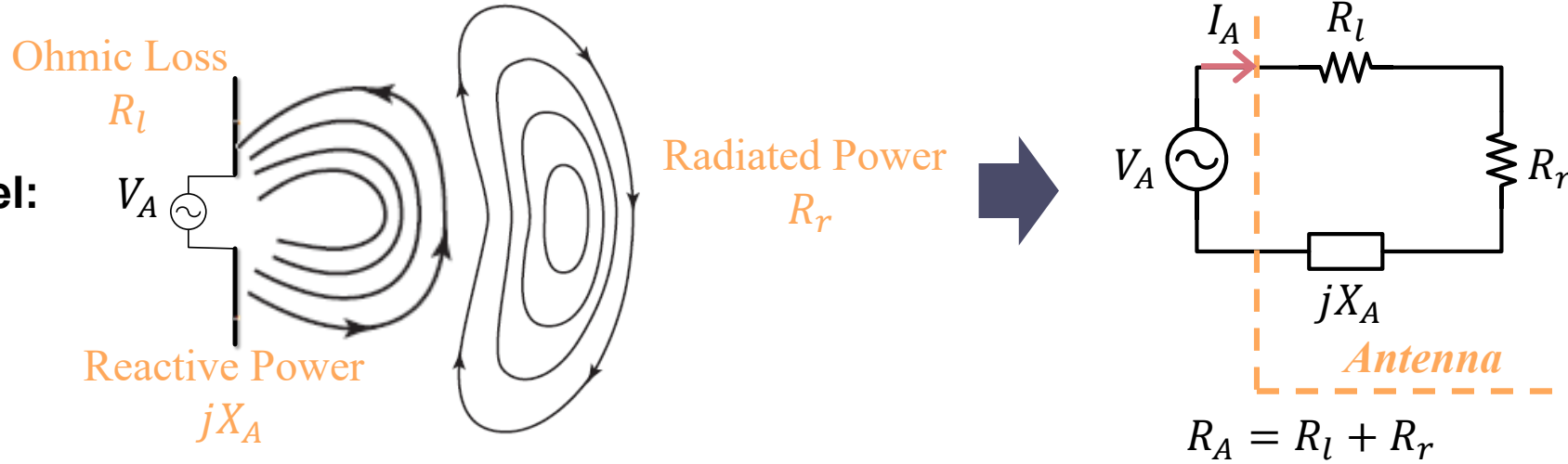

Power converter radiated EMI model:

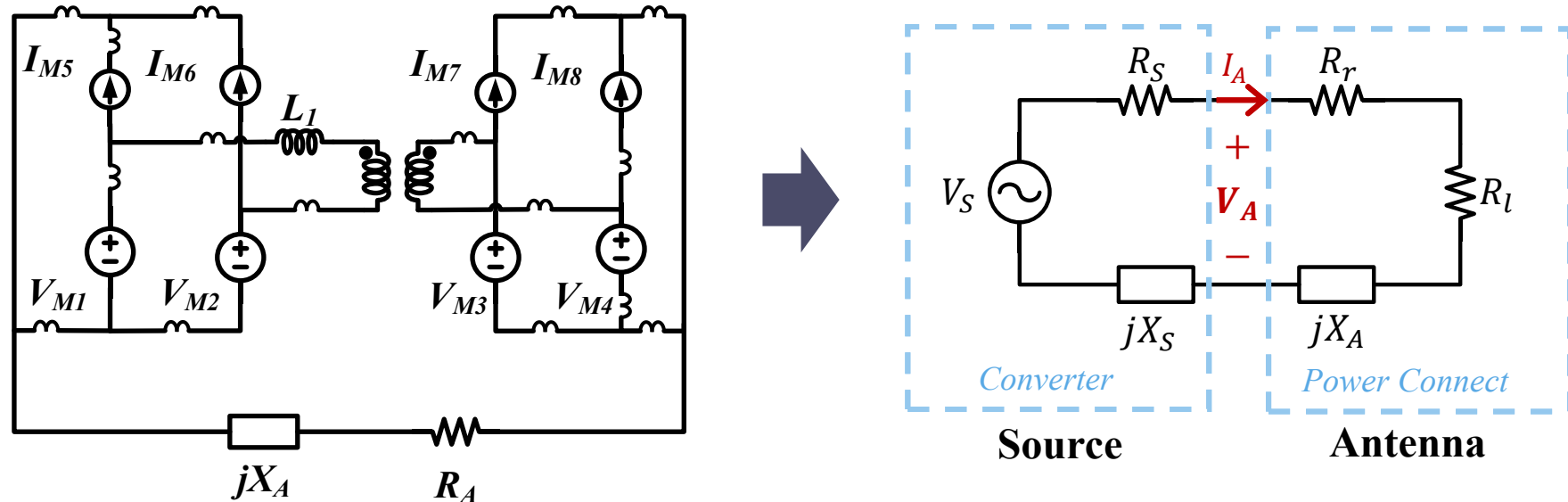

The Radiated Electric Field

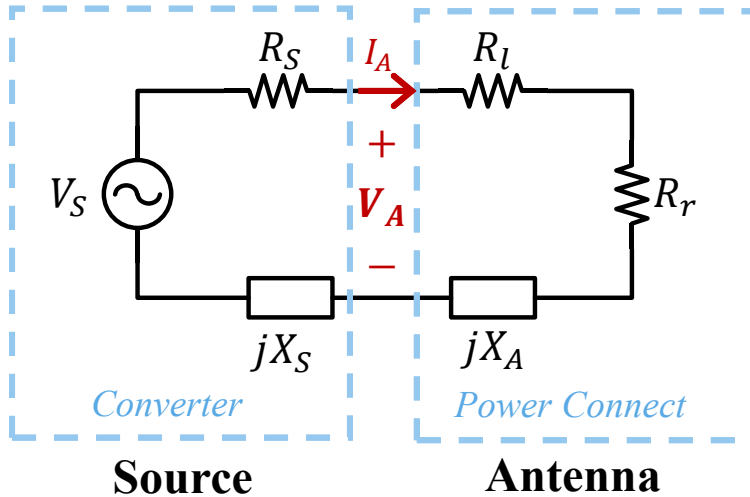


Radiated Power:

$$P_r = \frac{1}{2} |I_A|^2 R_r$$

$$|I_A| = \frac{|V_S|}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}} = |V_S| \times K_I$$

Maximum Power
density: $S_{\max}$

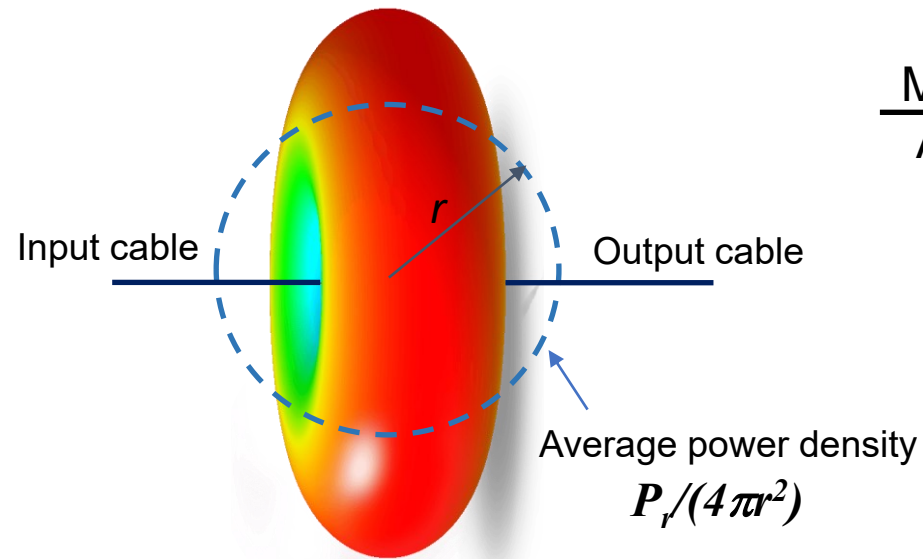

Directivity D:

Maximum power density
Average power density

$$D = S_{\max} (4\pi r^2) / P_r$$

$$S_{\max} = E_{\max}^2 / 2\eta$$

(η : wave impedance)


$$G_o = eD = DR_T / R_A = DR_T / (R_T + R_L)$$

$$E_{\max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times K_E$$

$$K_I = \frac{1}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

$$K_E = \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

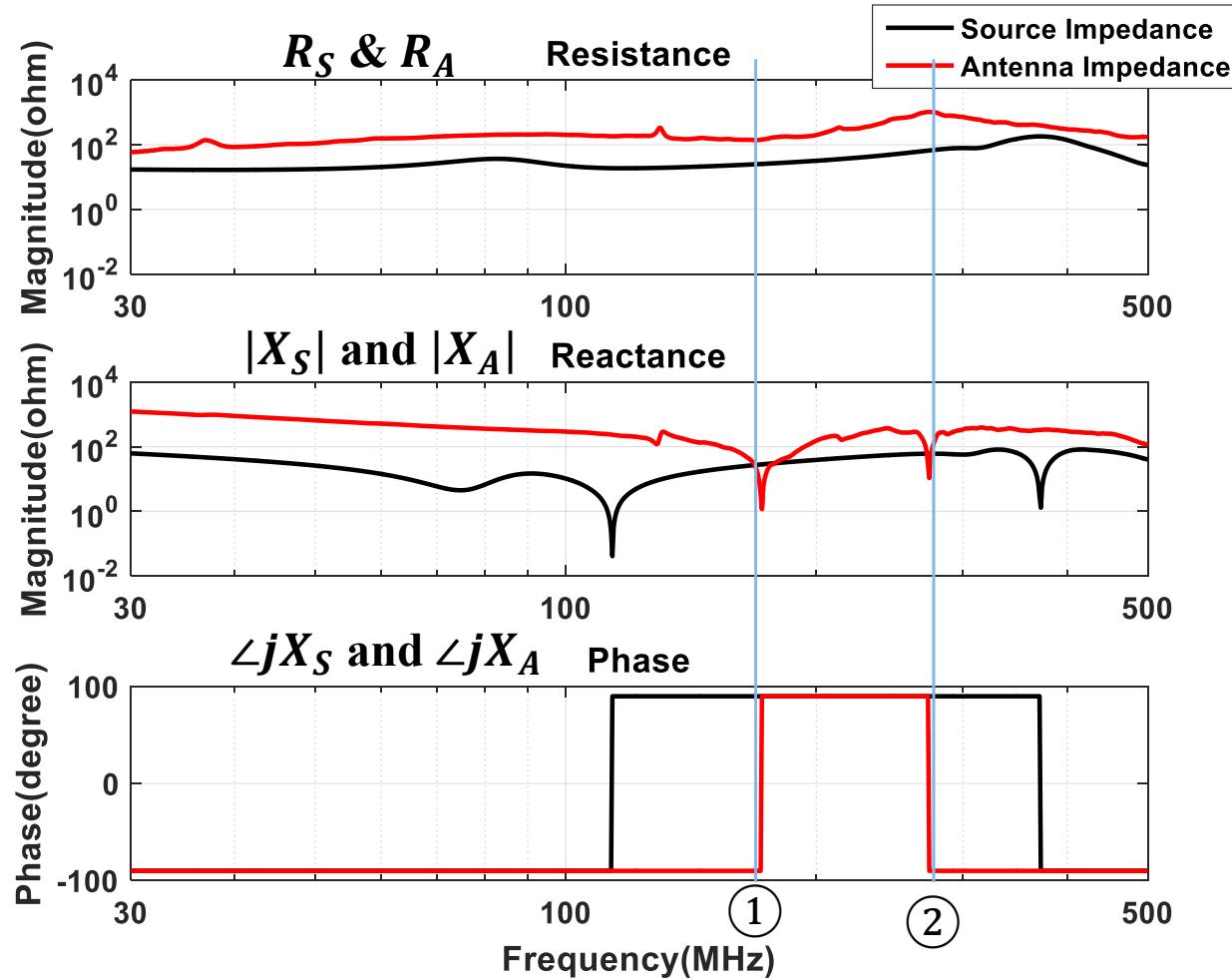EMI Spikes due to the Interaction of Antenna and Converter Impedances



$$|I_A| = \frac{|V_S|}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}} = |V_S| * K_I$$



$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times K_E$$

$$K_I = \frac{1}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$



$$K_E = \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

Number	Frequency (MHz)	R_S (Ω)	R_A (Ω)	K_I (S)	K_E ($\sqrt{S}$)
①	167	24	140	0.006	0.072
②	270	68	1030	0.0009	0.029




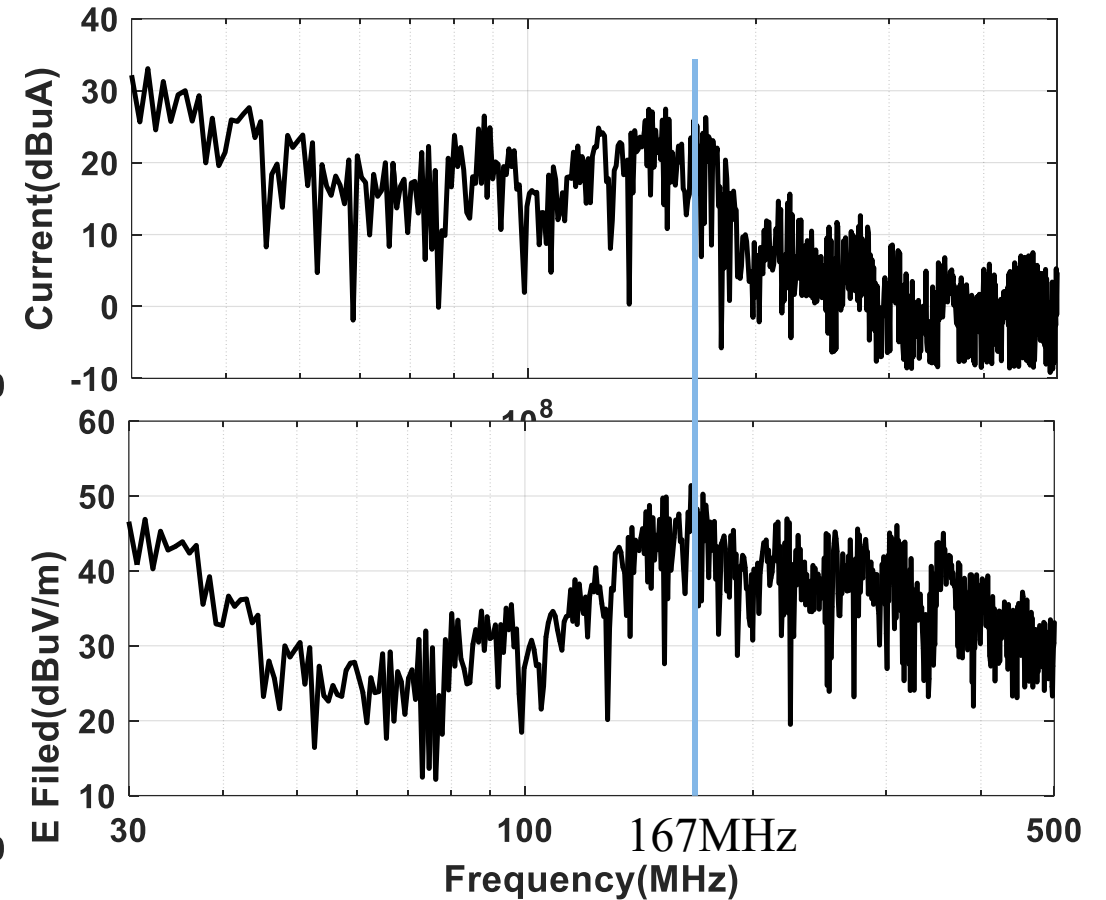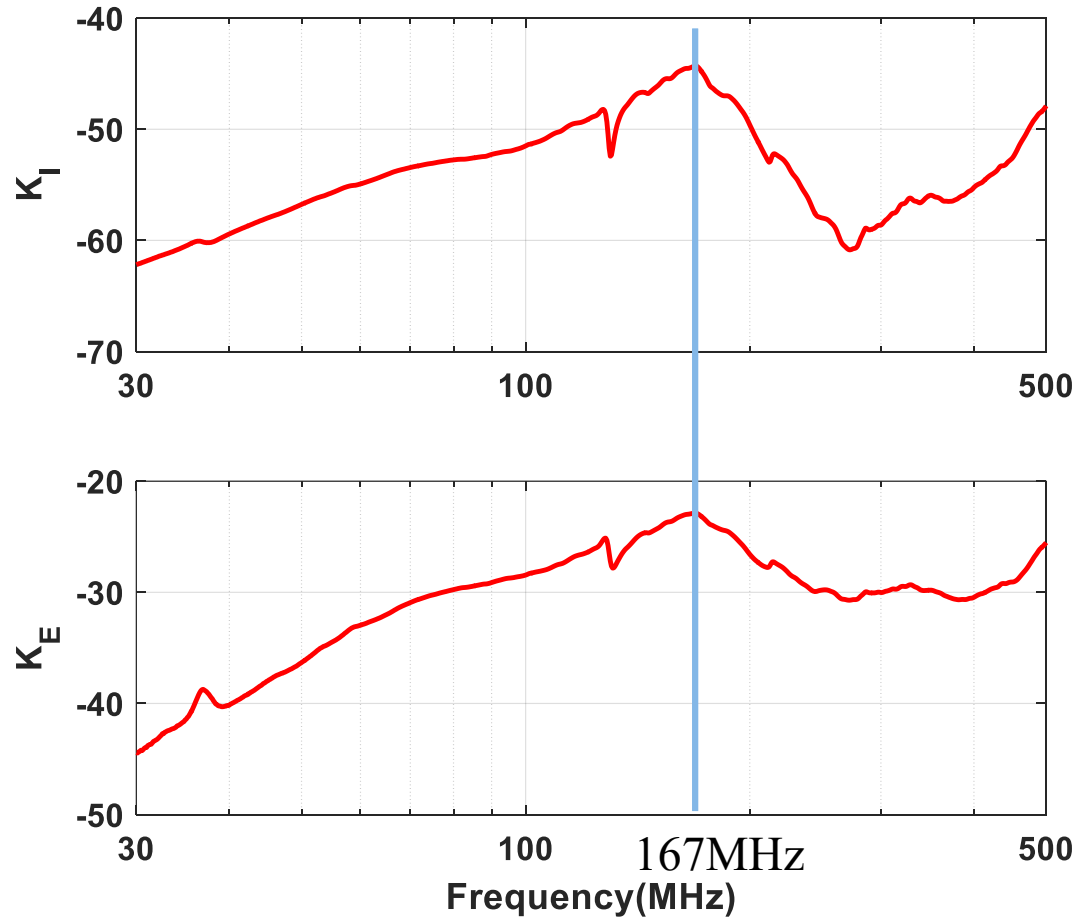

Inductor Design to Reduce Radiated EMI

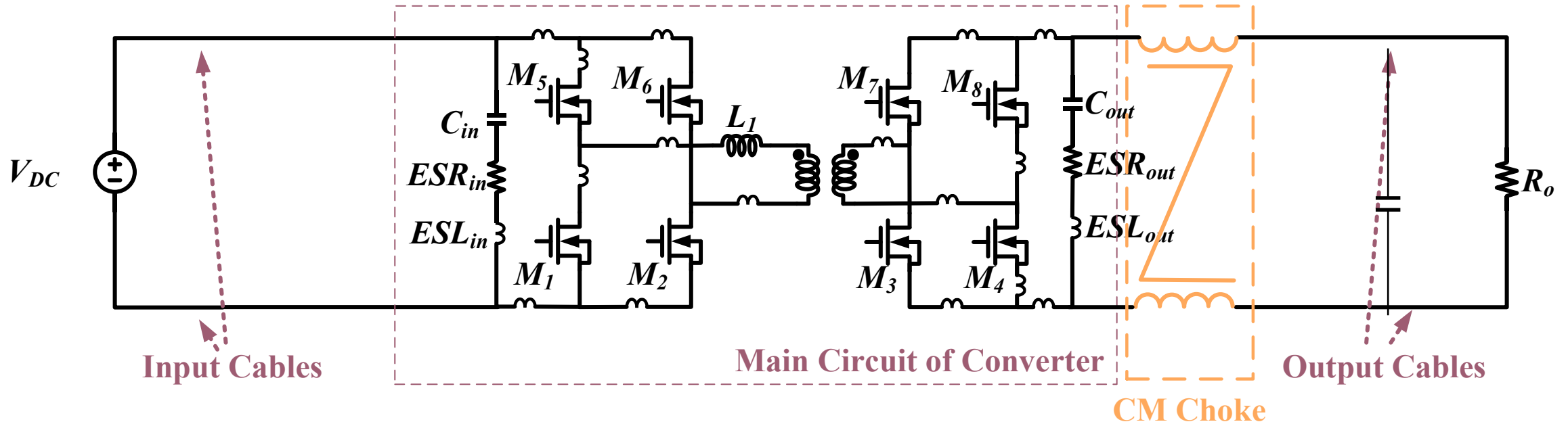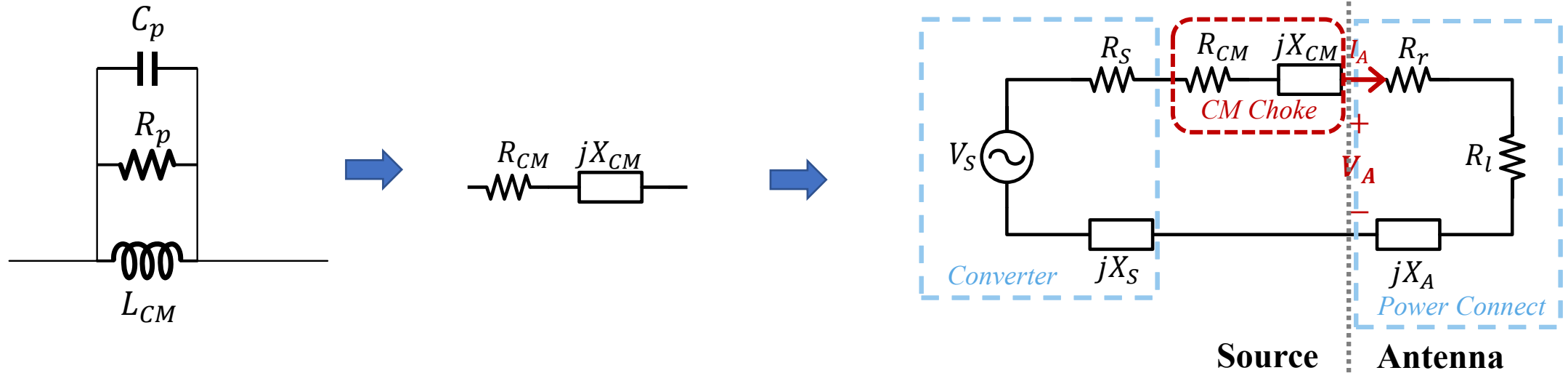

CM Inductor's Impact to Radiated EMI

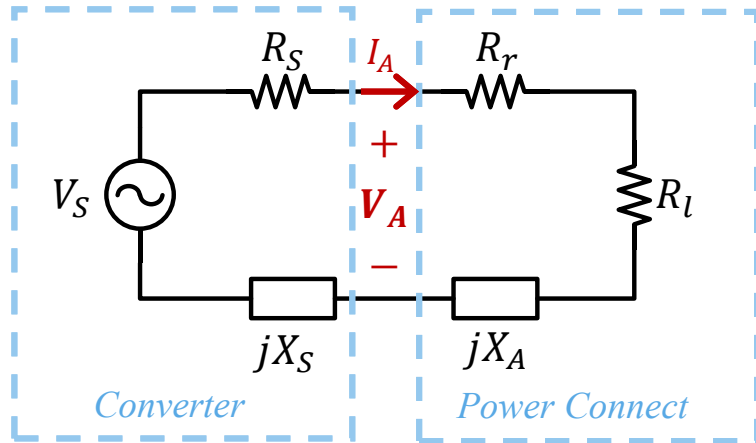

Source



Antenna

$$|I_A| = \frac{|V_S|}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

$$K_I = \frac{1}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$
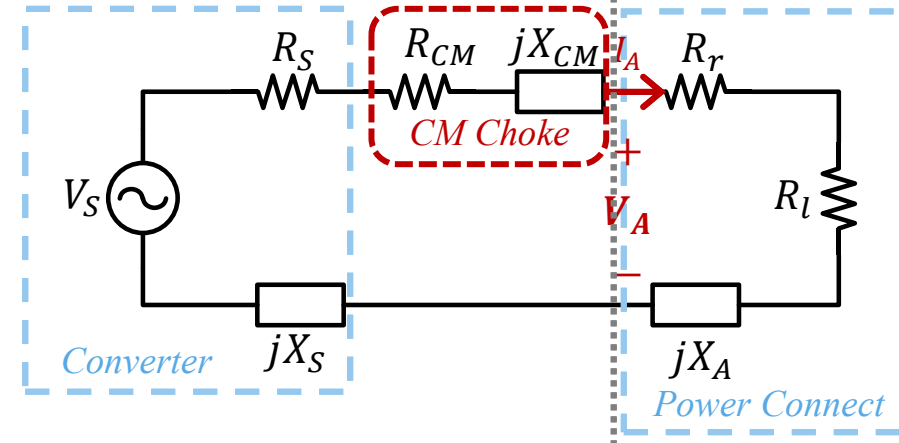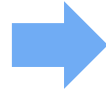
$$K_E = \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$



Source

Antenna

$$|I_A| = \frac{|V_S|}{\sqrt{(R_S + R_{CM} + R_A)^2 + (X_S + X_{CM} + X_A)^2}}$$

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_{CM} + R_A)^2 + (X_S + X_{CM} + X_A)^2}}$$


$$K_I = \frac{1}{\sqrt{(R_S + R_{CM} + R_A)^2 + (X_S + X_{CM} + X_A)^2}}$$

$$K_E = \frac{\sqrt{R_A}}{\sqrt{(R_S + R_{CM} + R_A)^2 + (X_S + X_{CM} + X_A)^2}}$$

- CM Choke will affect the radiation by**
- **Shifting the resonant frequency**
 - **Increasing the total resistance**
 - **Changing the total reactance**

Design of CM Inductor Reactance

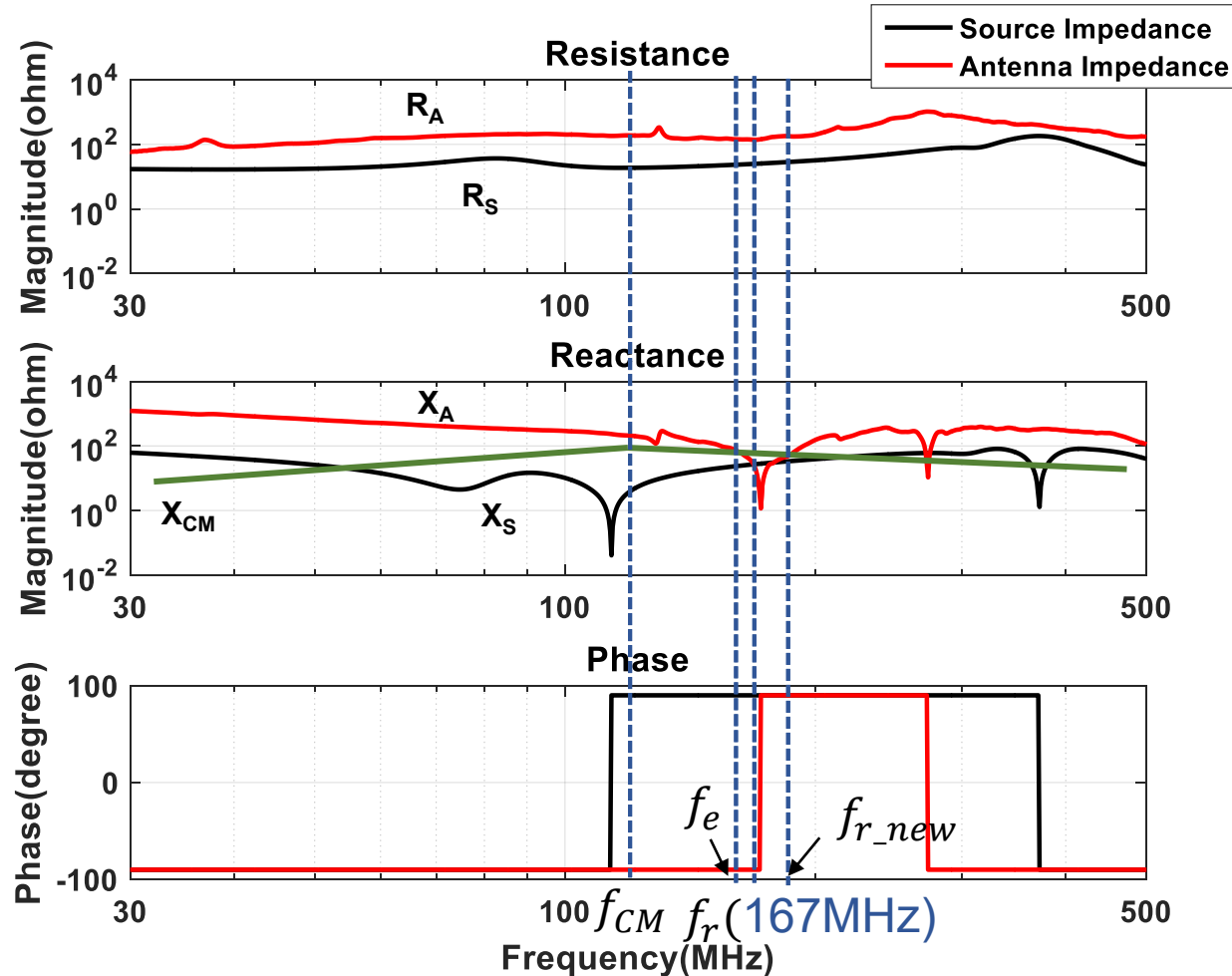At the resonant frequency f_r , antenna X_A is capacitive, source X_S is inductive



1. If $X_{CM} < 0$ at f_r , to push the new resonant frequency higher because source noise spectrum is lower at higher frequencies:

$$|X_{CM}| > |X_S| @ f_r$$

→ $|X_{CM}| > 35.74 @ 167MHz$ and CM choke is capacitive


$$\rightarrow \frac{1}{2\pi \cdot 167M \cdot C_p} > 35.74 \rightarrow C_p < 26.67pF$$

→ to avoid an additional resonant frequency at low f , two conditions should be met:

- A) $f_{CM} = \frac{1}{2\pi\sqrt{L_{CM}C_p}} < f_e$ where f_{CM} is the self-resonant frequency of the CM choke and f_e is the frequency at which $X_A = X_{CM}$
- B) $|X_{CM}| < |X_A|$ when $f < f_e$

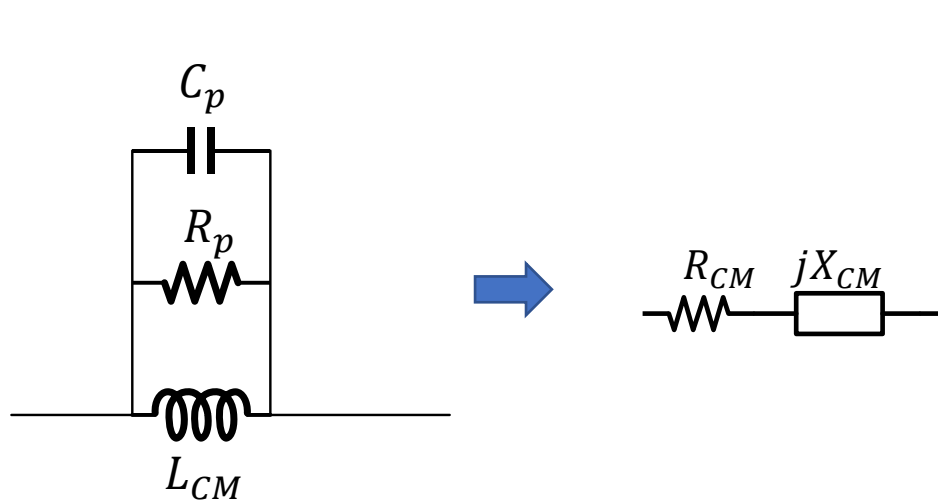2. If $X_{CM} > 0$ at f_r
the new resonant frequency will be lower, avoid!

Resistance and Reactance of the CM Inductor



$$R_{CM} = \frac{\frac{\omega^2 L_{CM}^2}{R_p}}{\omega^4 L_{CM}^2 C_p^2 + \omega^2 L_{CM}^2 \left(\frac{1}{R_p^2} - 2C_p \right) + 1}$$

$$jX_{CM} = j \frac{\omega L_{CM} (1 - \omega^2 L_{CM} C_p)}{\omega^4 L_{CM}^2 C_p^2 + \omega^2 L_{CM}^2 \left(\frac{1}{R_p^2} - 2C_p \right) + 1}$$


$$f_{CM} = \frac{1}{2\pi \sqrt{L_{CM} C_p}}$$

$$R_{CM} = \begin{cases} \frac{\omega^2 L_{CM}^2}{R_p} & f \ll f_{CM} \\ R_p & f = f_{CM} \\ \frac{1}{\omega^2 C_p^2 R_p} & f \gg f_{CM} \end{cases}$$


R_{CM} is the maximum at f_{CM}
 $\rightarrow$
 f_{CM} is better to be close to f_{rnew}



$$X_{CM} = \begin{cases} \omega L_{CM} & f \ll f_{CM} \\ 0 & f = f_{CM} \\ \frac{1}{\omega C_p} & f \gg f_{CM} \end{cases}$$

CM Inductor with the Desired Impedance


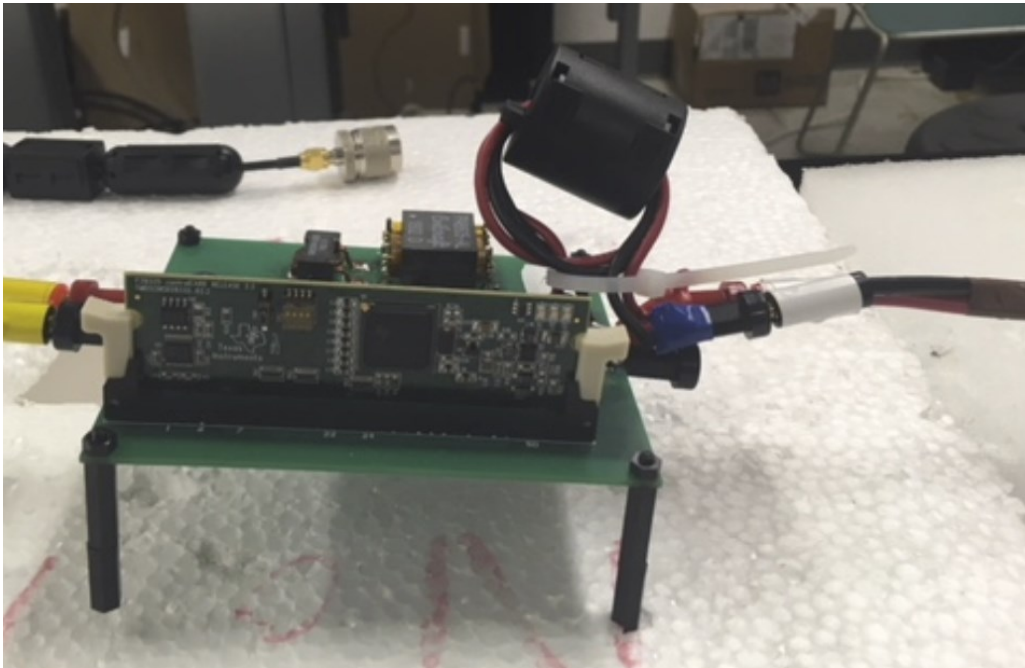


Impedance of CM Choke

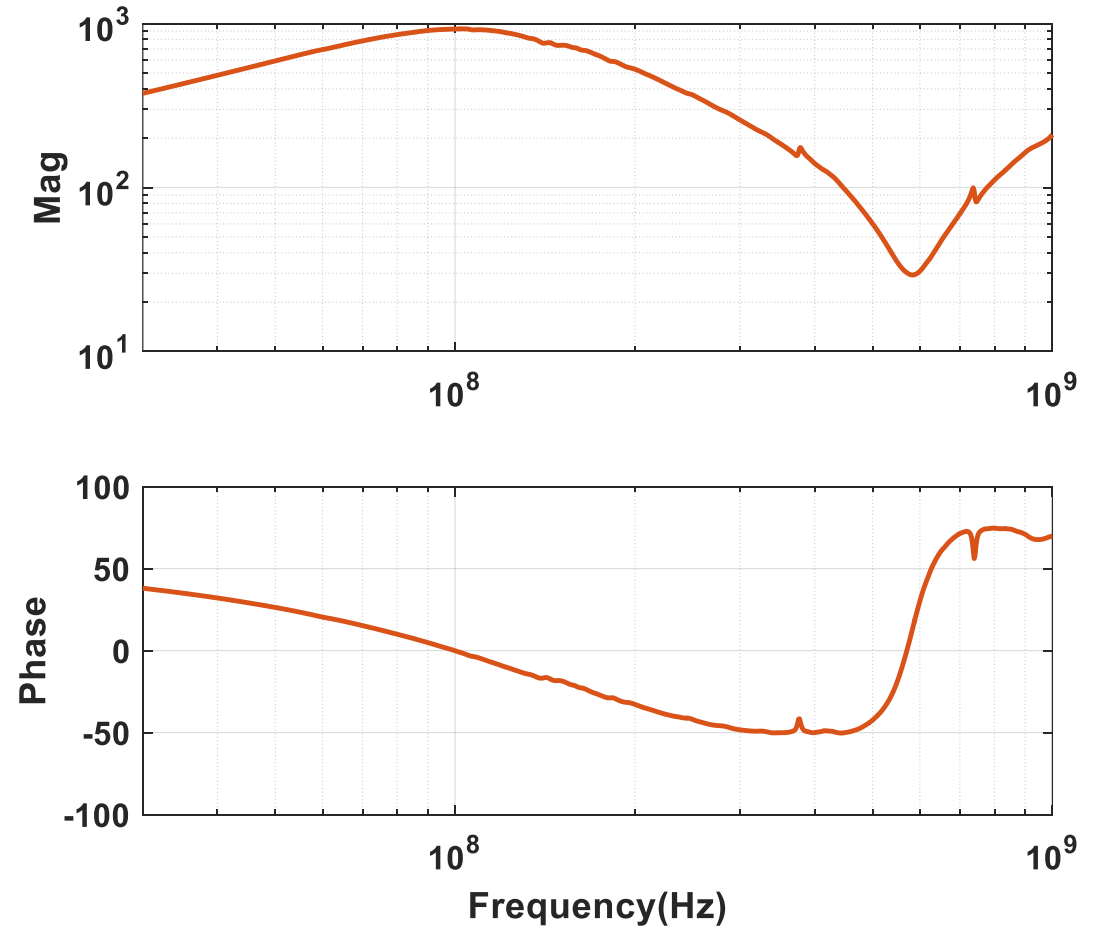


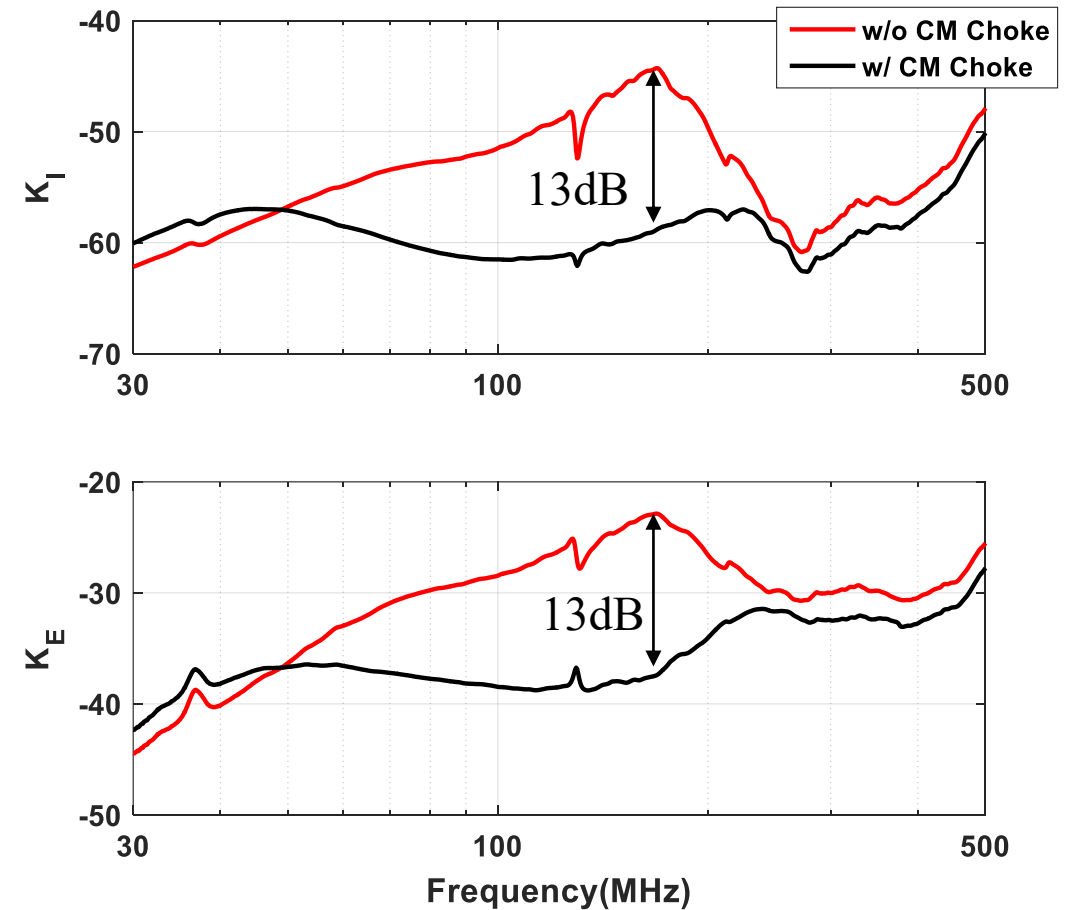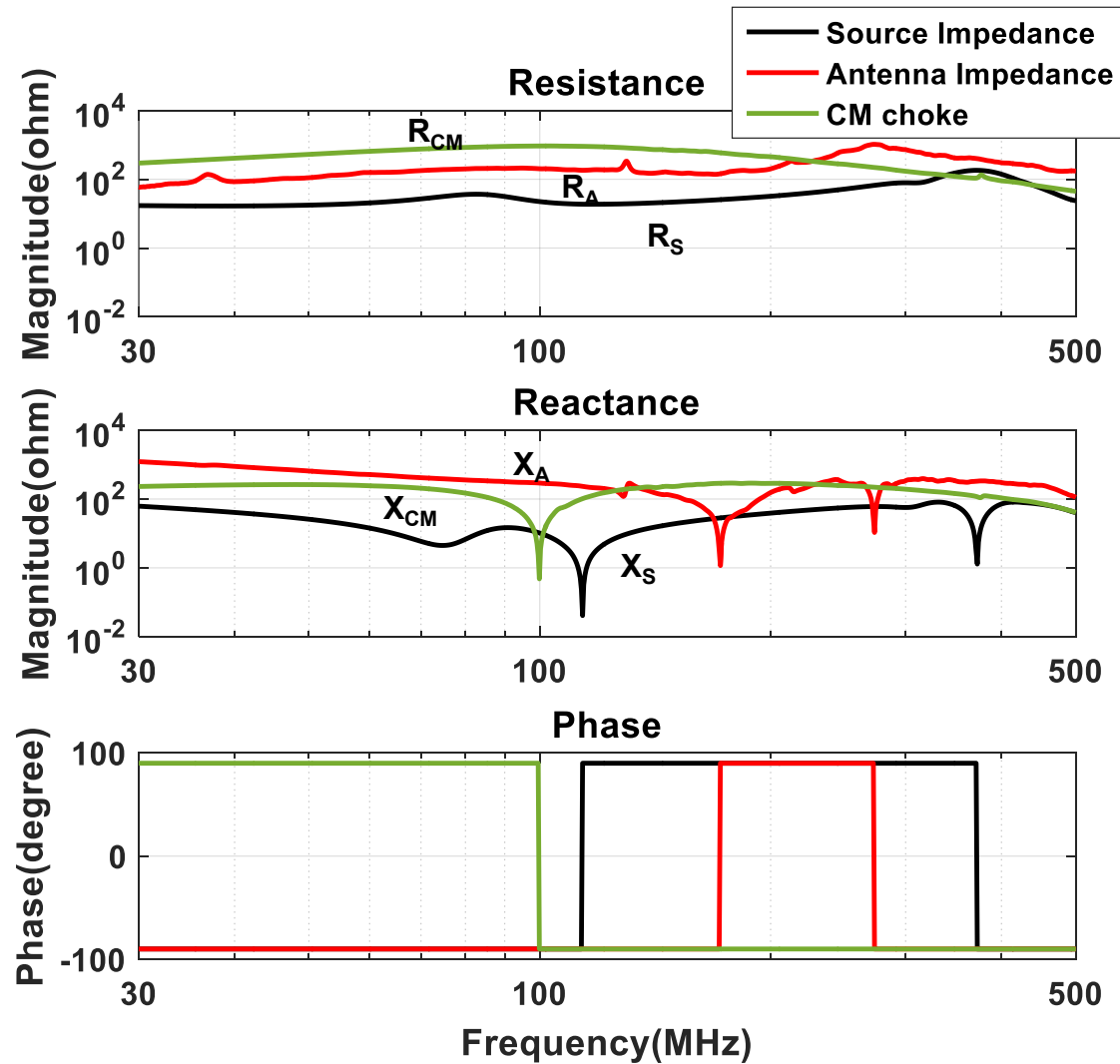


Experimental Verification

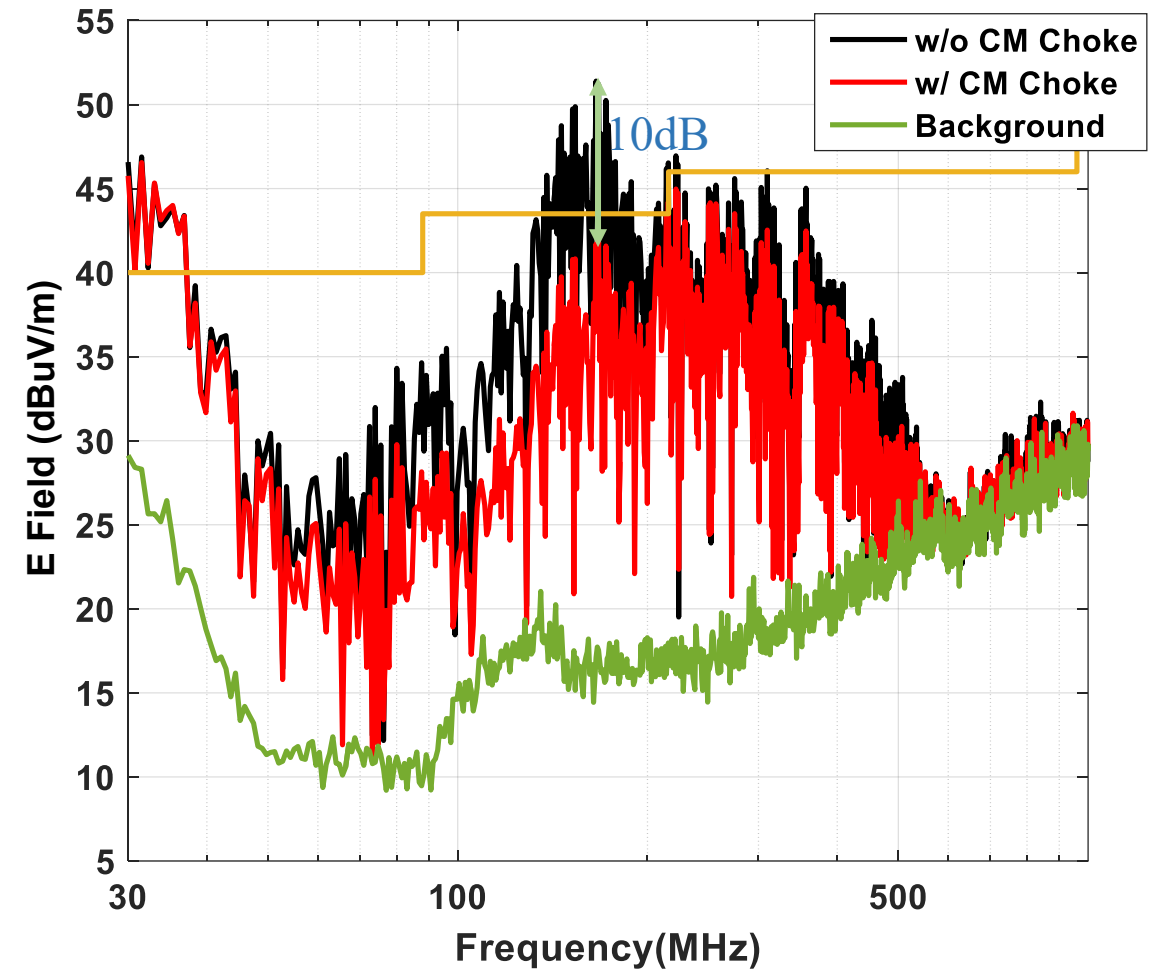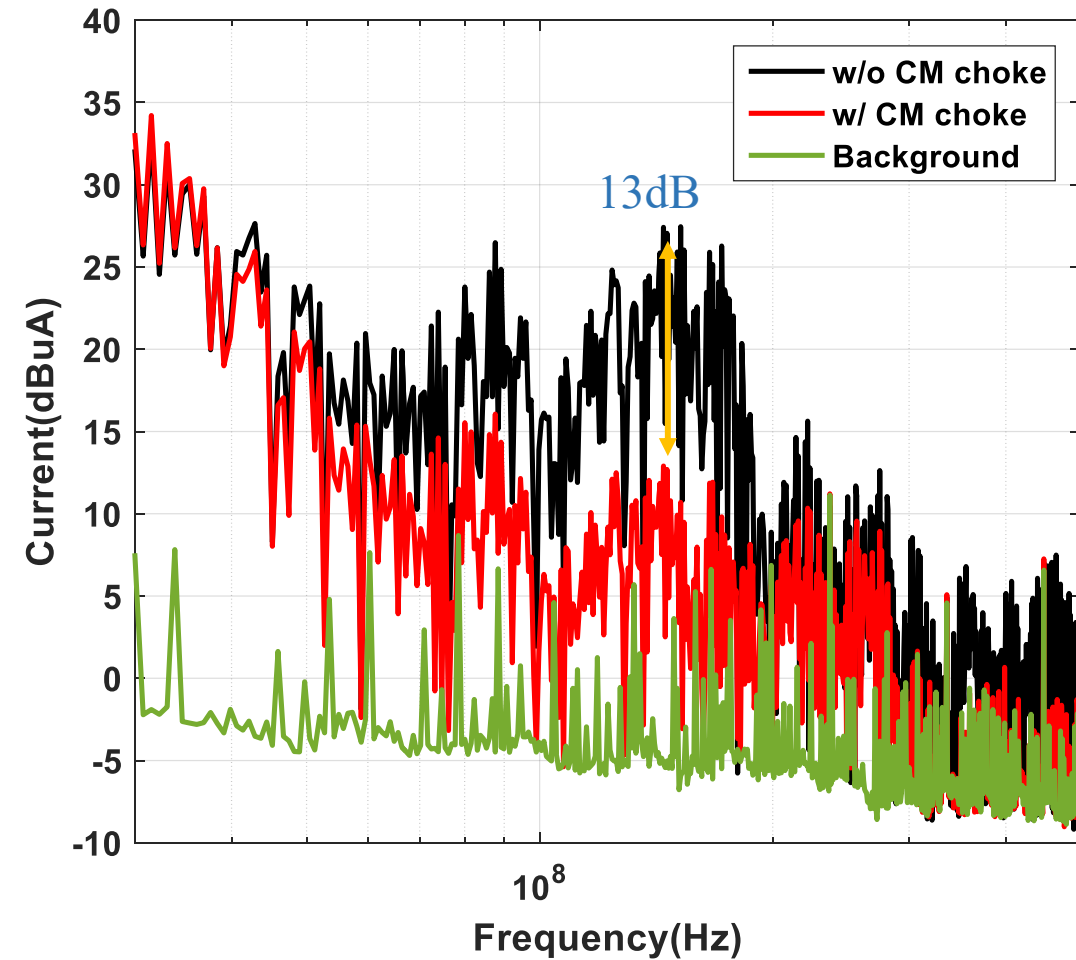

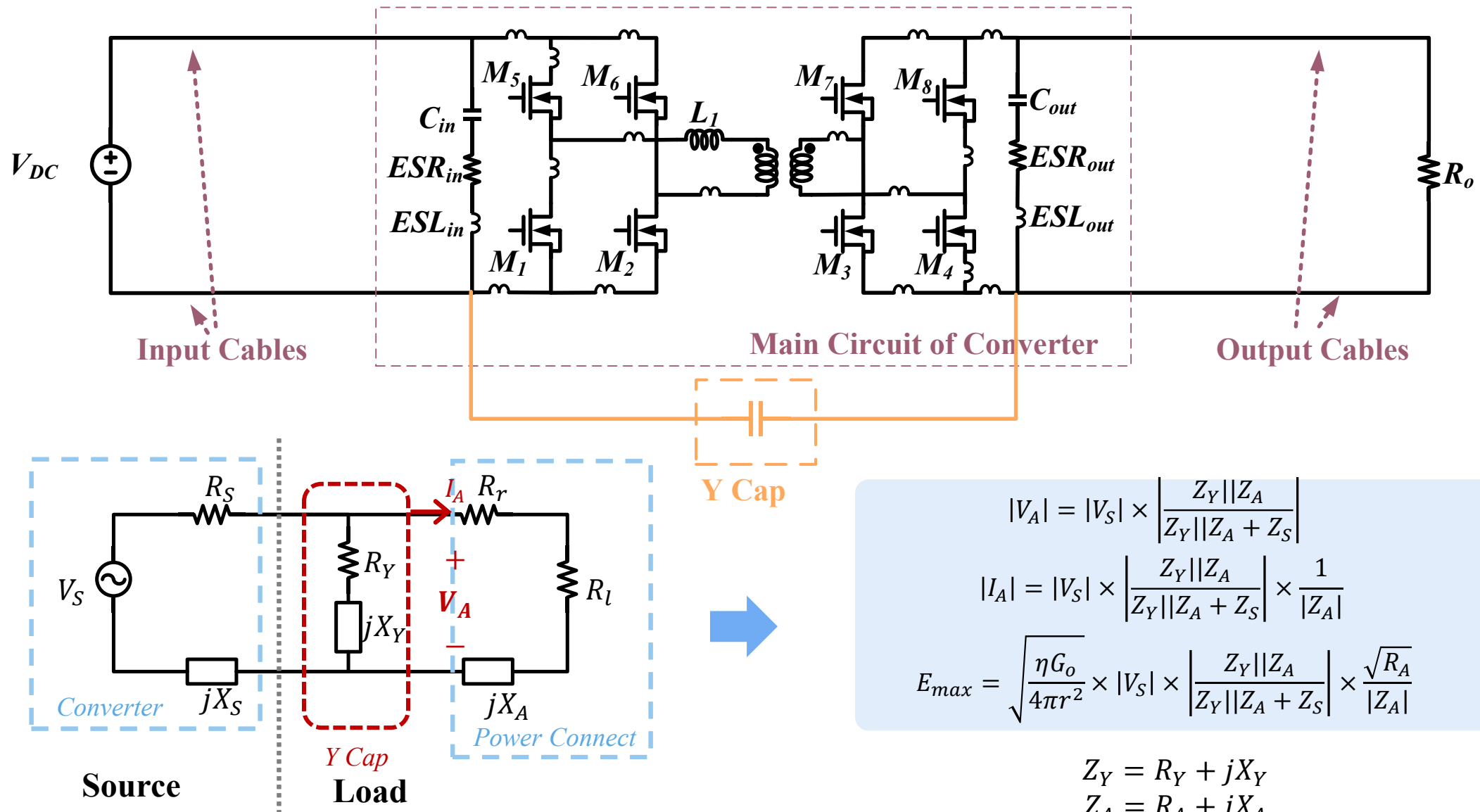CM Capacitor Design to Reduce Radiated EMI



Impact of CM Capacitor on Radiated EMI

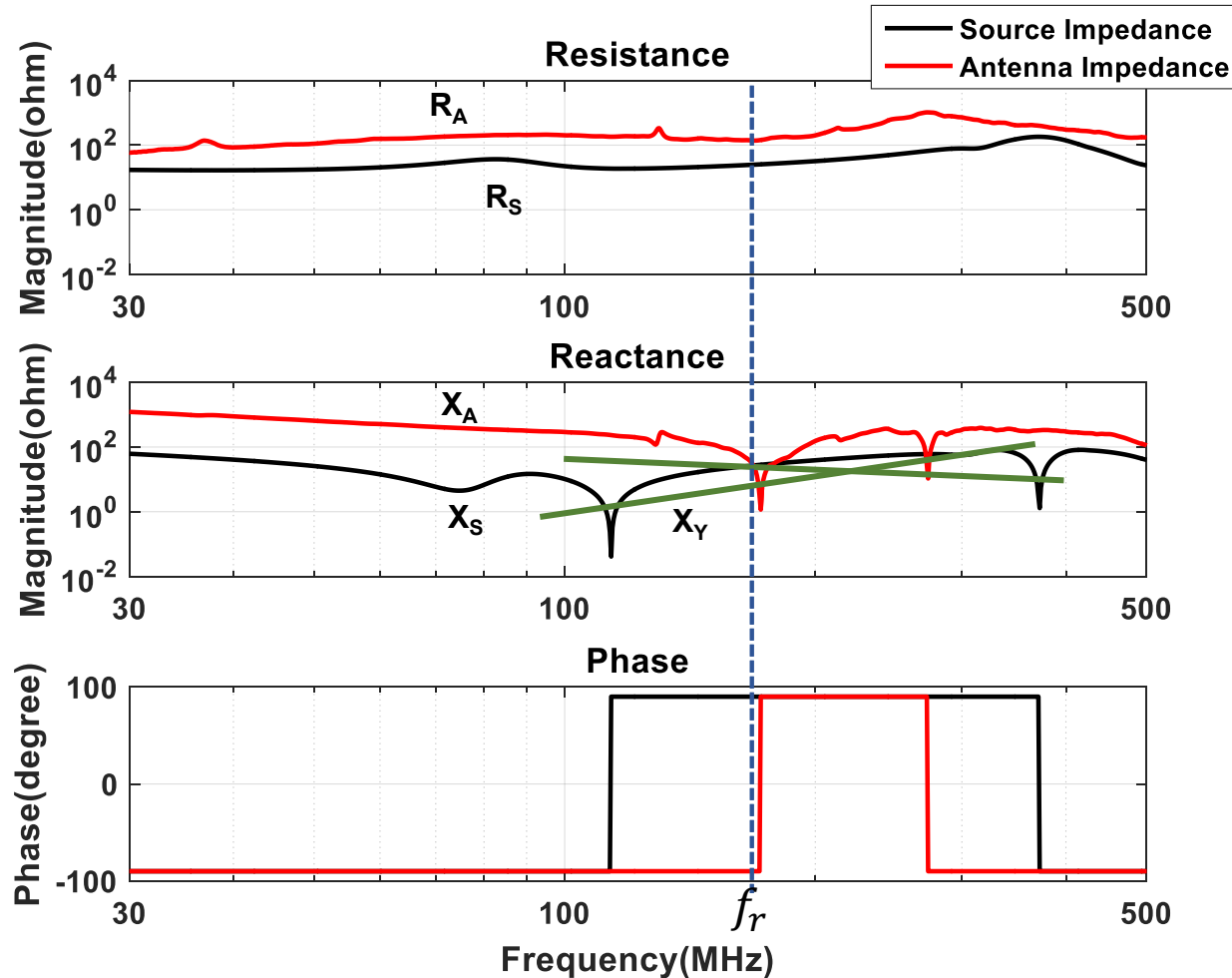

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_Y || Z_A}{Z_Y || Z_A + Z_S} \right| \times \frac{\sqrt{R_A}}{|Z_A|}$$

1. If the Y cap is effective $\rightarrow |Z_Y| < |Z_A|$


$$\begin{aligned} E_{max} &= \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_Y || Z_A}{Z_Y || Z_A + Z_S} \right| \times \frac{\sqrt{R_A}}{|Z_A|} \\ &= \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_Y}{Z_Y + Z_S} \right| \times \frac{\sqrt{R_A}}{|Z_A|} \end{aligned}$$

2. Around the resonant frequency of the antenna, because the reactance of the antenna is close to 0, $|Z_Y|$ may be larger than $|Z_A|$ in a narrow frequency range.

$$\begin{aligned} \rightarrow E_{max} &= \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_A}{Z_A + Z_S} \right| \times \frac{\sqrt{R_A}}{|Z_A|} \\ &= \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}} \end{aligned}$$

- $\rightarrow E_{max}$ is the same as the one without Y cap.


Simplify the Equations of Radiated EMI

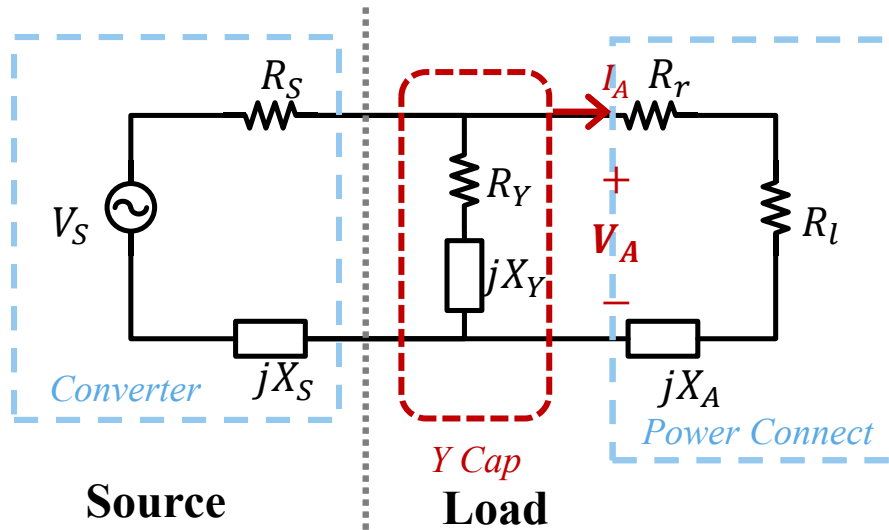

Usually, the parasitic resistance of the Y cap R_Y is smaller than R_S and $|X_Y|$

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{\sqrt{R_A}}{\sqrt{R_A^2 + X_A^2}}$$

$$|I_A| = |V_S| \times \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{1}{\sqrt{R_A^2 + X_A^2}}$$

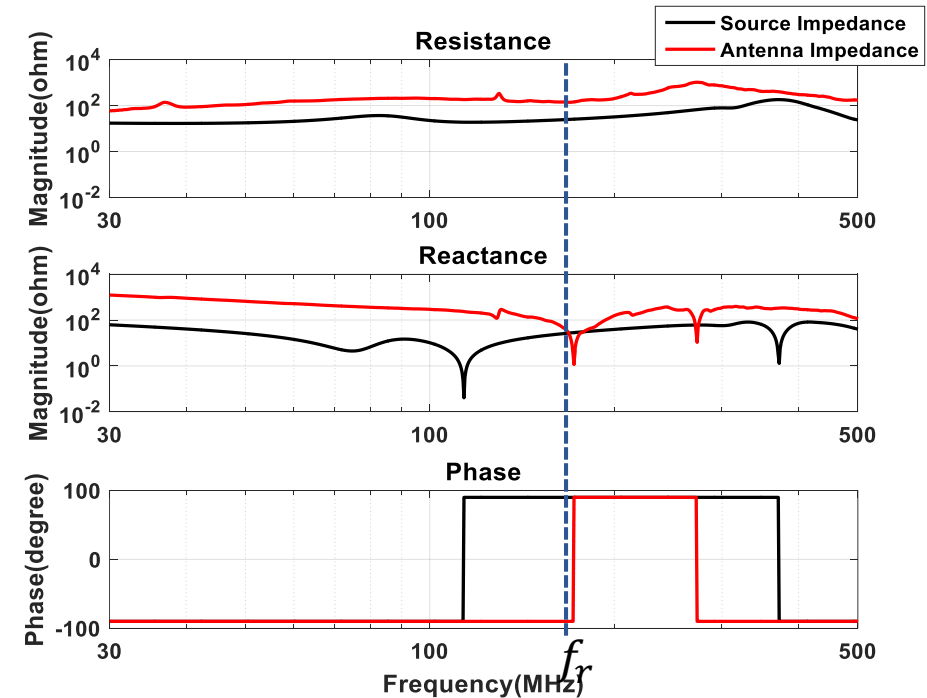


Around 30MHz

$$R_A \ll |X_A| \quad R_S \ll |X_A| \quad |X_S| \ll |X_A|$$

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{\sqrt{R_A}}{|X_A|}$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}}$$

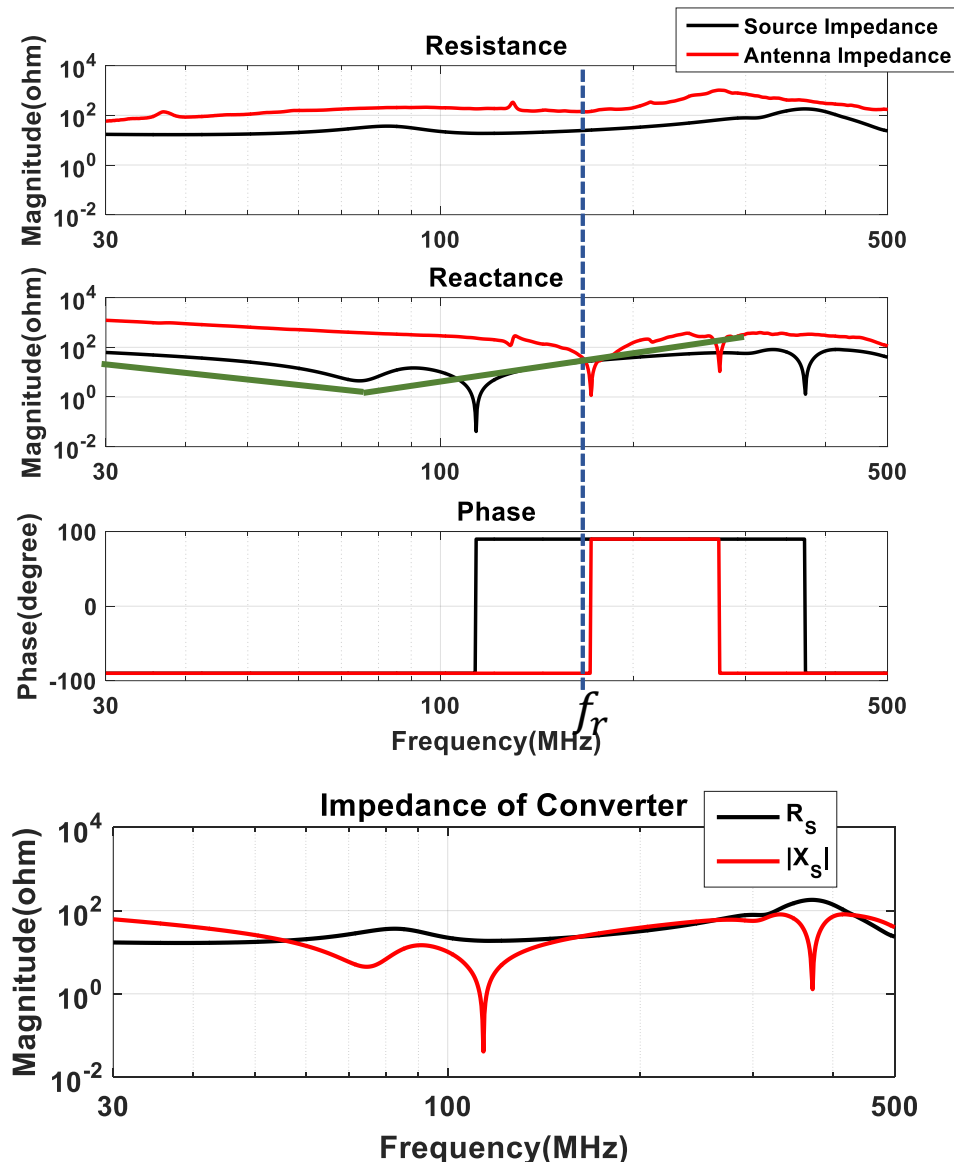CM Capacitor Impedance Design around 30MHz



$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}}$$

$$(1) |X_Y| < |X_S|$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + X_S^2}}$$

$|X_Y| \downarrow \rightarrow \text{Insertion Gain} \downarrow$

$$|X_Y| < |X_S| = 62 \text{ around } 30\text{MHz}$$



If X_Y is capacitive, $C > 85.6\text{pF}$

If X_Y is inductive, $L < 328.76\text{nH}$


$$(2) |X_Y| > |X_S|$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + X_Y^2}} = \frac{|X_Y|}{|X_Y|} = 1$$

The Y cap can reduce the radiation only if its impedance is smaller than that of the converter.

And smaller impedance is more effective in this range.

CM Capacitor Impedance Design Around f_r

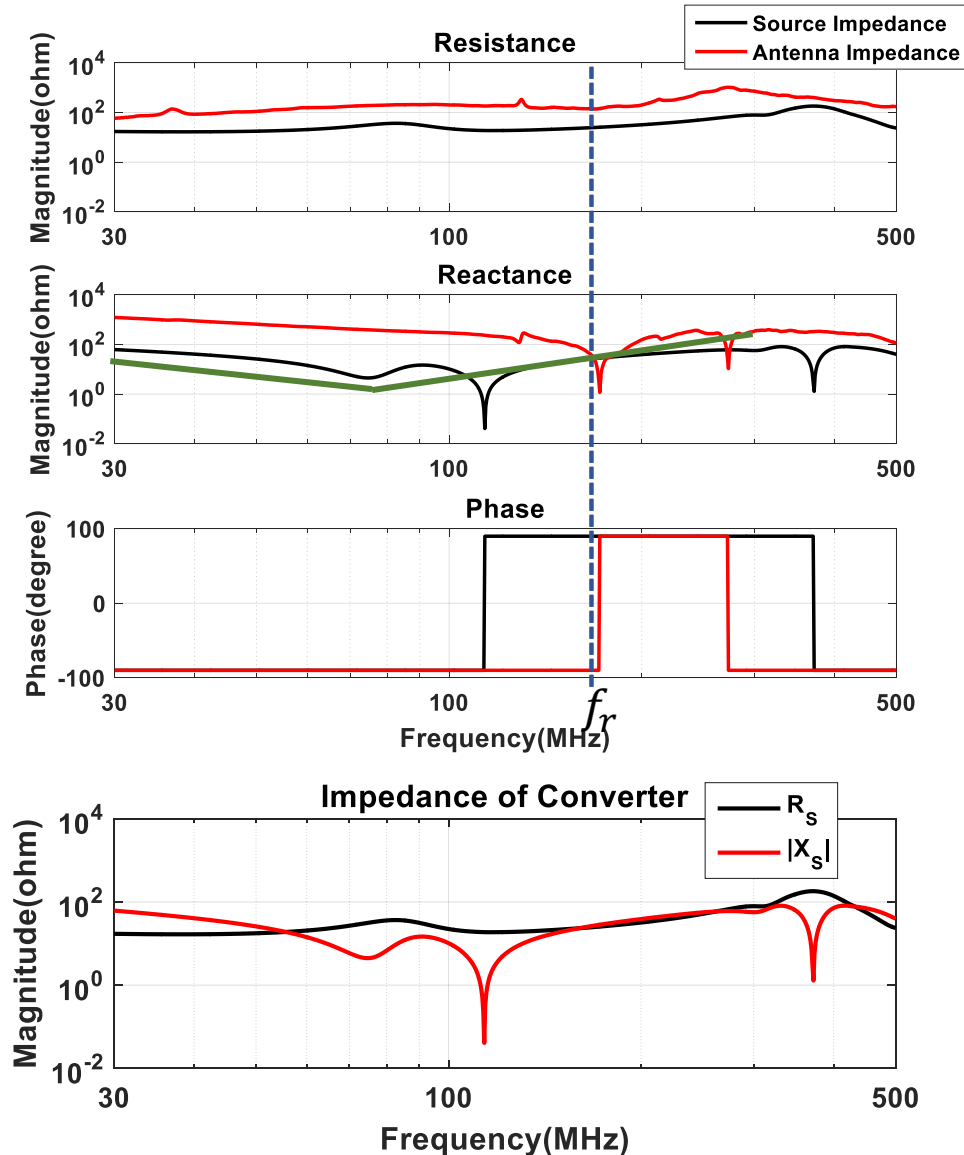

$$E_{max} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{\sqrt{R_A}}{\sqrt{R_A^2 + X_A^2}}$$

$$E_{max_old} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{\sqrt{(R_S + R_A)^2 + (X_S + X_A)^2}}$$

Around the original resonant frequency f_r

$$X_S = -X_A, X_A < R_A, R_S < R_A$$

$$E_{max_old} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{\sqrt{R_A}}{R_A}$$

$$E_{max_new} = \sqrt{\frac{\eta G_o}{4\pi r^2}} \times |V_S| \times \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{\sqrt{R_A}}{R_A}$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}}$$

Around f_r , R_S is close to X_S Insertion Gain < 1 $\rightarrow |X_Y| < |X_S| = 32.13$
 If X_Y is capacitive, $C > 29.67\text{pF}$
 If X_Y is inductive, $L < 30.62\text{nH}$

CM Capacitors with different Impedances

Around 30MHz: <62


If X_Y is capacitive, $C > 85.6pF$

If X_Y is inductive, $L < 328.76nH$




Around f_r : < 32.13

If X_Y is capacitive, $C > 29.67pF$



If X_Y is inductive, $L < 30.62nH$

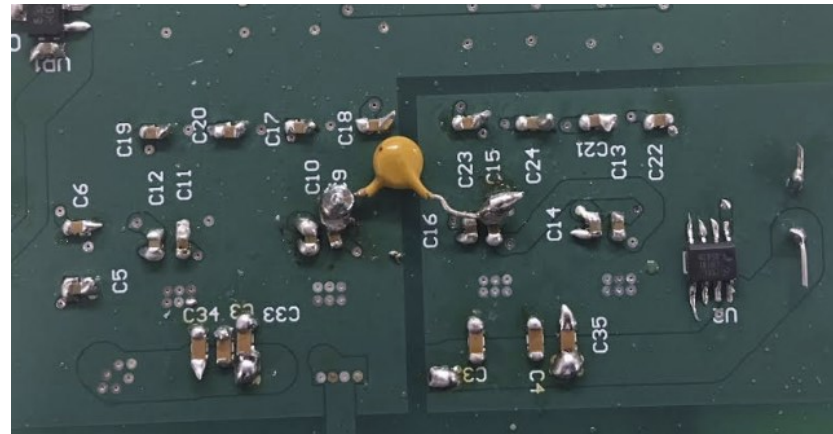

100pF

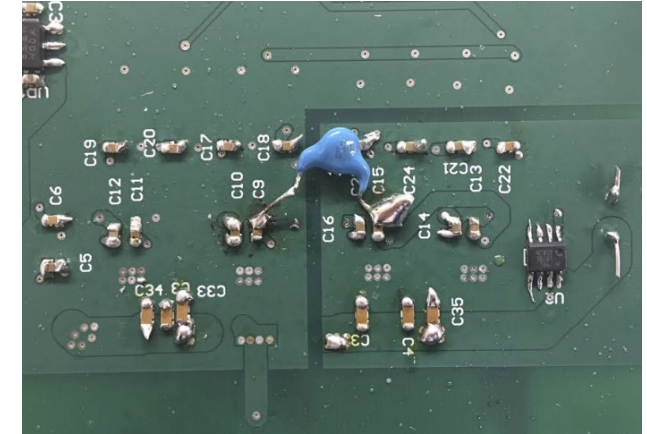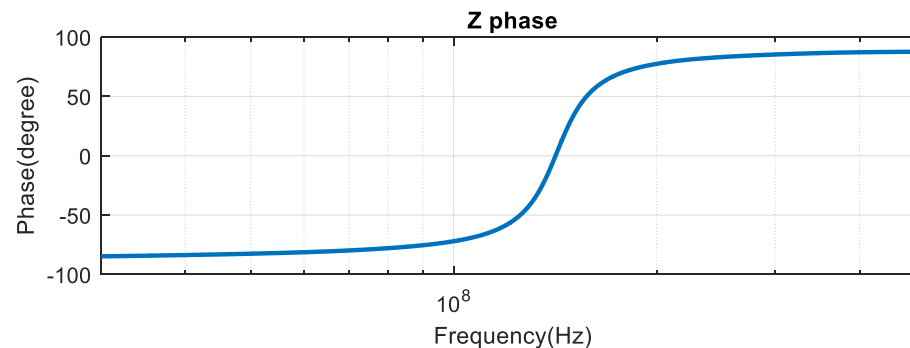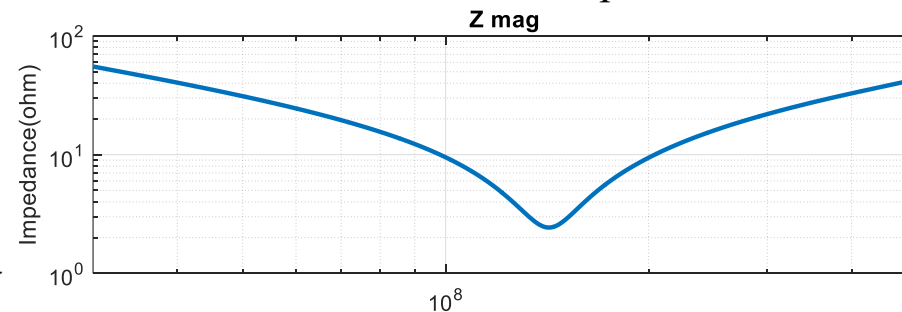

470pF

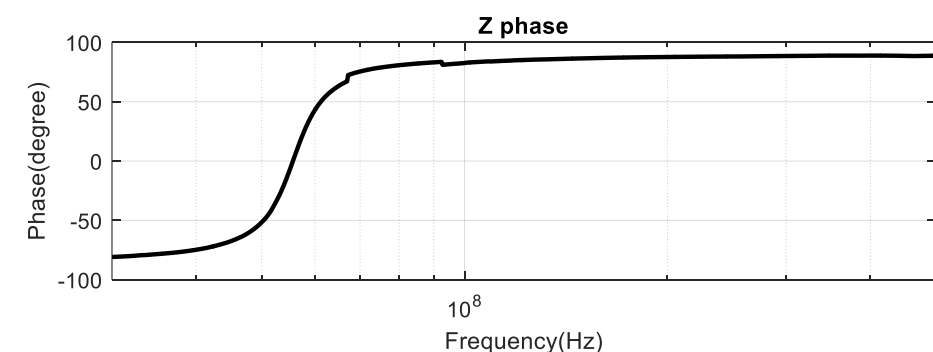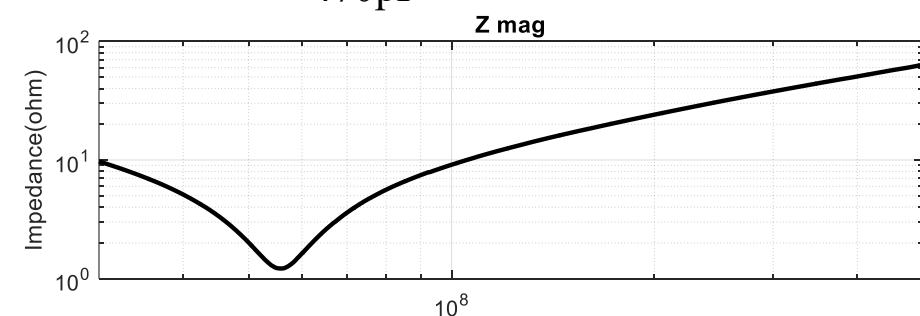


Both 30MHz and f_r :

If X_Y is capacitive, $C > 85.6pF$

If X_Y is inductive, $L < 30.62nH$

Performance of the 100pF CM Capacitor

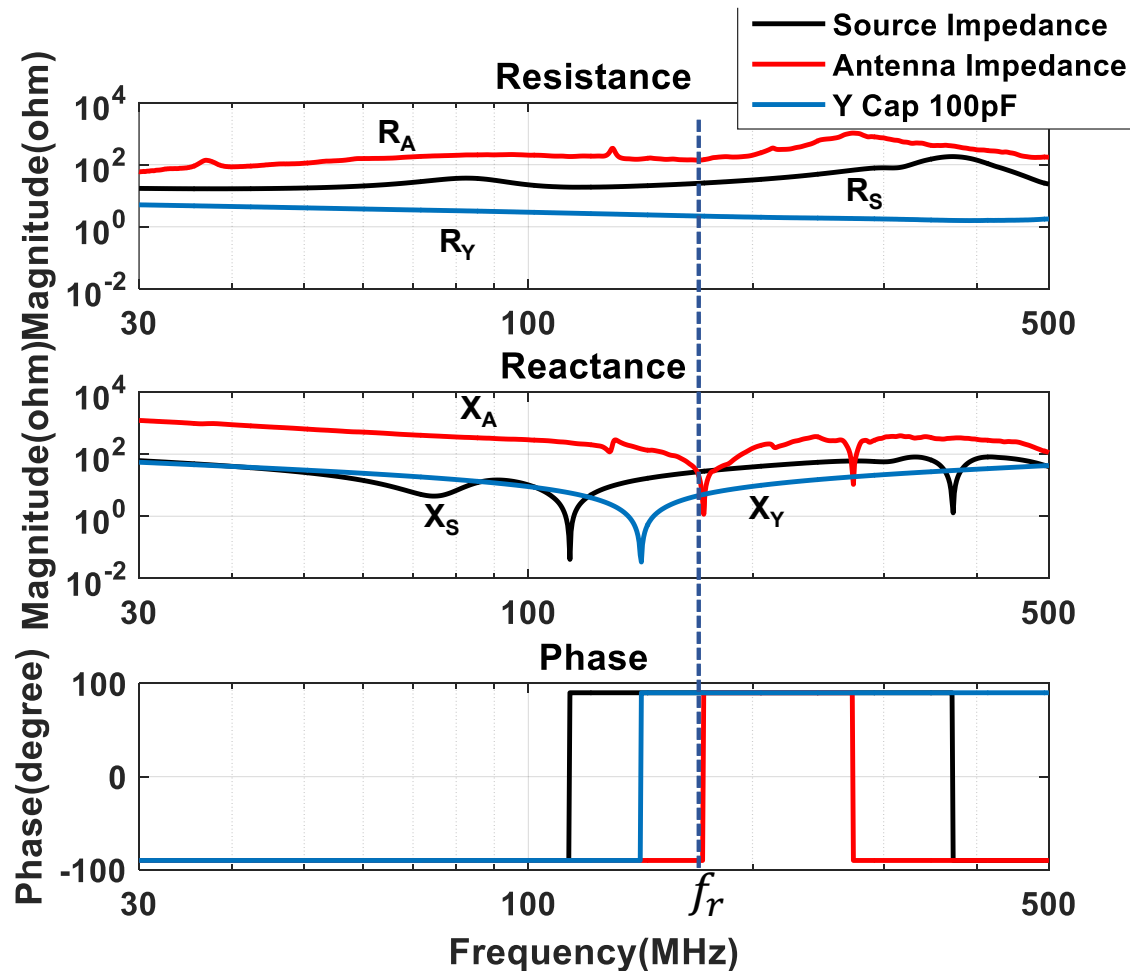

1. Around 30MHz

$$X_Y \approx X_S, R_S < |X_S|$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} = \frac{1}{2}$$

The current/radiated E field will be reduced by 6dB.


2. Around 167MHz(original resonant frequency f_r)

$$|X_Y| < |X_S|$$

The current/ radiated E field can be greatly reduced.

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}}$$

Performance of the 470pF CM Capacitor

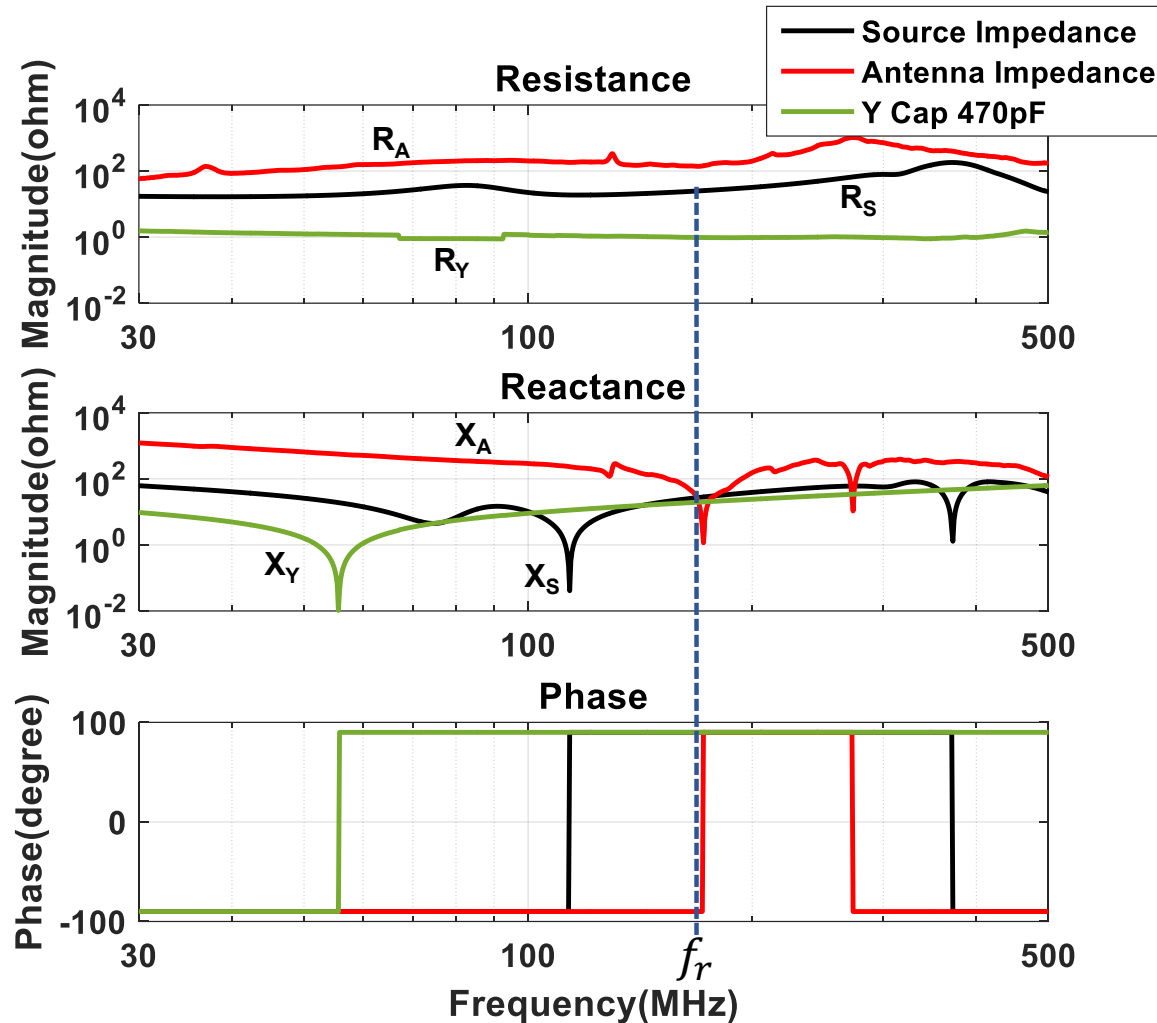

1. Around 30MHz

$$|X_Y| < |X_S|$$

Current/radiated E field can be greatly reduced



2. Around 167MHz

$$|X_Y| \approx |X_S|, |X_Y + X_S| > |R_S|$$

$$\text{Insertion Gain} = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}}$$

The reduction about 6dB.


Experimental Verification

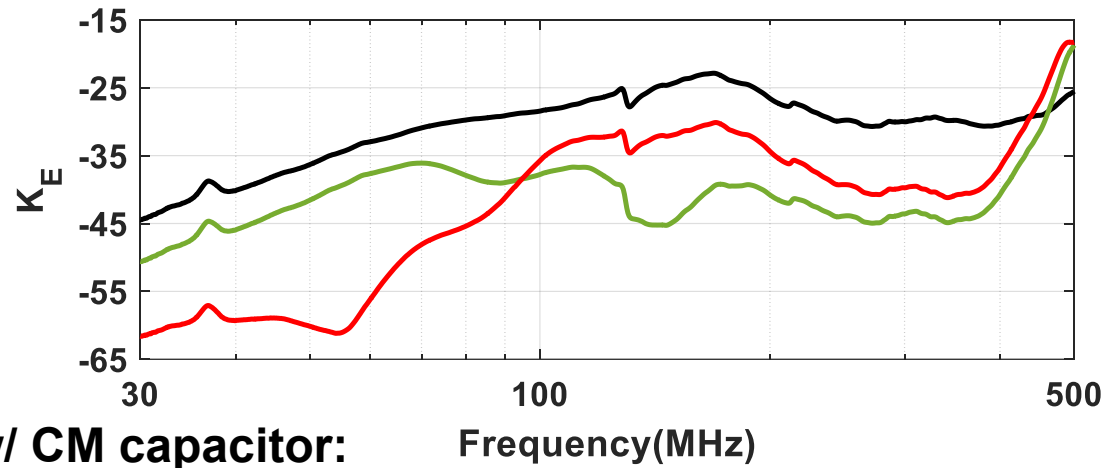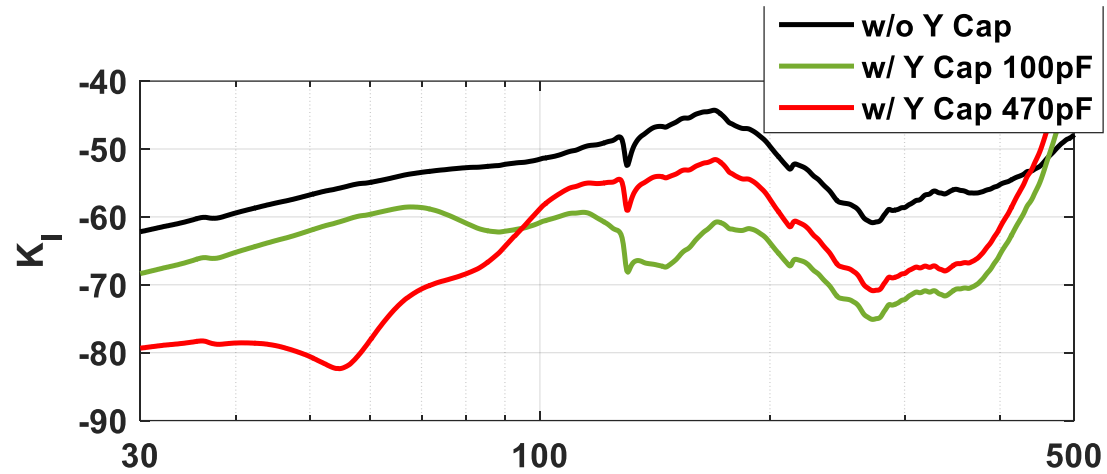


w/ CM capacitor:

$$K_I = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{1}{\sqrt{R_A^2 + X_A^2}}$$

$$K_E = \frac{|X_Y|}{\sqrt{R_S^2 + (X_Y + X_S)^2}} \times \frac{\sqrt{R_A}}{\sqrt{R_A^2 + X_A^2}}$$

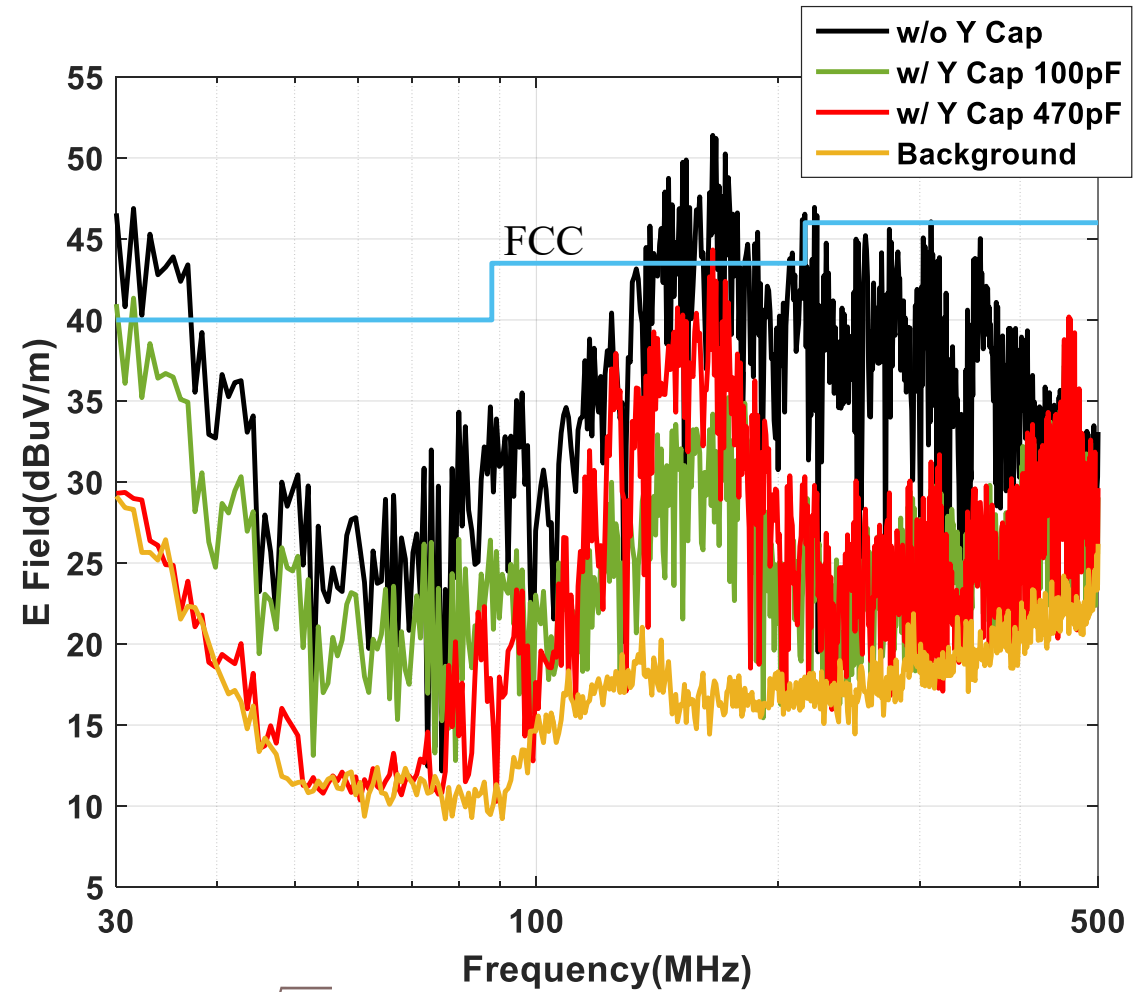


LC Type EMI Filter Design

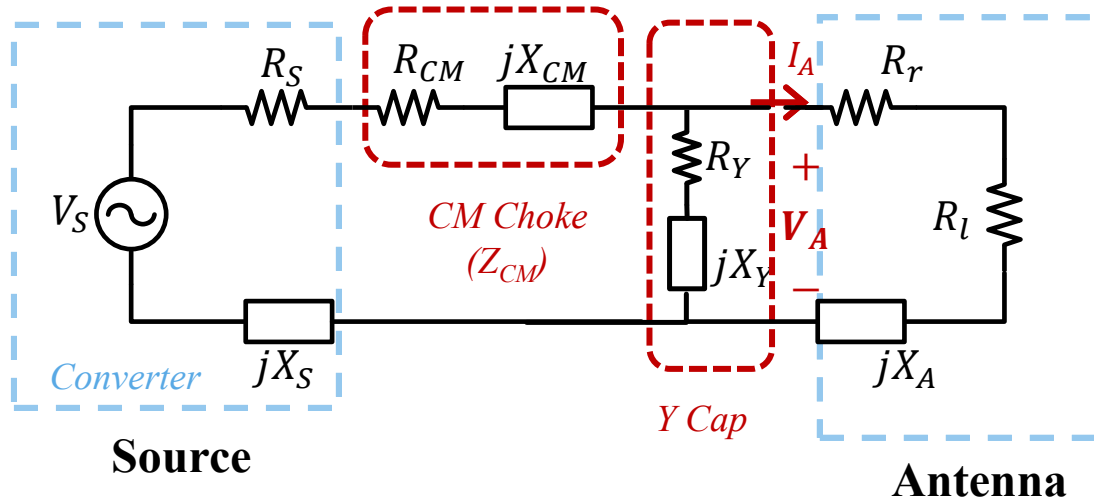


$$I_A = |V_S| \times \left| \frac{Z_Y \parallel Z_A}{Z_{CM} + Z_S + Z_Y \parallel Z_A} \times \frac{1}{Z_A} \right|$$

$$E_{\max} = \sqrt{\frac{\eta G}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_Y \parallel Z_A}{Z_{CM} + Z_S + Z_Y \parallel Z_A} \times \frac{1}{Z_A} \right| \times \sqrt{R_A}$$

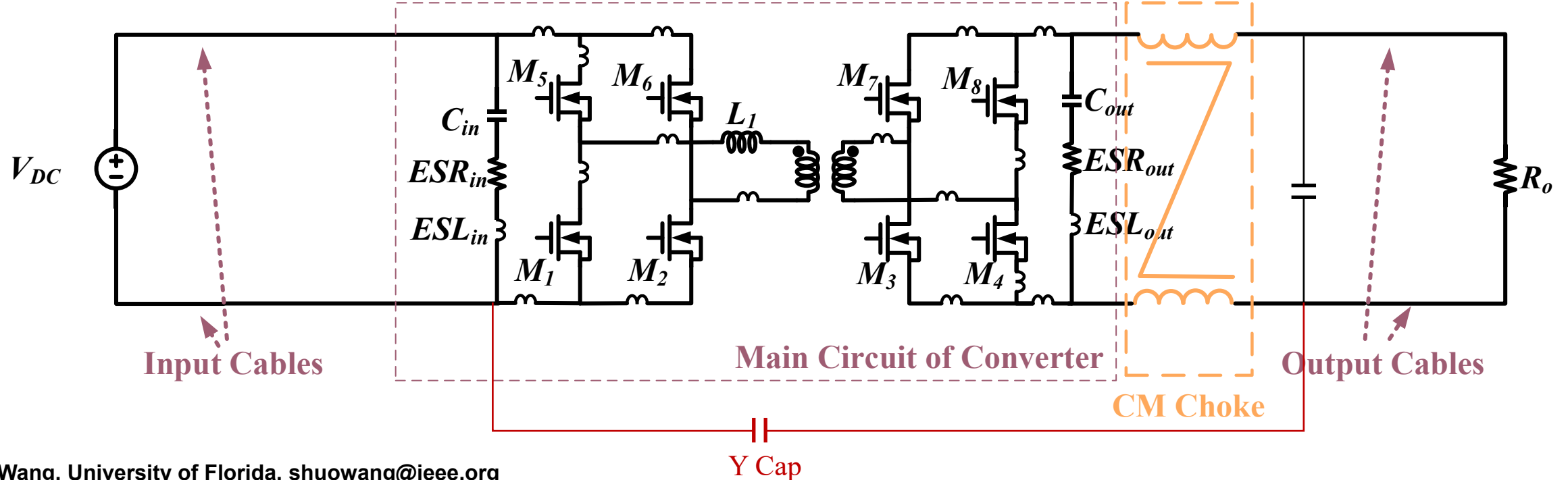

Filter Impedance Mismatch Design

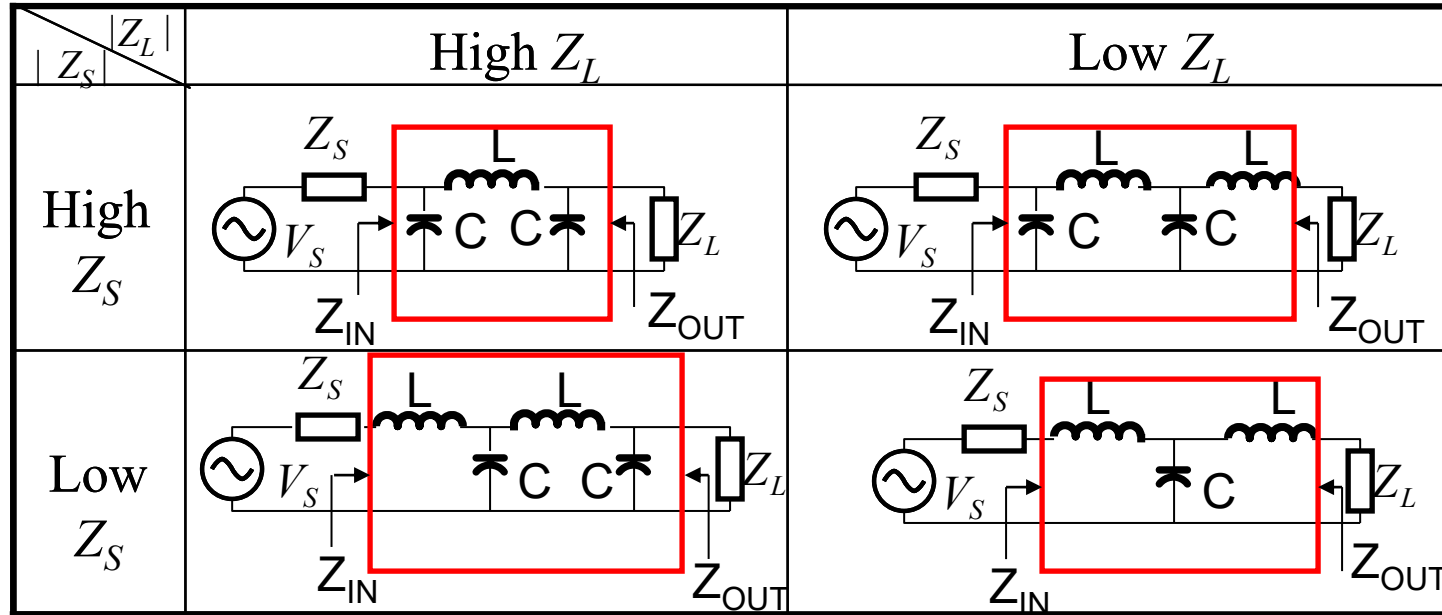

At new resonant frequency $f_{r_new_LC}$:

$$I_A = |V_S| \times \frac{|X_Y|}{R_{CM} + R_S} \times \frac{1}{\sqrt{R_A^2 + X_A^2}}$$


$$E_{\max} = \sqrt{\frac{\eta G}{4\pi r^2}} \times |V_S| \times \frac{|X_Y|}{R_{CM} + R_S} \times \sqrt{K_E}$$

Make f_{CM} close to $f_{r_new_LC}$

$$R_{CM} = \begin{cases} \omega^2 \frac{L_{CM}^2}{R_p} & f \ll f_{CM} \\ R_p & f = f_{CM} \\ \frac{1}{\omega^2 C_p^2 R_p} & f \gg f_{CM} \end{cases}$$

$$I_A = |V_S| \times \left| \frac{Z_Y \parallel Z_A}{Z_{CM} + Z_S + Z_Y \parallel Z_A} \times \frac{1}{Z_A} \right|$$

$$E_{\max} = \sqrt{\frac{\eta G}{4\pi r^2}} \times |V_S| \times \left| \frac{Z_Y \parallel Z_A}{Z_{CM} + Z_S + Z_Y \parallel Z_A} \times \frac{1}{Z_A} \right| \times \sqrt{R_A}$$

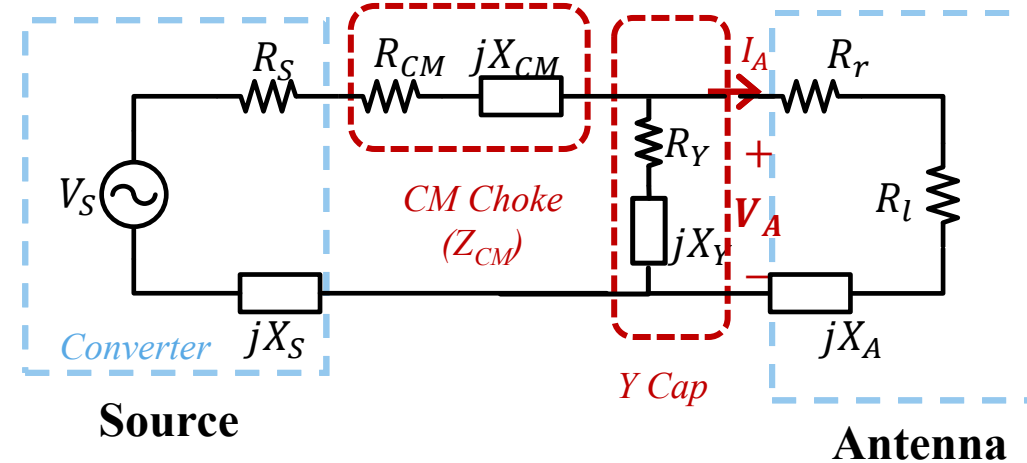

$|Z_{CM}| \gg |Z_S|$ and $|Z_Y| \ll |Z_A|$ should be met.

$|X_{CM}| > |X_S|$, & $|X_Y| < |X_A|$ to reduce EMI at f_r .

Questions?