

DC/DC Converter EMC Trouble-shooting

March 2022

MPS


Agenda

- **General Guidelines for DC/DC EMC Troubleshooting**
- **Optimization Examples with MPS DC/DC Evaluation Boards**
- **Conclusion**

Step of Troubleshooting

➤ Test background understanding

- Which EMC tests are failed by DUT? CE? RE? Or Immunity?
- What's the test standard and limit? CISPR? Or Customer specific (TL81000)?
- How does the test spec & set-up look like?
 Input and output voltage? Load?
 Input and output cable length?
 Voltage method CE or current method CE?
 Antenna type and placement, 1m or 3m?
- How does DUT look like?
 Load size, on board or out of board with long cable connection?
 Housing: metal or plastic? Heatsink? X/Y/Z placement?
- At what frequency does the DUT exceed the limits?
 Any regularity on failed frequency?
- Any modification/optimization done before and corresponding effect?

 

EMI	CE	电源线时域传导发射
		电源线频域传导发射
	RE	辐射发射-天线接收法
		辐射发射-TEM小室法
		辐射抗扰度-TEM小室法
		抗扰度-带状线法
		抗扰度-磁场环照射法
		静电放电实验

Step of Troubleshooting

➤ DUT information review

- **Schematic review**


How many DC/DC converters placed in the system?

Which topo for each DC/DC?

What's the switching frequency for each DC/DC?

If schematic and components value correct and reasonable?

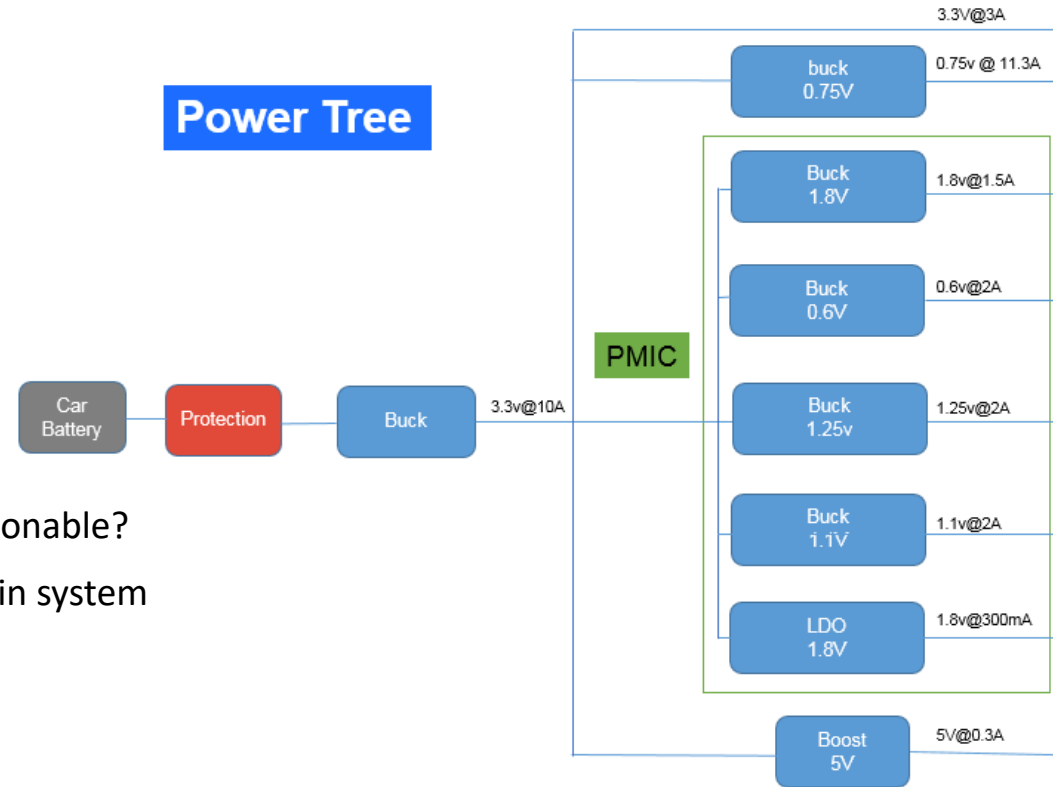Check all input and output filters or common choke in system



Step of Troubleshooting

➤ DUT information review

- **Schematic review**

How many DC/DC converters placed in the system?

Which topo for each DC/DC?

What's the switching frequency for each DC/DC?

If schematic and components value correct and reasonable?

Check all input and output filters or common chock in system

- **Layout and board review**



Where are the DC/DC converters placed in the system?

Identify and mark all high dV/dt and dI/dt circuit nodes

EMI filter placement

GND placement

Inductor type and size

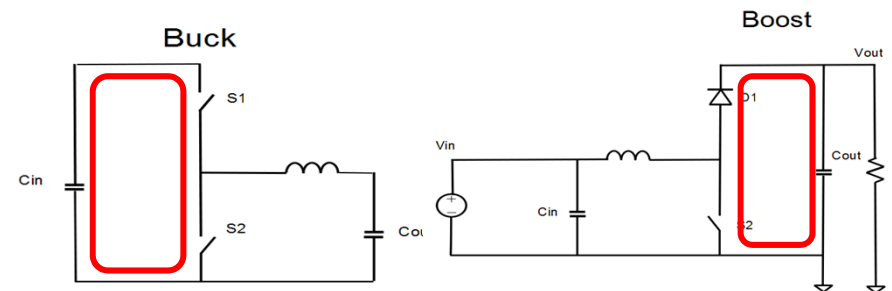 

Step of Troubleshooting

➤ Issue identification

- Quick EMI shot on DUT with default status

If can duplicate same of similar problem/ failure frequency?


Probe SW, Vout and other test point to confirm all circuit works normally

Measure the clock of each DC/DC, create a table with fundamental, harmonics


If failure frequency related with clock of any DC/DC? Failure by DM or CM noise?

	f1 [MHz]	f2 [MHz]	f3 [MHz]
Fsw	0.489	1.93	20.03
2x	0.978	3.86	40.06
3x	1.467	5.79	60.09
4x	1.956	7.72	80.12
5x	2.445	9.65	100.15
6x	2.934	11.58	120.18

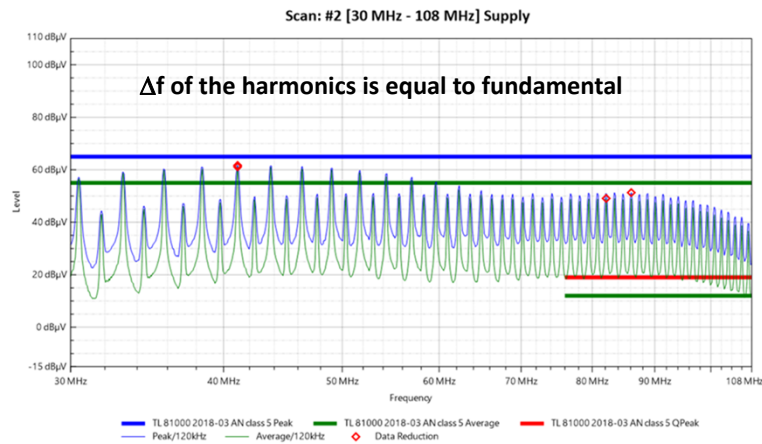Sometimes the source is obvious with discrete frequency lines



But sometimes as “mountains”

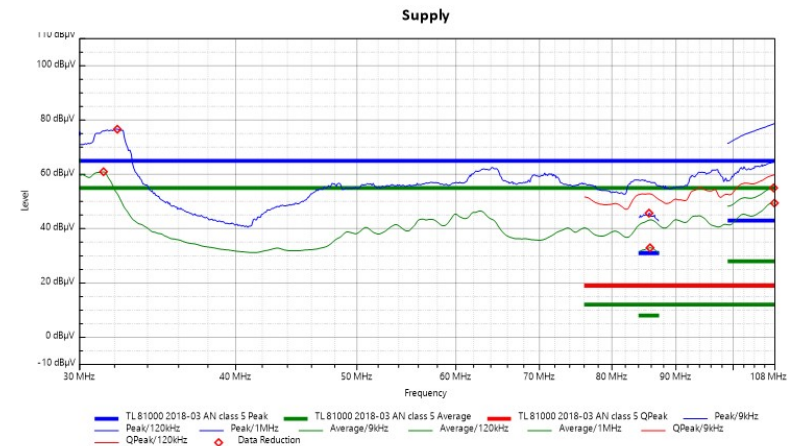

Step of Troubleshooting

➤ Issue identification

- **Identify issue place on DUT**

Change large and complex connectors to simple wire connection

Change load to small size and short cable

Remove heatsink or housing if any

Use snap-on ferrites on cables, and try to distinguish CM and DM noise

Disable each DC/DC converter one by one

Add small shielding on each DC/DC converter or small circuit area one by one

Use field probe to find detailed issue device and place



MPS


Step of Troubleshooting

➤ EMI performance optimization

- Add or increase input/output EMI filters
- Add small capacitance cap close to connectors
- Change switching frequency if allowable
- Change / decrease high frequency noise loop area
- Change inductor with smaller size one
- Adjust inductor, input/output caps placement
- Add BST resistor or snubber
- Adjust heatsink or housing connection to DUT GND
- Do cut on PCB
- Add common chokes if allowable
- Add shielding if allowable

Tool Set for Troubleshooting

 
- LC filter
- Small size inductor
- Cu-Foil / Shielding
- Snap-On Ferrite/ Common Choke
- Field Probes



Choose appropriate input filter

LC filter debug step

 
- Increase the input filter capacitors by 2x
- Increase the input filter coil by 2x
- Use two-stage filter
- What is the distance between the buck C_{IN} and the filter?
- Is an off-board filter effective?




Choose appropriate input filter

Single-Stage vs. Two-Stage

Single-Stage

 

Two-Stage

 

Input EMC Filter Calculation

=Enter your parameter

Single-Stage	Fundamental	1st Harm	2nd Harm	3rd Harm	4th Harm	5th Harm
f_{sw} :	2.2 MHz	4.40	6.60	8.80	11.00	13.20
Ωf_{sw} :	13.821 / μs	27.65	41.47	55.29	69.11	82.94
L _{single} :	0.33 μH					
XL:	4.56 Ω	9.12	13.68	18.25	22.81	27.37
C-effective:	0.70 μF					
XC:	0.10 Ω	0.052	0.034	0.026	0.021	0.017
Damping	-33.09 dB	-44.99	-52.00	-56.99	-60.86	-64.03
Two-Stage Filter Design:						
1st L:	0.10 μH					
XL:	1.38 Ω	2.76	4.15	5.53	6.91	8.29
1st C:	0.60 μF					
XC:	0.121 Ω	0.060	0.040	0.030	0.024	0.020
Damping 1	-21.91 dB	-33.42	-40.36	-45.32	-49.18	-52.33
2nd L:	0.10 μH					
XL:	1.38 Ω	2.76	4.15	5.53	6.91	8.29
2nd C:	0.40 μF					
XC:	0.181 Ω	0.090	0.060	0.045	0.036	0.030
Damping 2:	-18.73 dB	-29.99	-36.88	-41.82	-45.67	-48.82
Total Damping:	-40.65 dB	-63.40	-77.23	-87.13	-94.84	-101.16


Simplified calculation: $20 \log (X_c / (X_c + X_L))$ at f_{sw} , $2 \times f_{sw}$, etc.



Use Cu-Foil shielding

Start with the DC/DC converter and coil...

.... to part of the PCB.


 


Use snap-on ferrite / common choke

w/o common choke




w/ common choke

  


Use field probes





Small CIN

 

Large CIN


 


Cout

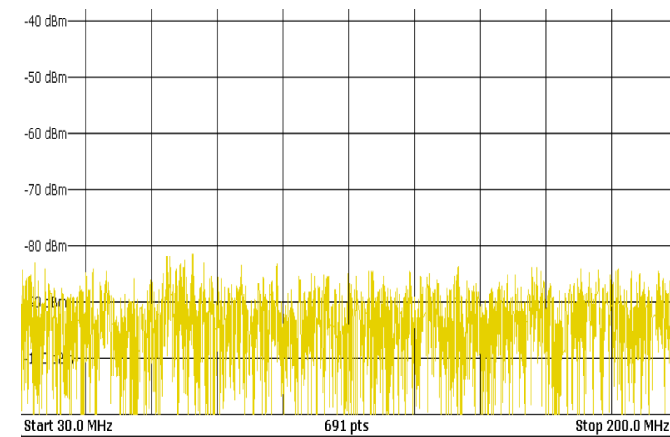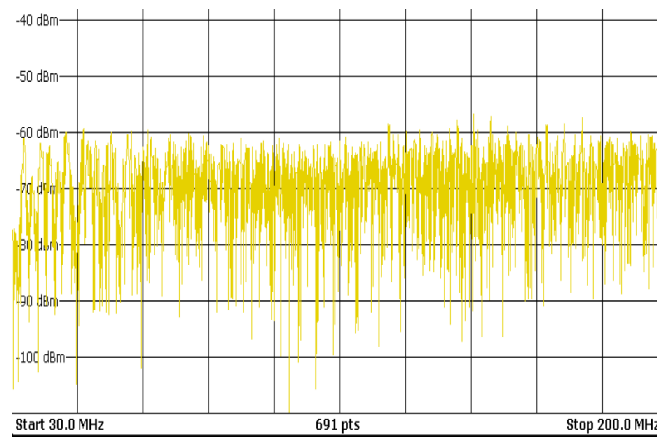 
 


Use field probes



Small CIN

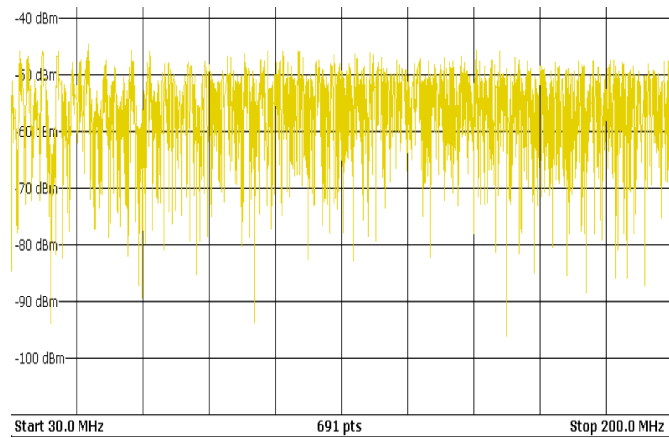 

IC

  


Inductor

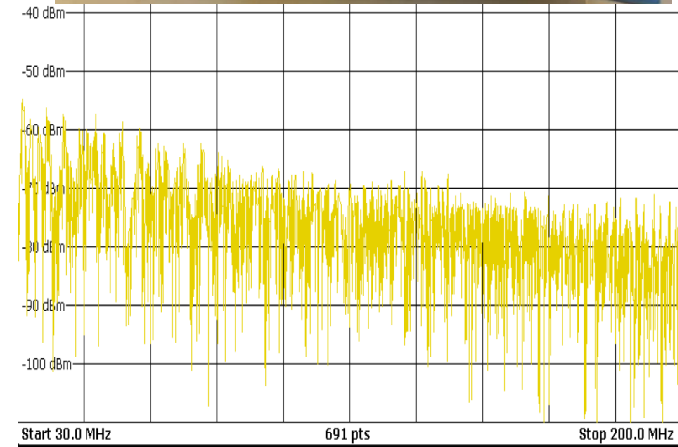 

Refresh: Buck Converter Voltage & Current Waveforms

Simplified ☺


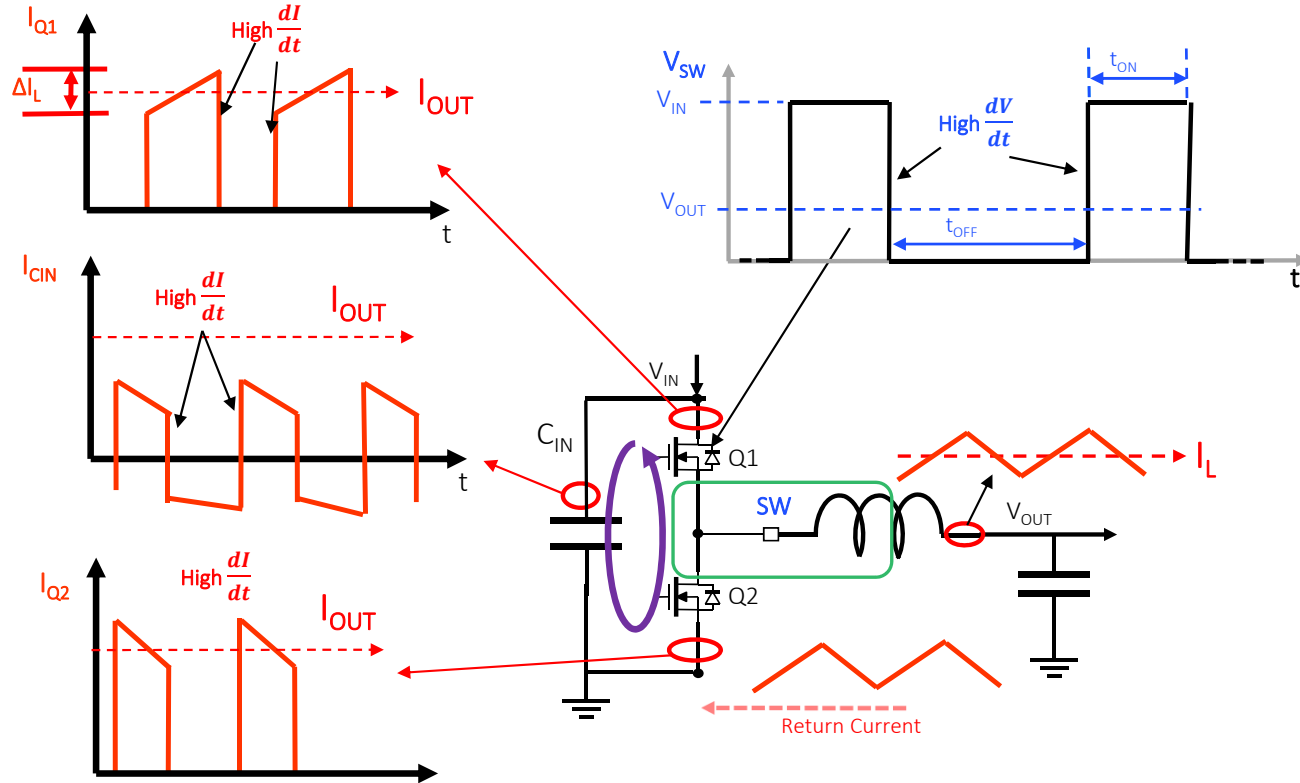


High $\frac{dV}{dt} \Rightarrow E - \text{Field}$
 Increases with voltage
 Increases with SW area size

High $\frac{dI}{dt} \Rightarrow H - \text{Field}$
 Increases with current
 Increases with loop size

A boost converter is just a mirror image.

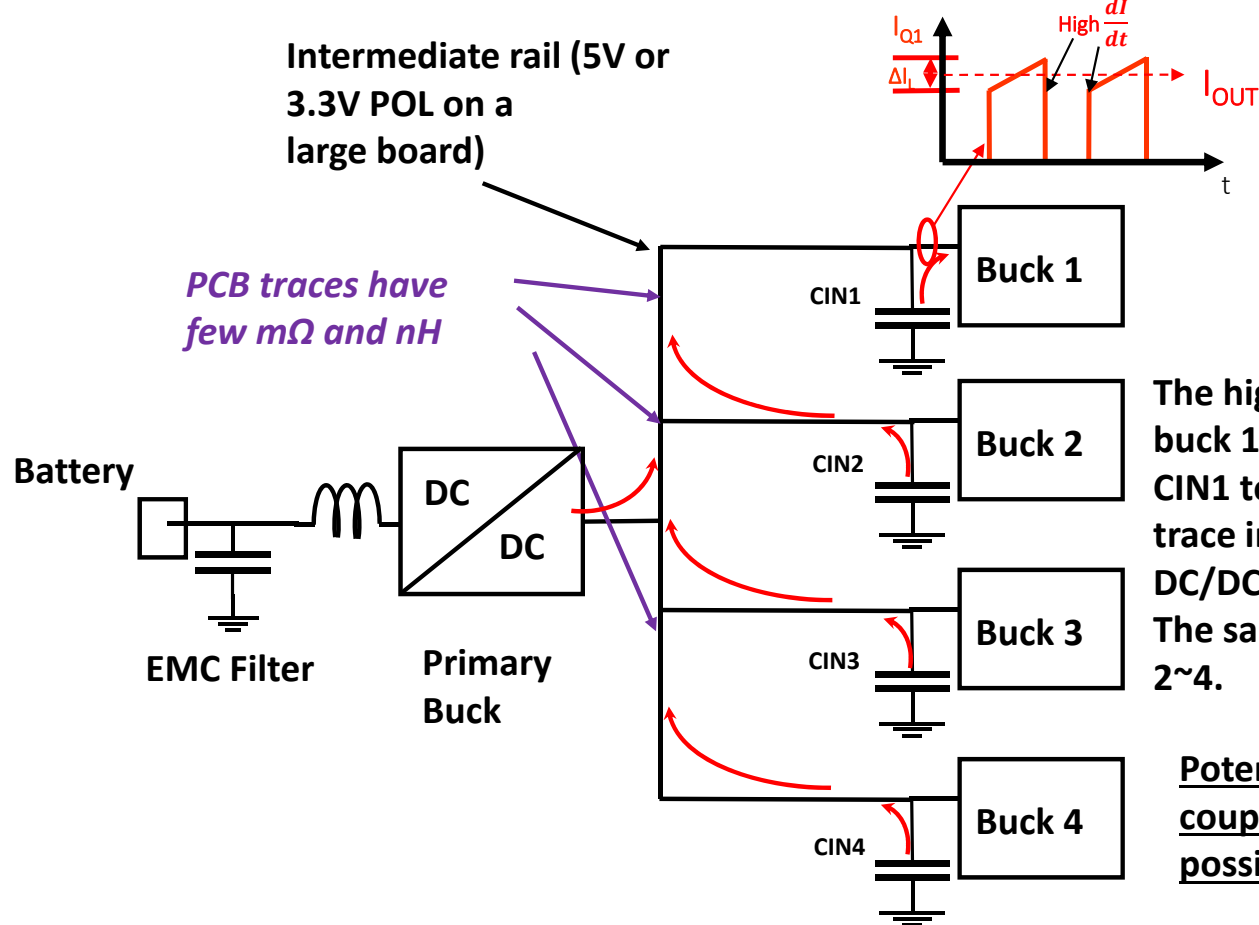 Several DC/DC Converters on One Large Board




The high dI/dt input current of buck 1 splits to CIN1 to CIN4, according to the trace impedance between DC/DC and CINx. The same applies for bucks 2~4.

Potential radiation and coupling in other circuits is possible!


Several DC/DC Bucks on One Large Power Rail

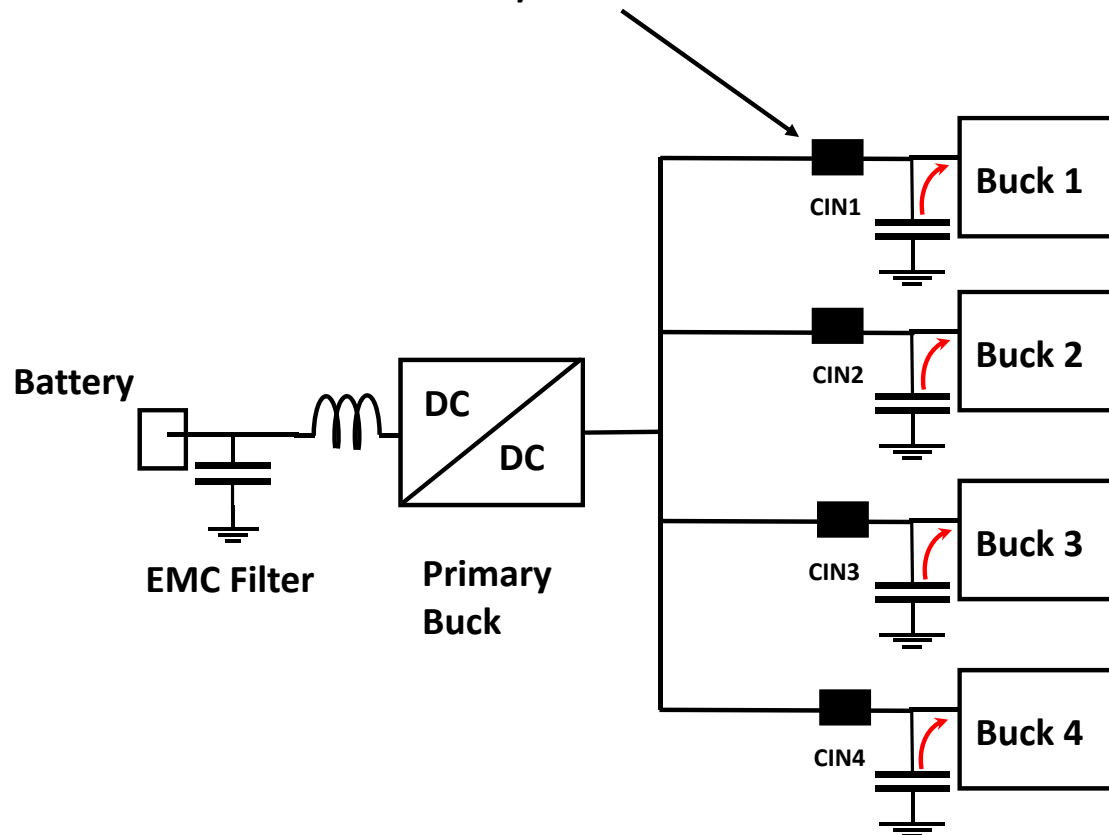Place a small coil (100nH to 1 μ H)
between individual DC/DC converters



This configuration forces the high di/dt of each buck to flow in its local CIN!


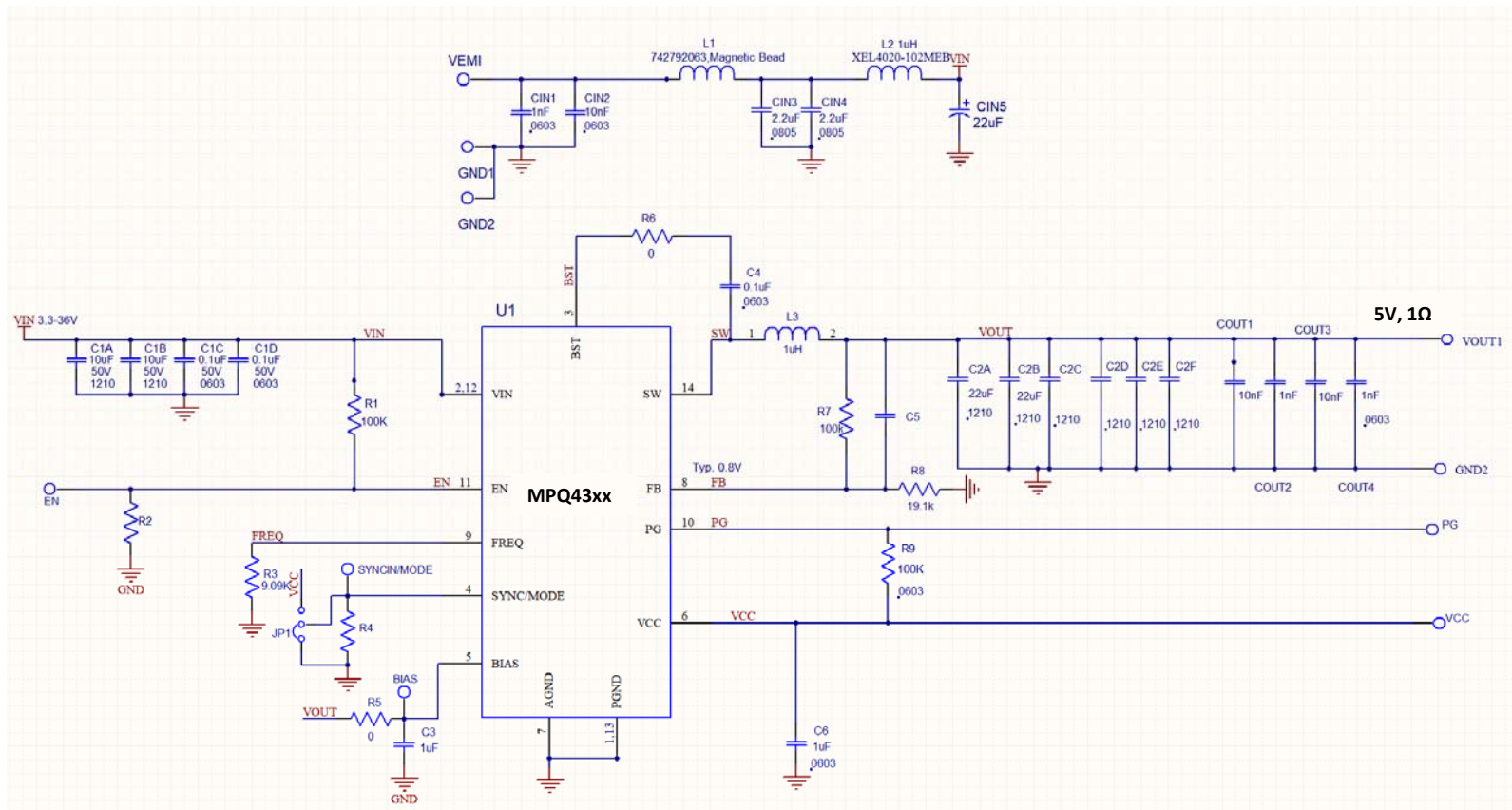
Optimization Example #1: 5A Buck $F_{sw} = 2\text{MHz}$ with SSFM



Optimization Example #1: 5A Buck $F_{SW} = 2\text{MHz}$ with SSFM



  
- Input Filter Placed on the Bottom Side
- Small size C_{in} placed close to V_{IN} and PGND pin for small hot loop
- Symmetric input cap placement
- Small SW copper and small size inductor



Optimization Example #1: 5A Buck $F_{sw} = 2\text{MHz}$ with SSFM

Reduce Input Filter

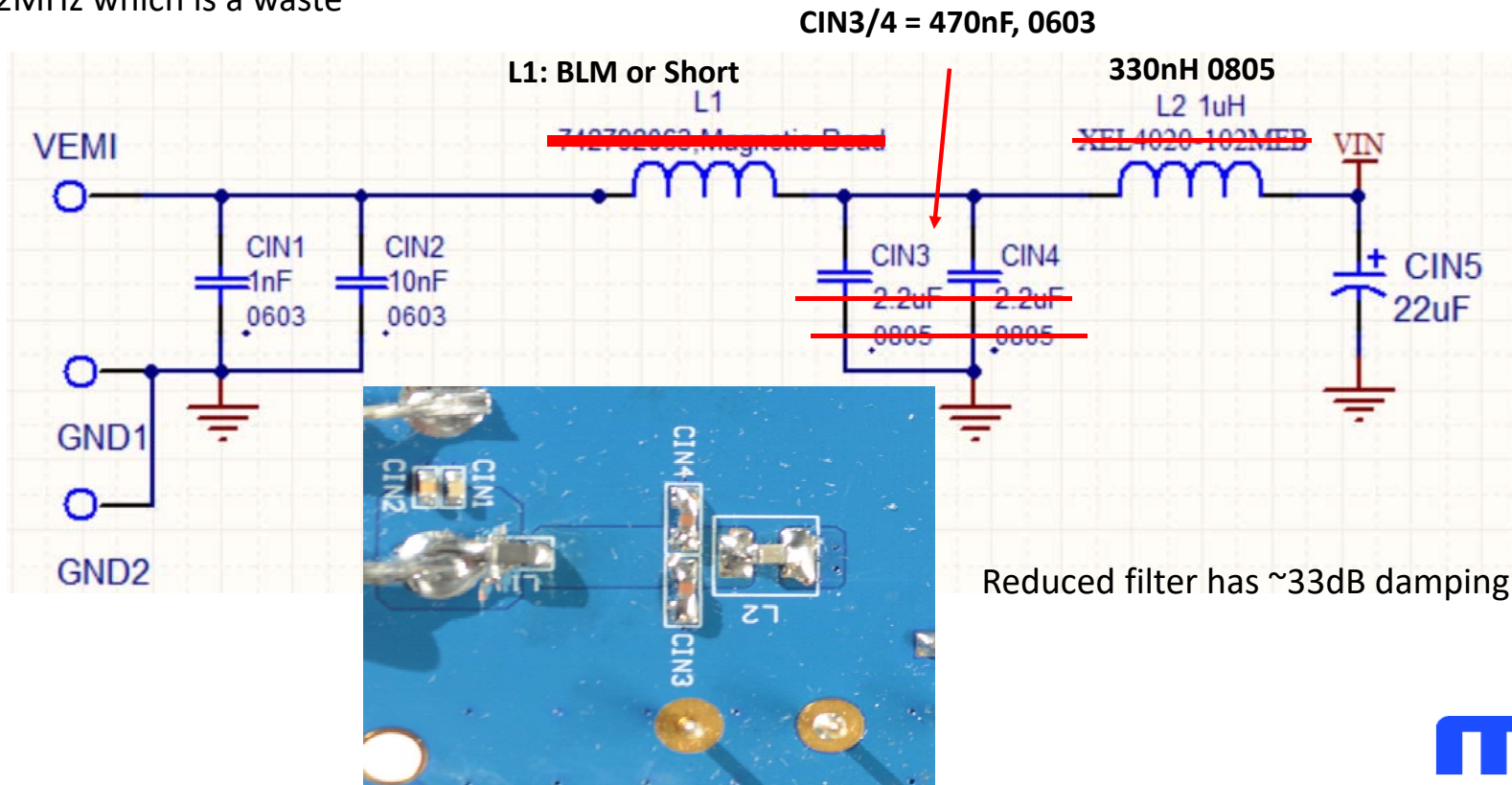
The initial input filter has about 50dB damping at 2MHz which is a waste



Optimization Example #1: 5A Buck $F_{sw} = 2\text{MHz}$ with SSFM

CE Test w/o & w/ Reduced Input Filter

Supply

 


Not good enough in the FM band




Optimization Example #1: 5A Buck $F_{SW} = 2\text{MHz}$ with SSFM

Comparison between inductor with different directions

B3

 

 
Comment: Start of winding at SW is 2dB to 3dB better



Inductance

Start of winding (SoW).
Connect high dv/dt here
for lowest EMI

Low height

 

High height


SoW

MPS


Optimization Example #1: 5A Buck $F_{SW} = 2\text{MHz}$ with SSFM

Replace XAL5030-1 μH by XAL4020-1 μH


B3

 

XAL5030

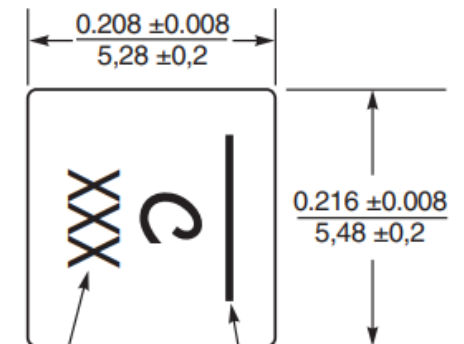



XAL4020

 

Optimization Example #1: 5A Buck $F_{SW} = 2\text{MHz}$ with SSFM


Add 4.7Ω Into BST Circuit

B3

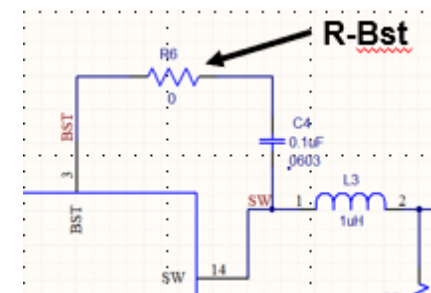 

Optimization Example #2: More about Inductor & EMC

4.5mm Height

 


Contact metal acts as an antenna for the E-field from the SW node dV/dt



End-of-winding side contact metal with two clips into airgap for mechanical robustness

Even if the SoW is at SW, the plate will cause trouble

SHAPES AND DIMENSIONS

 


Weight: 0.72g


Dimensions in mm

 Example Drawings from Murata, TDK and ABC

Optimization Example #2: More about Inductor & EMC




 
The SW node contact plate has been removed, and the winding is soldered directly to the PCB.
6dB lower emissions at 1MHz
in monopole antenna testing



A 4.5mm height contact plate acts as an E-field antenna for the SW node's high dV/dt . The optimum coil should have an SW contact at the bottom.


Optimization Example #2: More about Inductor & EMC

RE Monopole Test 0.1MHz to 30MHz

  

Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

 Initial / default board figure, already quite good on layout




Note for buckboost, both input loop and output loop are hot loop with high di/dt



Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

First EMI shot to duplicate customer test result



Customer Setup

 

Duplicate similar result with similar setup

MPS Setup

 
 
similar bad setup
long output cable
large heatsink LED





Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 1: smaller size load

Long wire and large heatsink LED load

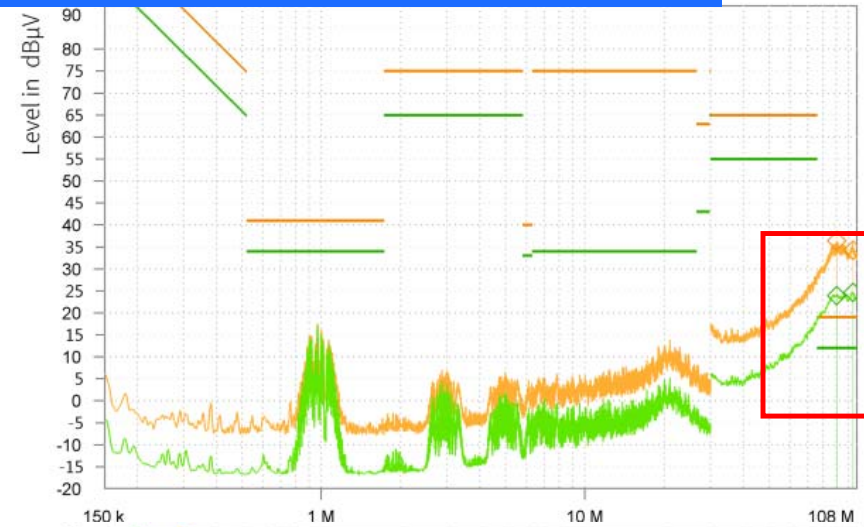 

  
Long wire but **small** heatsink LED load






Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 2: Shorter output cable

Long wire and small heatsink LED load

 




Short wire but small heatsink LED load

   


Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 3: Remove some Cout for small hot loop

With C2C & C2D as shown in SCH

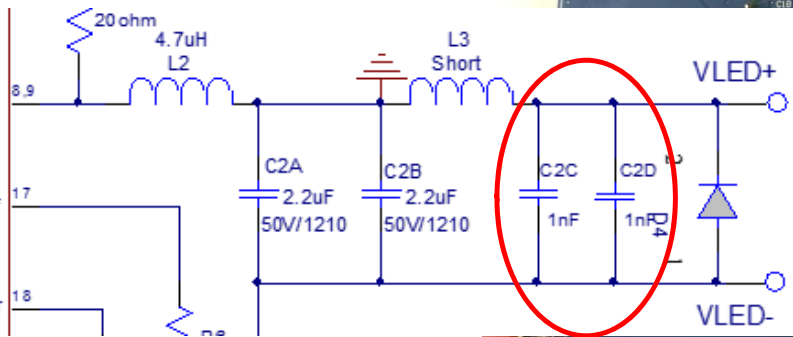  


Remove C2C & C2D

 




Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 4: Add output filter

No output filter
in default SCH

 

 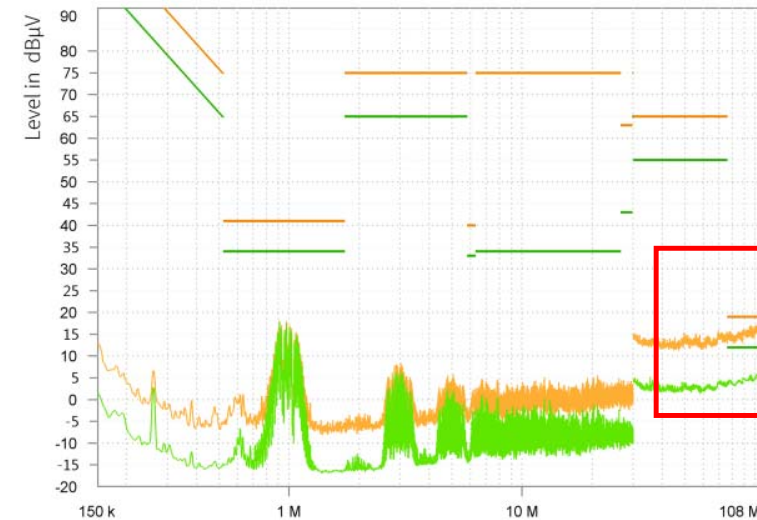
 
Add 330nH L and 100nF
Cap on LED- trace as
output filter



Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 5: Adjust L & Cout placement for RE 150k-30M

Placement as default layout

  


Place L2 closer to IC,
Place C2A & C2B closer
to L2 for some shielding






Case #3: 1.2A LED Driver, Buckboost, $F_{sw} = 1\text{MHz}$ with SSFM

Optimization 6: Add CM output filter for RE 200M-1G

Only 330nH+100nF
LED- filter

 

   330nH on LED- and
330nH on LED+ and
100nF between LED+
and LED-



Conclusion

➤ **Learn background**

Such as setup, standard, initial test result

➤ **Review schematic, layout, board**

Focus on filter, high di/dt loop and dV/dt area

➤ **Issue identification**

An appropriate filter, good inductor, Cu-foil shielding, snap-on ferrite, field probe can help

➤ **Performance optimization**

According to theory and experience, following steps, try more times