

Driving Power MOSFETs

Jian Zhao




Oct. 2021




Driving Power MOSFETs

- MOSFET Basics
- Driving Loads: H-Bridges and Half-H-Bridges
- Driving the Gate
- Effects of MOSFET Switching Speed
- Conclusion


Power MOSFETs

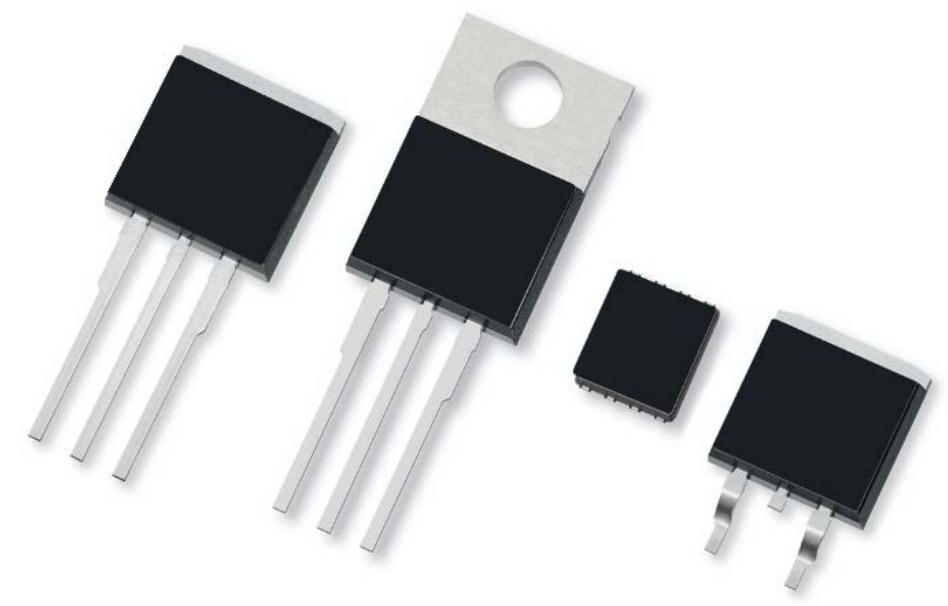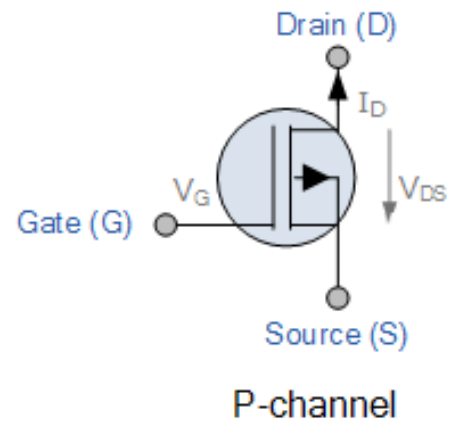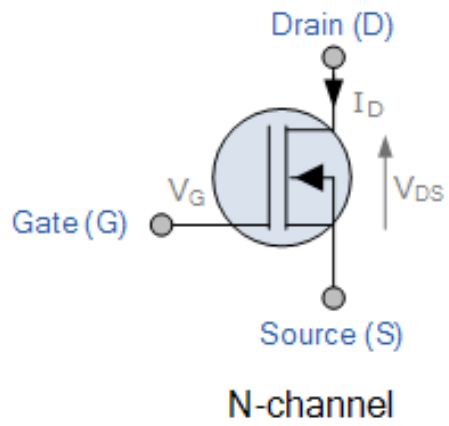


Power Drive Circuits

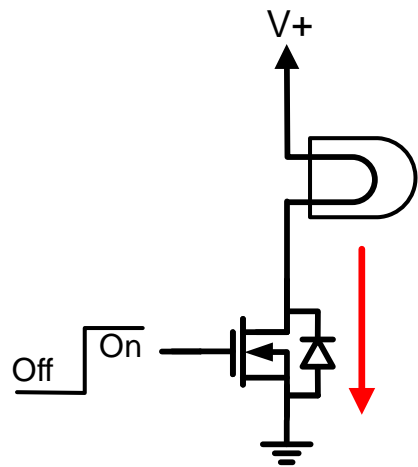

Low side

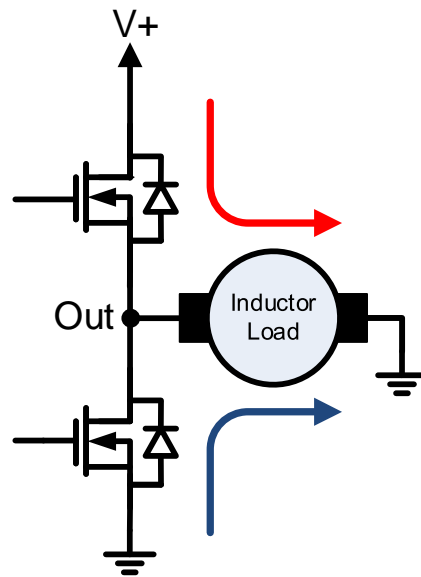



Half Bridge

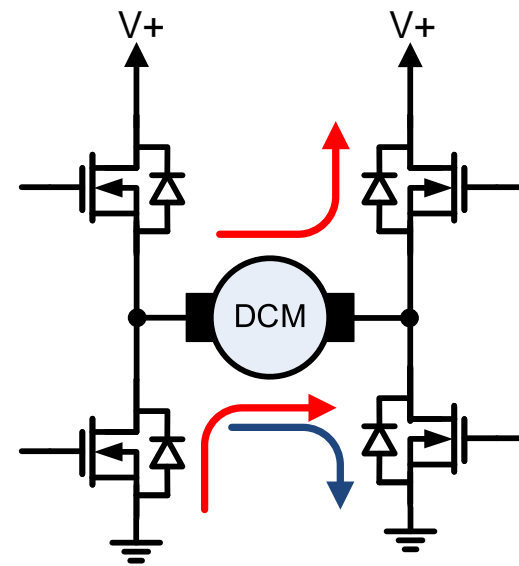

H-Bridge



Red: PWM On
Blue: PWM Off

Half Bridges: N and P

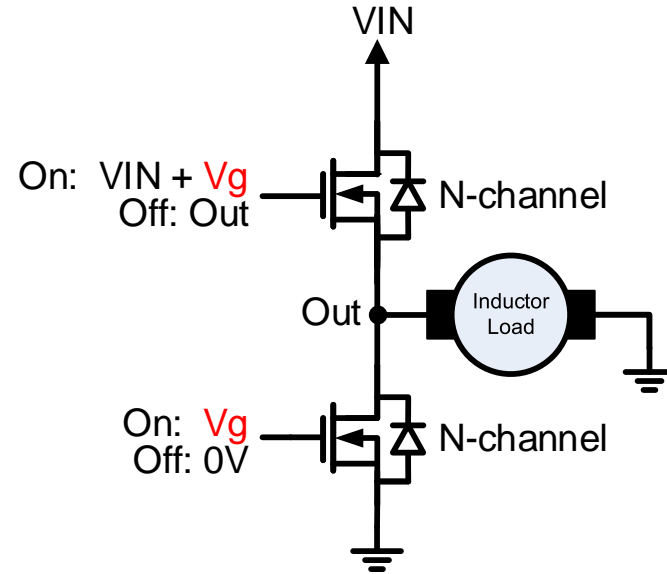
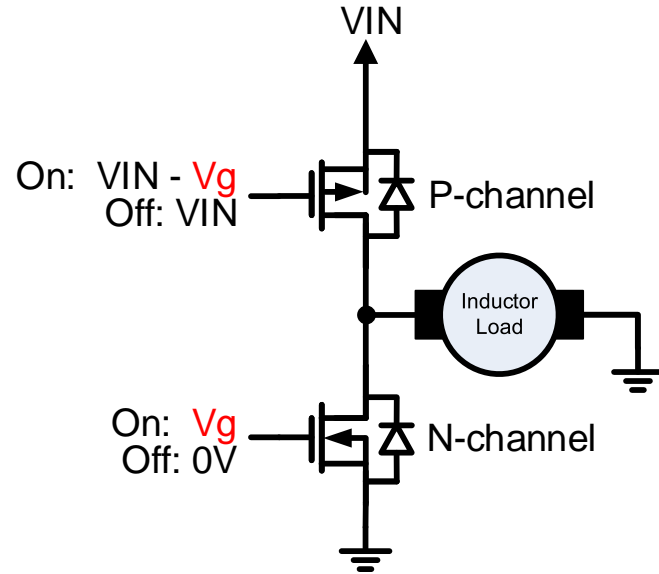


V_{IN} – Load Supply Voltage
 V_g – Gate Drive Voltage

MOSFET Structure

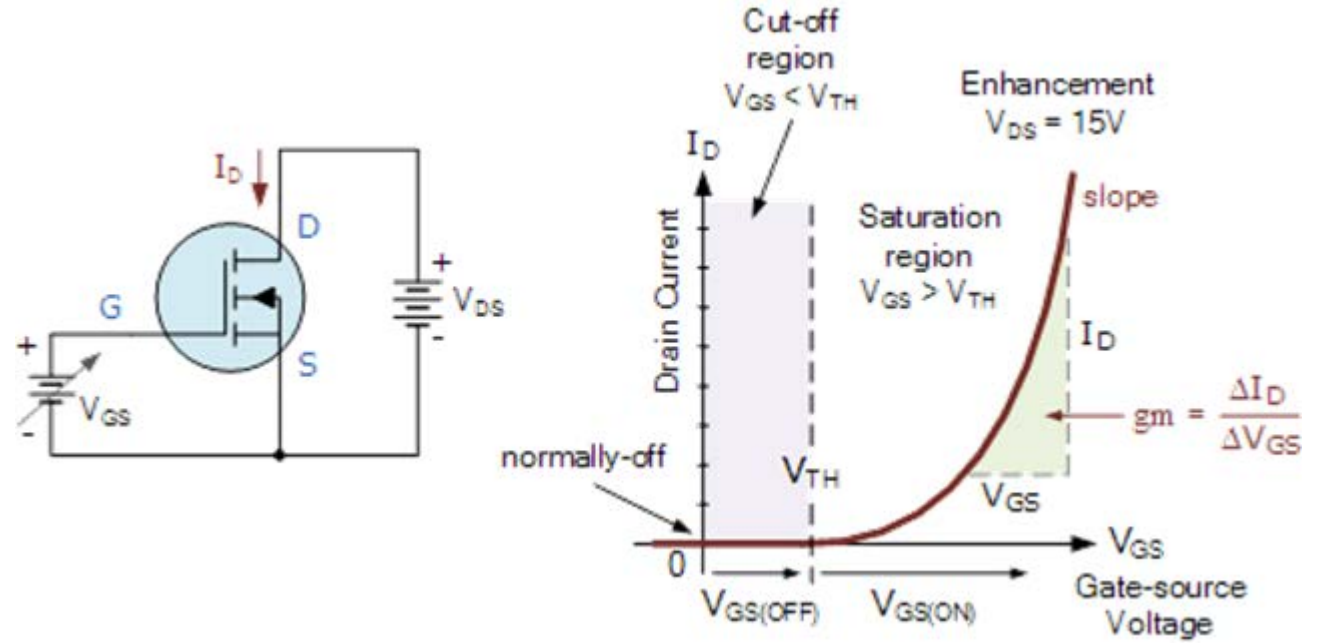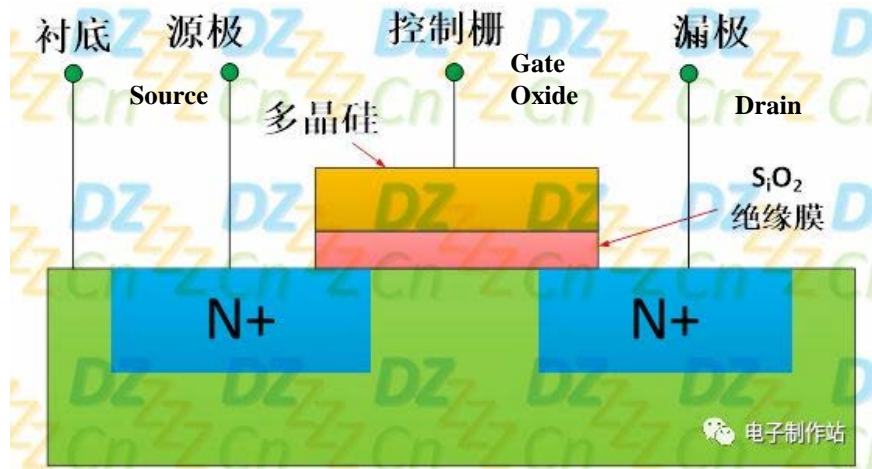

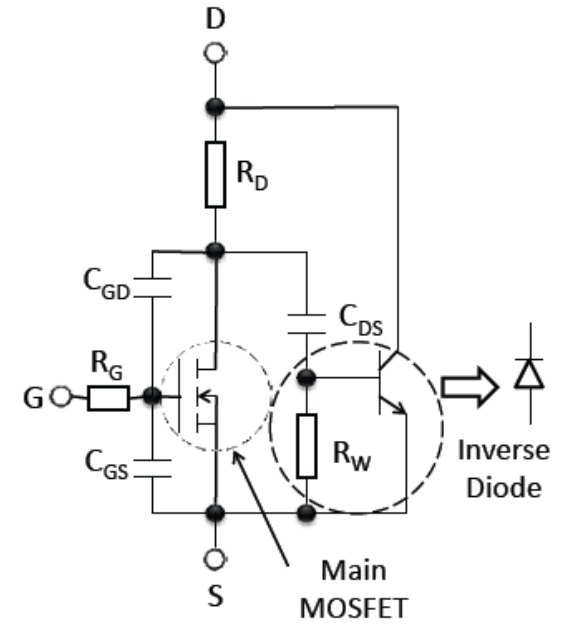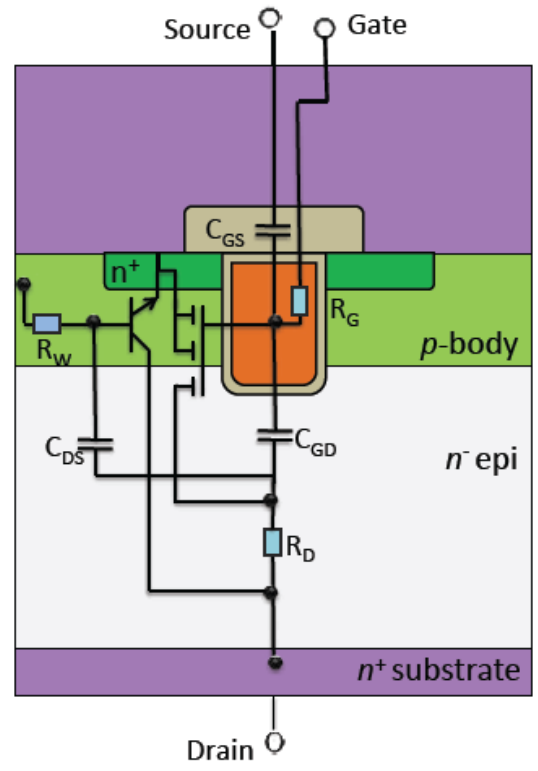Simplified Model of an N-channel Power MOSFET



Datasheet Specs and Total Gate Charge

$$1 \text{ Coulomb} = 6.28 \times 10^{18} \text{ Electrons}$$

that is:

6,280,000,000,000,000,000
ELECTRONS

$$Q = CV \text{ (Charge = Capacitance x Voltage)}$$

$$I = Q/t \text{ (Current = Charge / Time)}$$


IPP015N04N

VDS max	40.0 V
RDS (on) (@10V)	max 1.5 mΩ
ID (@25°C) max	120.0 A
Ptot max	250.0 W
Ciss	15000.0 pF
Coss	4000.0 pF
QG (typ @10V)	188.0 nC
VGS(th) min / max	2.0 V / 4.0 V

C_{ISS} – Input capacitance
(gate-to-source + gate-to-drain)

Q_G – Total gate charge



Driving the Gate

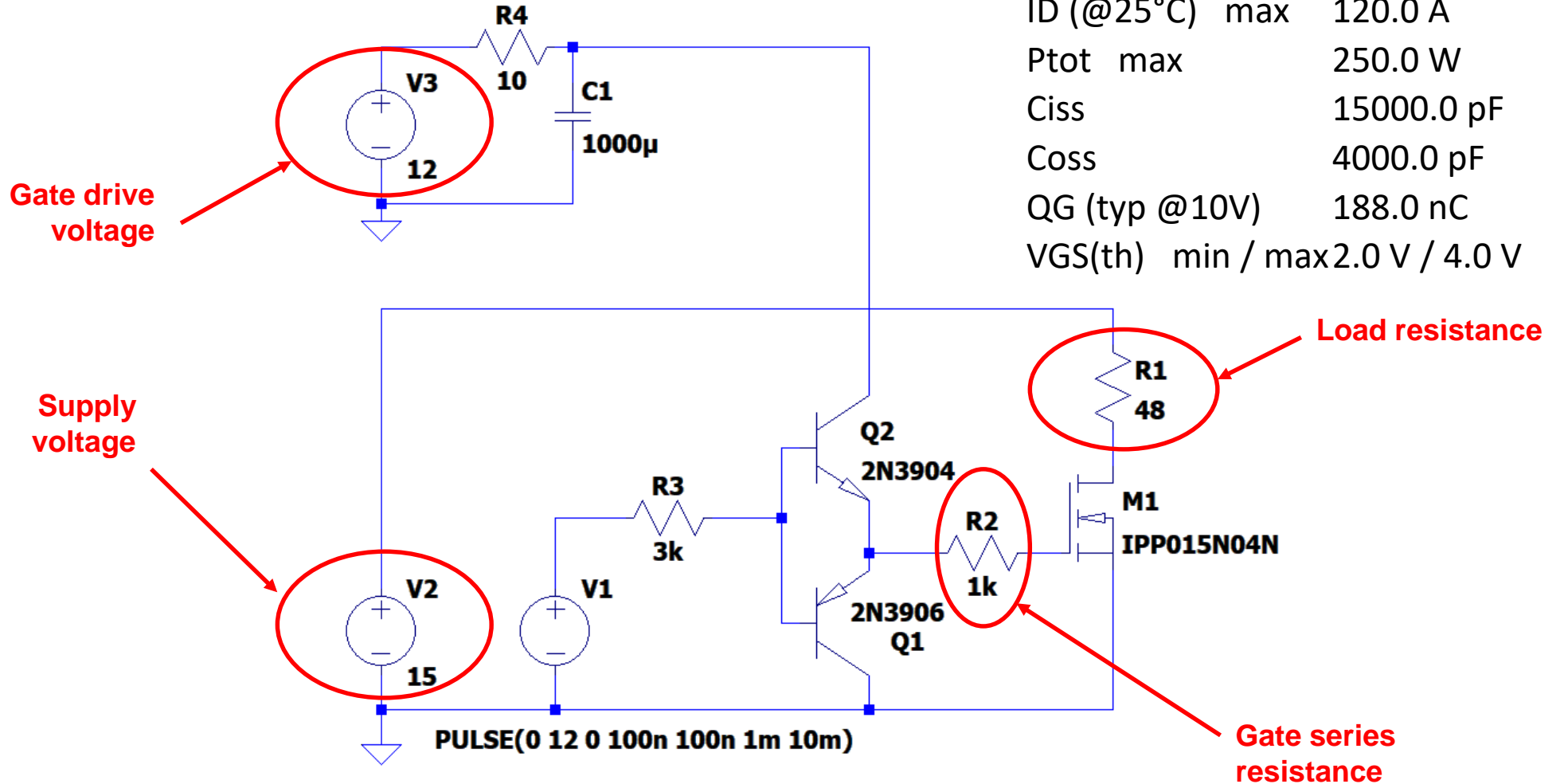

IPP015N04N



VDS max	40.0 V
RDS (on) (@10V)	max 1.5 m Ω
ID (@25°C) max	120.0 A
Ptot max	250.0 W
Ciss	15000.0 pF
Coss	4000.0 pF
QG (typ @10V)	188.0 nC
VGS(th) min / max	2.0 V / 4.0 V

Low Resistance Gate Drive

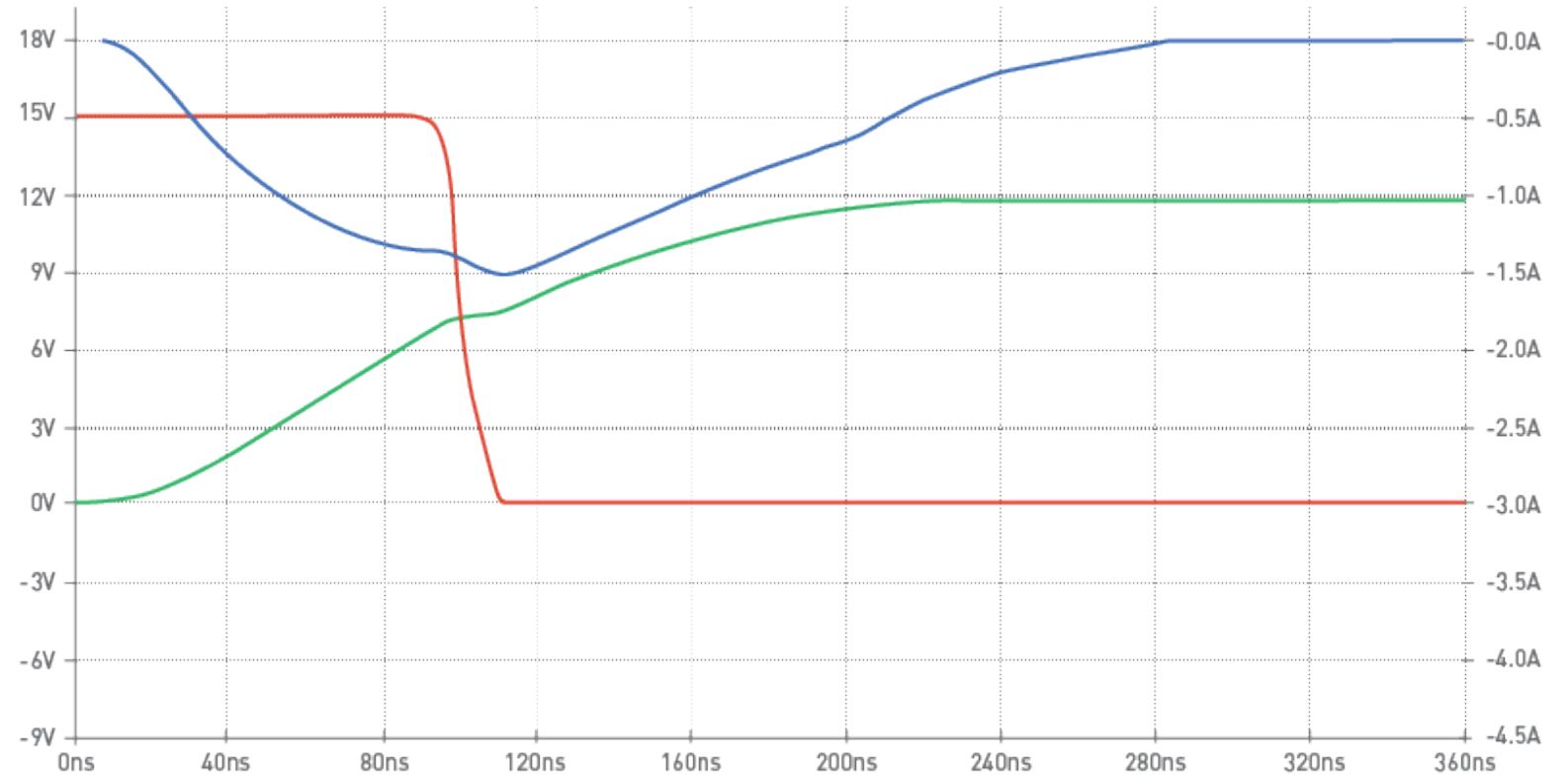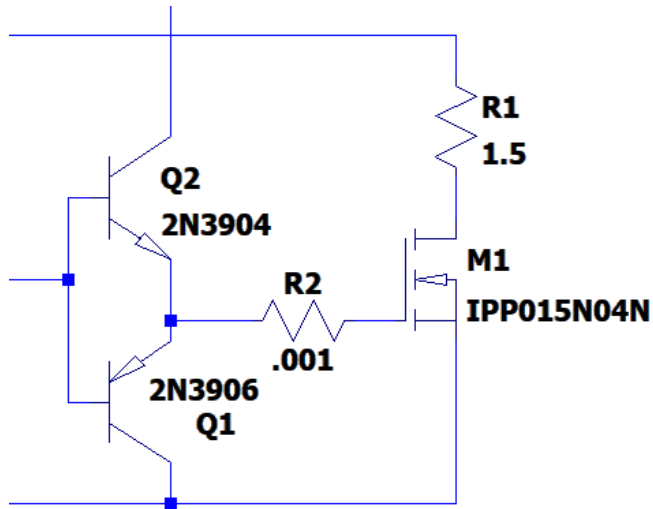



Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current

Low Resistance Gate Drive

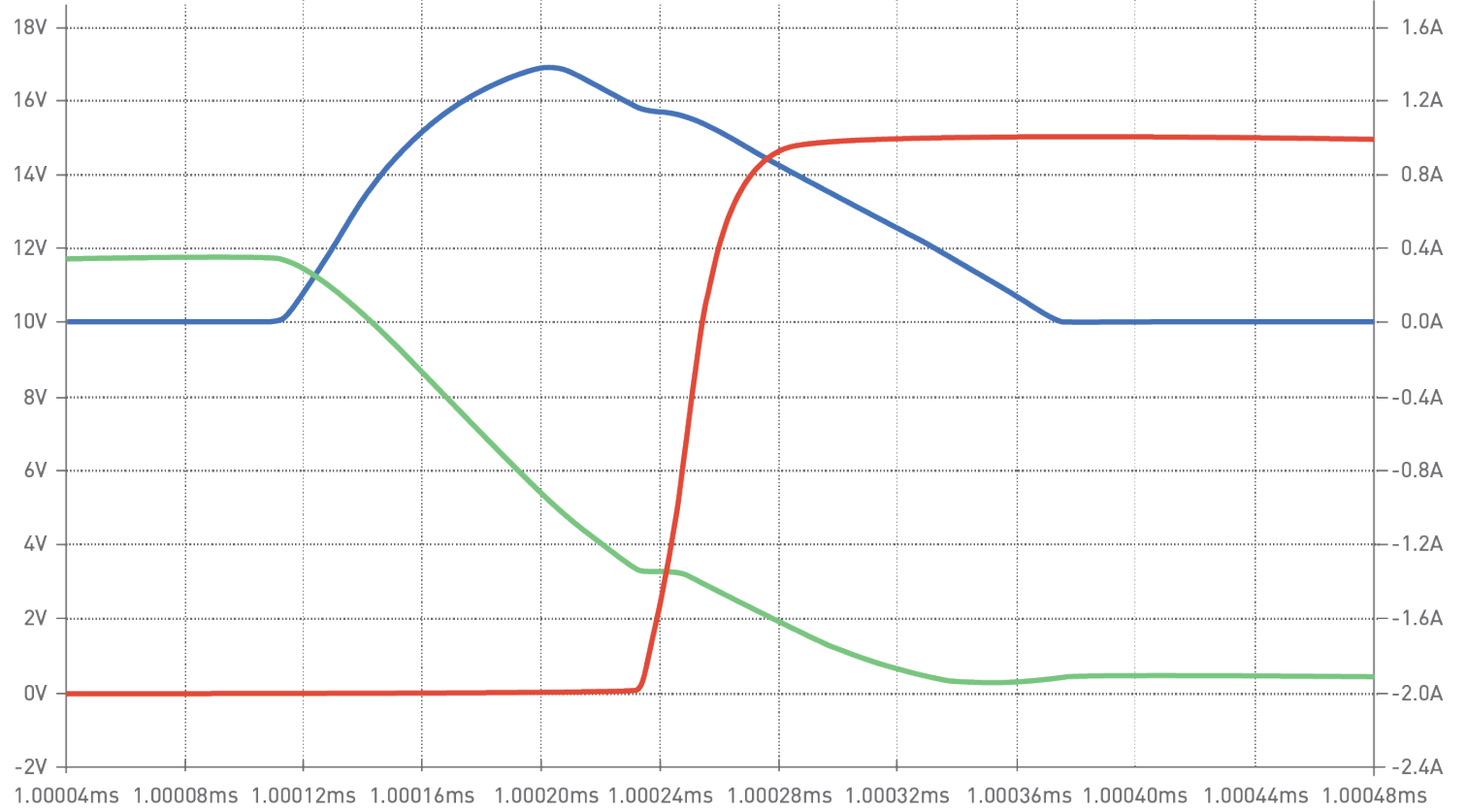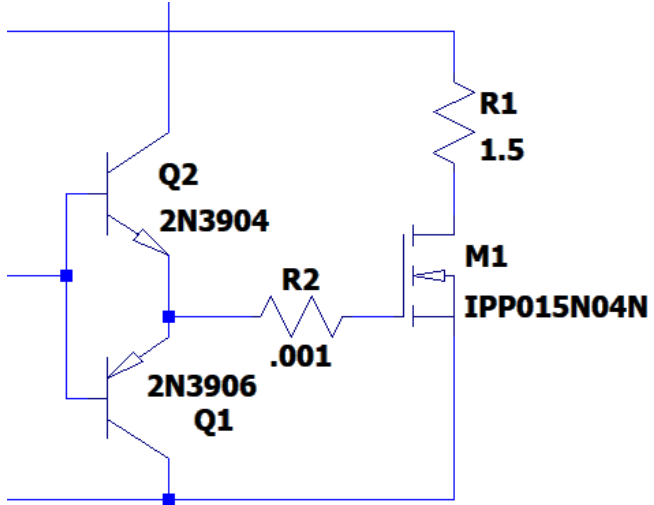



Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current

Adding Series Resistance

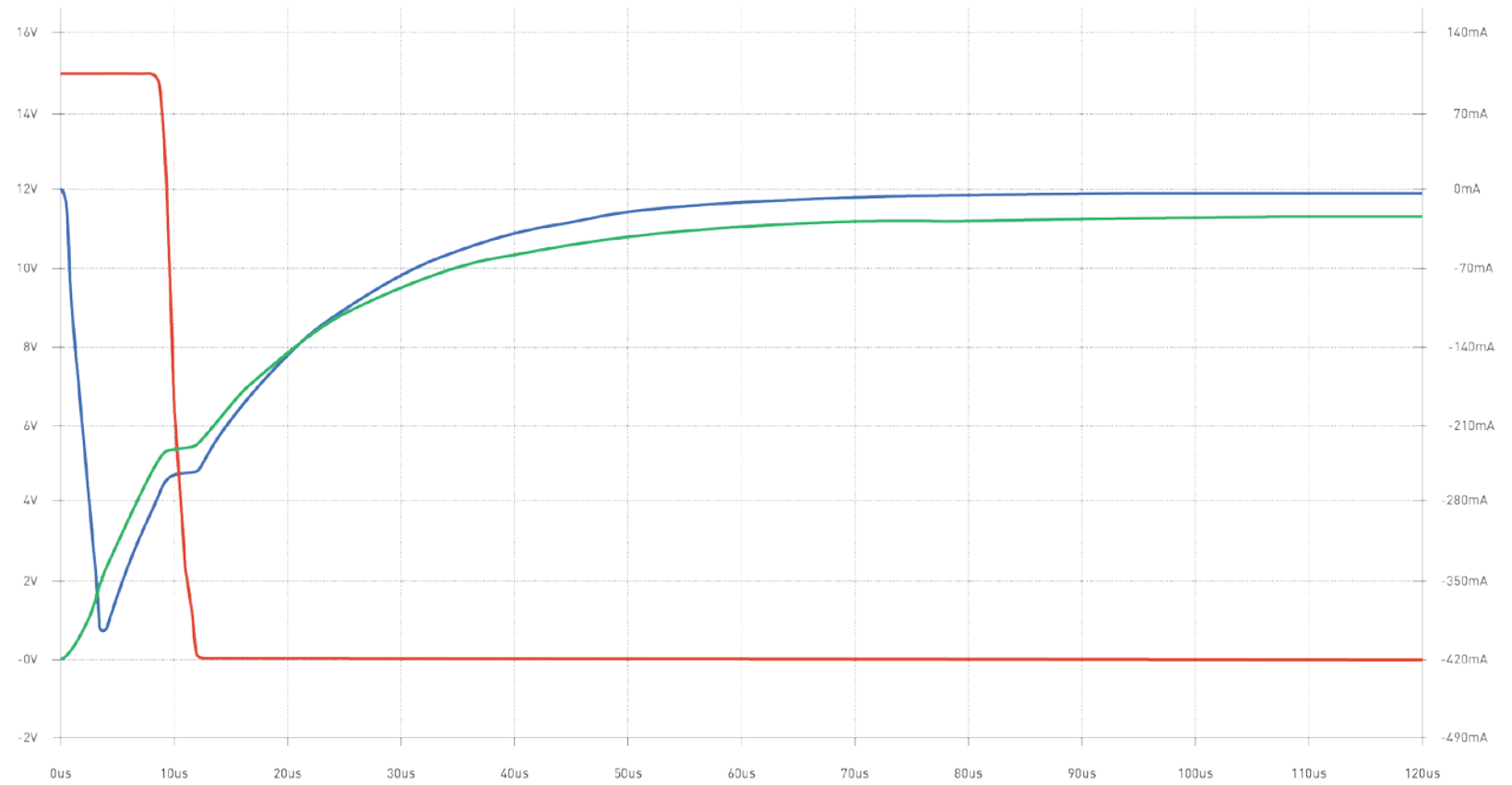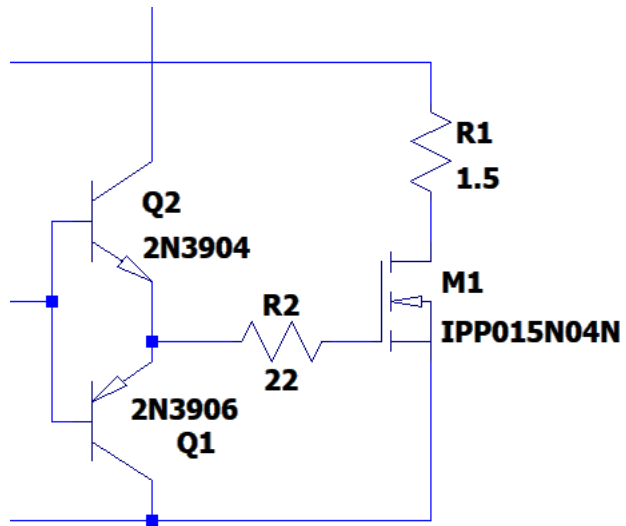



Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current

Adding Series Resistance

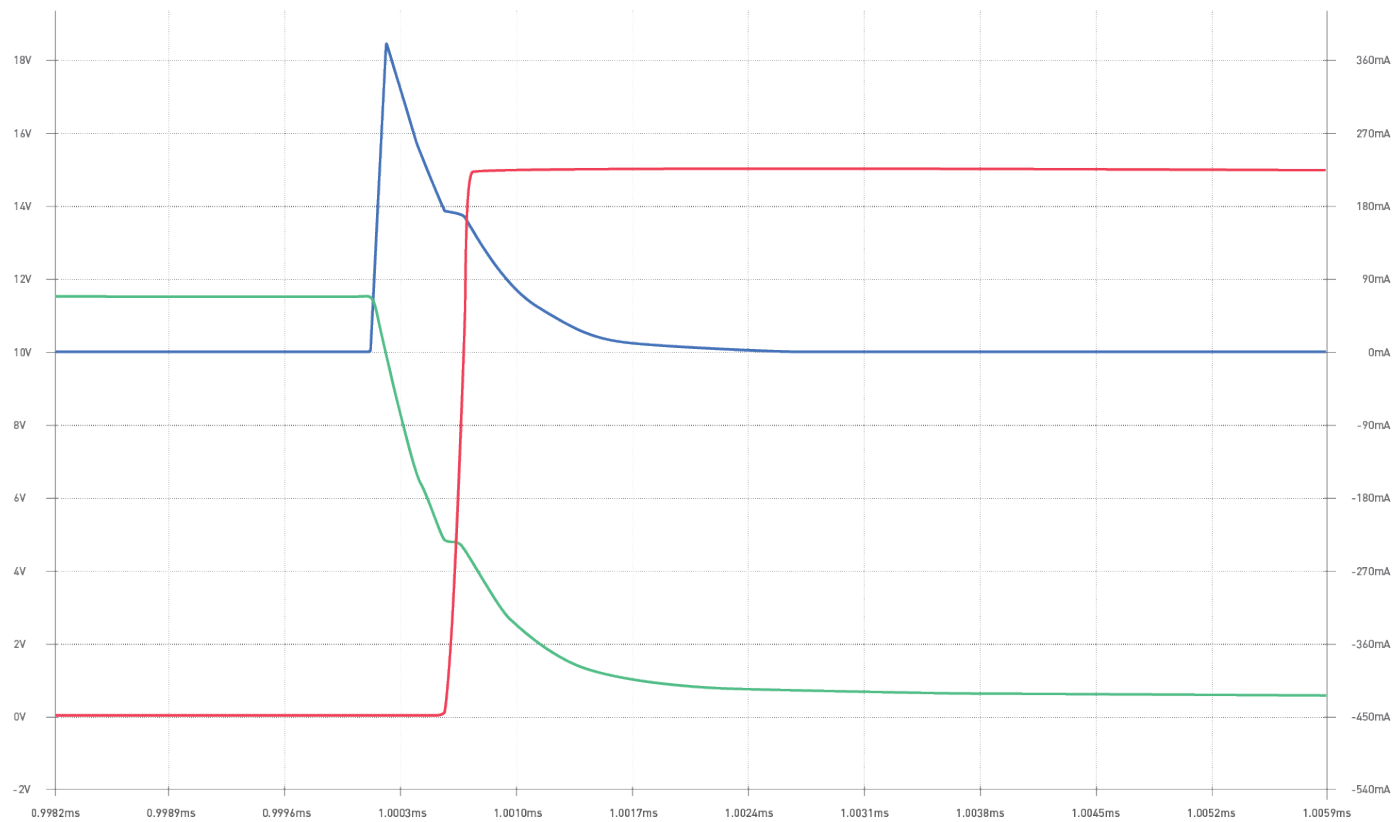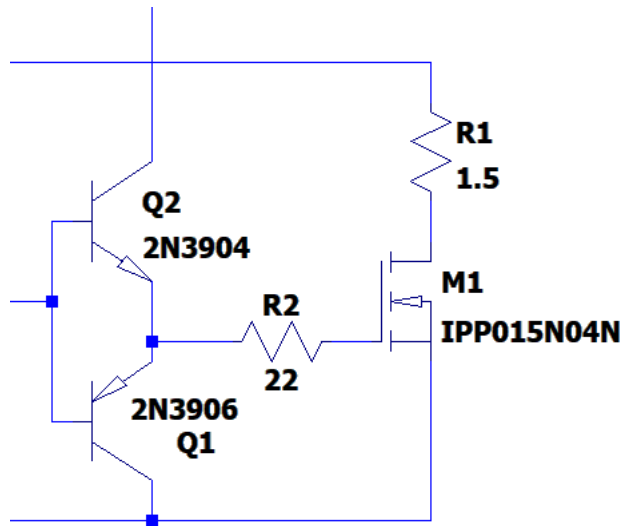



Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current

Too Much Series Resistance?

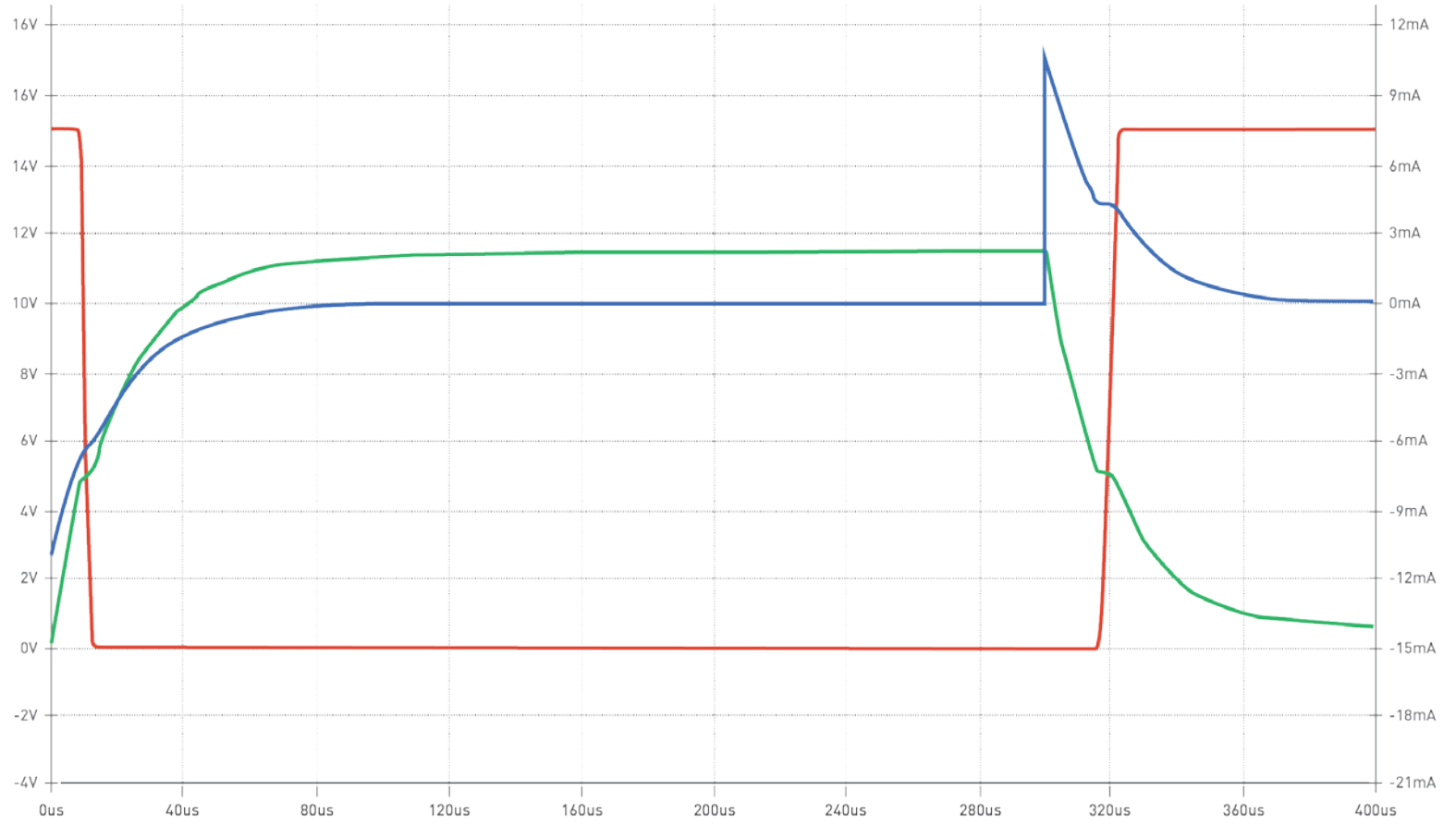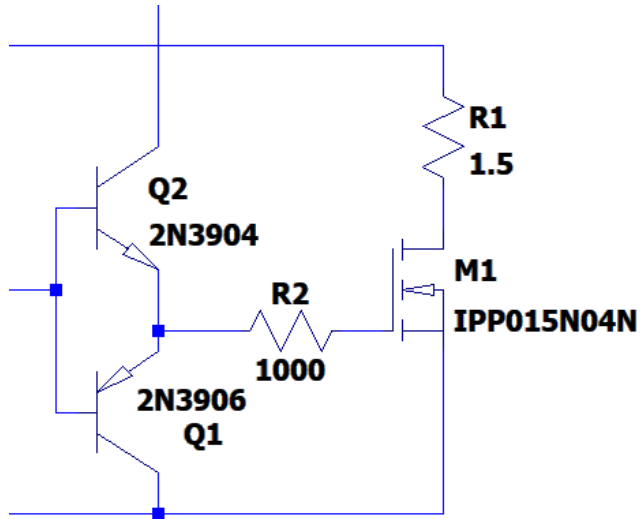



Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current

Too Much Series Resistance?

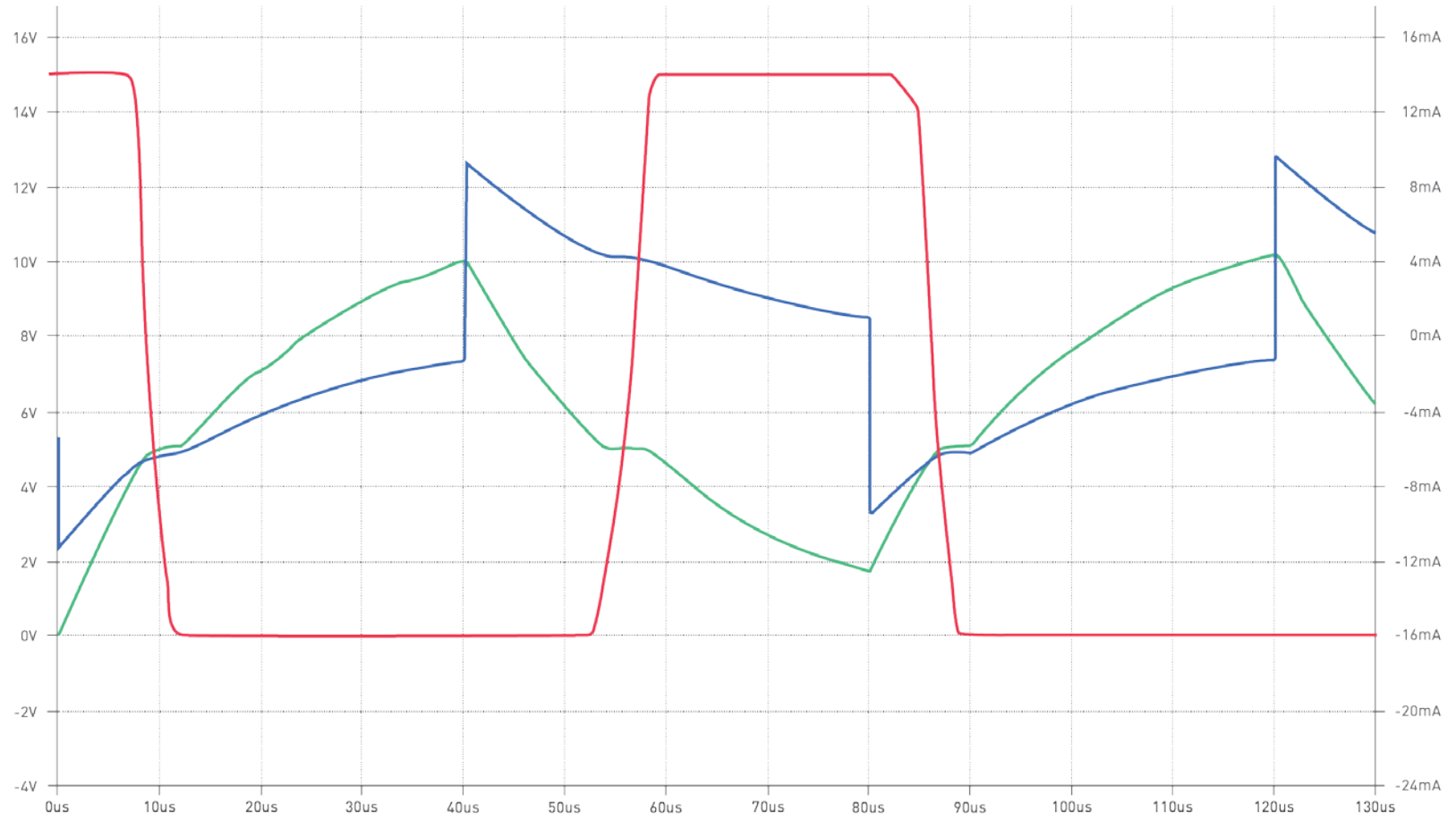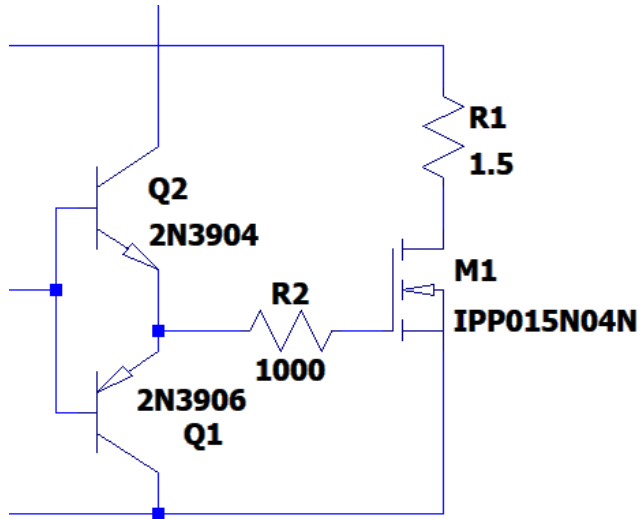

Red: Drain Voltage
Green: Gate Voltage
Blue: Gate Current



False Turn-On

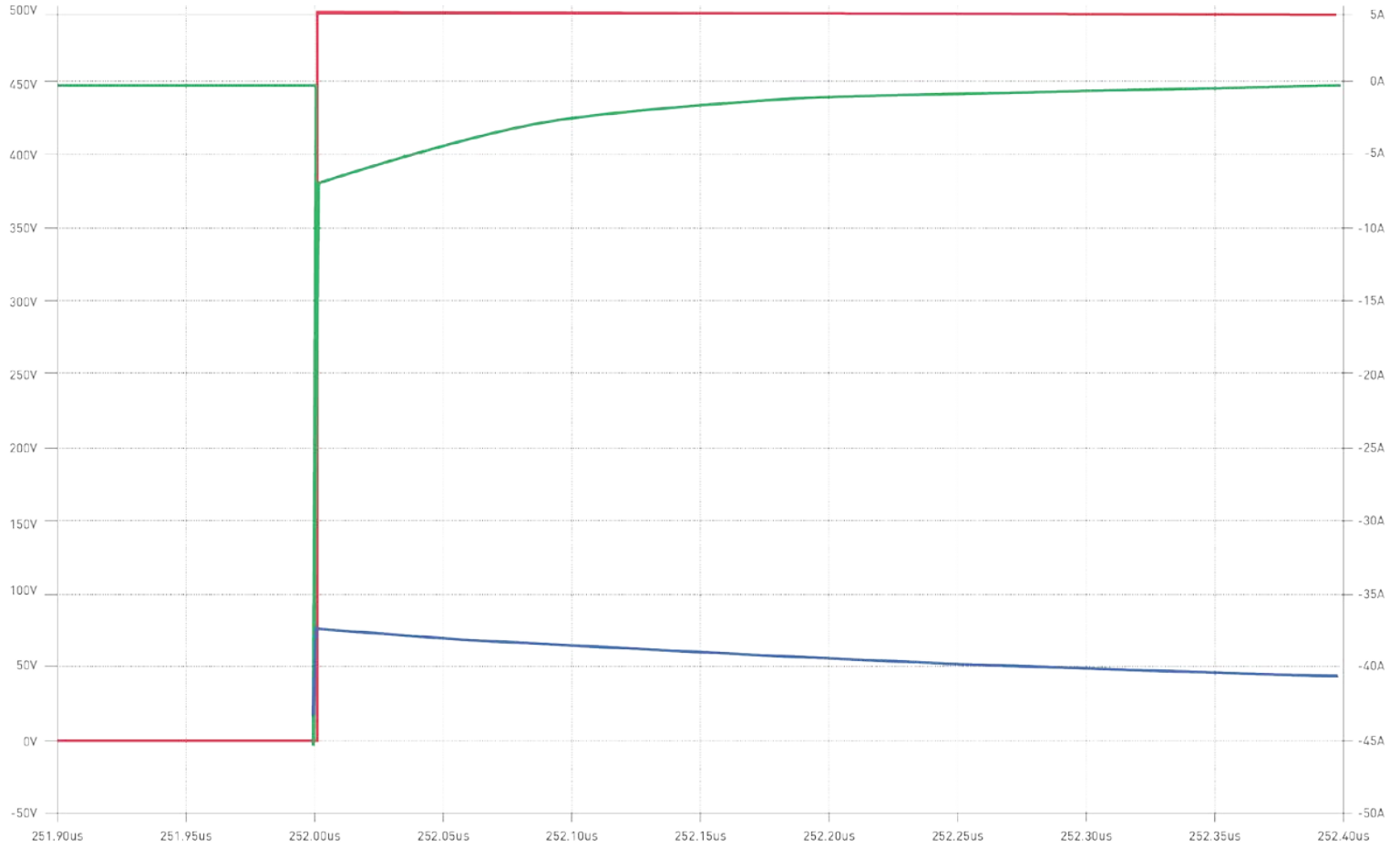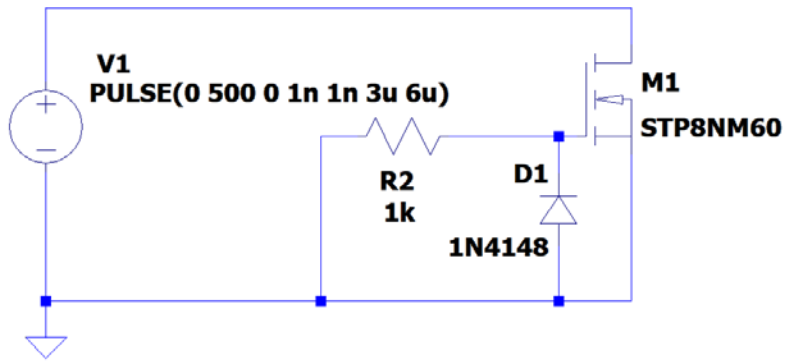

Red: Drain Voltage
Blue: Gate Voltage
Green: Drain Current





Asymmetric Gate Drive

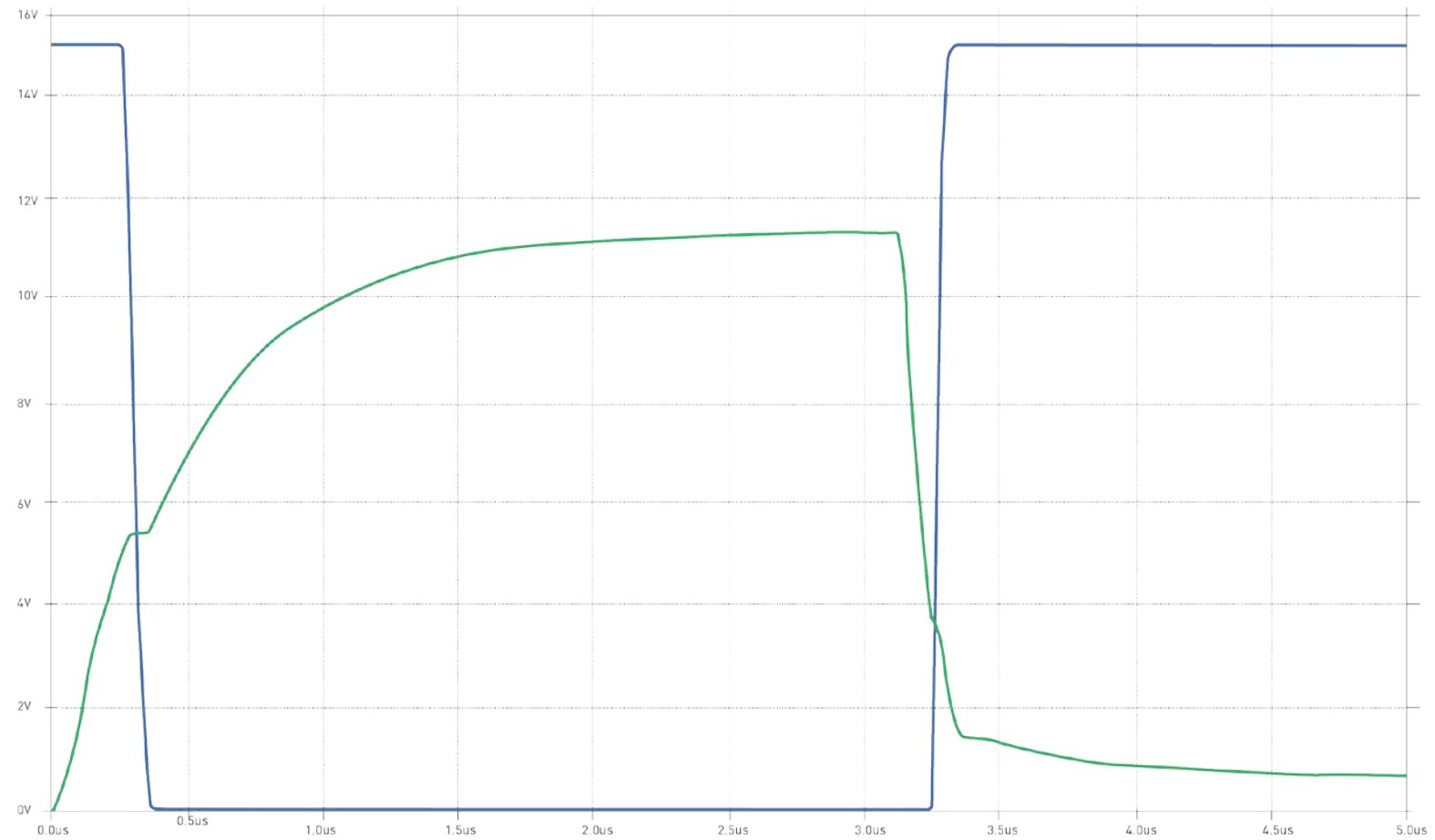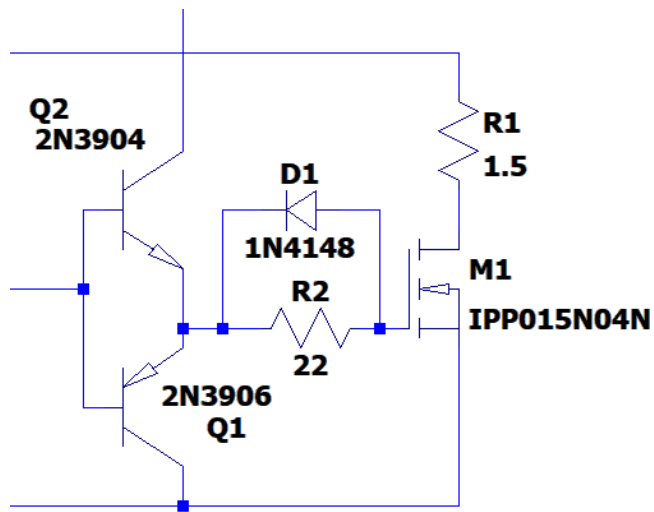


Blue: Drain Voltage
Green: Gate Voltage

MOSFET Switching Speed

Why Slow the Gate Down?

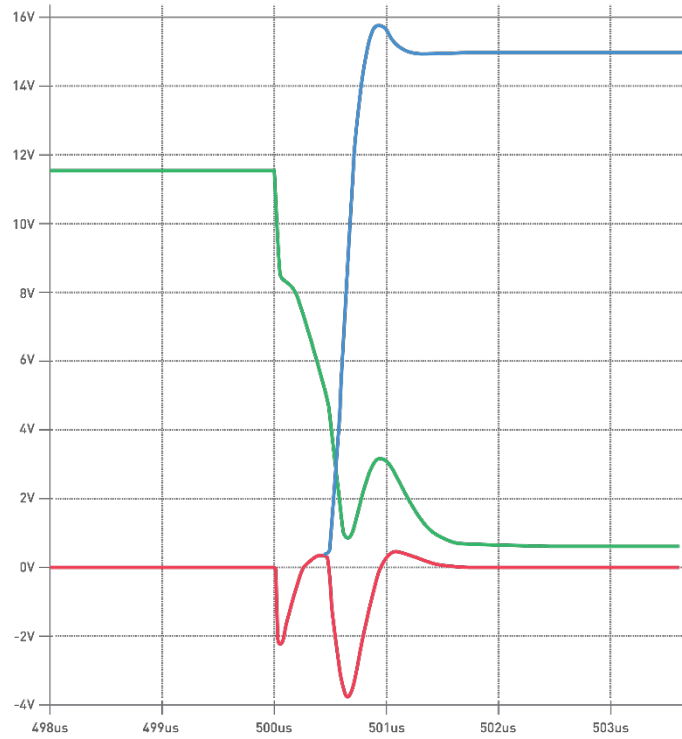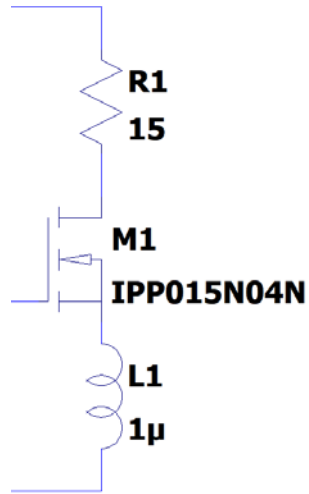





Fast

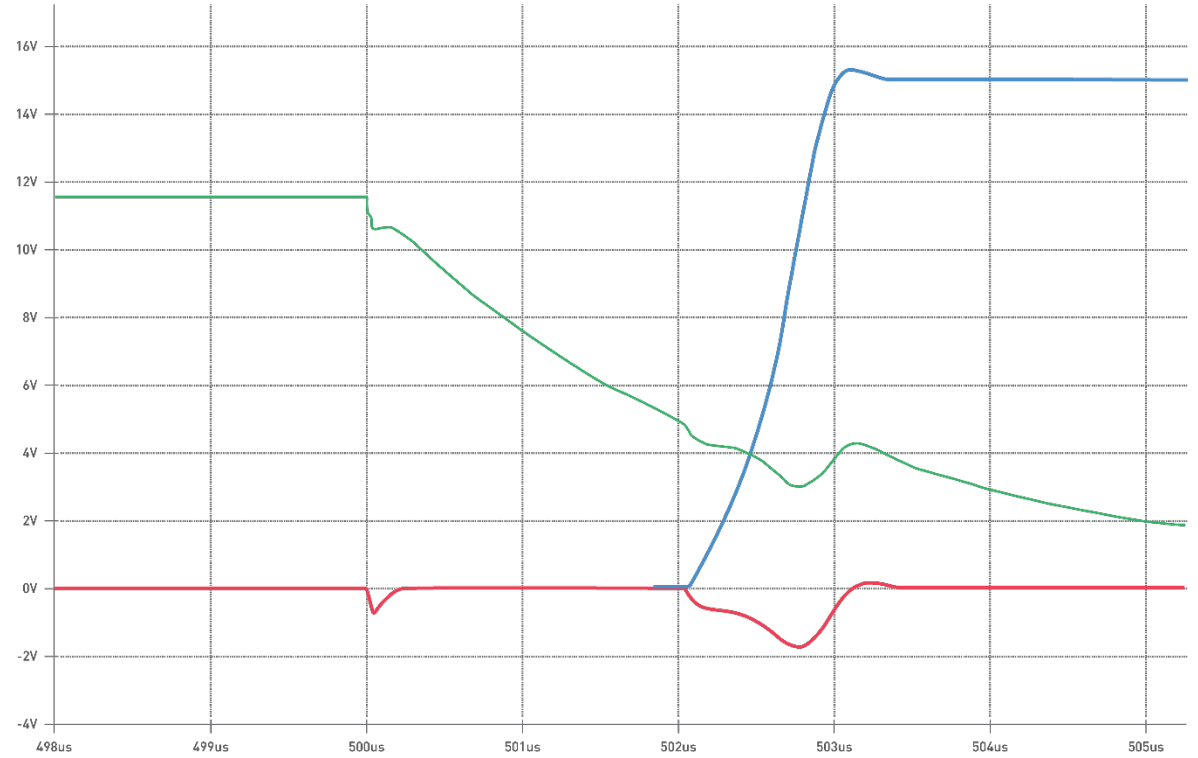




Slow

Green: Gate Voltage
Blue: Drain Voltage
Red: Source Voltage

EMI Concerns

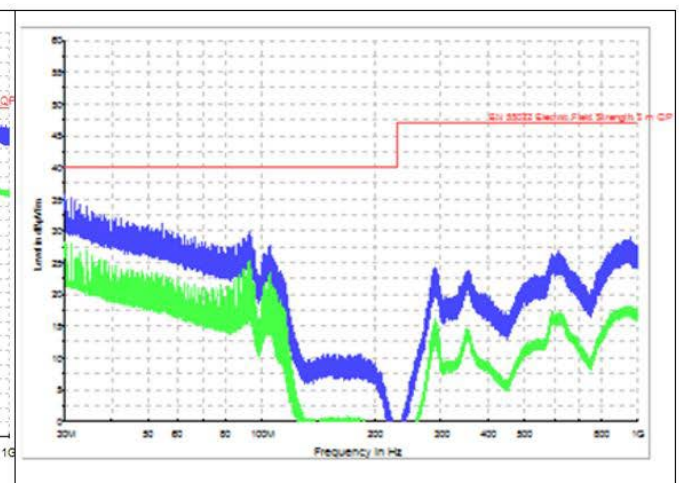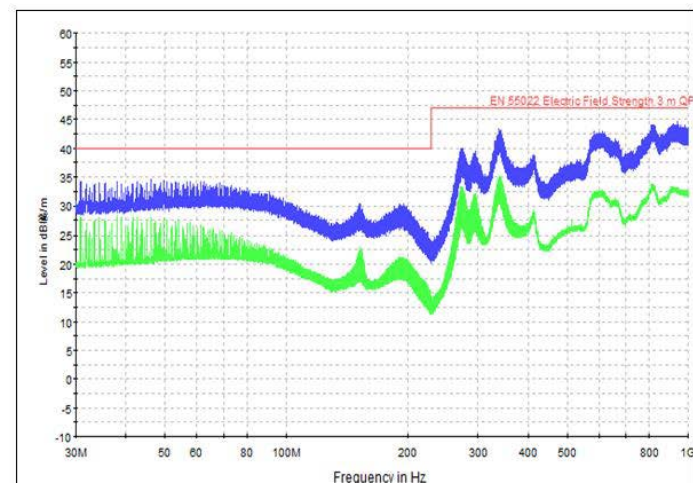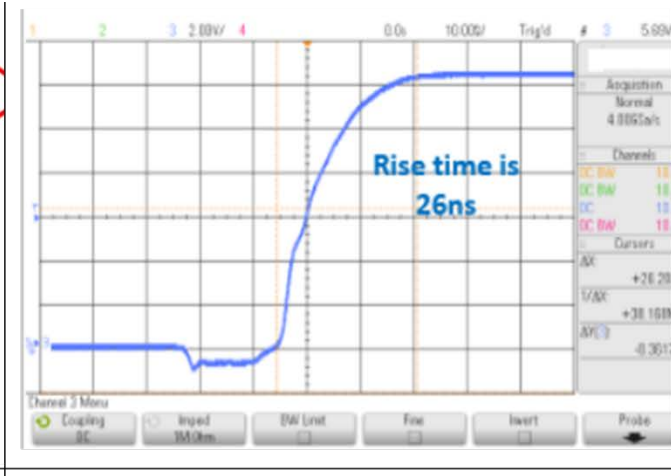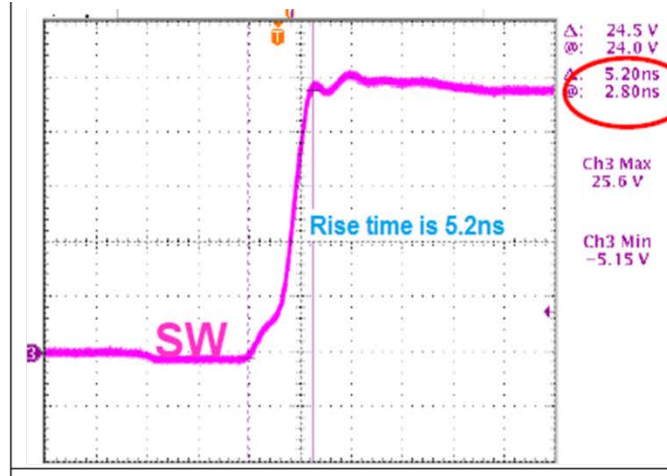

Body Diode Reverse Recovery

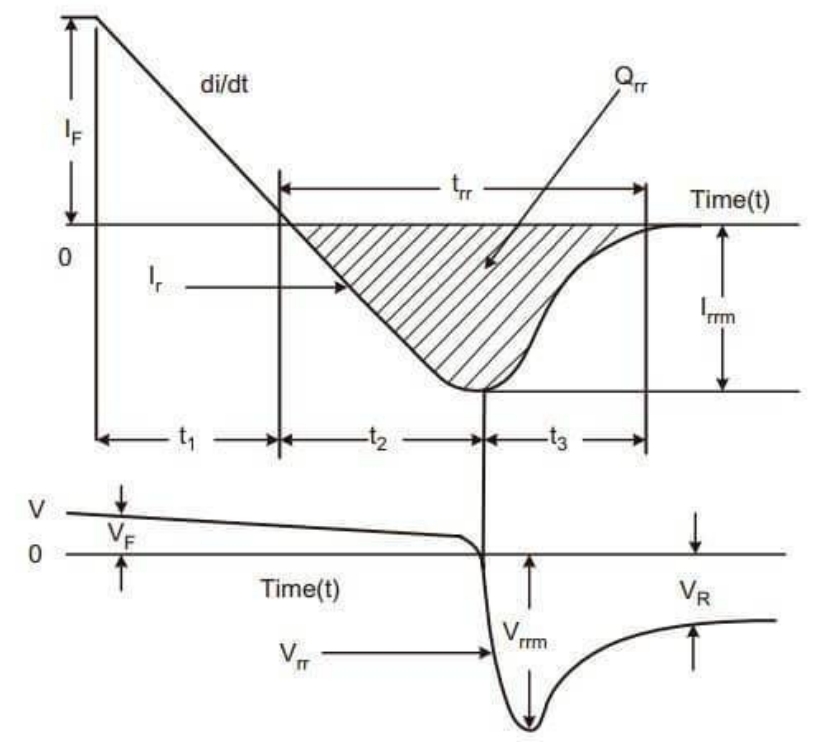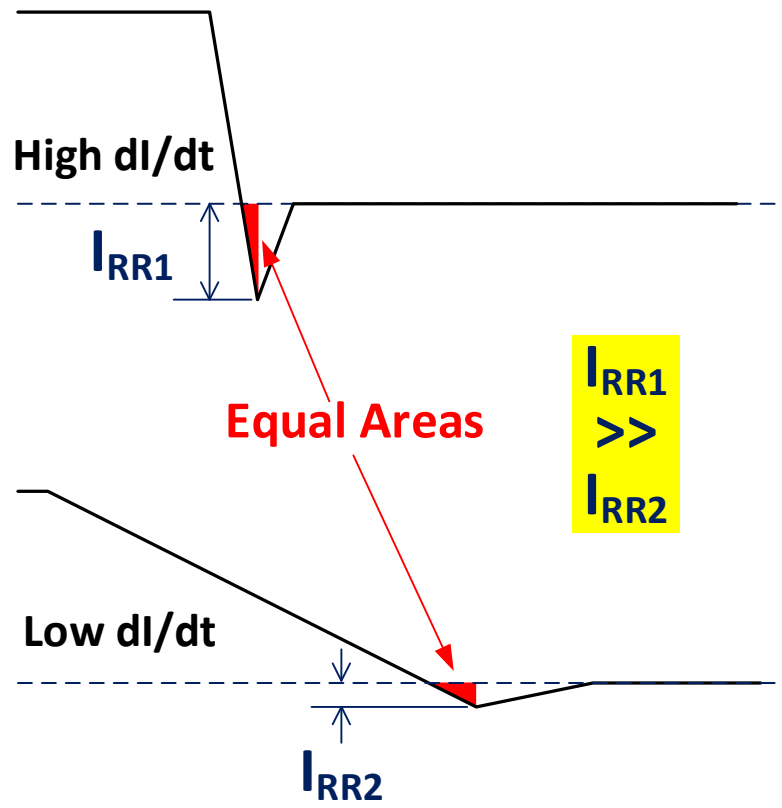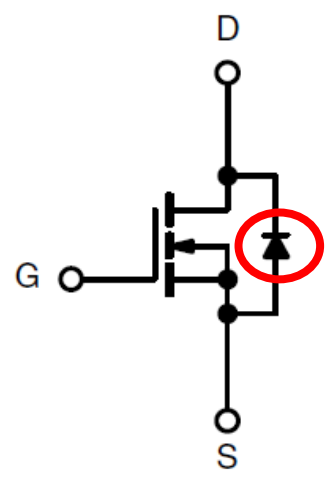

- **Key takeaways:**
 - Understand how MOSFETs work to implement a successful power circuit
 - Optimize the gate drive to control slew rate, transients, and EMI
 - Carefully design the PCB with consideration of parasitic inductances and impedances