

Conducted EMI Analysis and Mitigation in 48V Automotive

Case Study Based on a 48V-12V DCDC Converter

48V汽车电子传导EMI分析与降噪：以一个
48V-12V DC/DC变换器为例

Speaker: Yiming Li

Agenda

EMI challenge for 48V Automotive



48V LLC Introduction and Application



Conducted EMI Noise Analysis for Various Cases




Summary and Conclusion

EMI Challenge for 48V Automotive



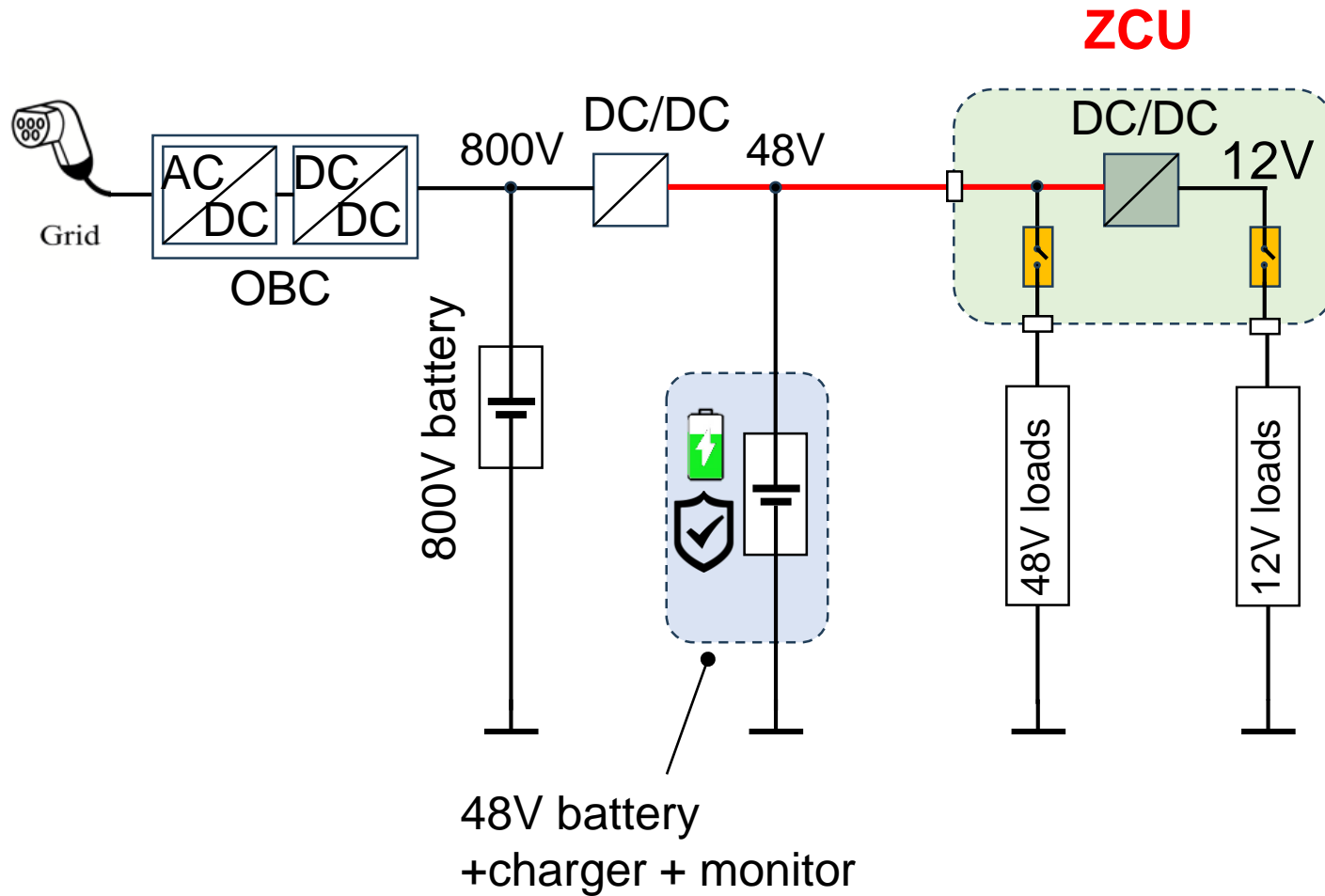Power Architecture: 48V Bus + local 48V->12V




Advantage:

- 48V wire harness has best weight saving
- 12V Battery not required because:
 - 48V battery as a buffer for loads
 - HV battery charges 48V battery
- Easy to upgrade:
in the future when more load move to 48V, only need to size the local 48V->12V DCDC w/o touching the architecture
- Good total Efficiency
- Low cost


Architecture of Zonal Control Unit

48V battery

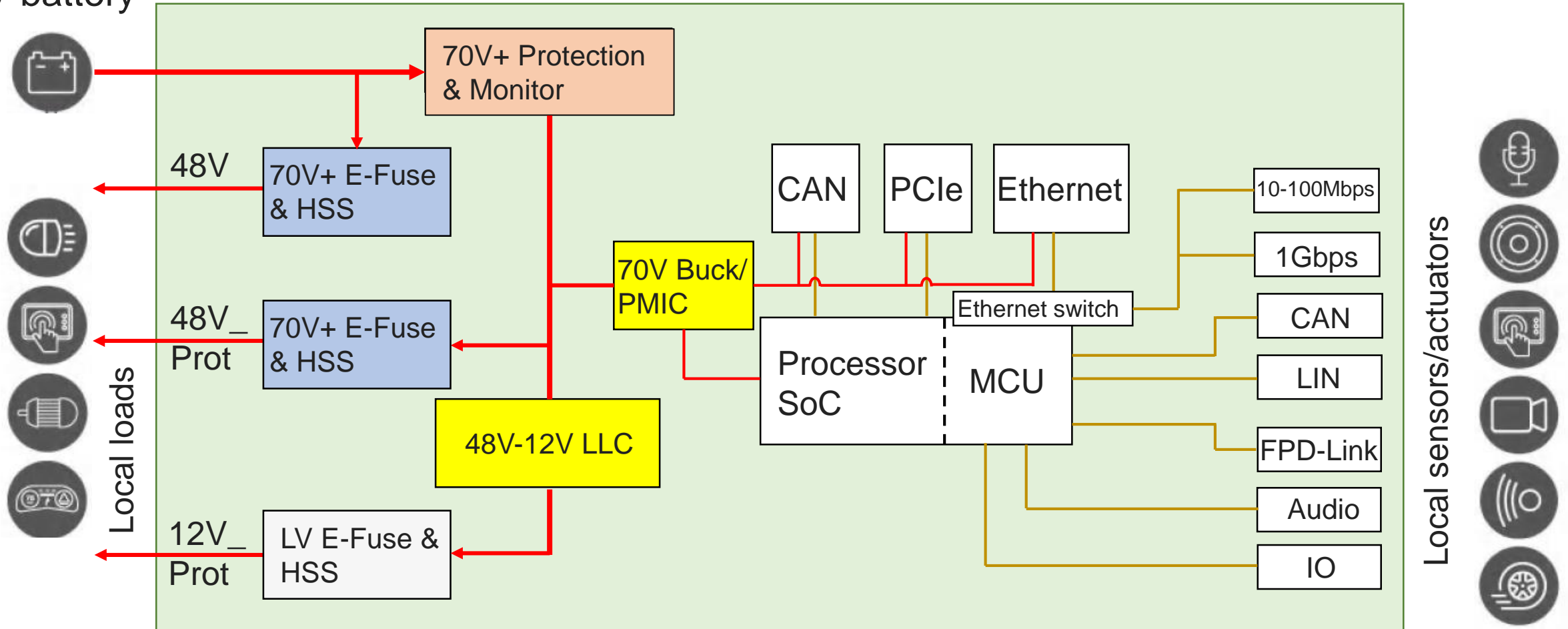


- Notes:
1. DC/DC input voltage increases from 12V to 48V.
 2. An additional 48-12V DC-DC is applied for 12V power rail.

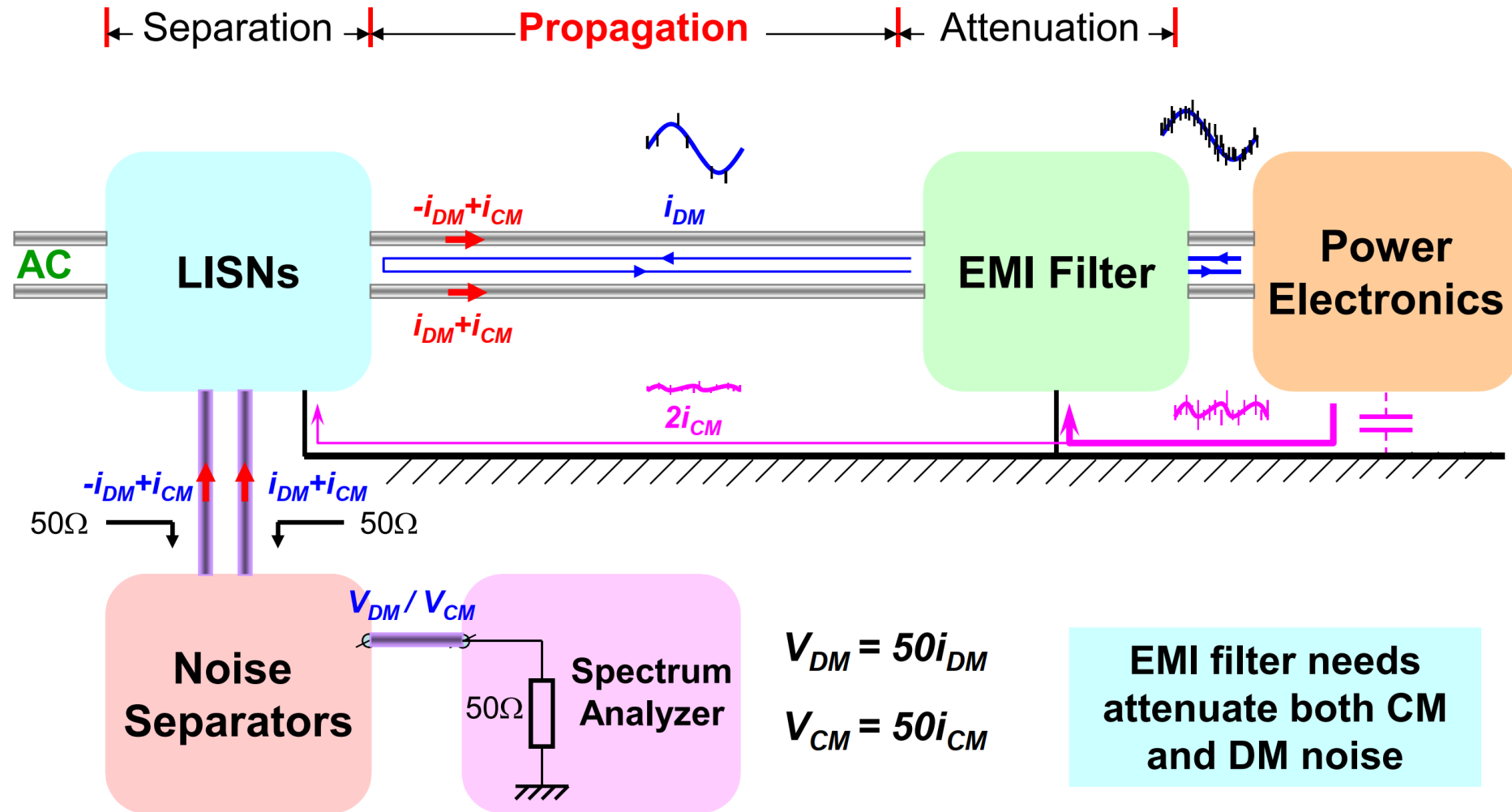Conducted EMI: Modeling and General Reduction Technique




Spectrum of a Trapezoidal Wave

Time Domain

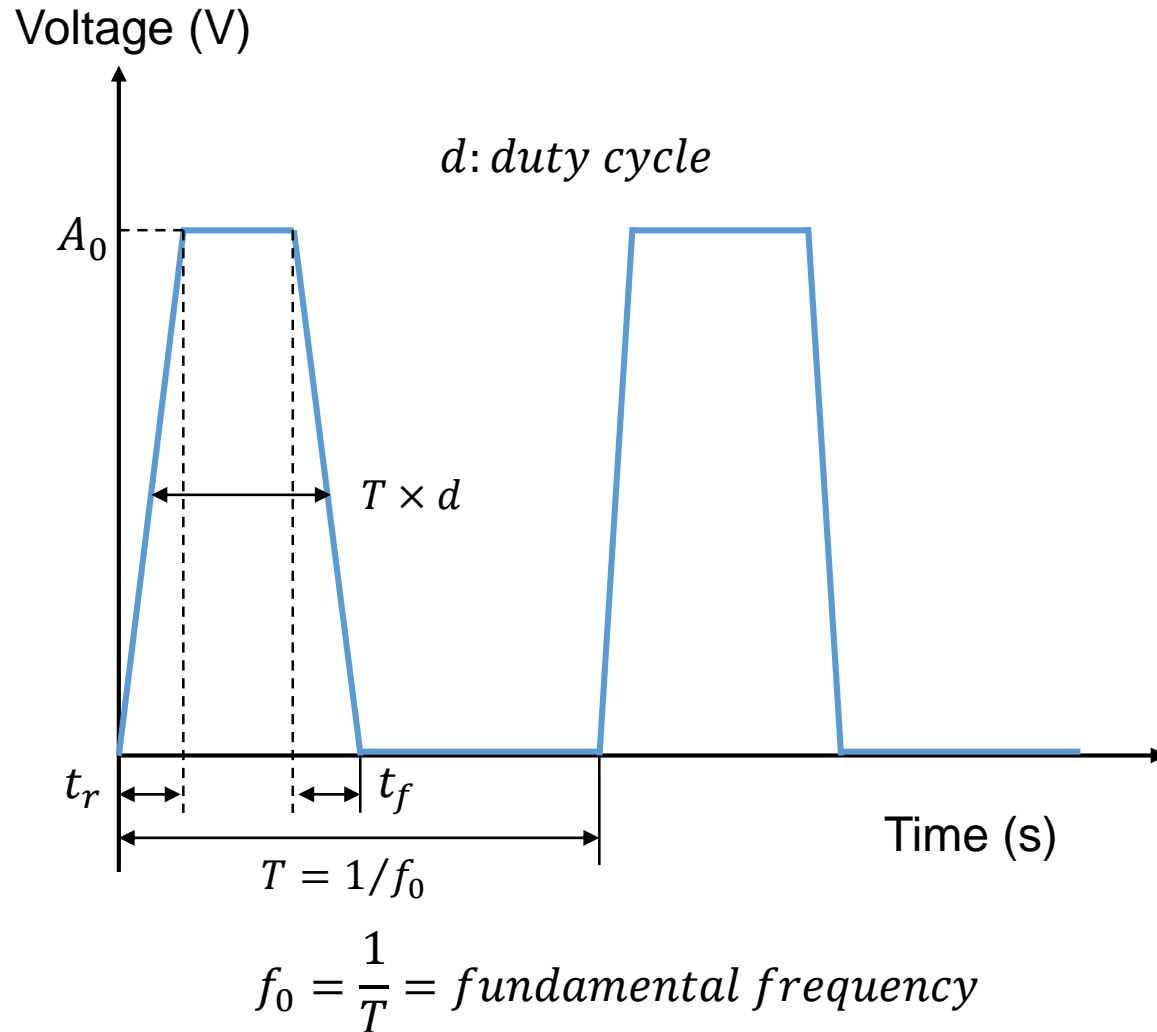


Frequency Domain

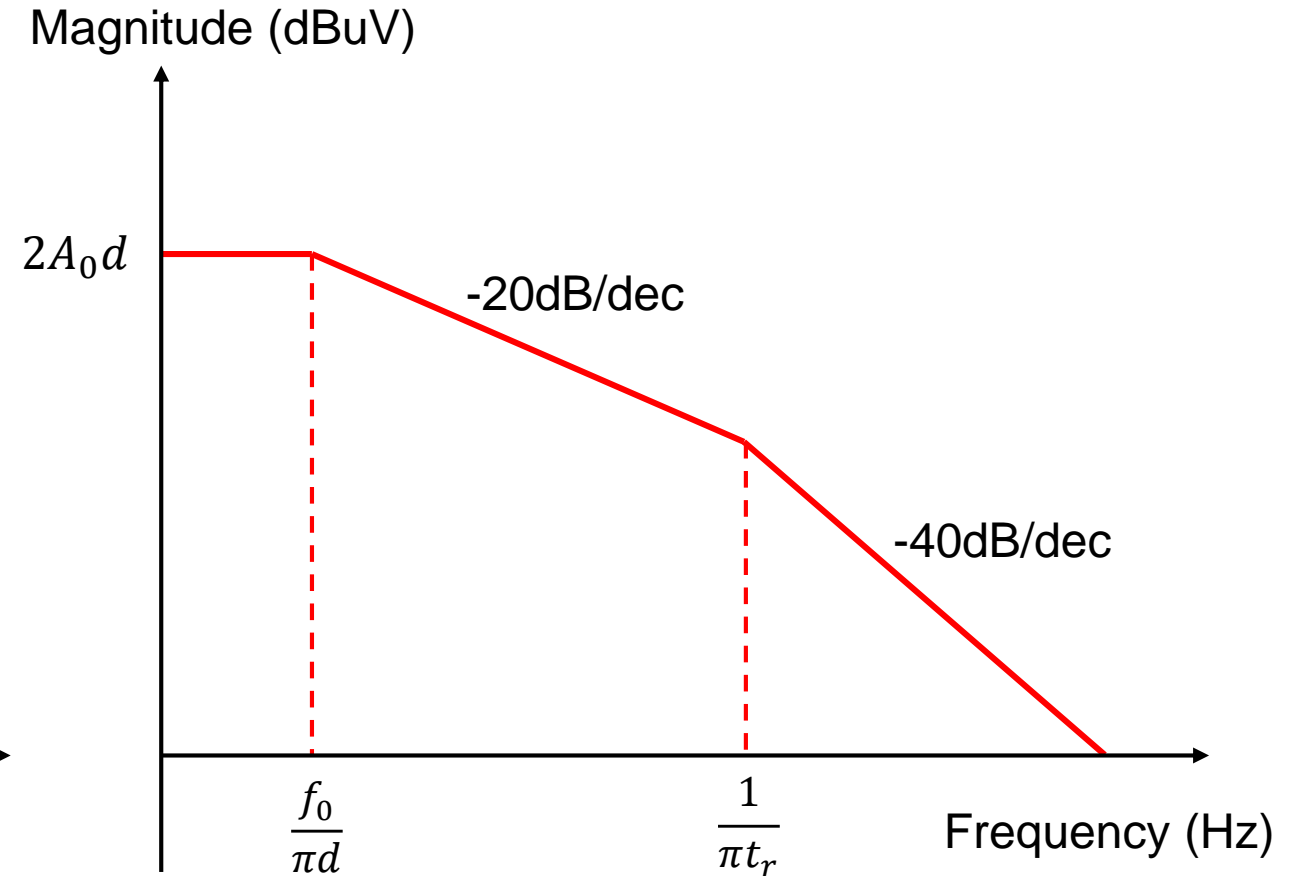

Fourier Expression of a Trapezoidal Waveform

A_n represent the magnitude of the nth order harmonic

$$A_n = 2A_0 \cdot d \cdot \left| \frac{\sin(n\pi d)}{n\pi d} \right| \left| \frac{\sin\left(\frac{n\pi t_r}{T}\right)}{\frac{n\pi t_r}{T}} \right|$$

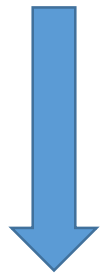

$$\frac{\sin(x)}{x} < 1 \text{ if } x < 1$$


$$\frac{\sin(x)}{x} \leq \frac{1}{x} \text{ if } x \geq 1$$

$$V(f) = \begin{cases} 2A_0 d & f < \frac{f_0}{\pi d} \\ \frac{2A_0}{\pi} \left(\frac{f_0}{f} \right) & \frac{f_0}{\pi d} < f < \frac{1}{\pi t_r} \\ \frac{2A_0}{\pi^2 t_r} \left(\frac{f_0}{f^2} \right) & f > \frac{1}{\pi t_r} \end{cases}$$

where $V(f)$ is the envelope of the spectrum


$$A_0 = 10V, d = 0.5, f_0 = 1MHz, t_r = t_f = 10ns$$

Magnitude (dBuV)

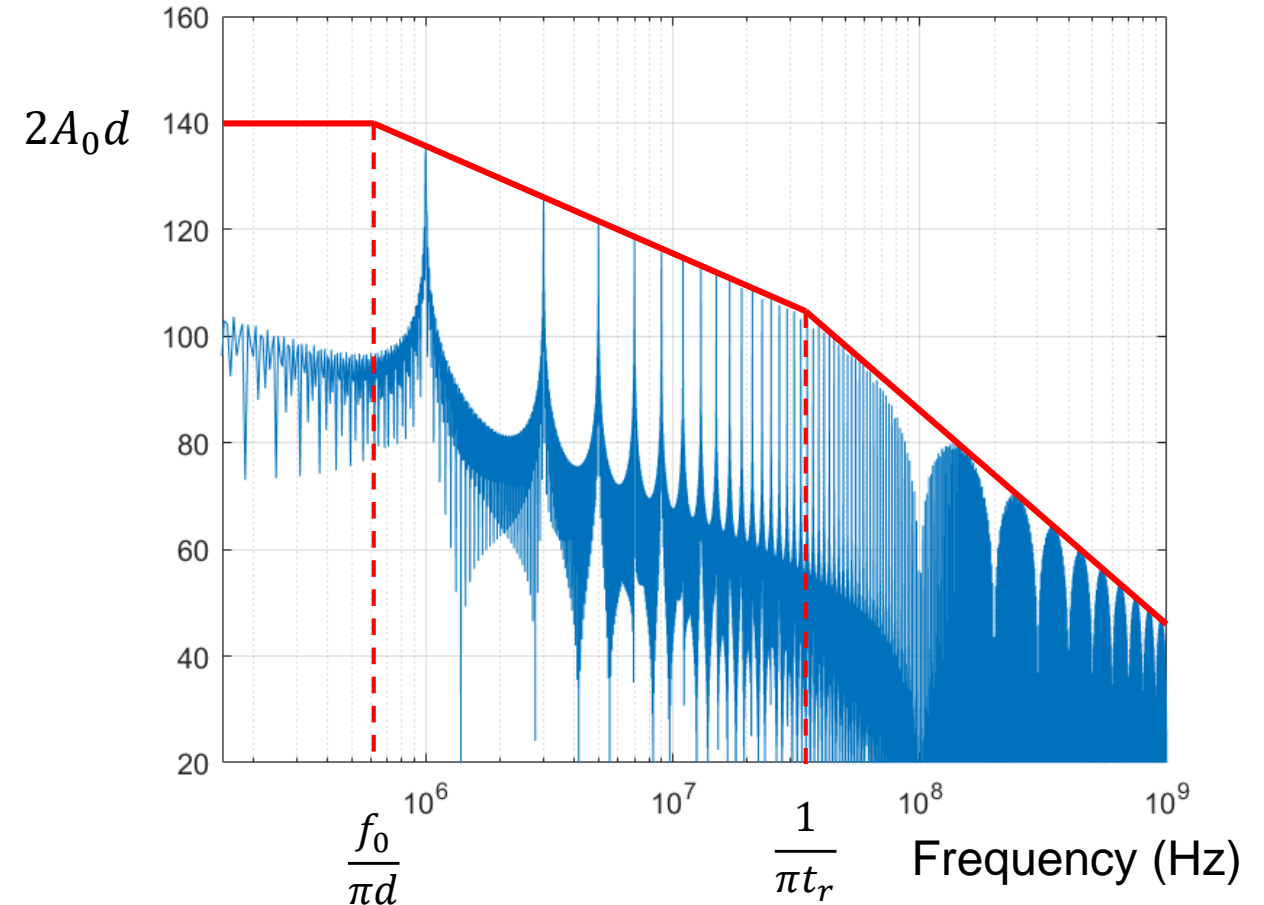


Spectrum of a Trapezoidal Wave

Time Domain

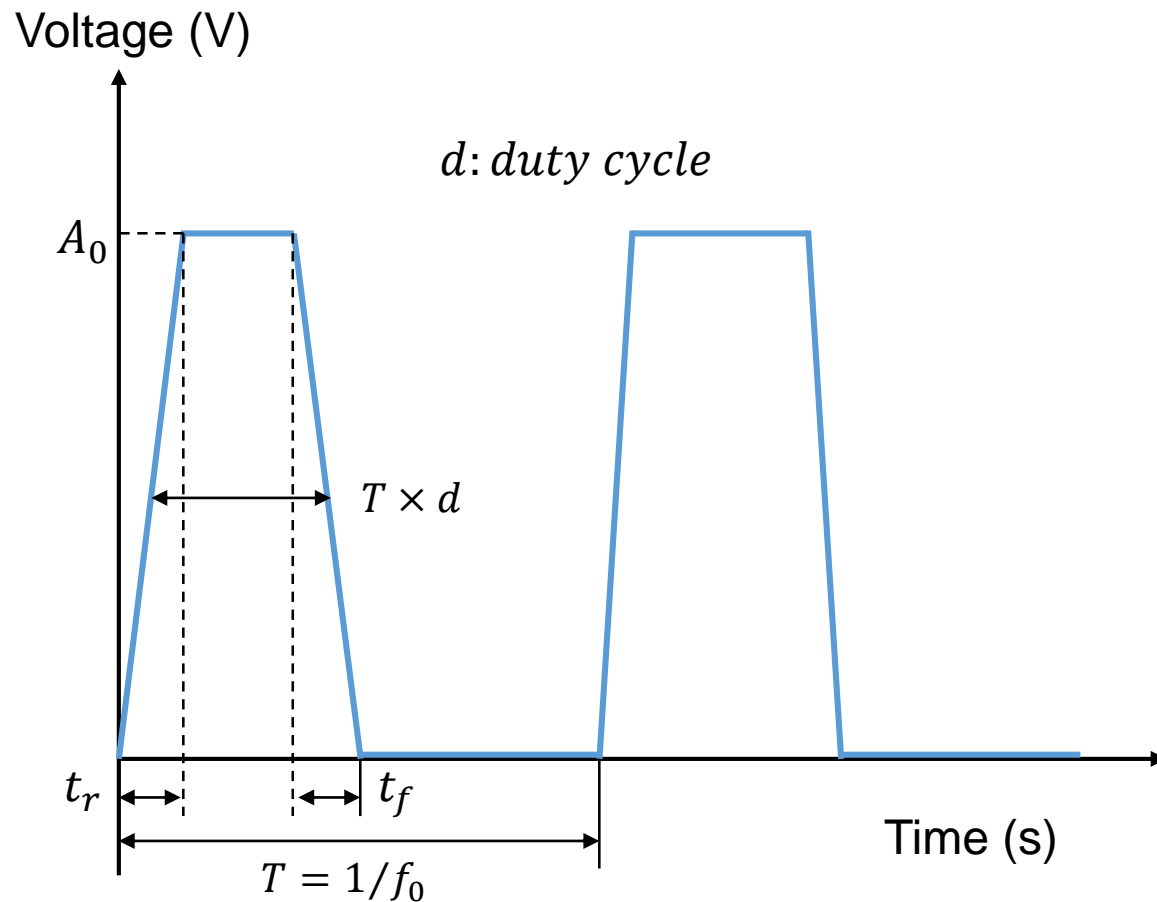


$$f_0 = \frac{1}{T} = \text{fundamental frequency}$$

Frequency Domain

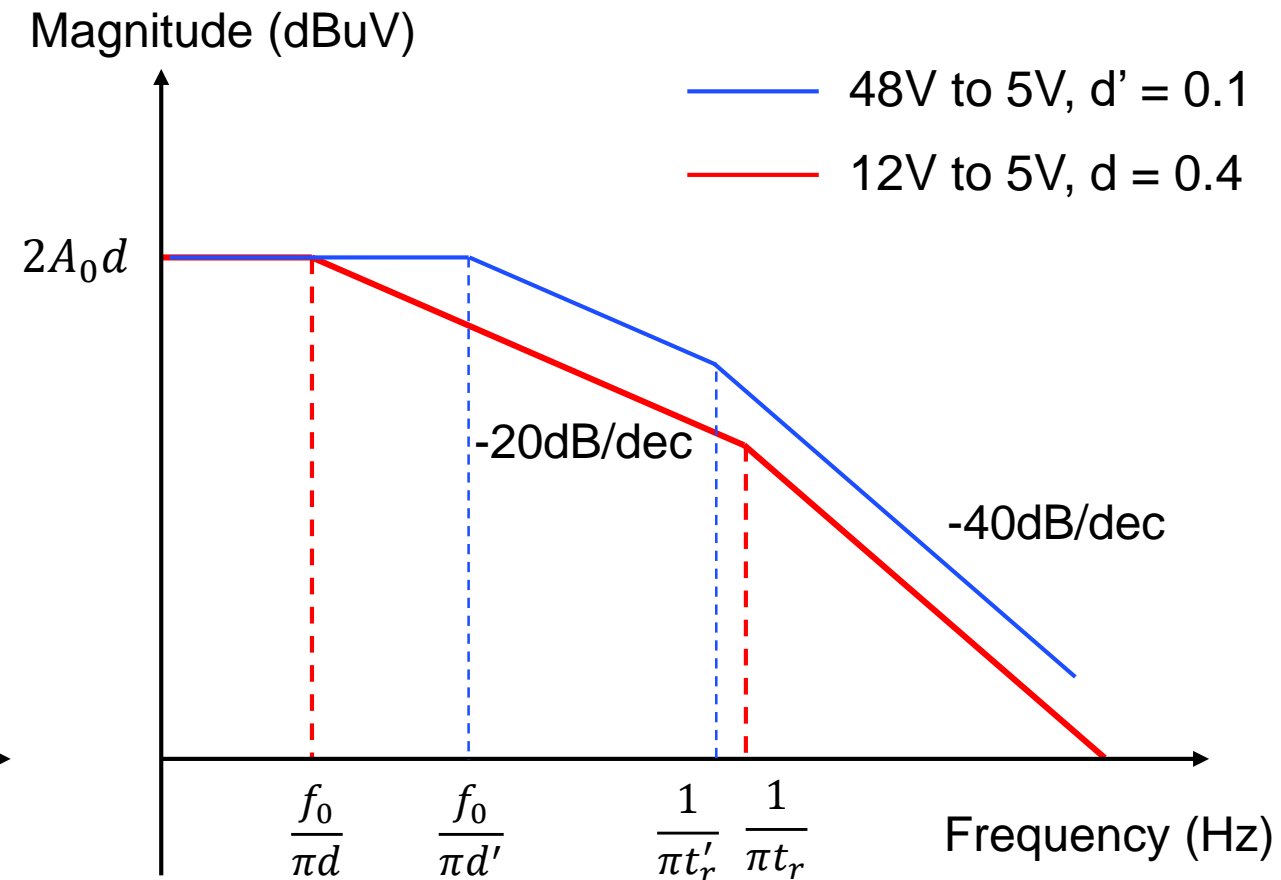


EMI Comparison, CE, 150k-30MHz

12V-5V, CE

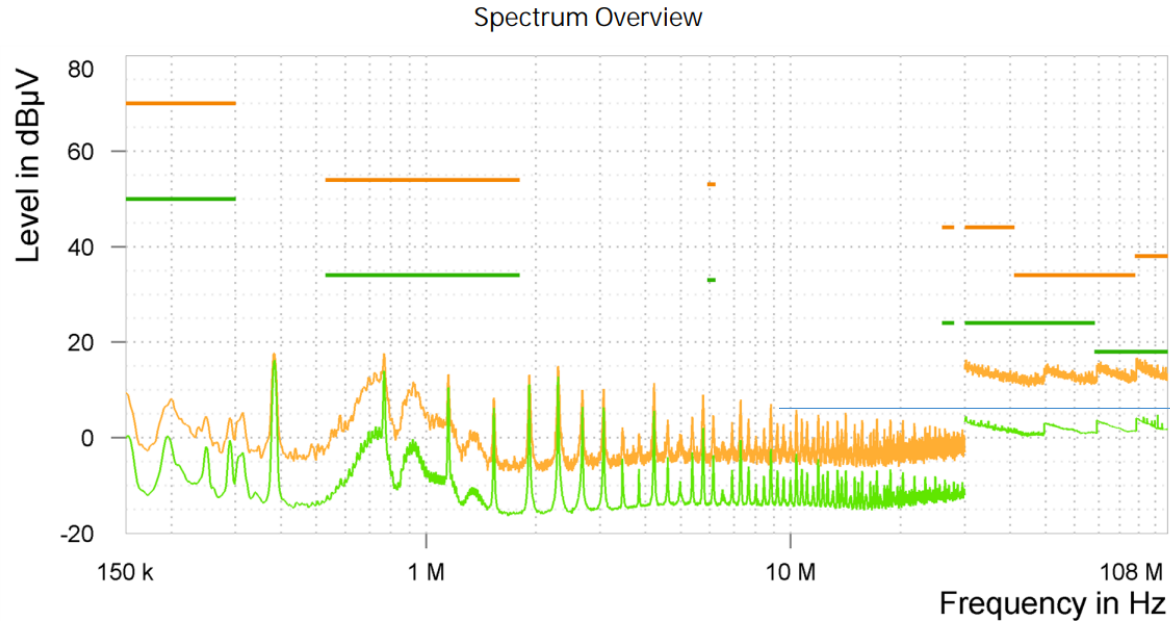

48V-5V, CE

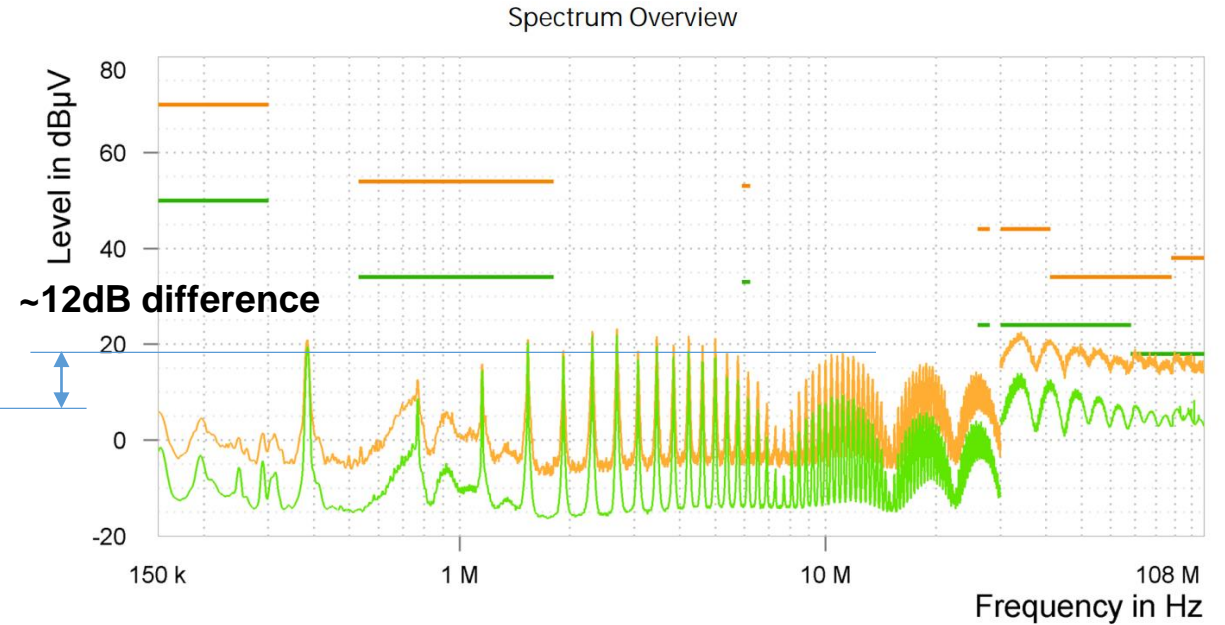

Note:

Fundamental Frequency: No too much difference.
After 3rd harmonic: There is 12dB difference.



LLC Introduction and Application



LLC Benefits for 48V ZCU

- Soft-Switching mitigates EMI source
- Allow Bi-directional Operation
- Support high peak power with small magnetic component size
- Can be fully-isolated

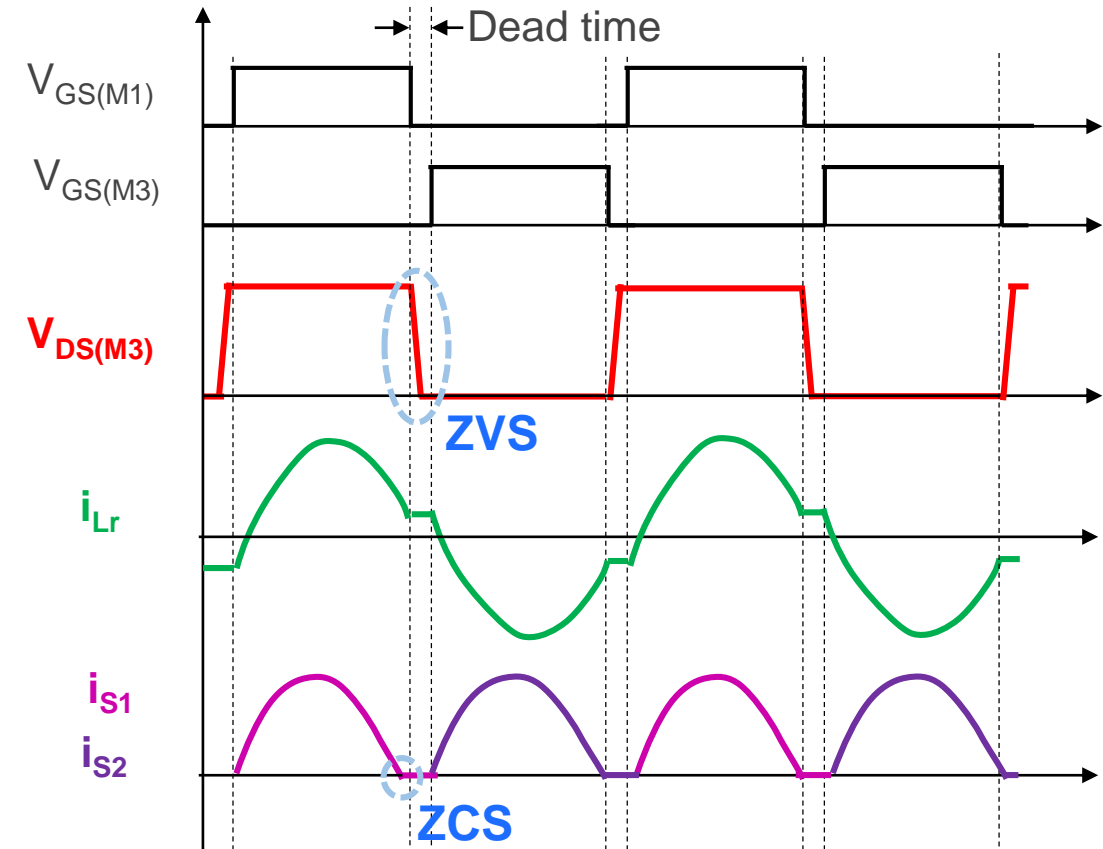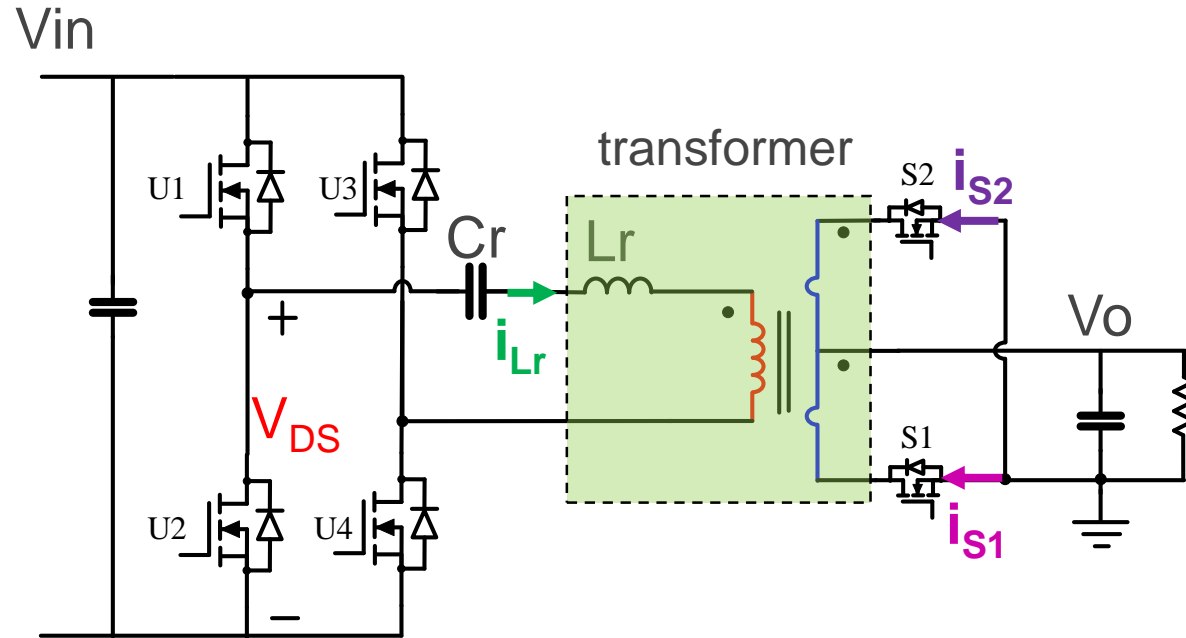
Soft Switching Characteristics of MPS LLC Topology



- ZVS(zero-voltage switching) for all FETs
 - Transformer current discharge or charge C_{oss} of FETs
- ZCS(zero-current switching) for all secondary FETs

- **Benefits of soft switching:**
 - High switching frequency
 - High efficiency and high power density
 - Low EMI (No ripples)

High-Performance Bidirectional Operation

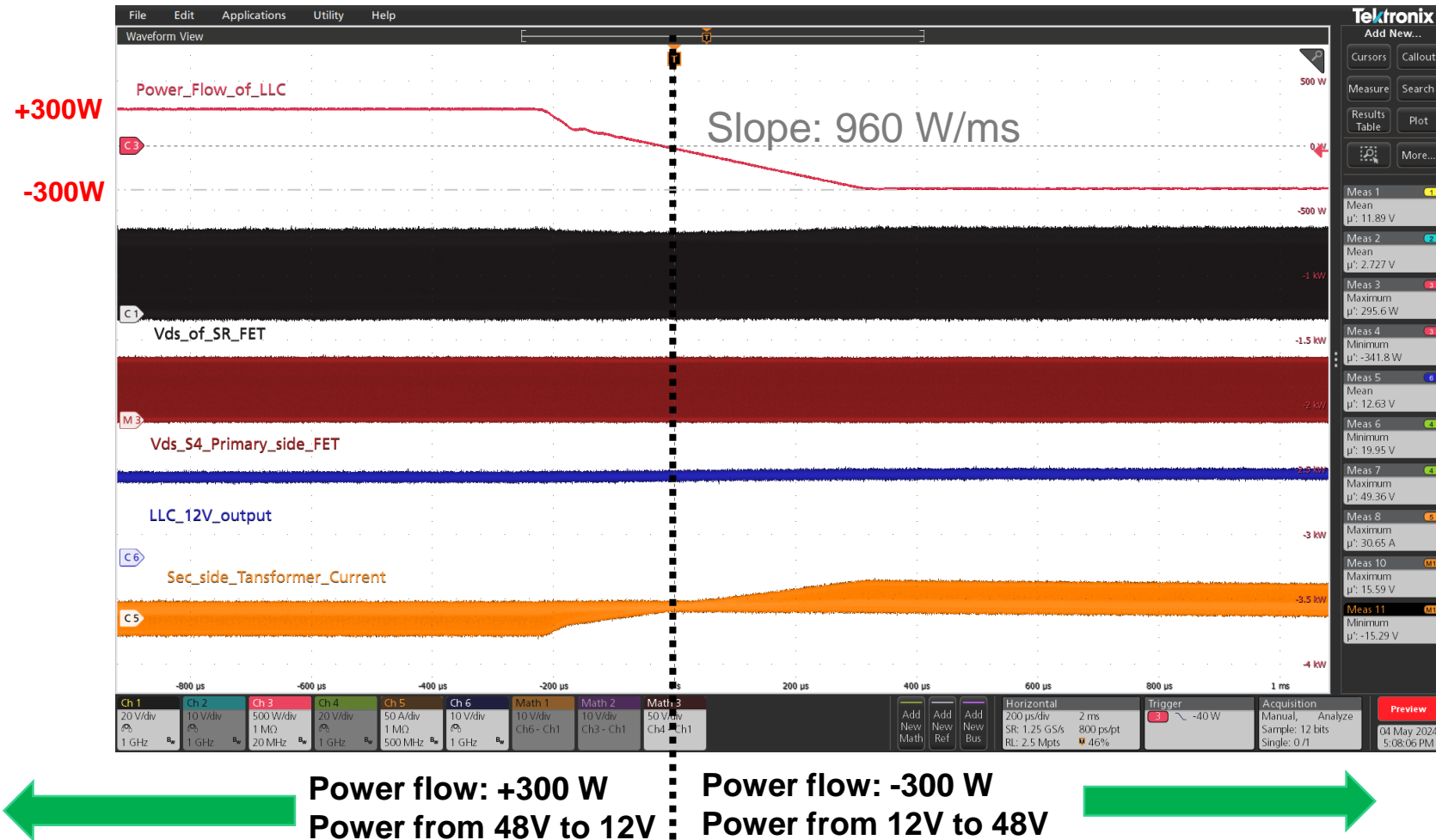


- Power flow changes from +300 W to -300W. Direction is reversed suddenly.
- 12-V output voltage is stable, and no over-voltage/under-voltage is observed

Occasions for Bidirectional Power Conversion

Normal Operation:

Power source: 48-V battery.


Load: 12-V loads

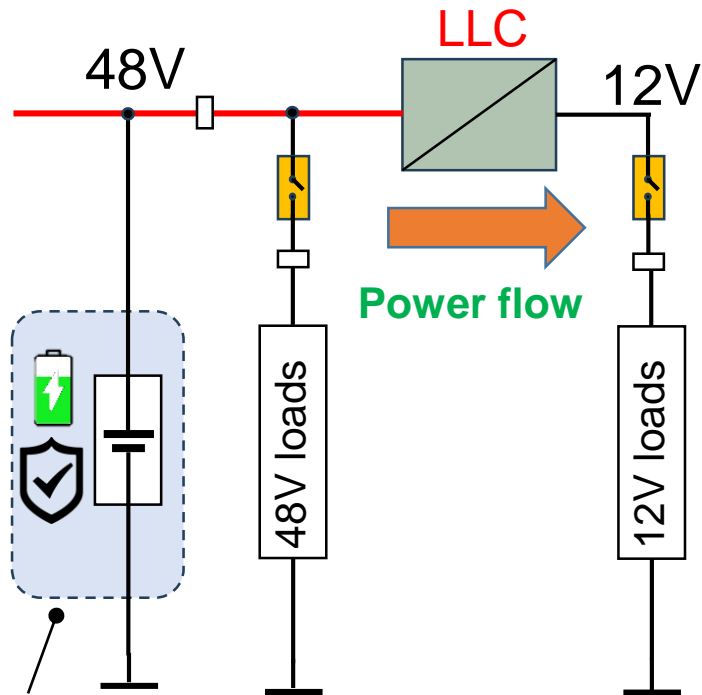

48V battery +charger +
monitor

Occasion 1 of reverse power flow:

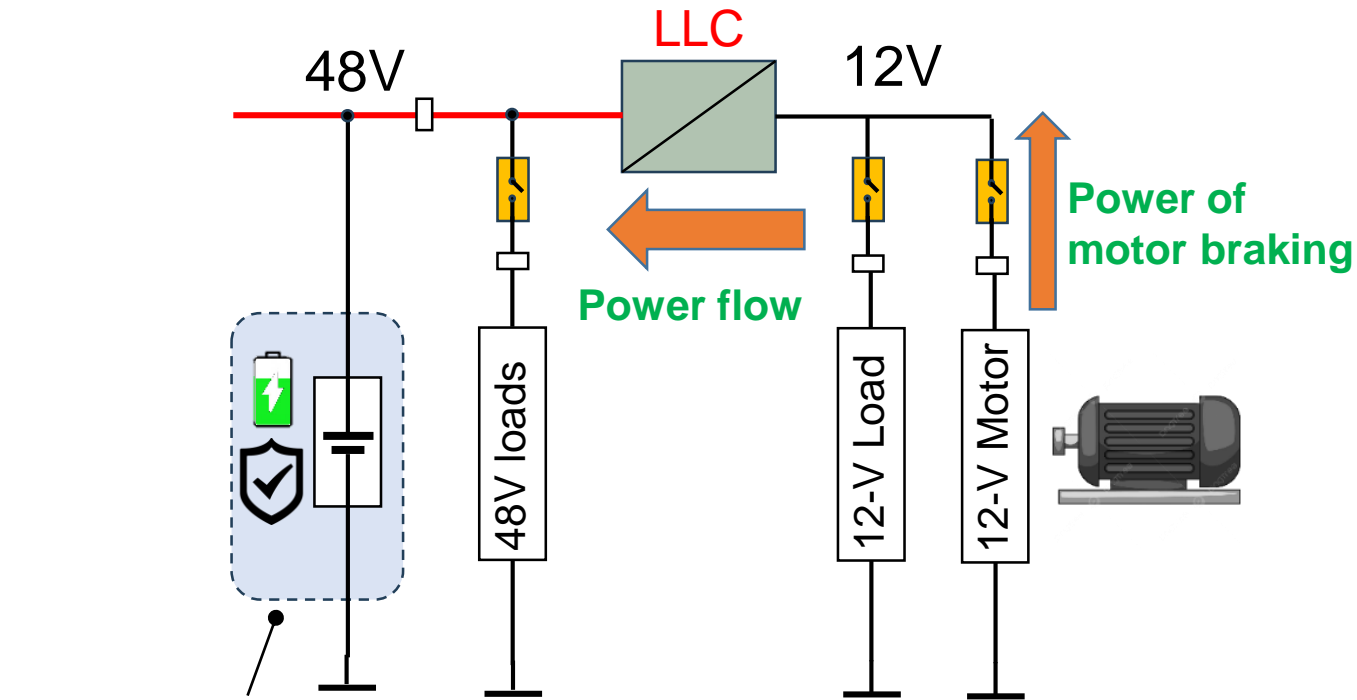12-V load such as motors return power to 48-V battery




48V battery +charger +
monitor

- If LLC cannot sink the power from 12-V loads, 12-V bus is charged, and over-voltage may happen.

Occasions for Bidirectional Power Conversion


Occasion 2 of reverse power flow:

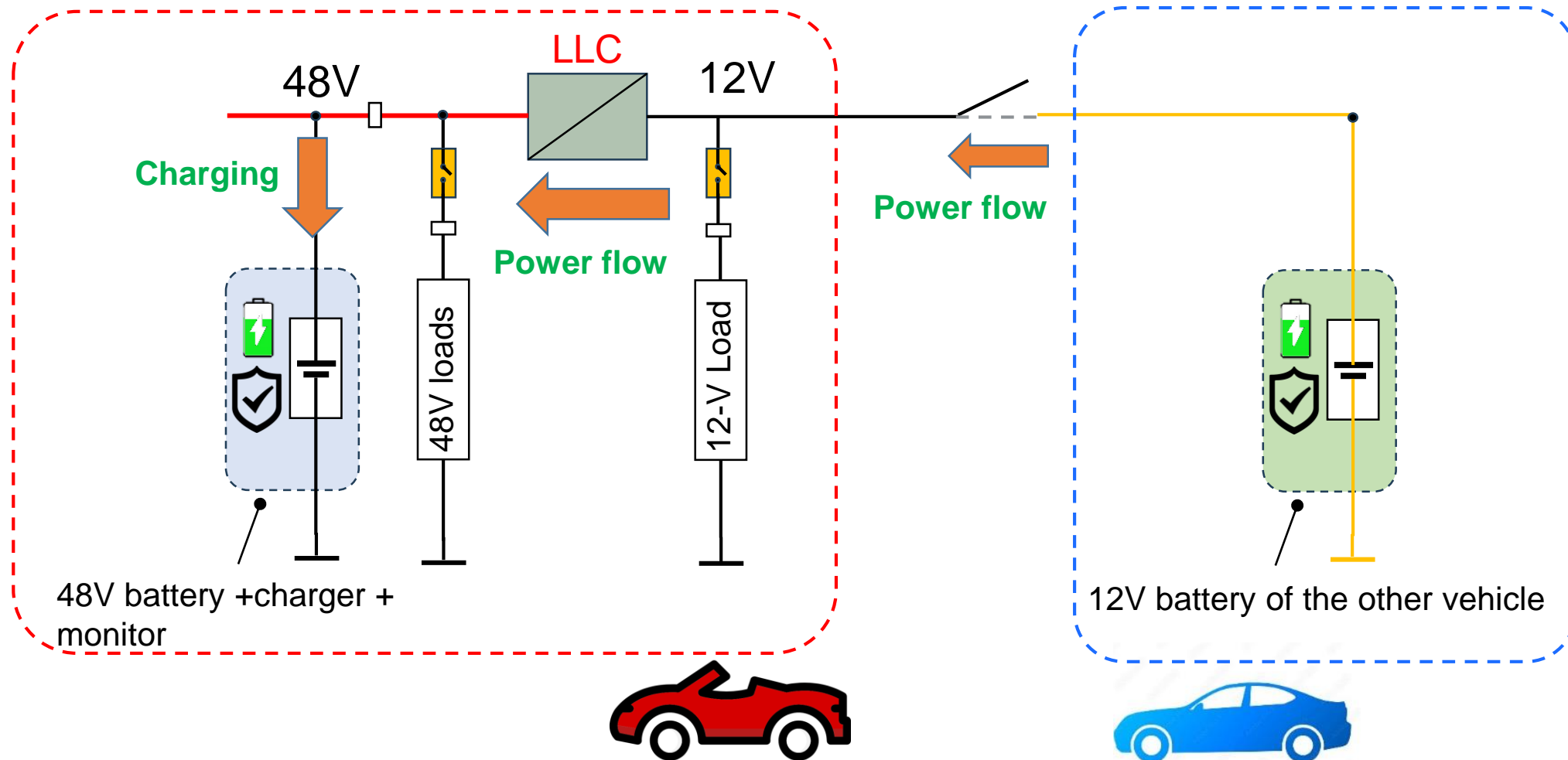12-V battery of another vehicle used to jump-start 48-V battery




Peak Power Capability

Buck:

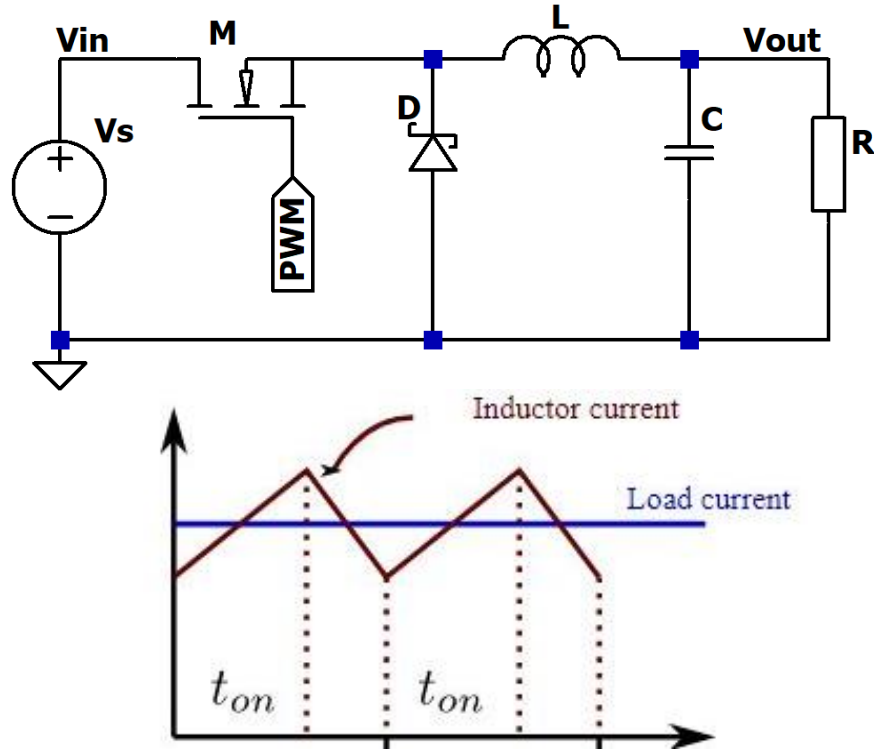

- Inductor stores energy
- Larger peak power requires larger magnetic core size to avoid inductor saturation

LLC:

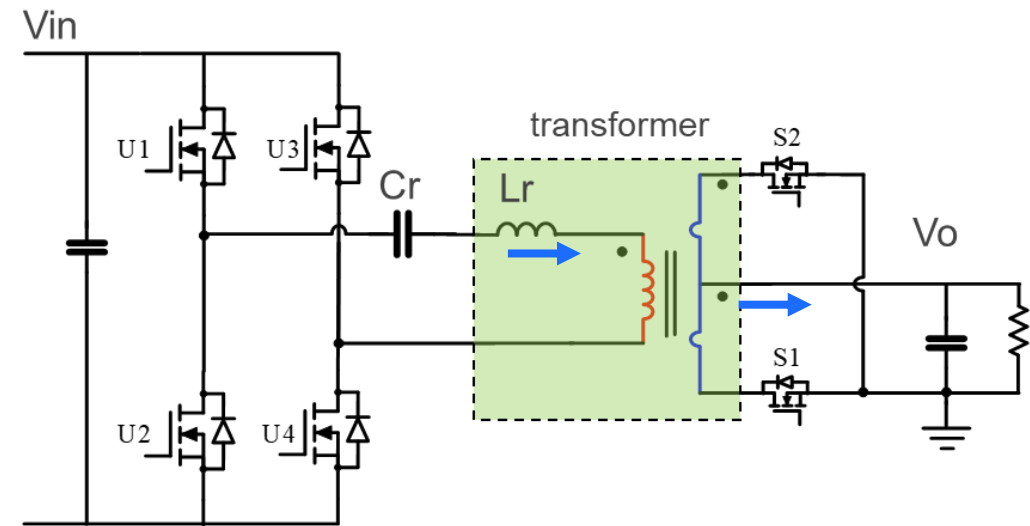

LLC uses transformer rather than inductor:


- Transformer doesn't store energy
- Peak power has no impact on magnetic core size



Magnetic Size Comparison


With 150A peak current capability:

Buck:

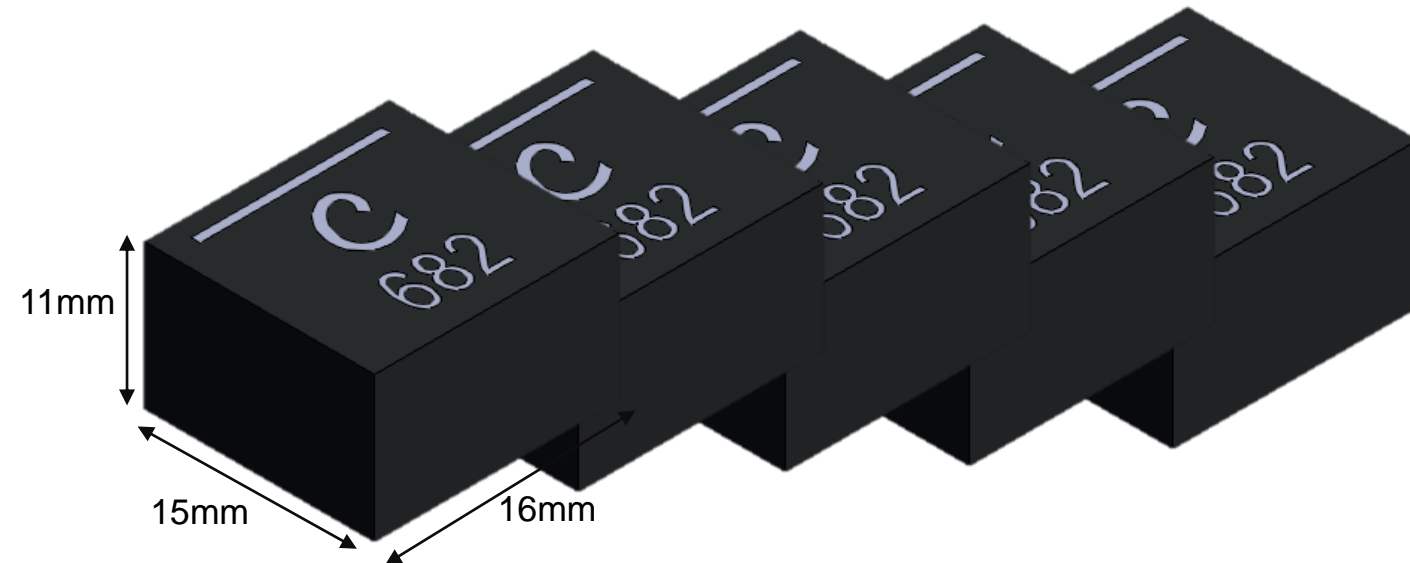

1200mm²

MPS LLC:

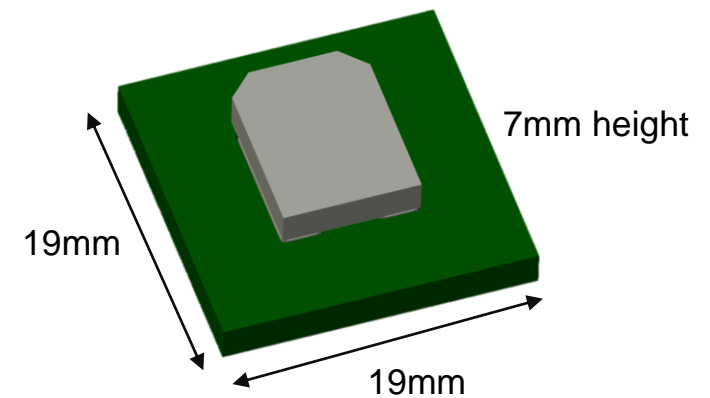


360mm²


LLC EMI Modeling and Reduction



Traditional LLC Setup

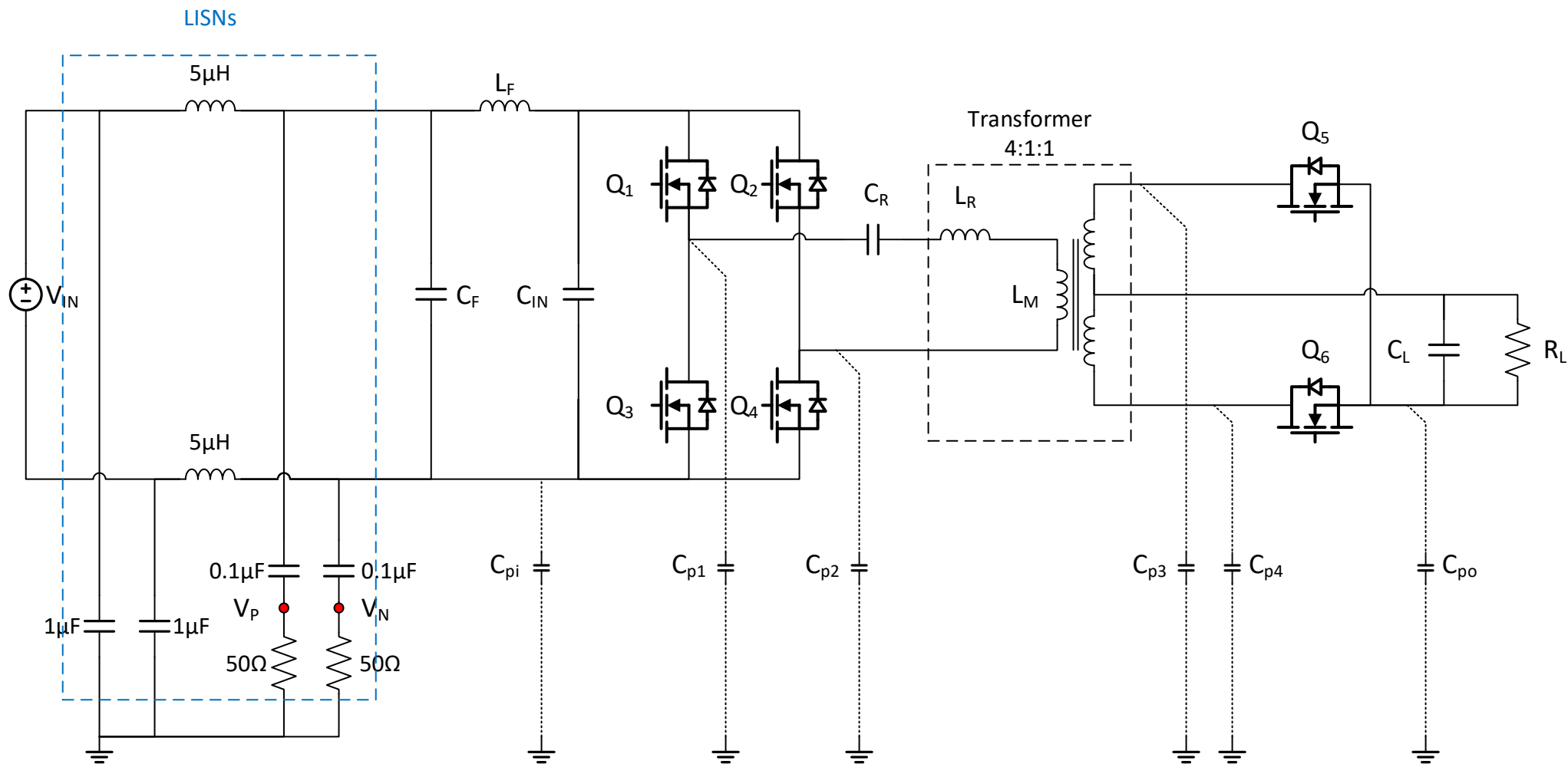


DM Noise Path Analysis

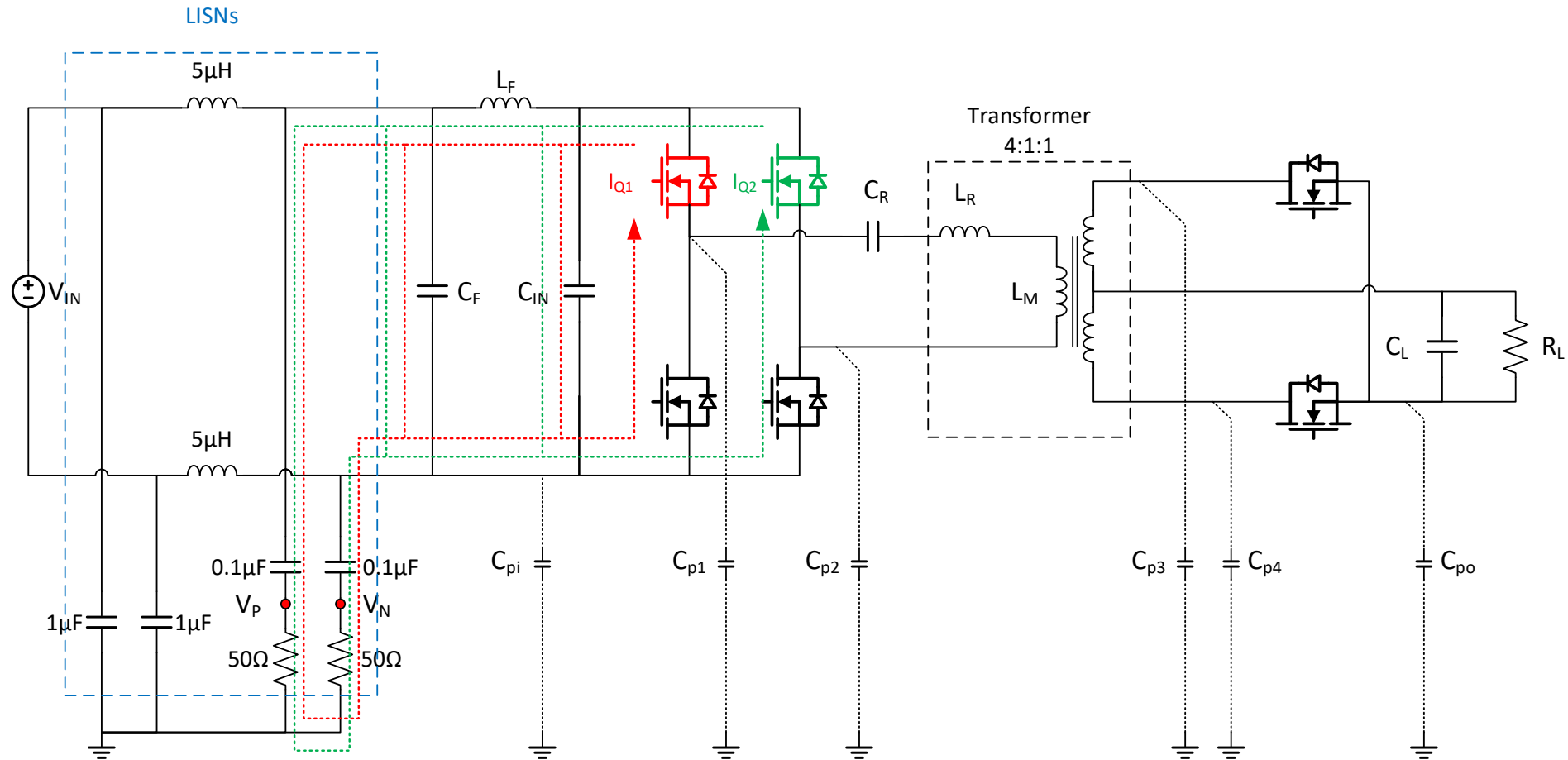


Note: The DM noise source is the sum of Q1 and Q2 current. Input filter helps to reduce DM noise.

CM Noise Path Analysis

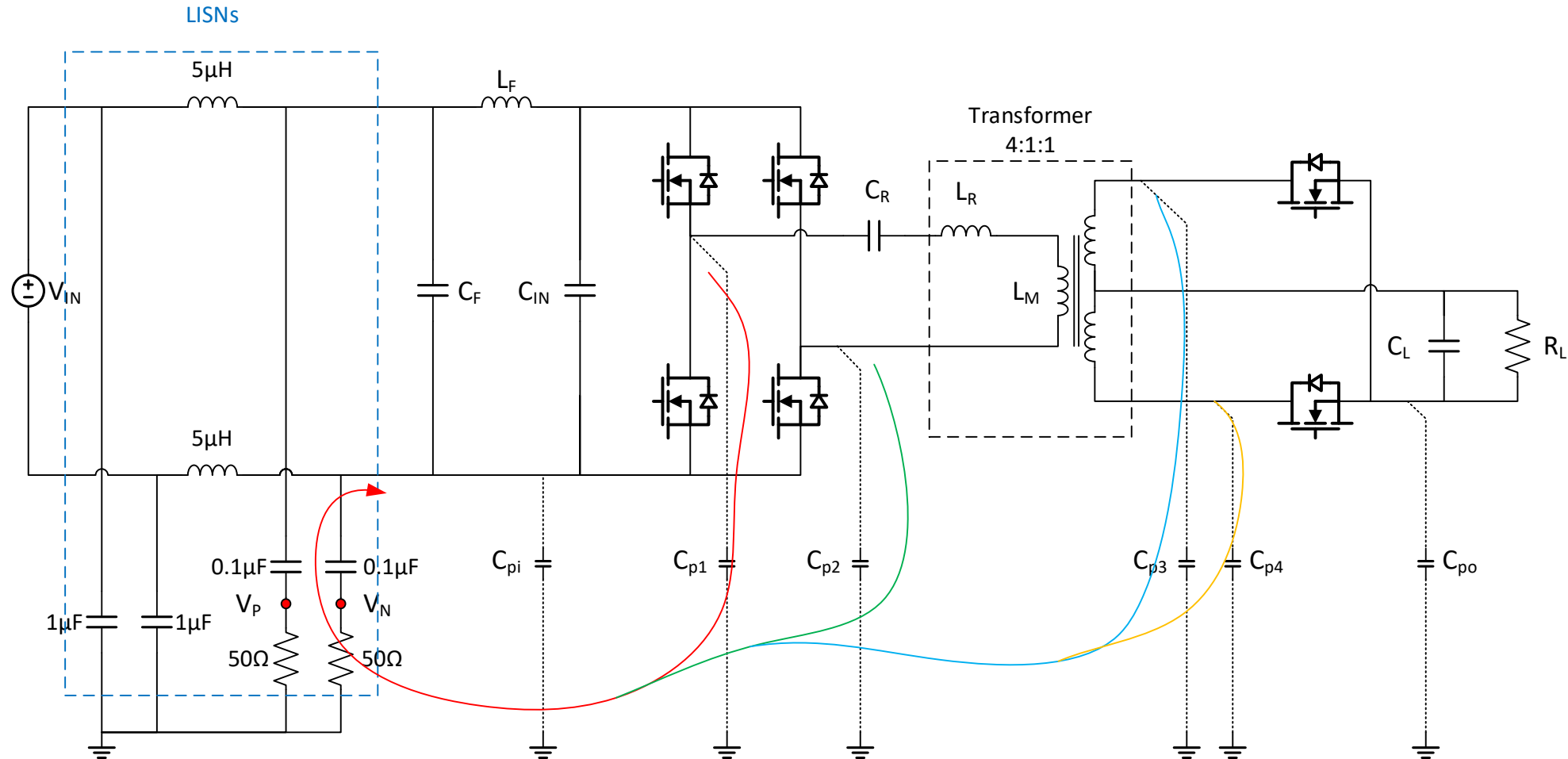

Note: The CM noise paths are relatively complicated to analyze. There are many switching nodes.

Substitution & Superposition Theory

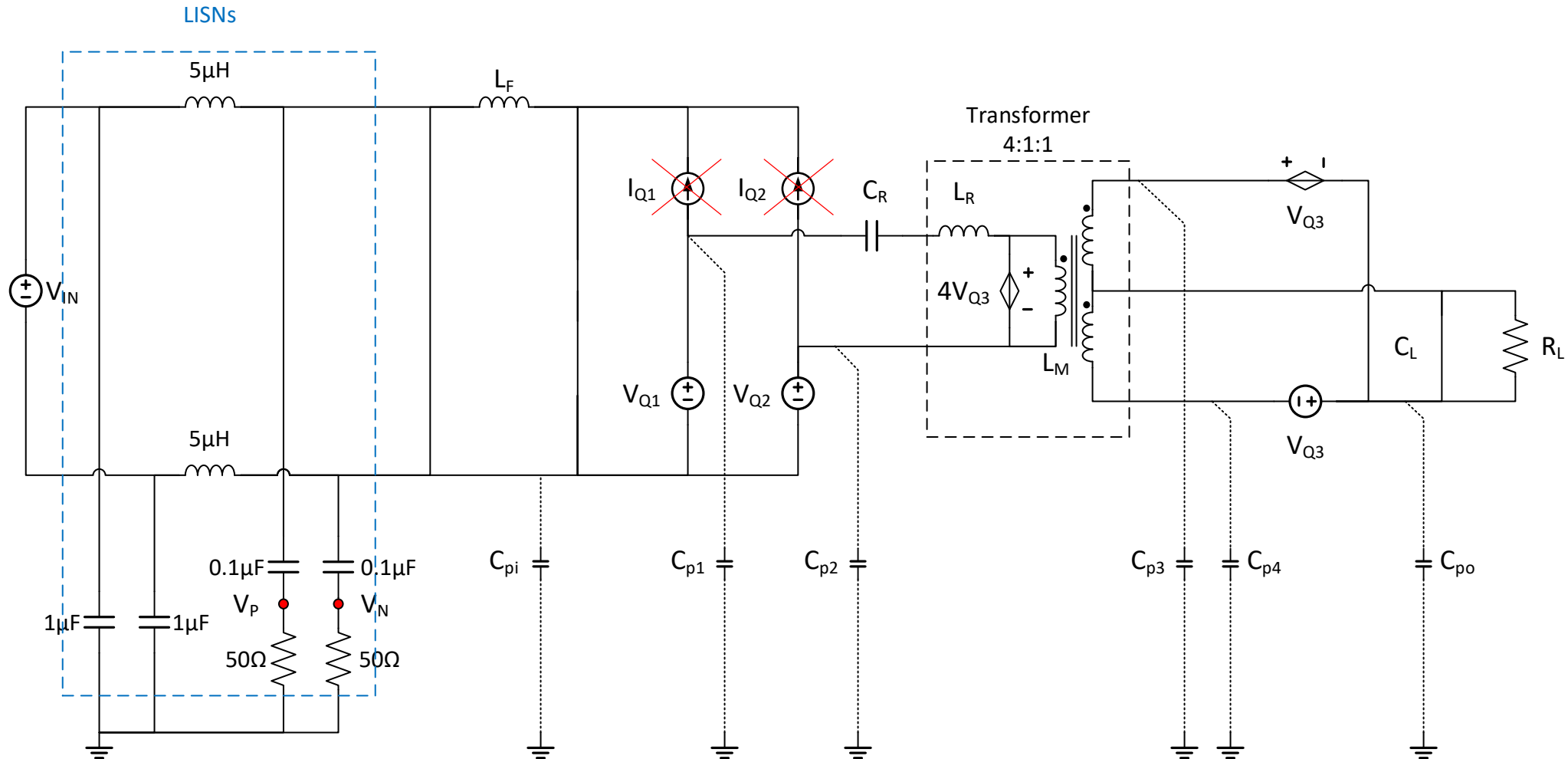

Note: I_{Q1} and I_{Q2} does not generate CM noise. V_{Q1} , V_{Q2} and V_{Q3} can be CM Noise sources.

How to Analyze the Transformer?


Two-capacitor Transformer Winding Capacitance Model [1]

- 1) The transformer's leakage inductance is small so its effect can be ignored.
- 2) At least one winding of the transformer are connected to an equivalent independent voltage source. This source can be the equivalent voltage source used to substitute nonlinear switches.



[1] H. Zhang, S. Wang, Y. Li, Q. Wang and D. Fu, "Two-Capacitor Transformer Winding Capacitance Models for Common-Mode EMI Noise Analysis in Isolated DC–DC Converters," in *IEEE Transactions on Power Electronics*, vol. 32, no. 11, pp. 8458-8469, Nov. 2017.

CM Noise Model of LLC

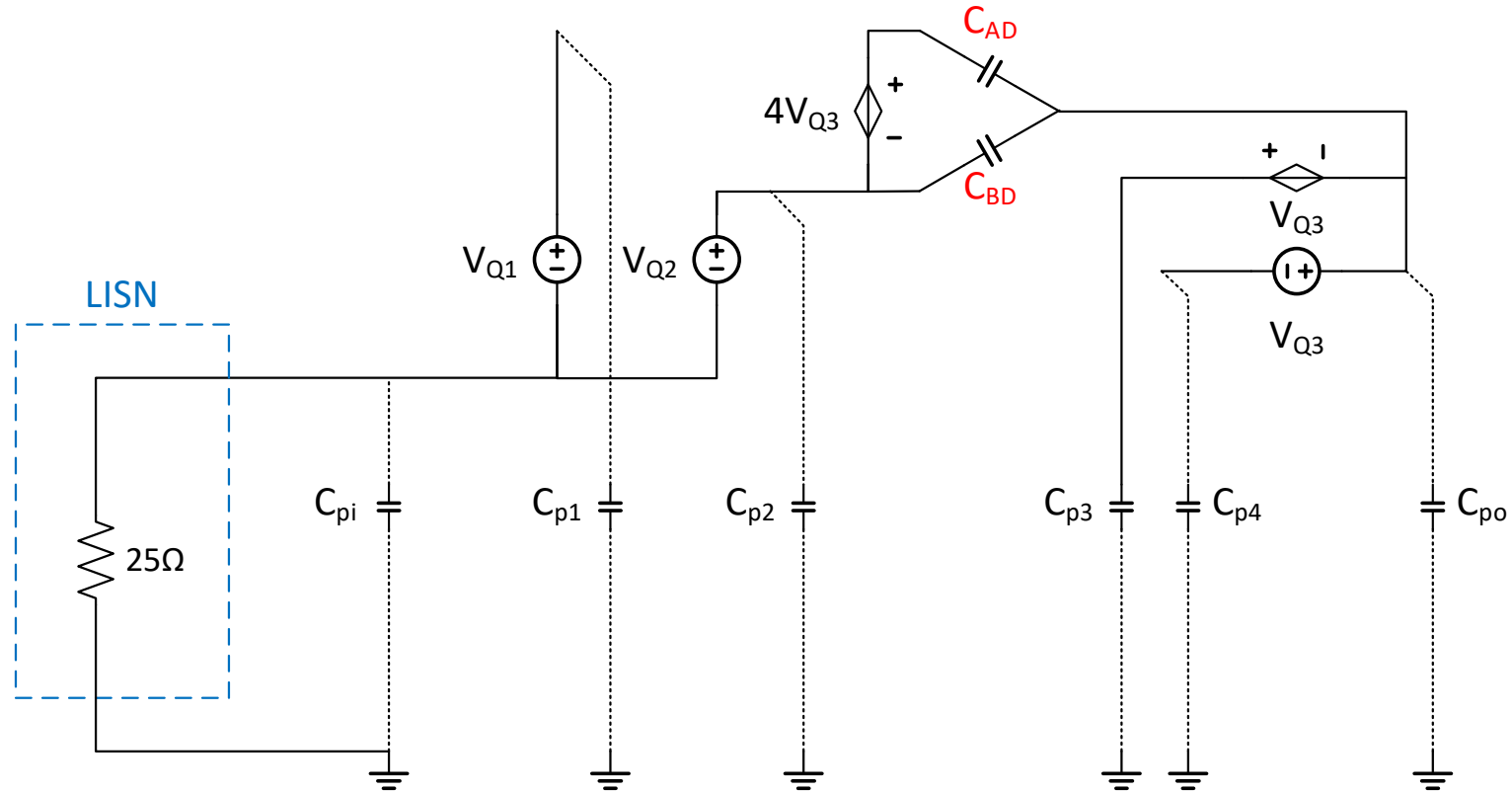


Note: The CM noise model of isolated LLC can be further simplified as above.

Balance Condition Derivation

$$V_{Q1} \approx -V_{Q2}$$
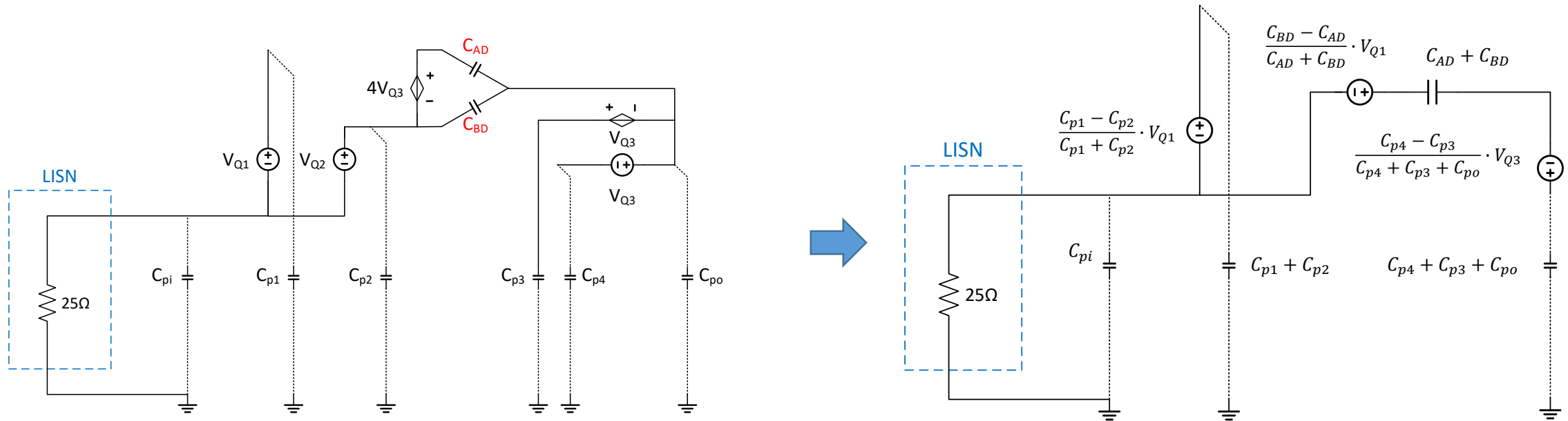
$$4V_{Q3} \approx V_{Q1} - V_{Q2} \quad \text{Assume that the switching frequency is equal or very close to the resonant frequency.}$$




$$\text{Balance Condition: } C_{p1} = C_{p2} \quad C_{p3} = C_{p4} \quad C_{AD} = C_{BD}$$

Note: The isolated LLC CM noise can be cancelled with proper PCB/transformer design to balance the parasitics.


LLC EMI for a Special Setup

A Special Setup for Automotive

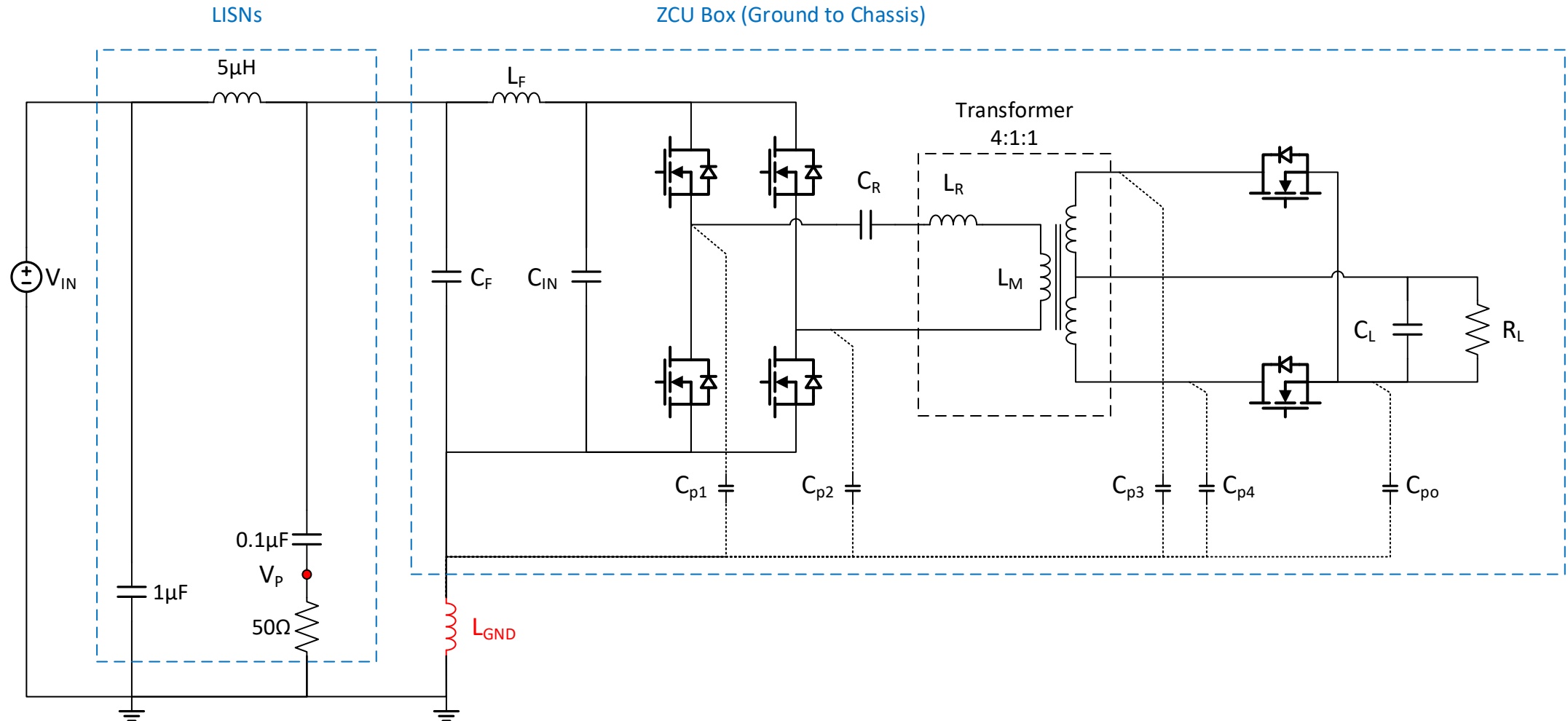


Note: In some applications, there is only positive line as the input. The negative line is grounded to the chassis. In this case, only one LISN noise needs to be measured.

Noise Path Analysis – V Source

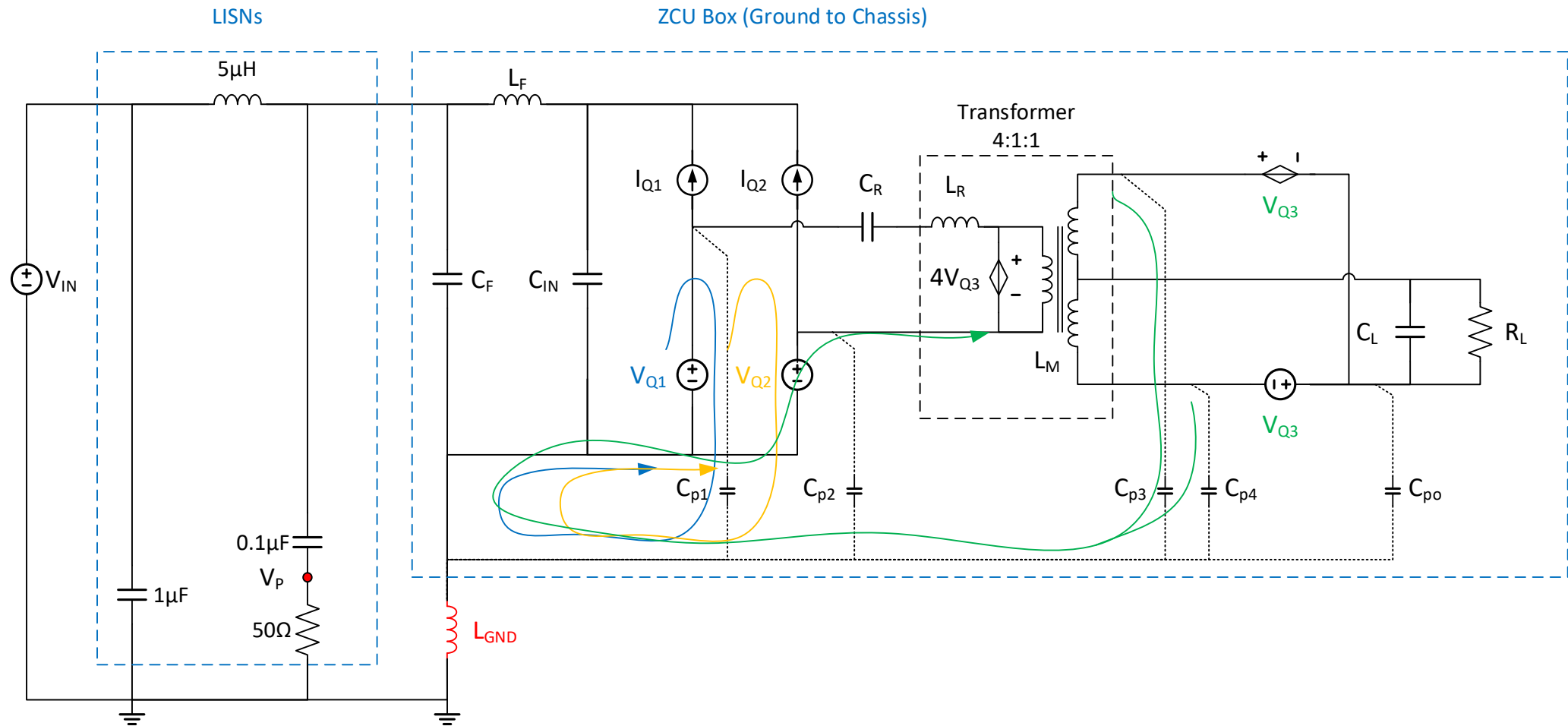


Note: Voltage sources' noise current does not flow through LISN.

Noise Path Analysis – I Source

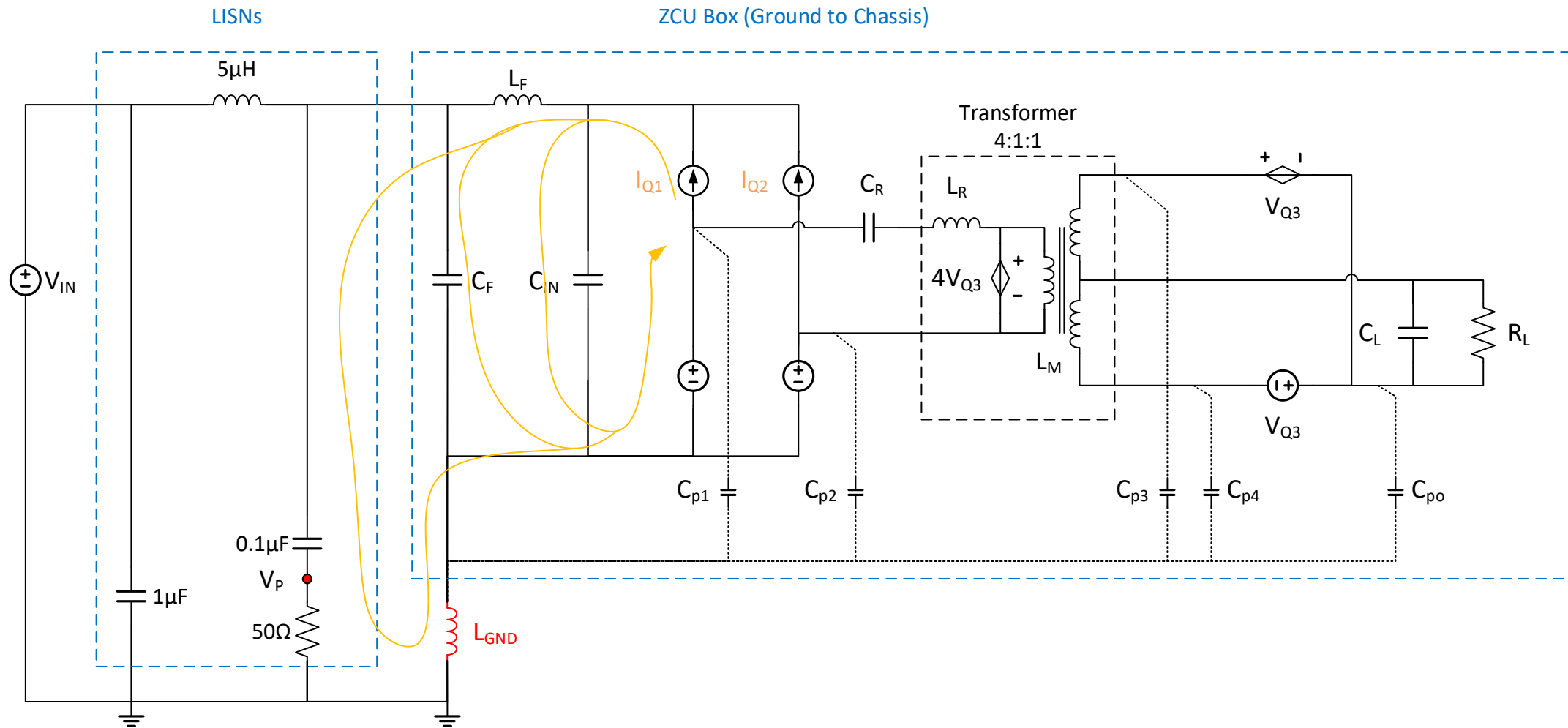


Note: Current sources' noise current flows through LISN. The EMI can be analyzed similar to DM.

Baseline EMI Noise

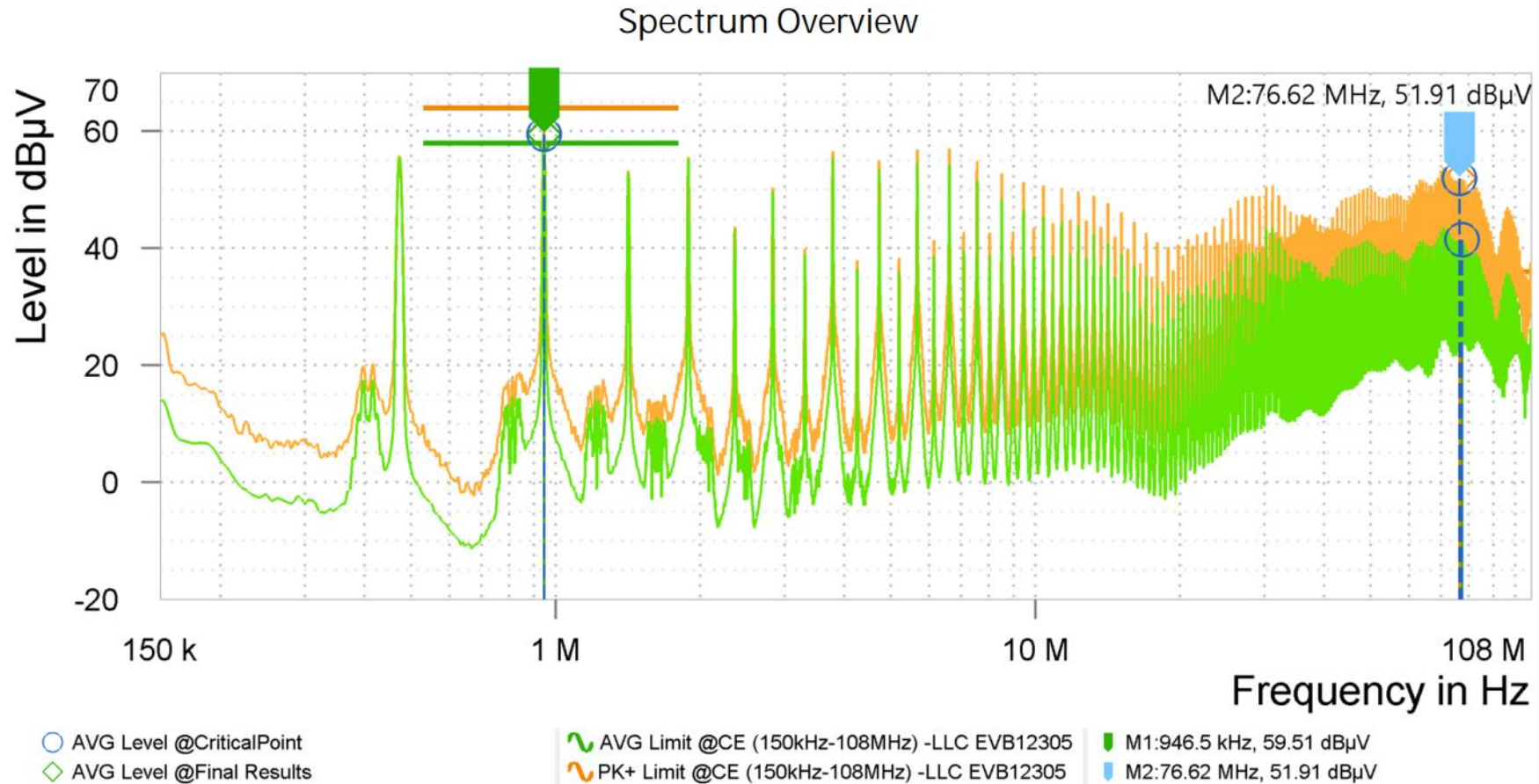


Note: It is found that the EMI is higher than the standard.

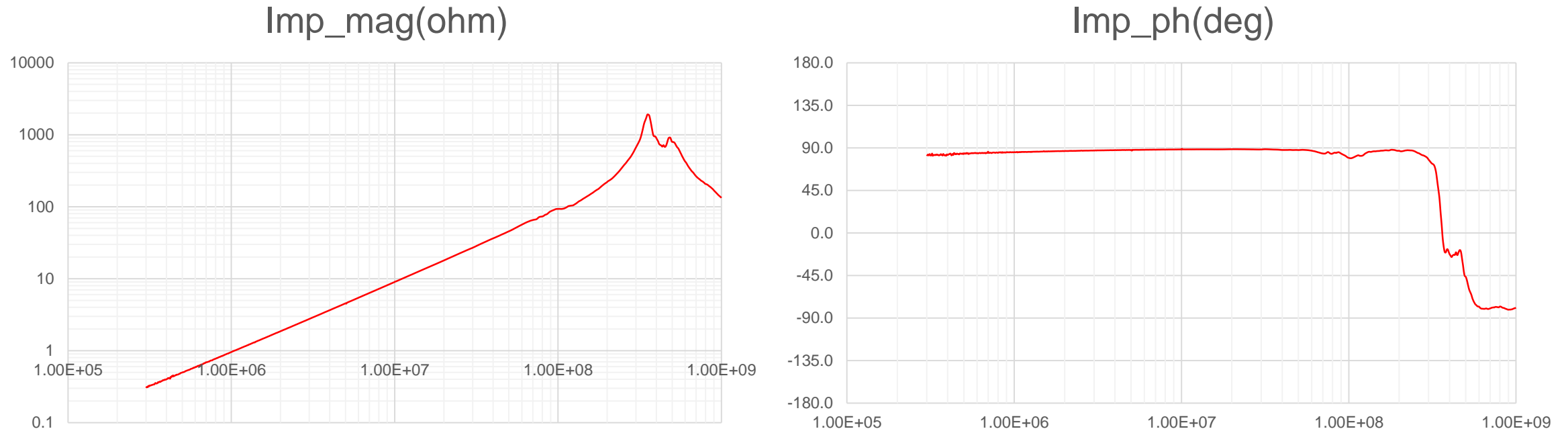Measure Impedance of the Grounding Harness L_{GND}



Note: The grounding impedance L_{GND} presents a 0.14uH inductance below 350MHz. And presents as a capacitor between 350MHz and 1GHz. Its impedance is 100ohm at 100MHz.


Reduction Method

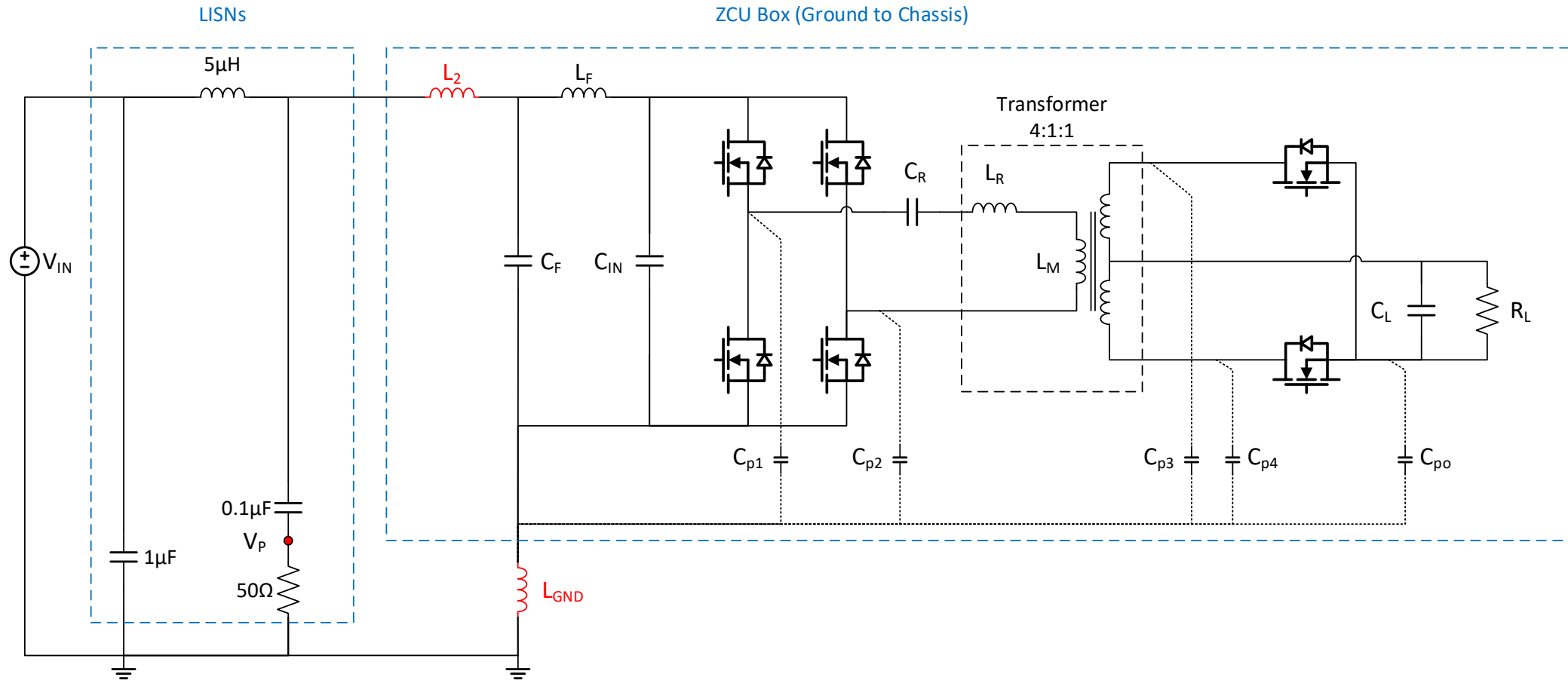

Note: An additional DM inductor L_2 can be applied to reduce the EMI noise.

Find L2 with high Impedance high Frequency

Typical Impedance Characteristics:

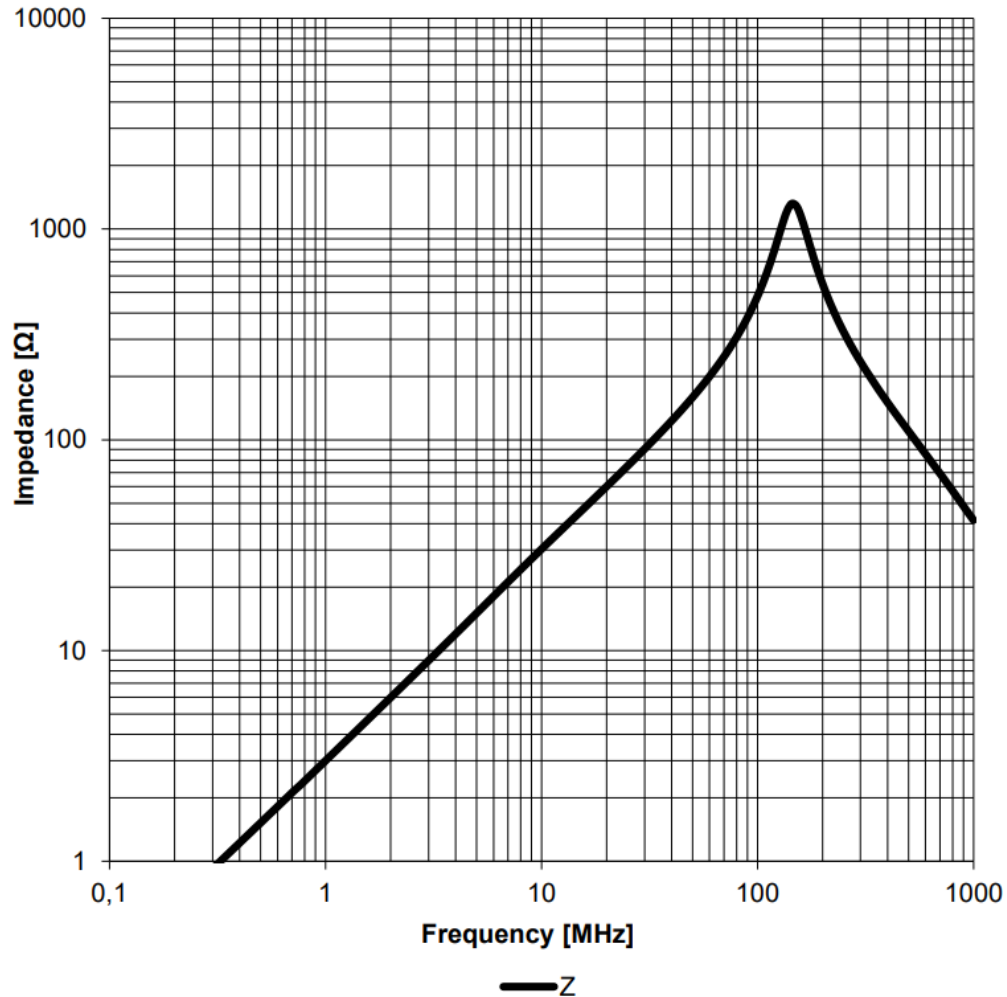


Ni-Zn Core, the Ni-Zn inductor provides high impedance at high frequency range.


$$Z_{L2} = 400\Omega \text{ at } 100\text{MHz}$$

Result Comparison with L2

CE, VIN = 48V, No Load, No L2

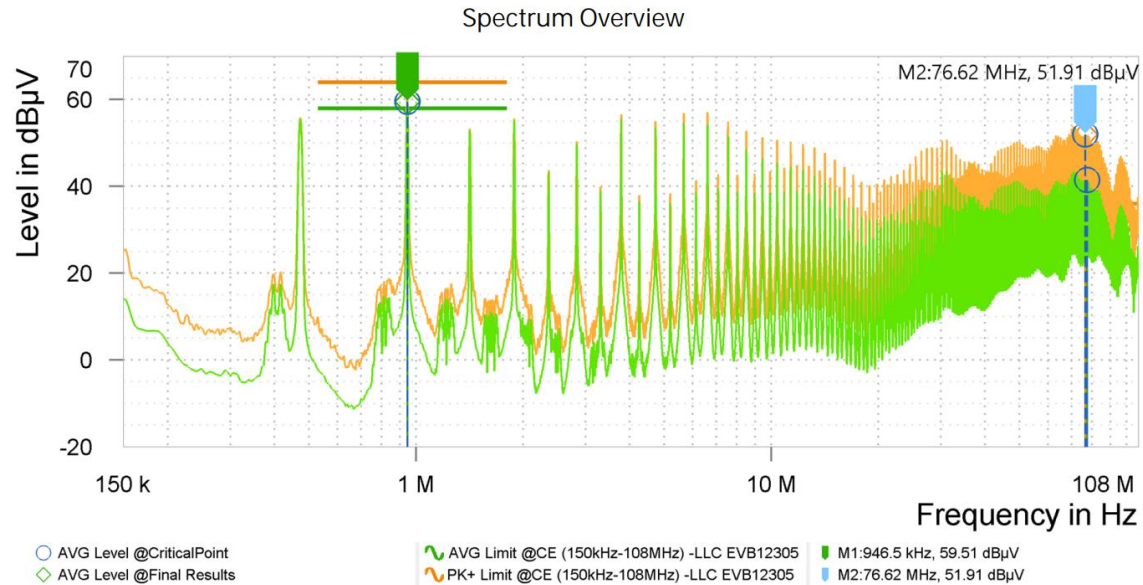


CE, VIN = 48V, No Load, L2 = 2.2uH

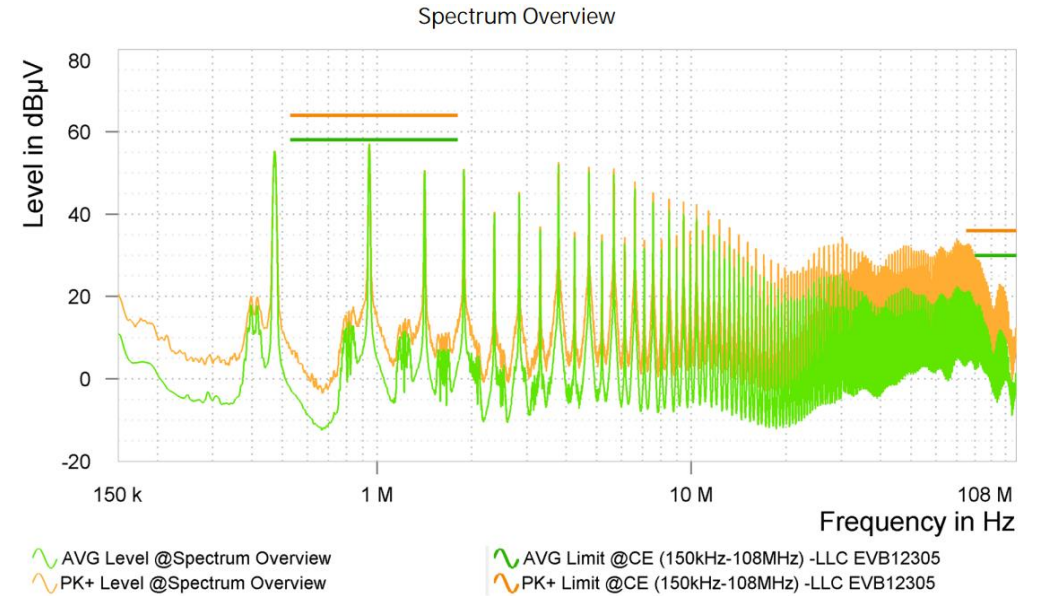


Note: As now the impedance of L2 is 8 times of L_{GND} , the high frequency noise reduced further by 5-6dB. The result passed the CE standard with 3dB margin.

Result Comparison with Load = 12A

CE, VIN = 48V, Load = 12A, No L2

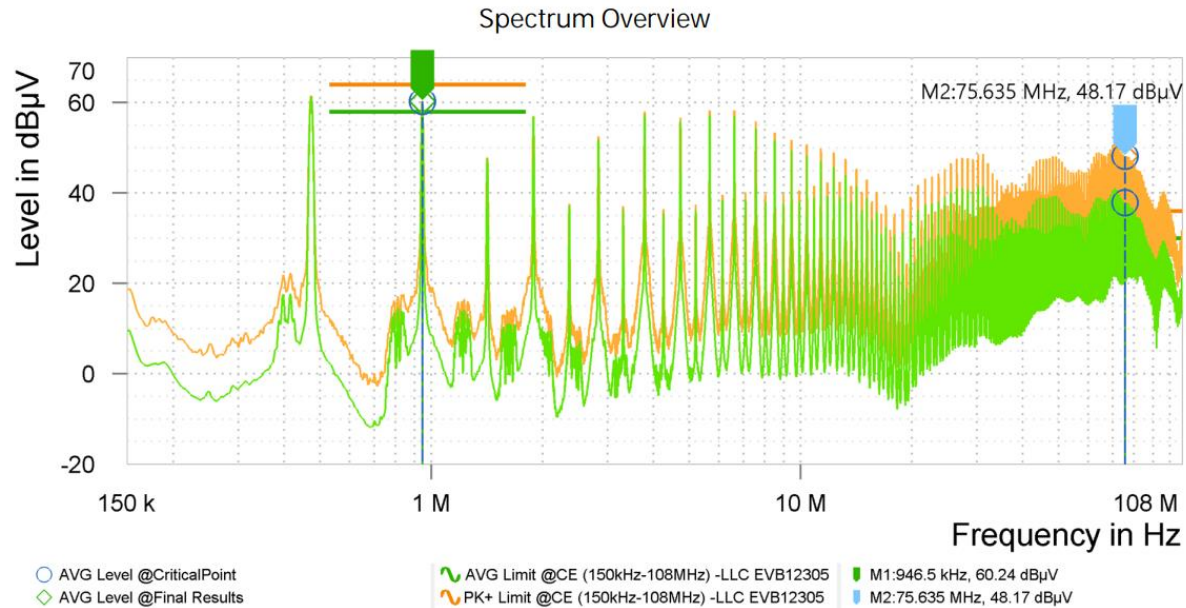

CE, VIN = 48V, Load = 12A, L2 = 2.2uH

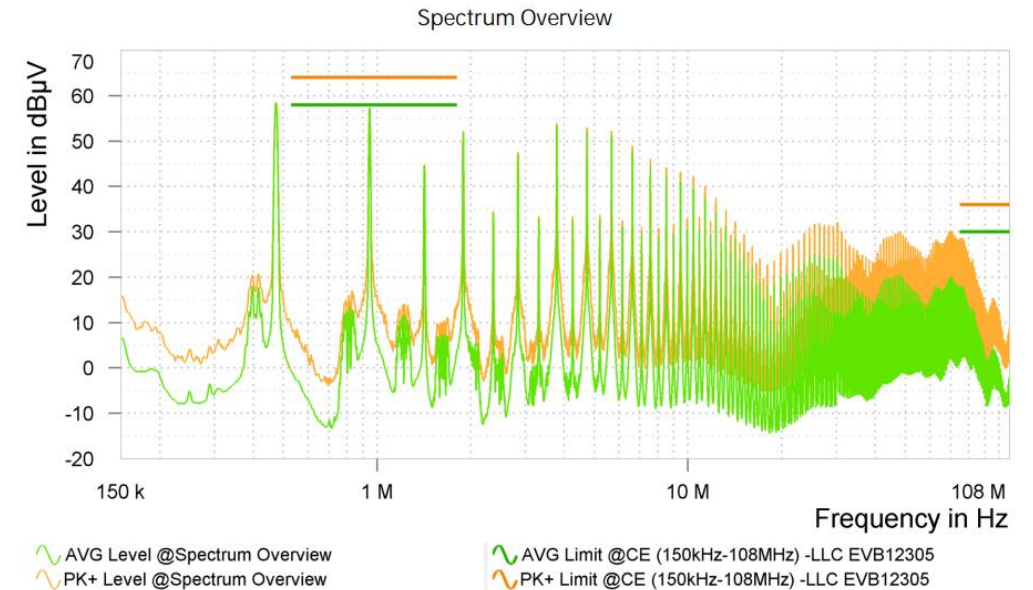

Note: With a proper L2 selection, the CE EMI meets with standard with enough margin under 12A.

Conclusion

For a DC/DC converter, higher supply voltage will induce worse EMI.

48V-12V DC/DC will be a new challenge for 48V system.

The LLC's operation principle is briefly introduced.

The Non-Isolated and Isolated LLC is compared.

The DM/CM LLC Conducted EMI model is introduced.

LLC CM EMI balance condition is discussed.

Chassis Grounding LLC EMI test setup in Automotive is introduced.

CE EMI reduction method for Chassis Grounding LLC is presented.

Thank you!